



System Level Protection for High-Voltage Multiplexers in Multi-Channel Data Acquisition Systems



Fault protection schemes using discrete components

Protection scheme #1:

Diodes in series with supplies


- Diode in series with the supplies blocks the ESD diode and parasitic SCR current flows.

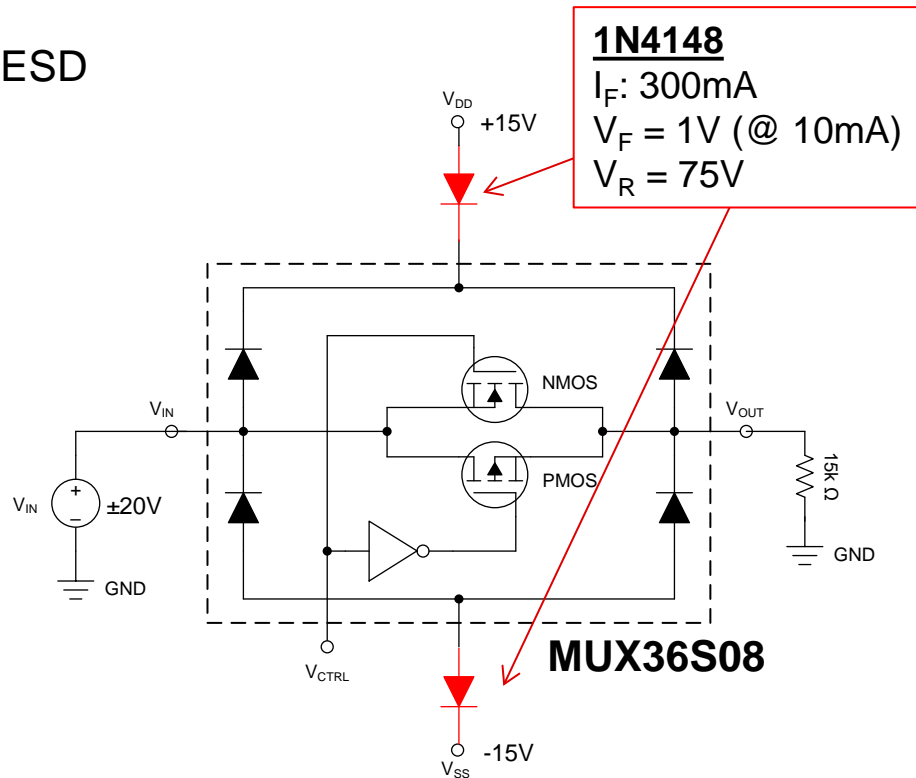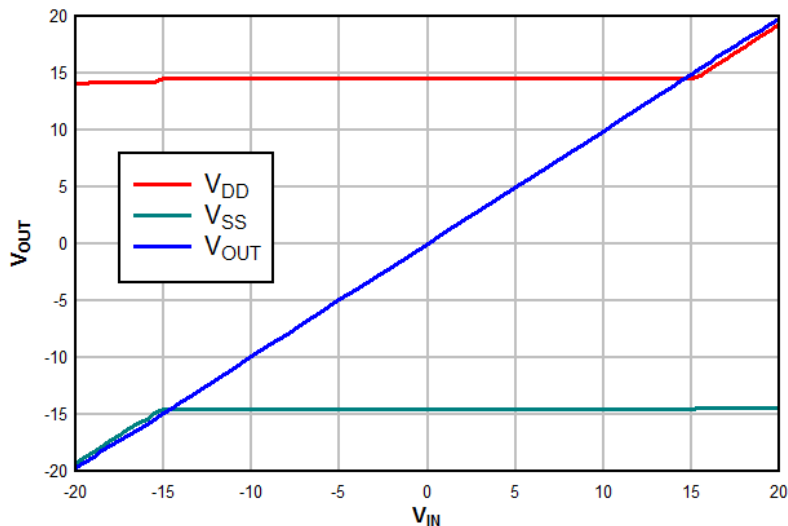Protection Scheme # 1: Diodes in series with supplies:



Protection scheme #1:

Diodes in series with supplies


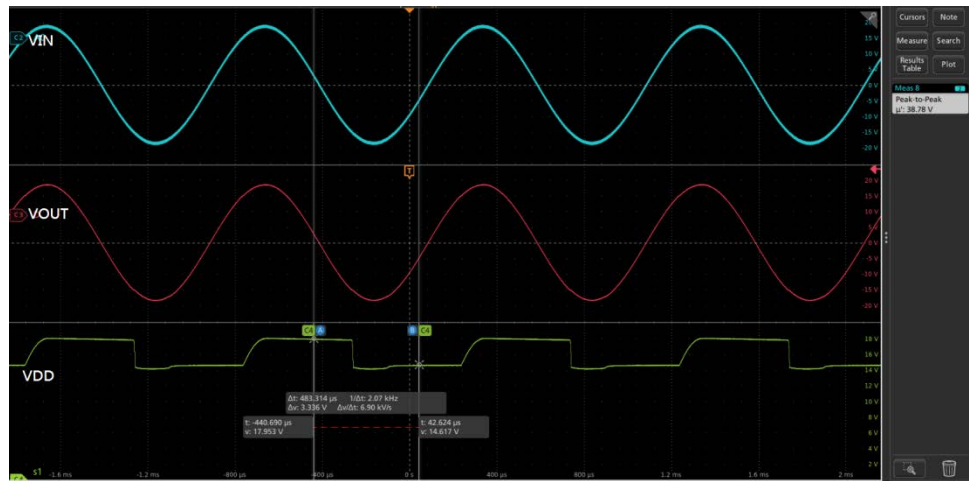


- Good:
 - No impact on the switch R_{ON} and leakage performance
 - Fault channel continues to operate with minimal distortion
 - Low cost
- Bad:
 - V_{DD} and V_{SS} go up together with the input voltage in the fault condition → potential damage to other system components on the same supplies
 - Allows the full input fault voltage to pass through → may cause damage to the downstream device
 - Changing supplies causes changes in MUX R_{ON} even for channels not at fault → impact measurement accuracy for all channels

Protection scheme #2:


Series resistor + Zener diodes on supplies

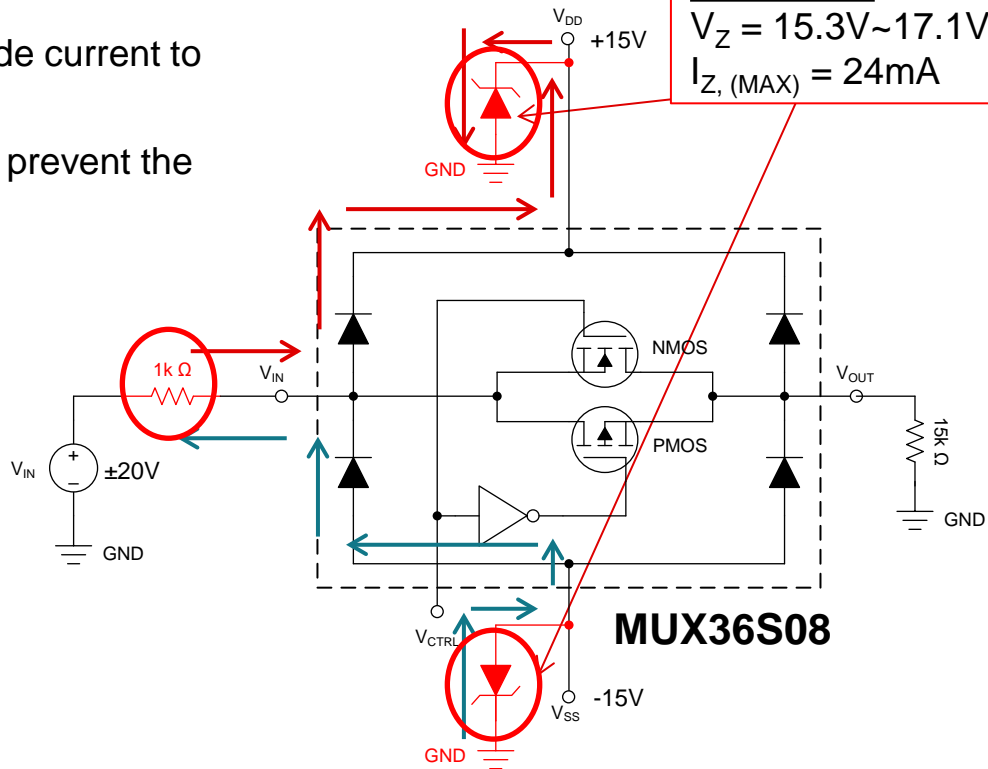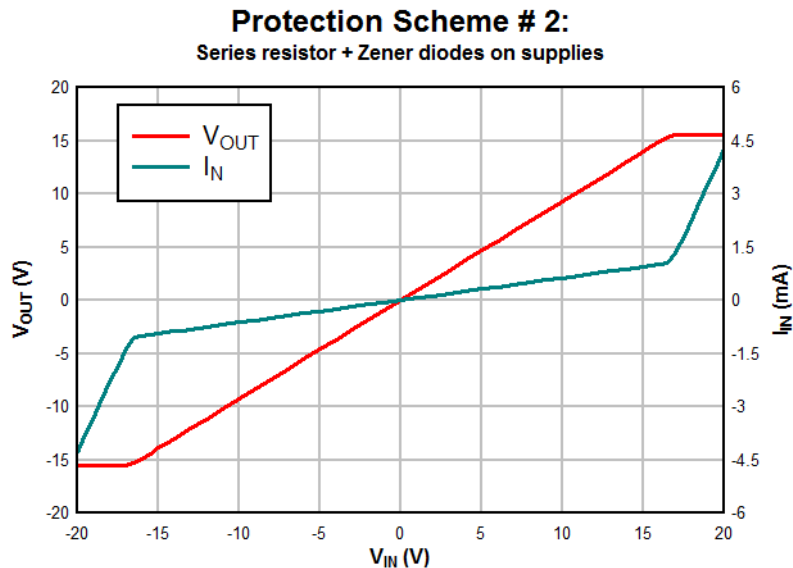- Current limiting resistor is used to limit the diode current to <math><10\text{mA}</math>.
- Zener diodes help sink and source currents to prevent the supplies from going over



Protection scheme #2:

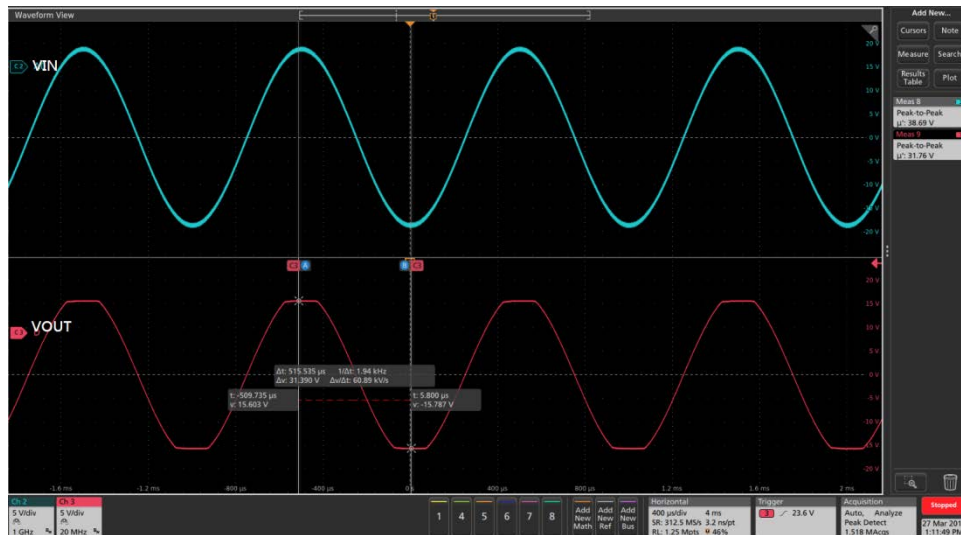Series resistor + Zener diodes on supplies





- **Good:**
 - Output clamped to $V_{DD} + 0.7V$ or $V_{SS} - 0.7V$
 - No overvoltage stress on the supplies and downstream circuitry.
- **Bad:**
 - Increased series resistance → worse THD and impacts accuracy
 - Increased settling time due to the RC combination → slower sampling speed
 - Heat produced from current through internal ESD diode → Persistent DC fault might cause internal heating and long-term reliability issue.
 - Potential uncontrolled behavior due to other parasitic path on the device.

Protection scheme #3:


Series resistor + Schottky + Zener diodes on supplies

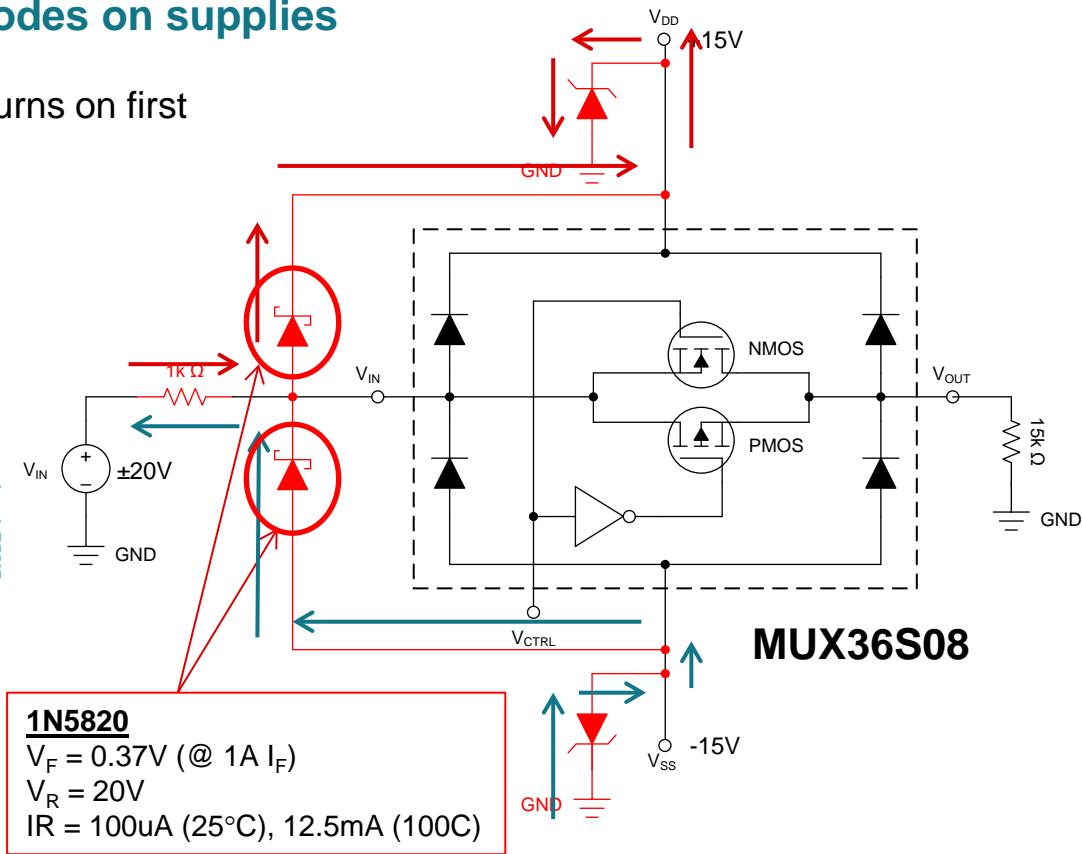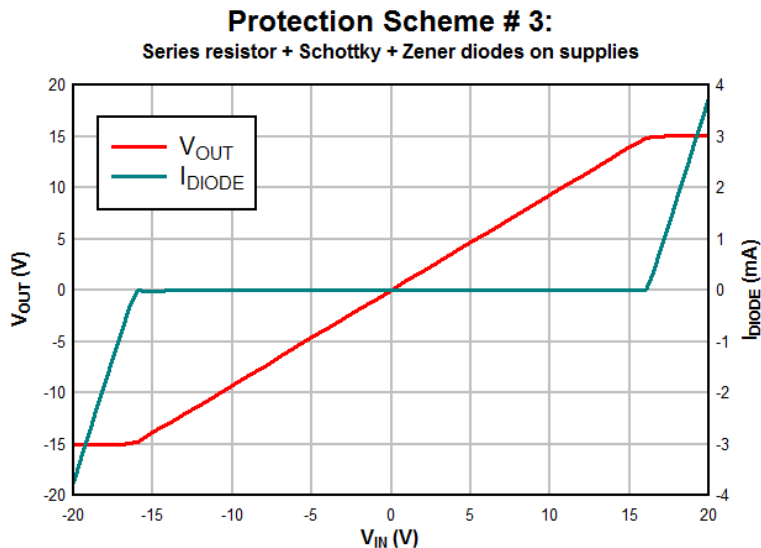- Schottky diodes (forward voltage $\sim 0.3V$) turns on first before the multiplexer's internal diodes.



Protection scheme #3:

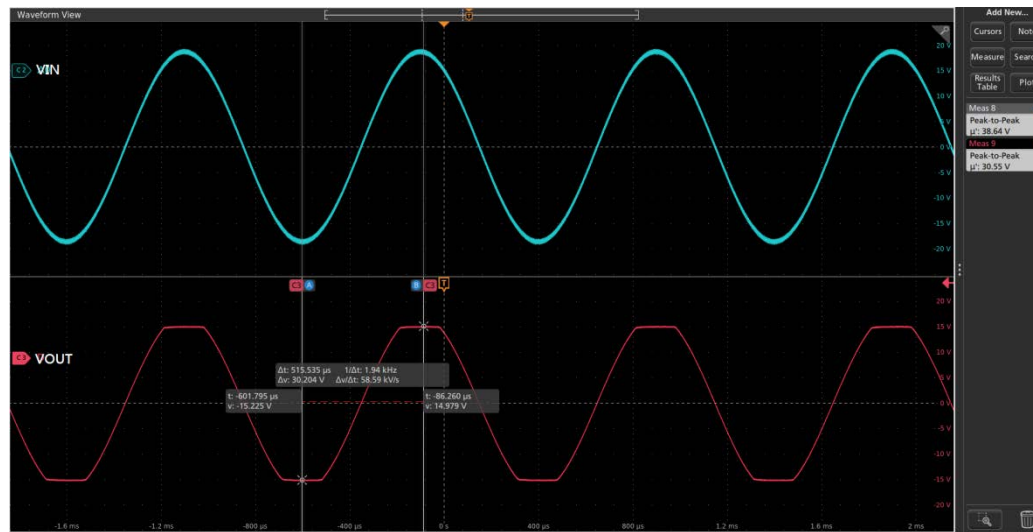Series resistor + Schottky + Zener diodes on supplies





- Good:
 - No overheating concern from ESD diode
 - Output clamped to $V_{DD} + 0.3V$ or $V_{SS} - 0.3V$
 - No overvoltage stress on the supplies and downstream circuitry.
 - Much higher current carry capability on the Schottky diodes than internal ESD diodes
- Bad:
 - Increased series resistance → worse THD and impacts accuracy
 - Increased settling time due to the RC combination → slower sampling speed
 - Lower reverse voltage rating and worse leakage number for the Schottky diodes → Impact signal dynamic range and measurement accuracy
 - Cost

Protection scheme #4:

Series resistor + TVS (or Zener) diodes

- TVS (for faster transient fault) or Zener (for DC fault) help clamp the input voltage below V_{BR} .
- Series resistor placed after the TVS helps reduce transient current injected into the device

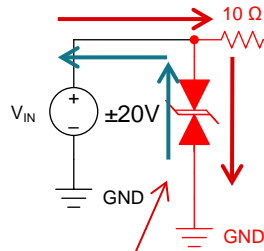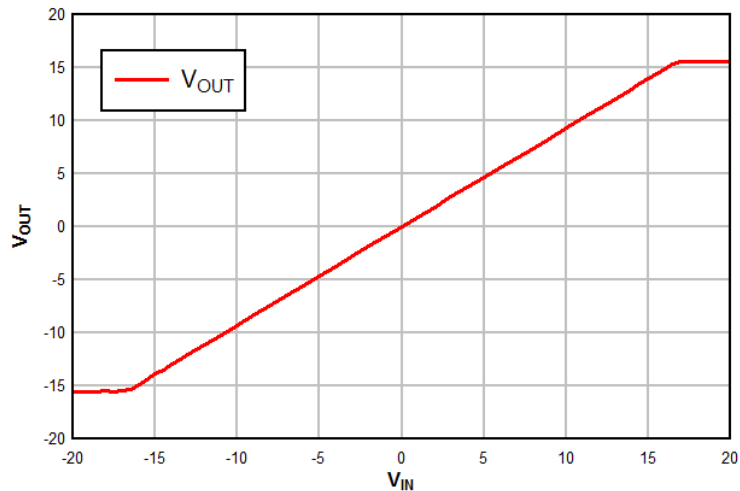Protection Scheme # 4: Series resistor + TVS diodes




P6KE15CA

$V_{WM} = 12.8V$

$V_{BR} = 14.3V$ to $15.8V$


$V_C = 21.8V$

$I_R = 1\mu A$

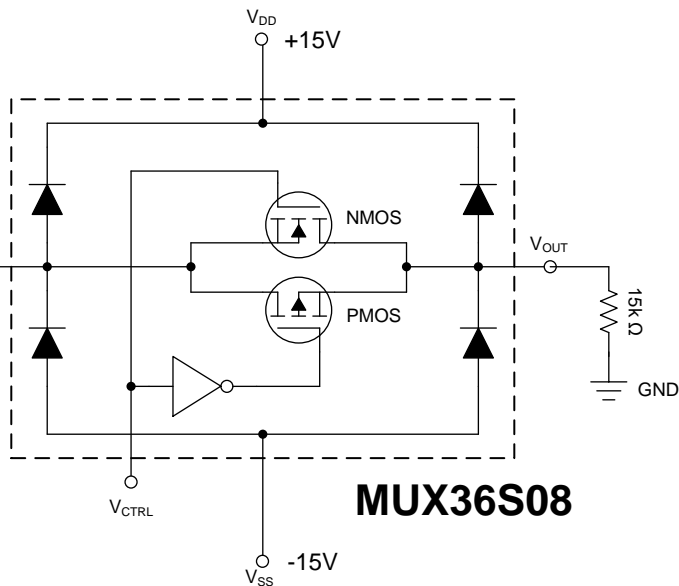

Protection scheme #4:

Series resistor + TVS (or Zener) diodes

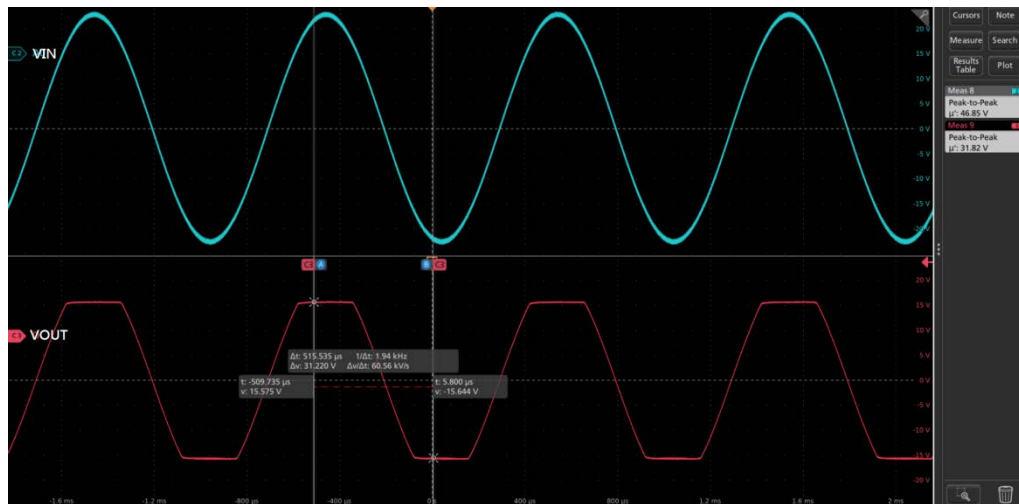

- **Good:**
 - Output clamped to the Zener or TVS reverse breakdown voltage
 - No overvoltage stress on the supplies or downstream circuitry
 - No overheating concern from ESD diode
 - Much lower reverse leakage current compared to Schottky diodes
 - Transient fault (ie. ESD) protection from TVS
 - Lower series resistor required
- **Bad:**
 - Higher parasitic capacitance → slower sampling speed
 - Cost (one TVS or Zener on every channel)