

Basics of Analog Multiplexers 2

TIPL 2602

TI Precision Labs – Op Amps



Created by Abhijeet Godbole, Art Kay

Presented by Peggy Liska

Analog Multiplexer Parameters Summary



- Part 1: Understanding Performance parameters of Multiplexer
 - 1) Leakage Current
 - Types of Leakage Current
 - Offset issues Related to Leakage Current
 - 2) Charge Injection
 - Understanding Charge Injection Phenomenon
 - Effect of Charge Injection on Multiplexer Output Voltage Error
- Goals:
 - 1. To understand performance parameters of multiplexers
 - 2. Understand their importance while designing data acquisition system

Leakage Current

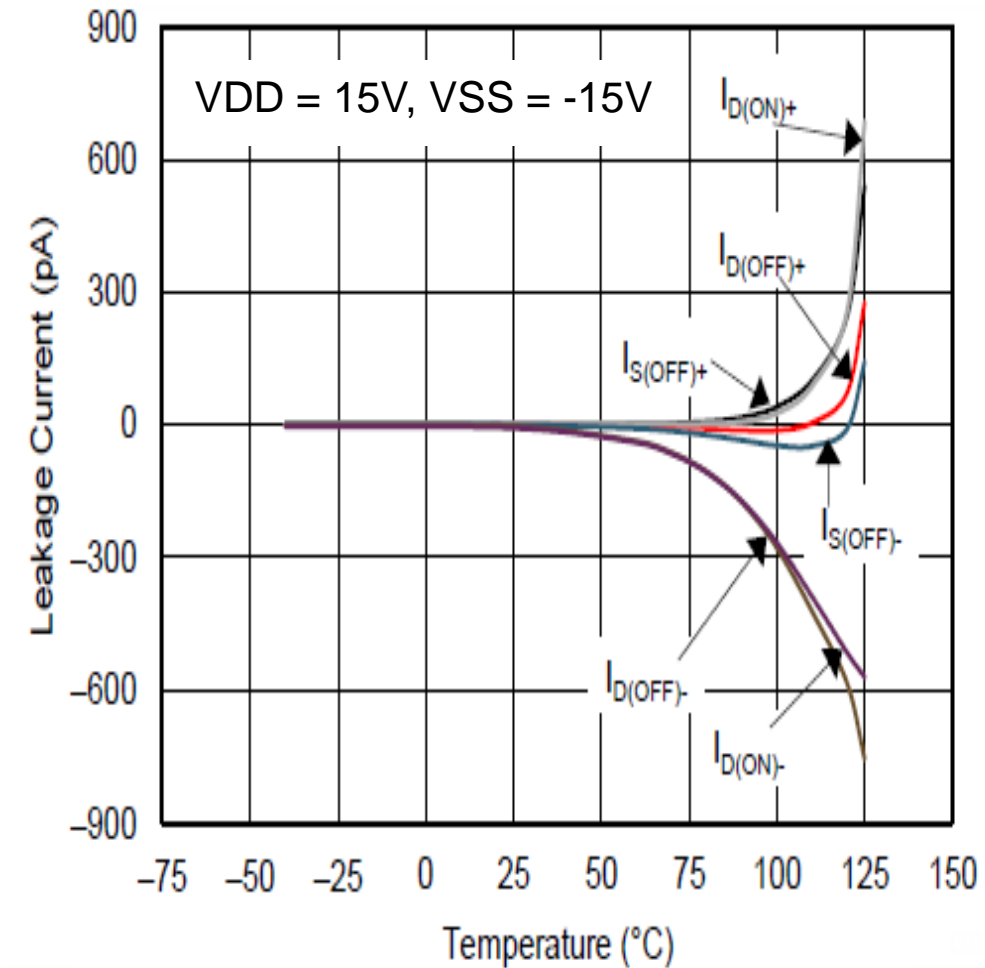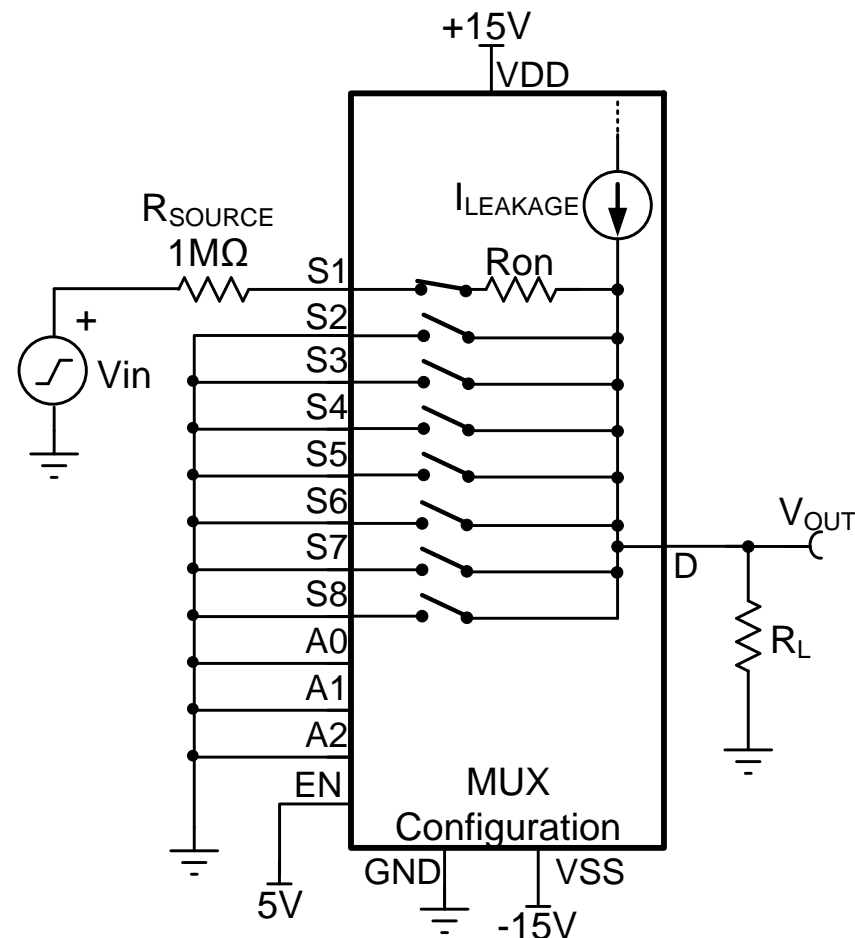


- **Leakage Current:** Current flowing out Source (S) and Drain (D) pins when MUX switch is ON or OFF
- **Switch = OFF:** Leakage current flows out Source pin and Drain pin, $I_{S(OFF)}$ and $I_{D(OFF)}$
- **Switch = ON:** Approximate leakage current out Source and Drain pin is $I_{S(ON)} = I_{D(ON)}$

Leakage Current

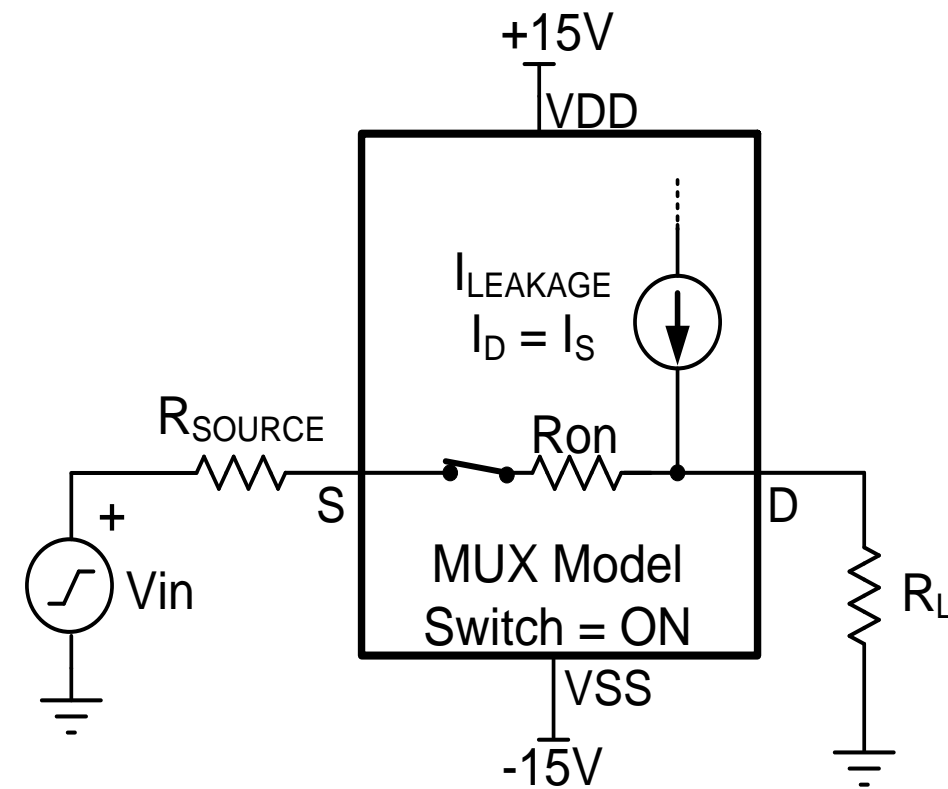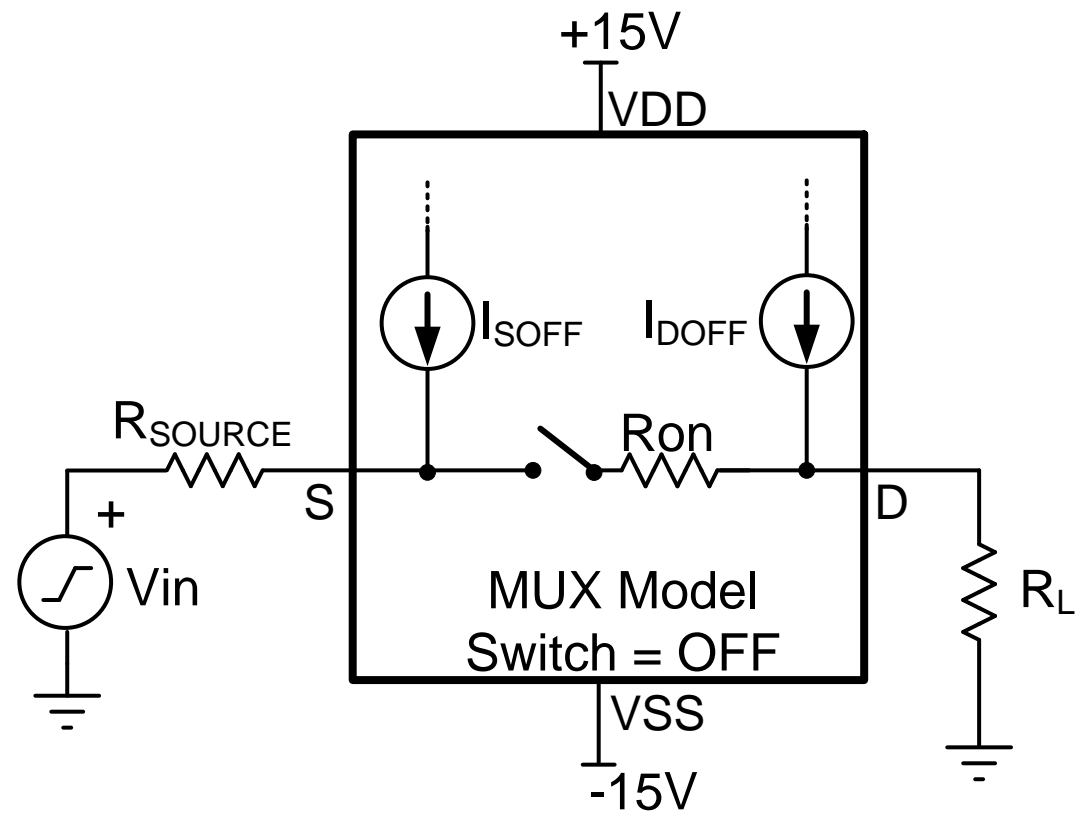

- **Switch = OFF:** $I_{S(OFF)}$ flows through R_{SOURCE} and $I_{D(OFF)}$ flows through R_L
- **Switch = ON:** Error introduced by leakage current: $V_{ERROR} = (R_{ON} + R_{SOURCE}) \times I_{D(ON)}$

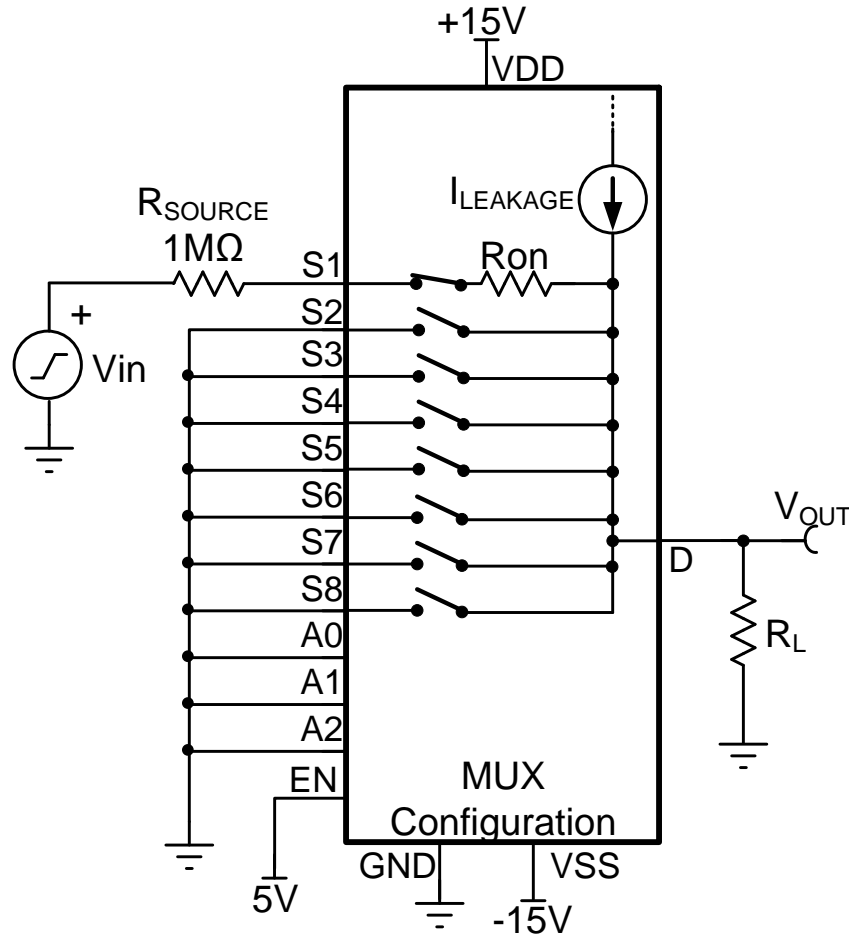Offset Error Introduced by Leakage Current



18-bit System Example Calculation

$$V_{\text{ref}} = 5\text{V}$$


$$V_{\text{LSB}} = \frac{5\text{V}}{2^{18}} = 19.073\mu\text{V}$$

$$\text{OffsetError(V)} = I_{\text{LEAKAGE}} \cdot R_{\text{SOURCE}} = (100\text{pA})(1\text{M}\Omega) = 100\mu\text{V}$$

$$\text{OffsetError(Bits)} = \frac{\text{OffsetError(V)}}{V_{\text{LSB}}} = \frac{100\mu\text{V}}{19.073\mu\text{V}} = 5.24 \text{ codes}$$

Multiplexer Examples	Multiplexer leakage current (25°C/85°C)	Offset error (25°C/85°C) ($I_{\text{LEAKAGE}} \times R_{\text{Source}}$)	Offset Error 18 bit System (in bits)
MUX1 (Low Leakage)	10pA/50pA	10μV/50μV	0.52 / 2.62
MUX2 (High Leakage)	100pA/500pA	100μV/500μV	5.24 / 26.22

Review: Charge Equation

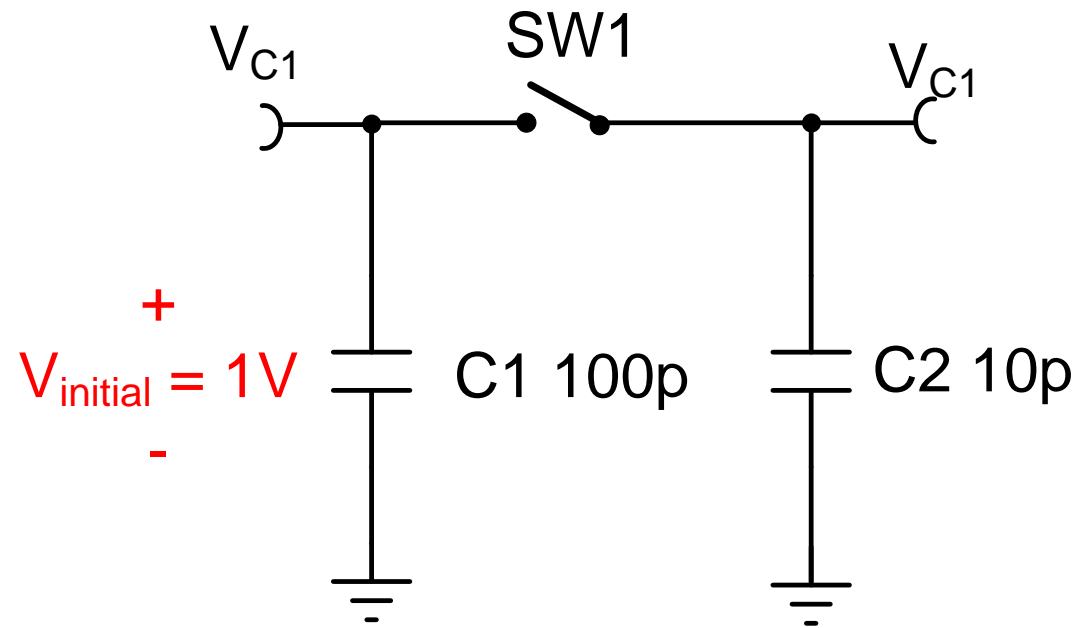

Definition

Q = Charge in Coulombs

C = Capacitance in Farads

V = Voltage in Volts

Charge of C1,
Assuming initial 1V

Close switch

New Voltage after charge
redistribution

Charge Equation Example



$$Q = C \cdot V$$

$$Q = C_1 \cdot V_1 = (100pF) \cdot (1V) = 100pC$$

$$C_{\text{total}} = C_1 + C_2 = 110pF$$



$$V_{\text{final}} = \frac{Q}{C_{\text{total}}} = \frac{100pC}{110pF} = 0.909V$$

Charge Injection (Q_{INJ})

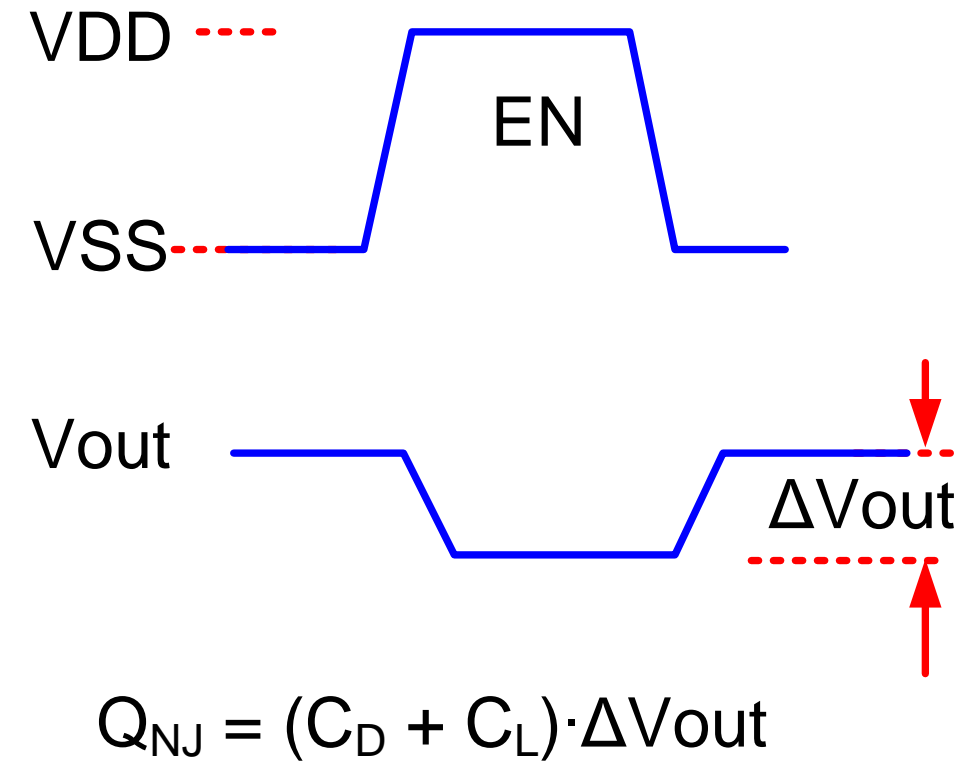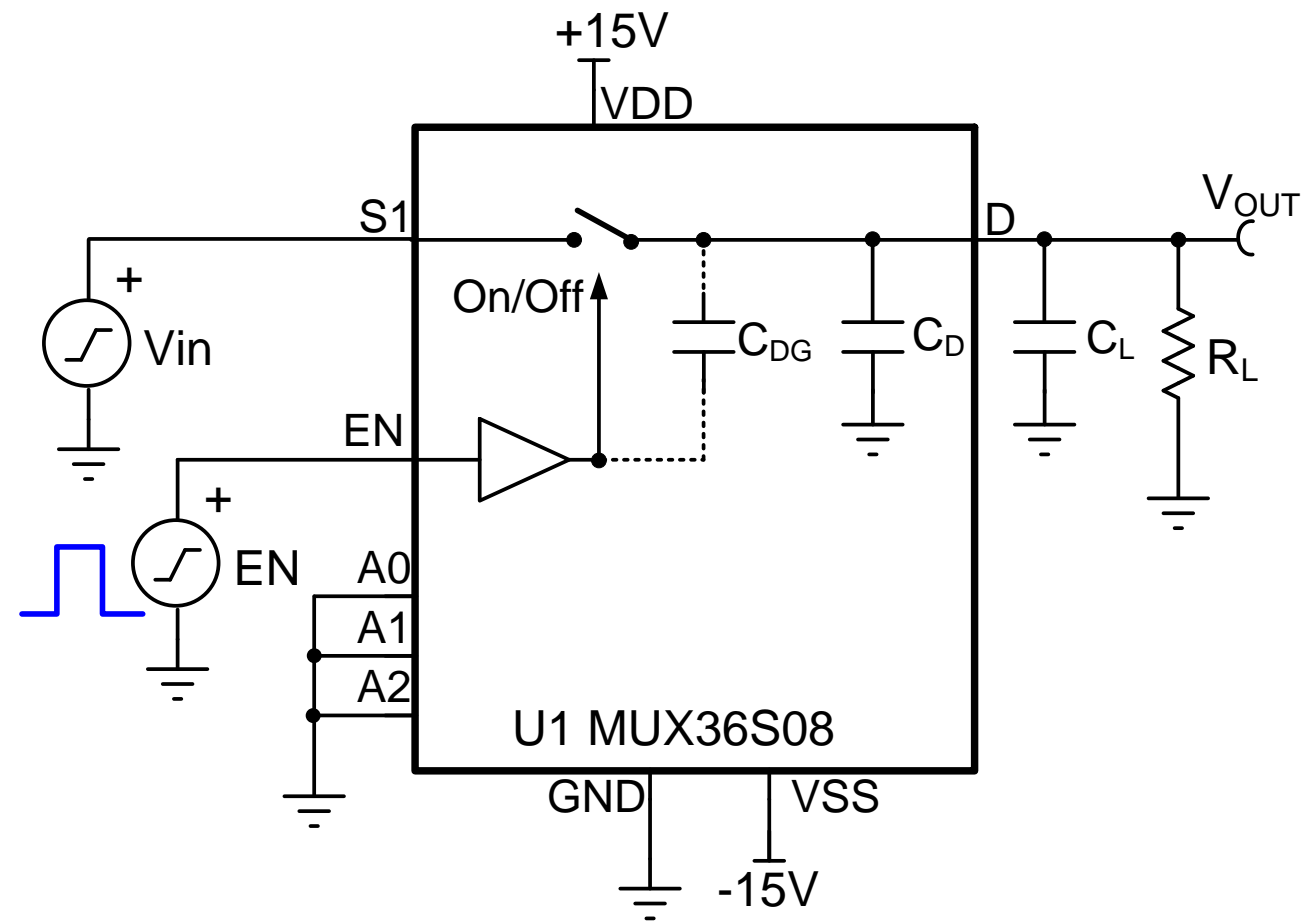

- **Charge injection Error:** Voltage change introduced at the output of switch when switch is turned ON or OFF
- Larger load capacitance minimizes the effect of charge Injection at the multiplexer output

Charge Injection Error vs. Input Voltage

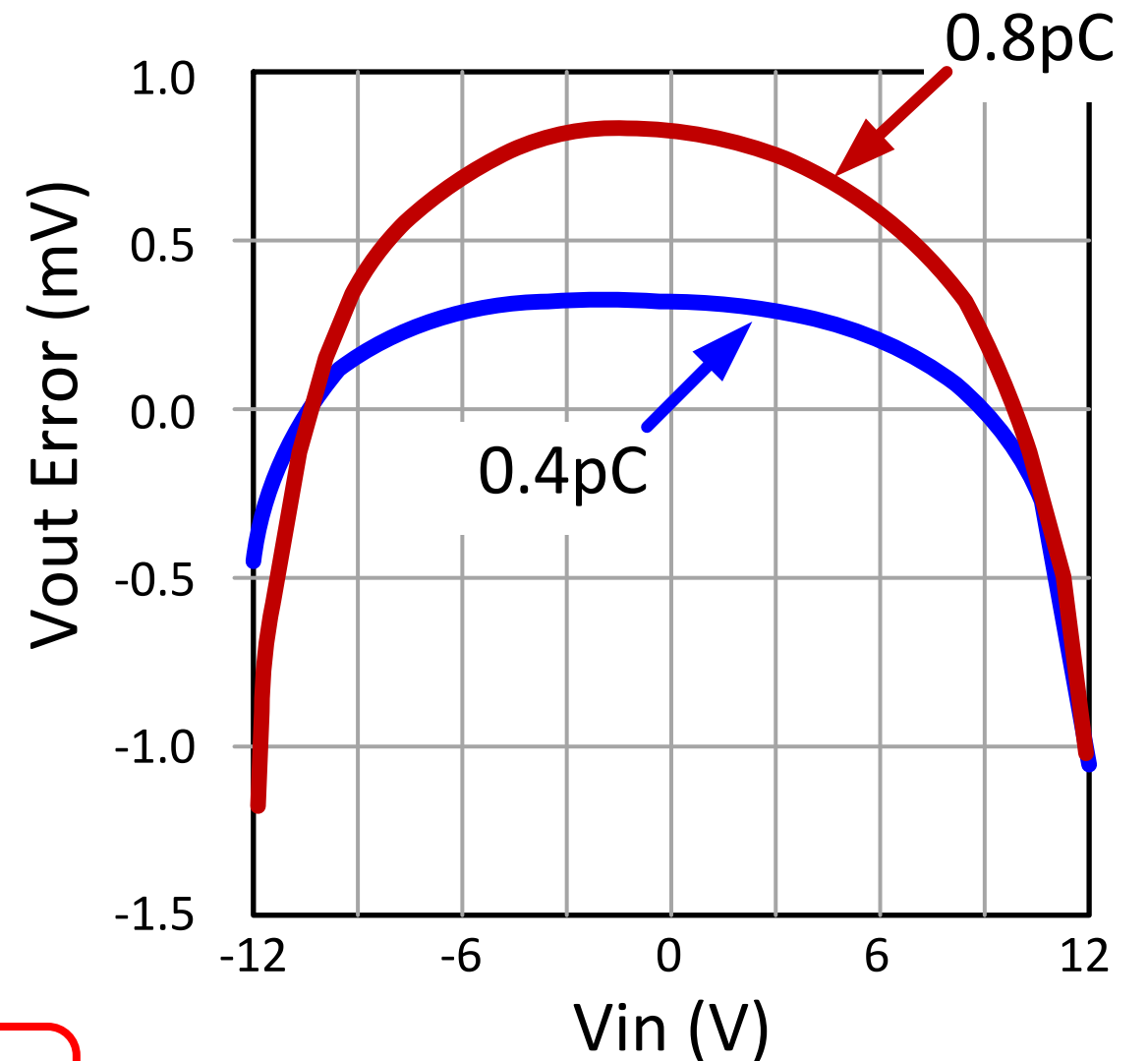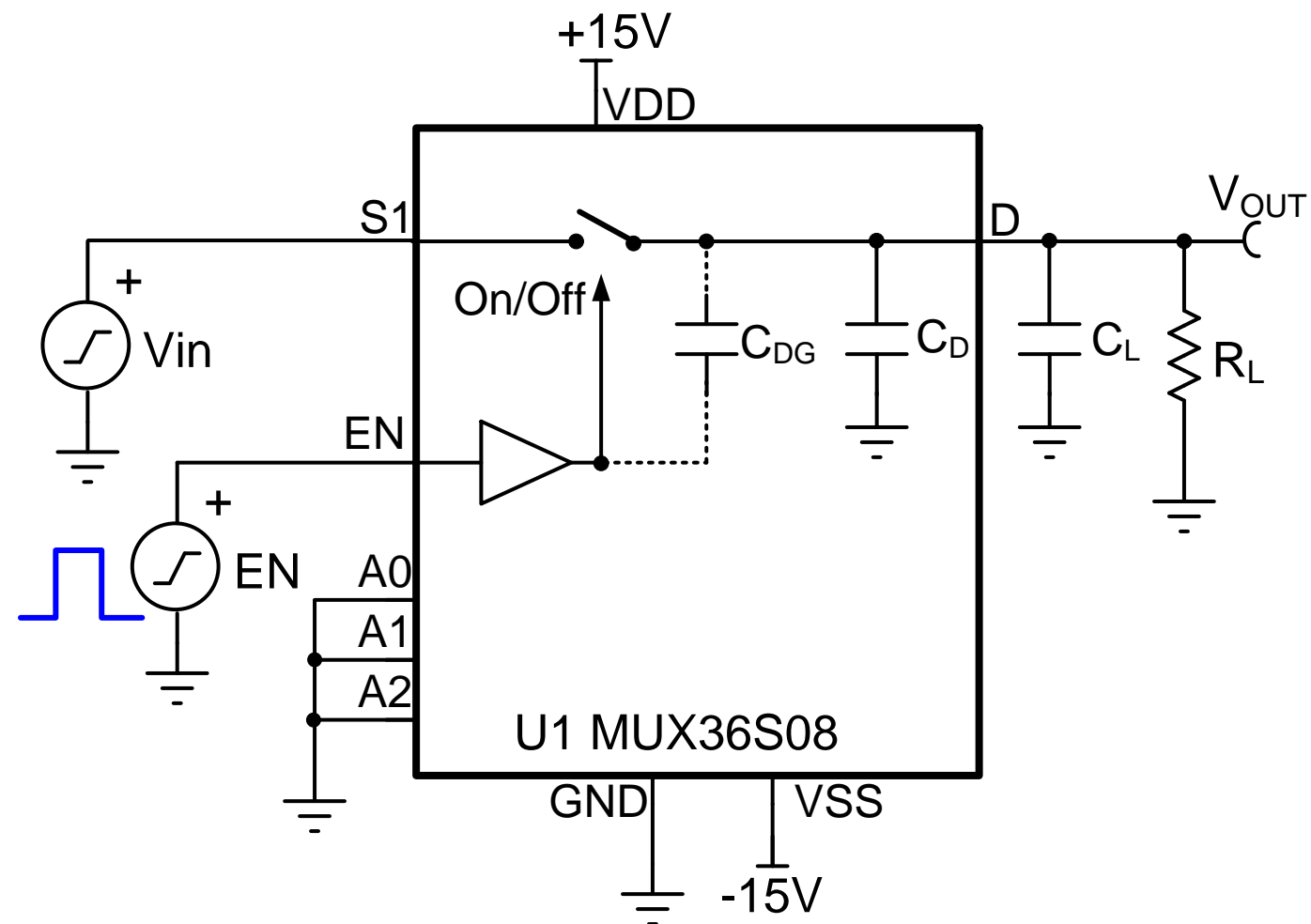

$$\text{Error} = Q_{INJ} / C_L$$

Summary: MUX Leakage Current and Charge Injection

Leakage Current

- Introduces DC offset Error
- Varies with temperature and can introduce linearity errors too
- Important parameter for high input impedance data acquisition systems

Charge Injection

- Introduces output voltage error when control logic is switched
- Typically worse on multiplexers with large Con.
- Smaller the load capacitor higher the error introduced due to charge injection
- Important parameter for fast switching systems

Thanks for your time!
Please try the quiz.