

Basics of Analog Multiplexers 3

TIPL 2603

TI Precision Labs – Op Amps



Created by Abhijeet Godbole, Art Kay

Presented by Peggy Liska

Analog Multiplexer Parameters Summary

- Part 1: Understanding Performance parameters of Multiplexer
 - 1) Bandwidth
 - How MUX bandwidth is defined
 - Factors affecting MUX bandwidth
 - 2) Channel to Channel Crosstalk
 - Understanding Channel to Channel Crosstalk
 - Factors affecting Crosstalk
 - 3) OFF Isolation
 - Understanding OFF Isolation of MUX
 - Factors affecting OFF Isolation
 - 4) THD+Noise
 - Understanding THD+Noise parameter
- Goals:
 - 1. To understand performance parameters of multiplexers
 - 2. Understand their importance while designing data acquisition system

Bandwidth

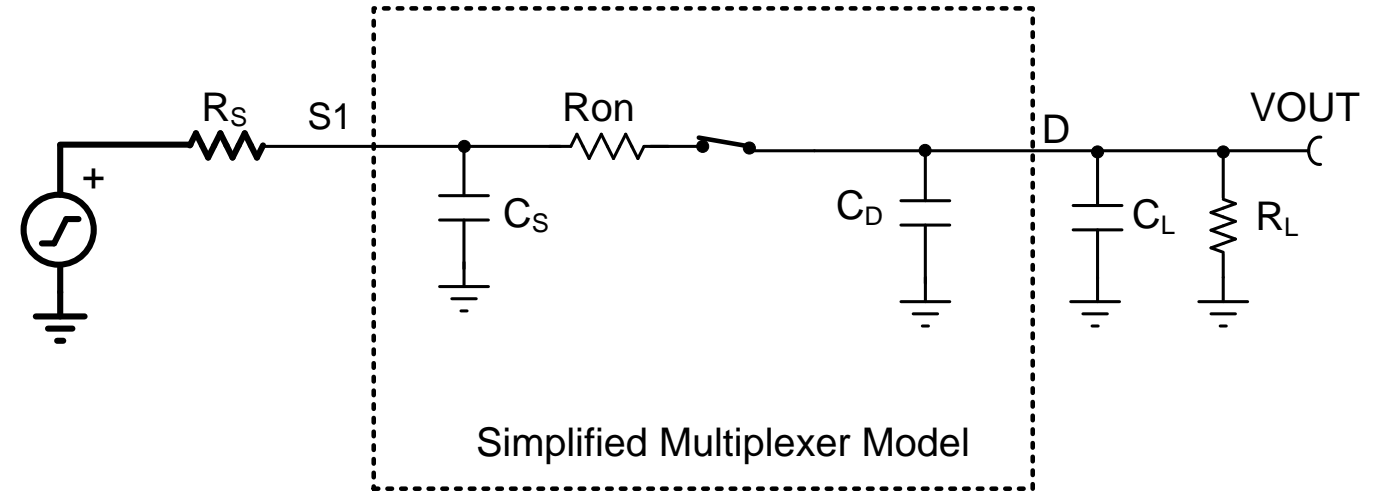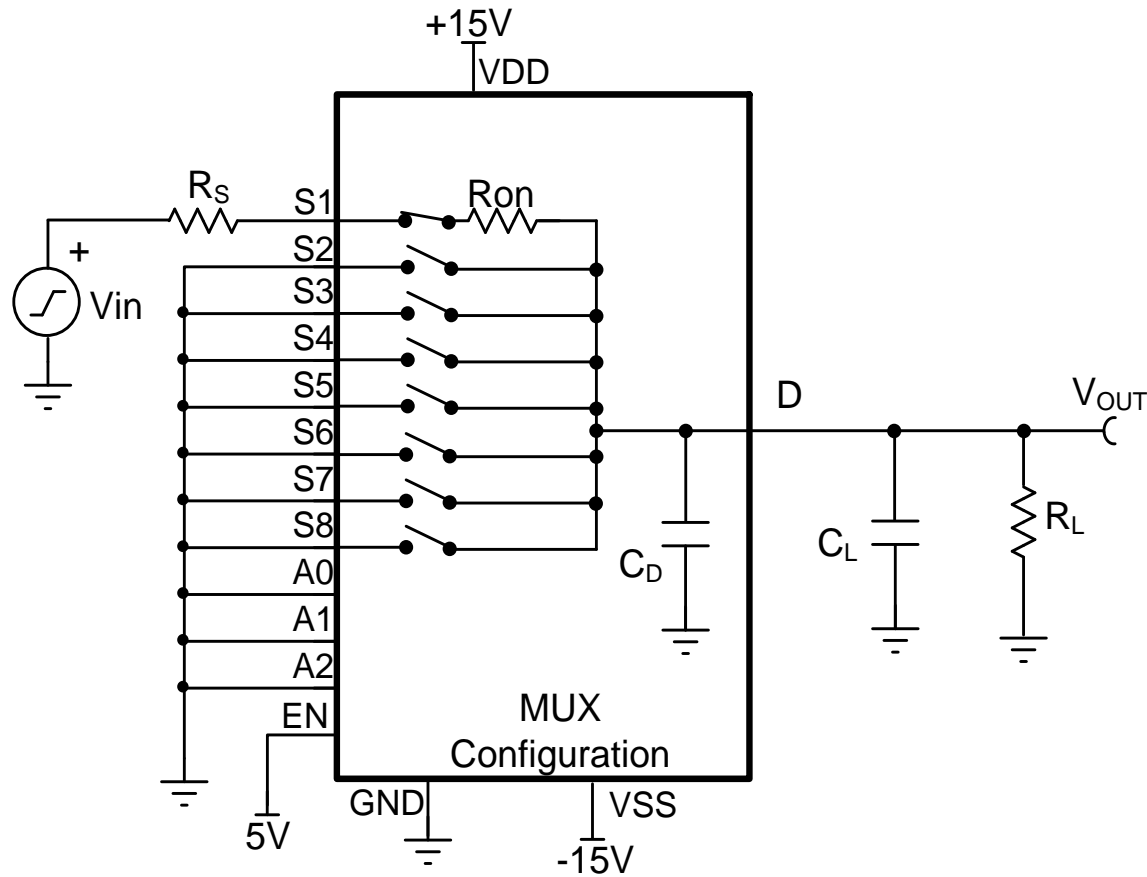

Bandwidth : The frequency at which the output is attenuated by 3 dB from the pass band (dc) response.



Transfer function

$$\frac{V_{OUT}}{V_{in}} = \left(\frac{R_L}{R_L + R_{on}} \right) \left(\frac{1}{\left(\frac{f}{f_c} \right) + 1} \right)$$

3 dB Cut OFF Frequency:

$$f_c = \frac{(R_L + R_{on})}{2 \cdot \pi \cdot (R_L \cdot R_{on}) \cdot (C_D + C_L)}$$

Bandwidth

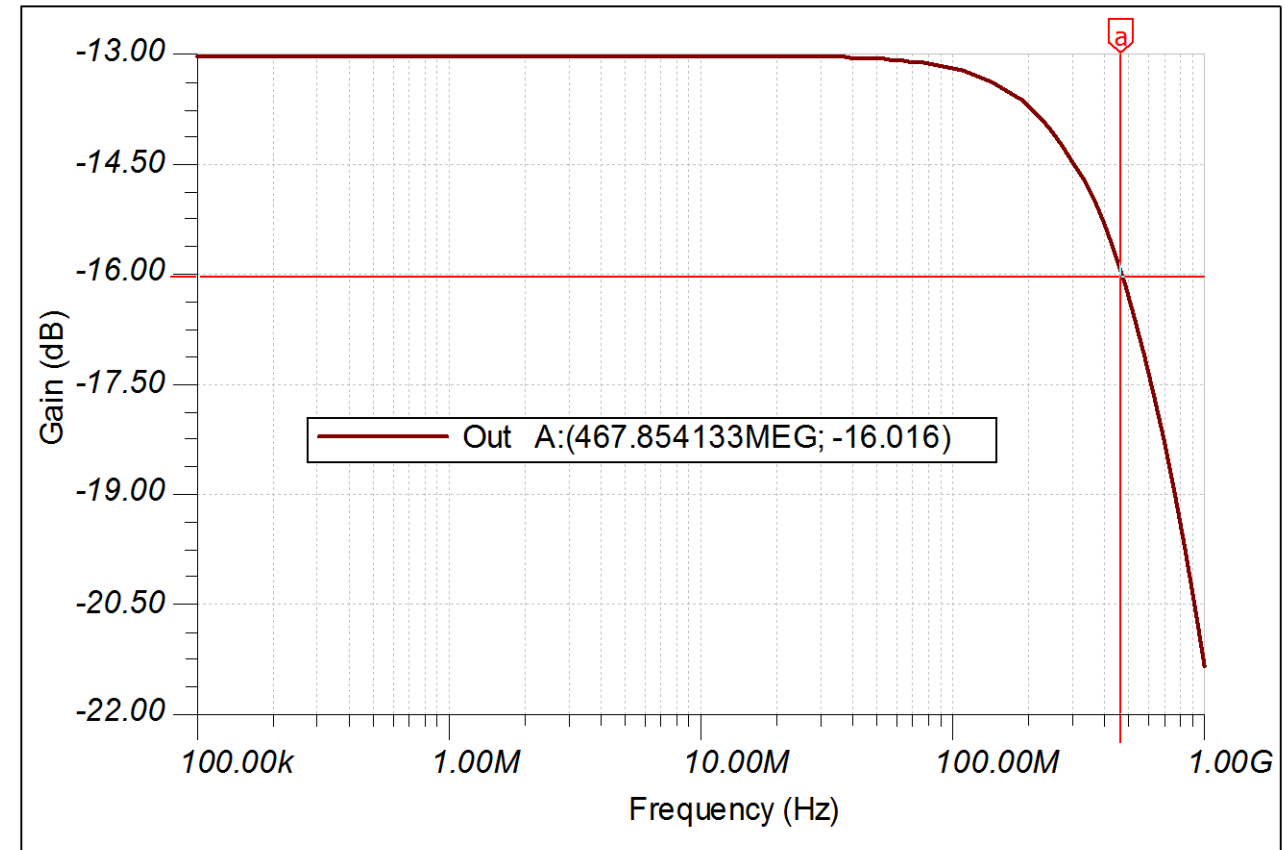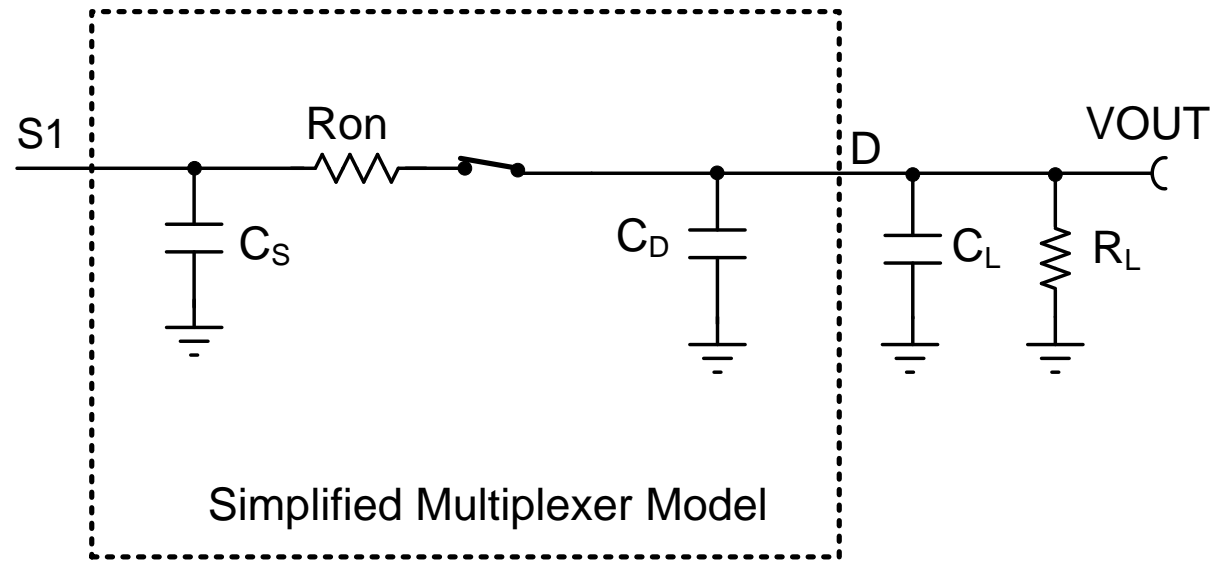


3 dB Cut OFF Frequency:

$$f_c = \frac{(R_L + R_{on})}{2 \cdot \pi \cdot (R_L \cdot R_{on}) \cdot (C_D + C_L)}$$

$R_L \gg R_{ON}$ Cutoff Frequency

$$f_c = \frac{1}{2 \cdot \pi \cdot (R_{on}) \cdot (C_D + C_L)}$$

Channel to Channel Crosstalk

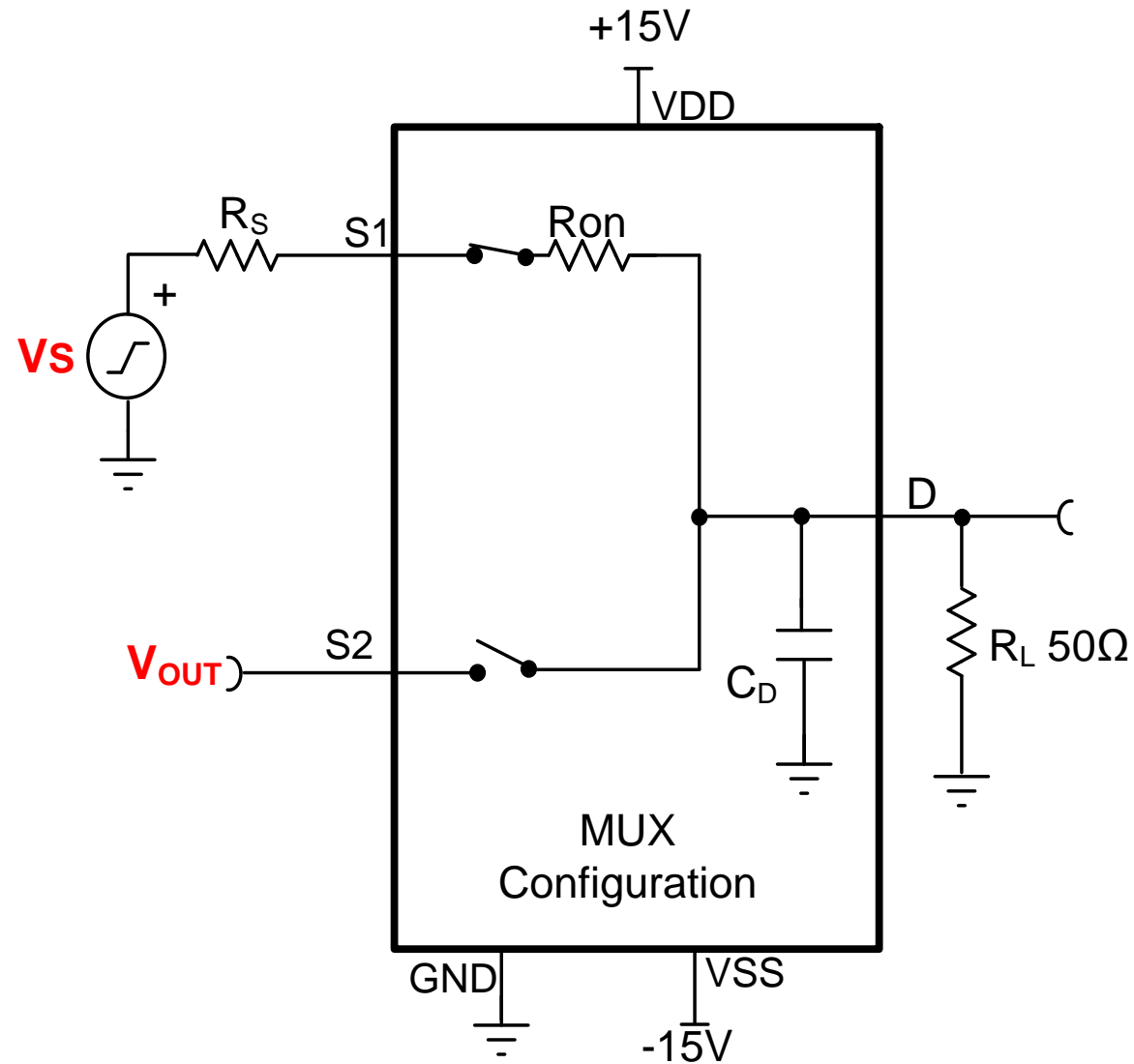

Crosstalk: voltage feed through to the source pin of an off-channel from a known signal is applied to the source pin of an on-channel

Channel to Channel Crosstalk (dB)



$$= 20 * \log \left(\frac{V_{OUT}}{V_S} \right)$$

Where

V_S : Voltage applied to source pin of on channel


V_{OUT} : Voltage measured at source pin of off channel

Channel to Channel Crosstalk

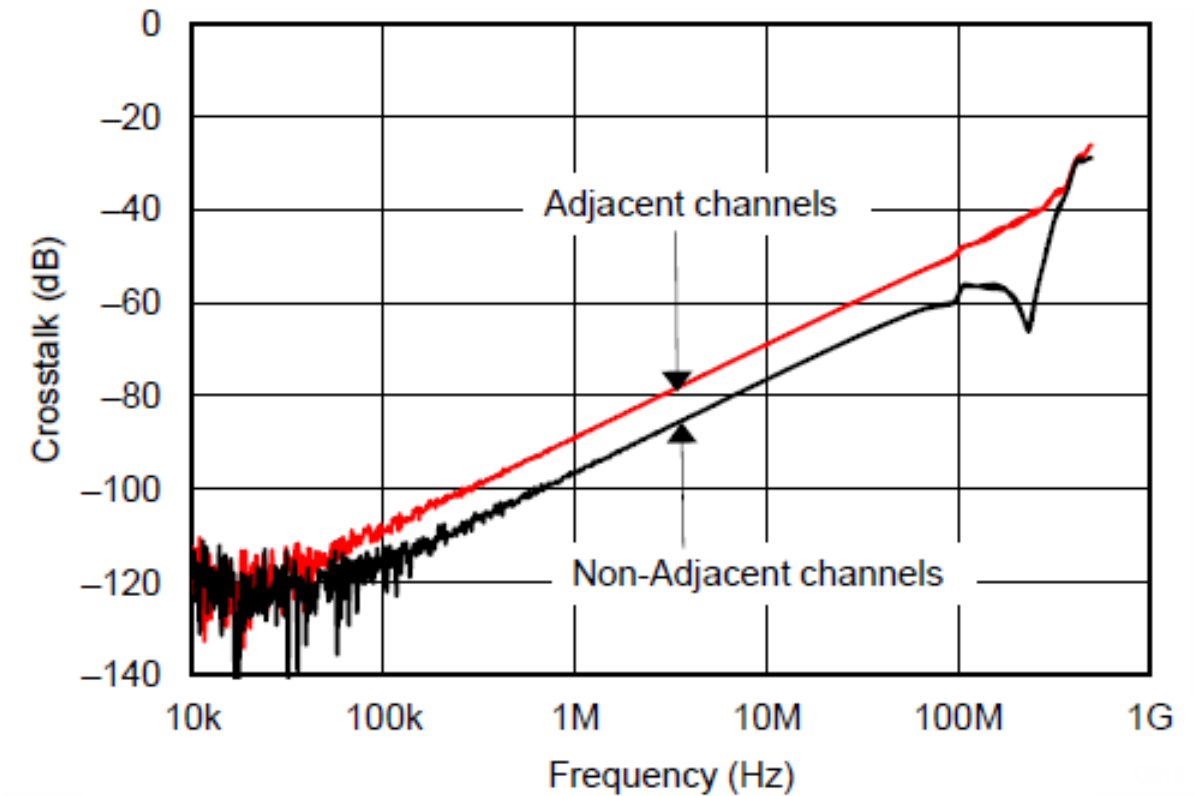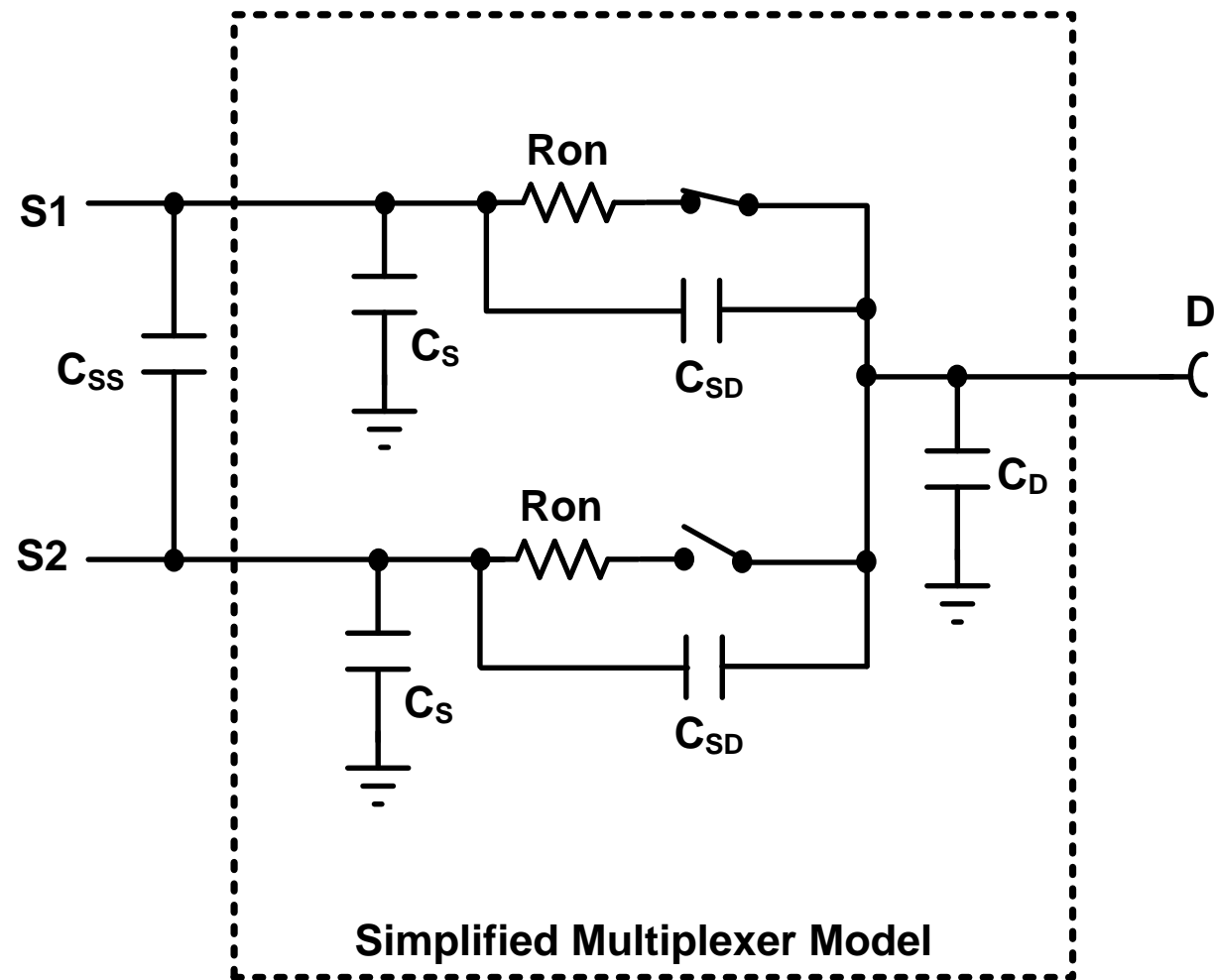

MUX36S08 Channel to Channel Crosstalk vs. Frequency

OFF Isolation

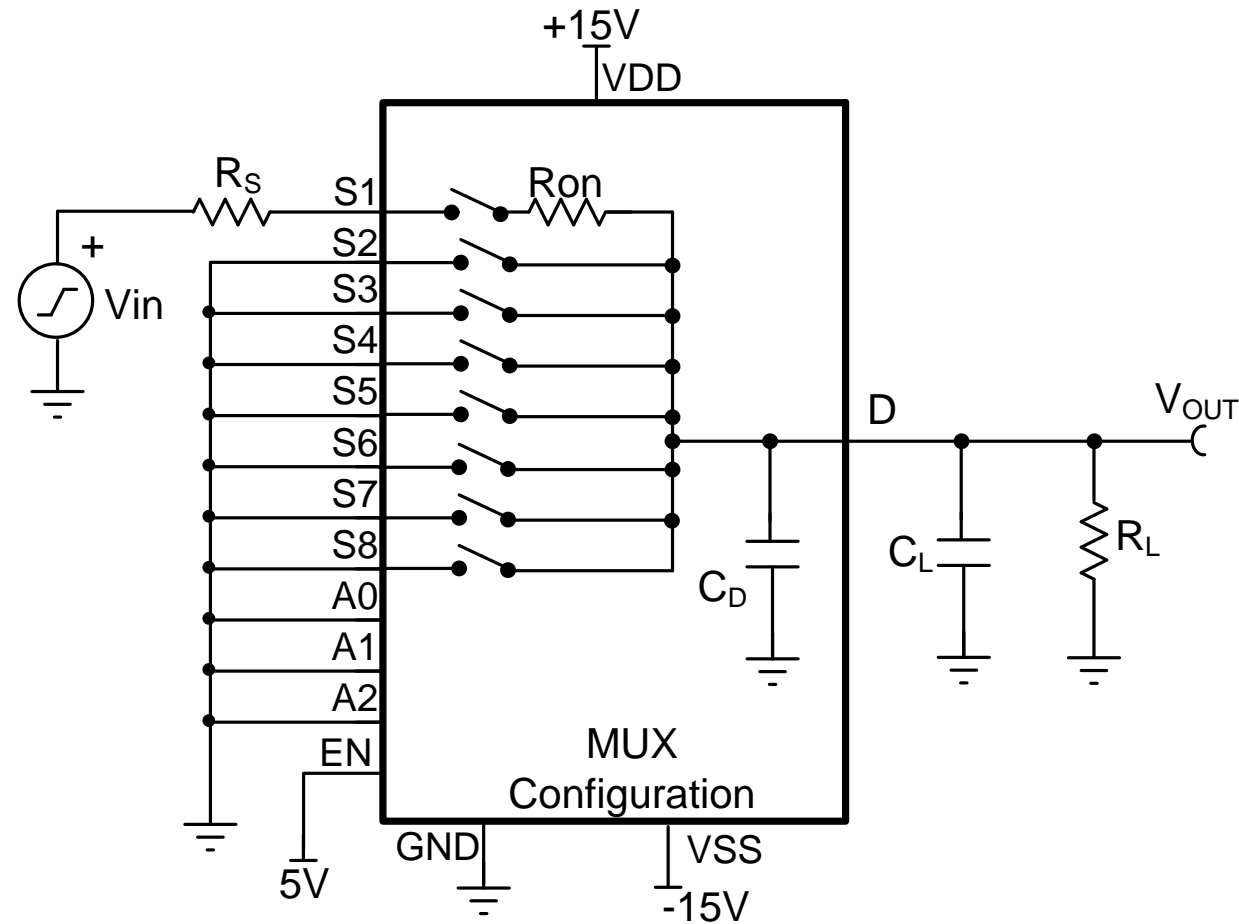

OFF Isolation: voltage at output pin of an multiplexer when a known signal is applied at the source pin of an OFF-channel

OFF Isolation (dB)



$$= 20 * \log \left(\frac{V_{OUT}}{V_{in}} \right)$$

Where



V_{in} : Voltage applied at source pin of off channel

V_{OUT} : Voltage measured at source pin of off channel



OFF Isolation

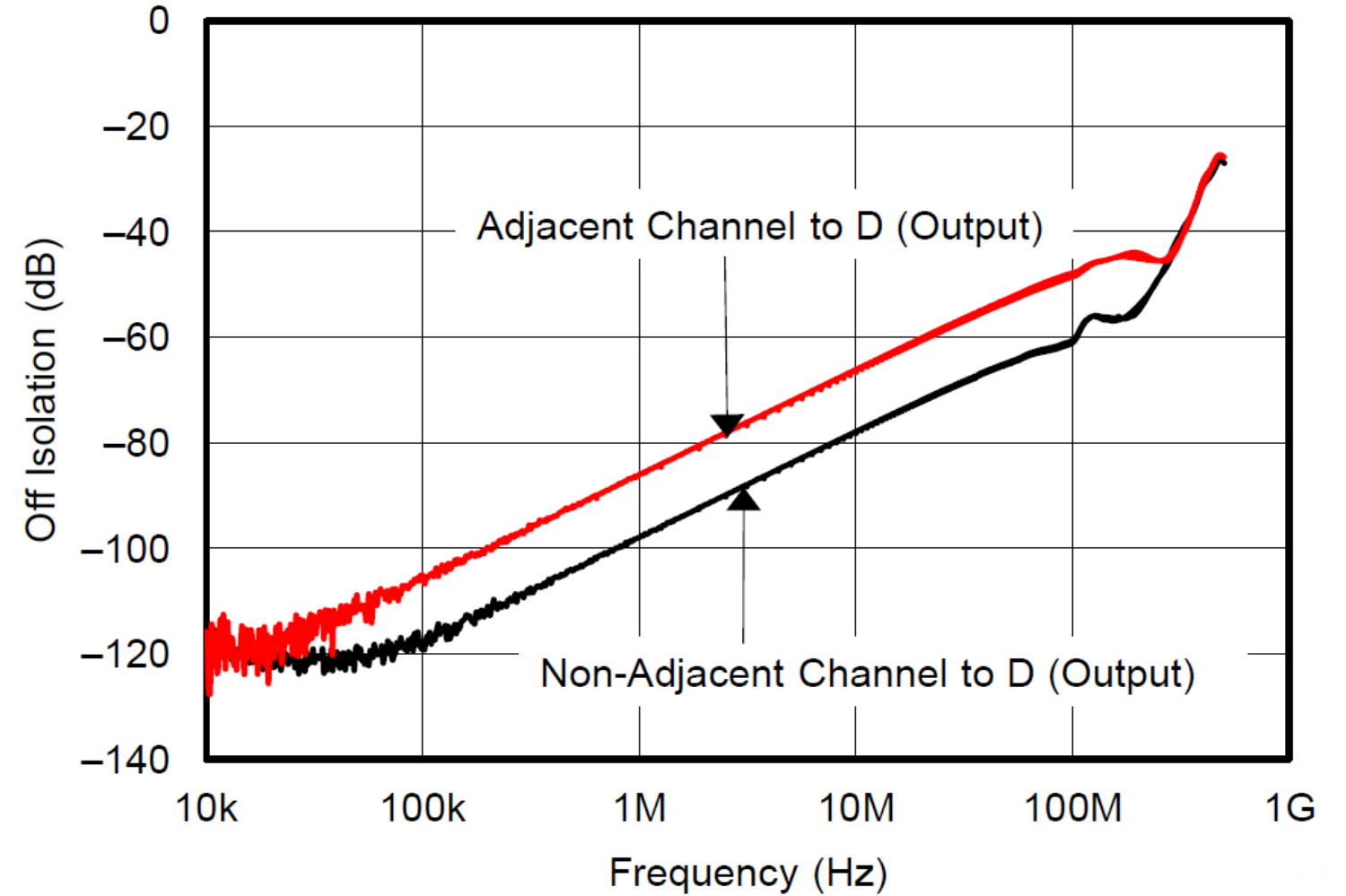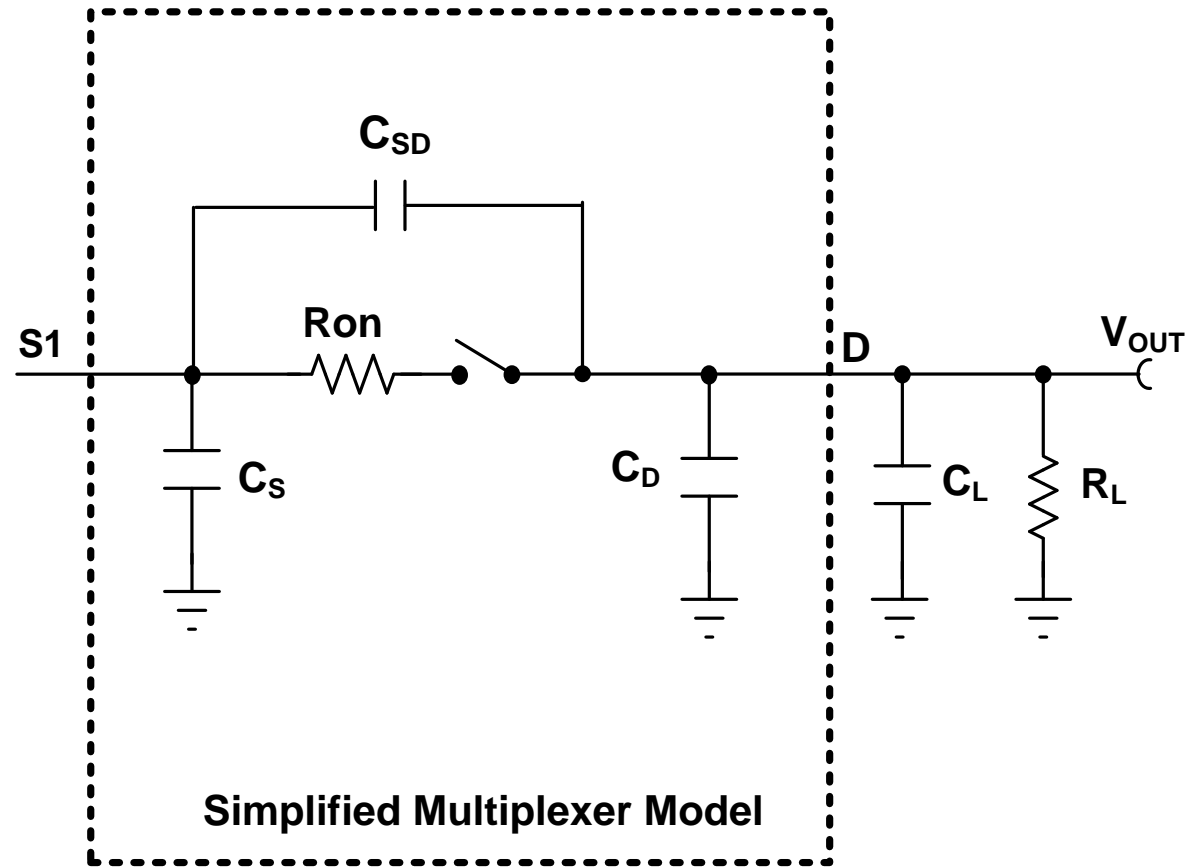

Off Isolation: Adjacent Channels

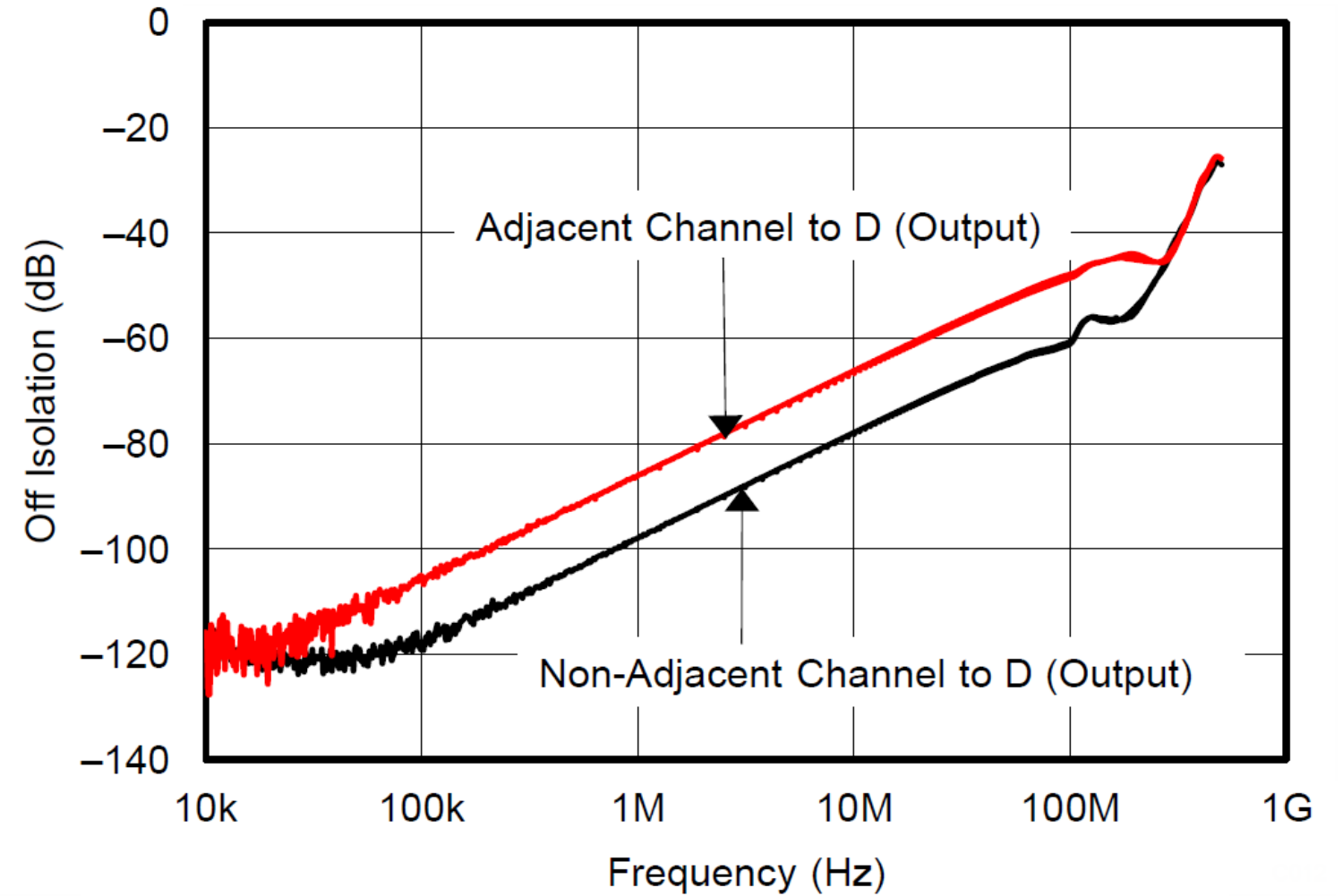
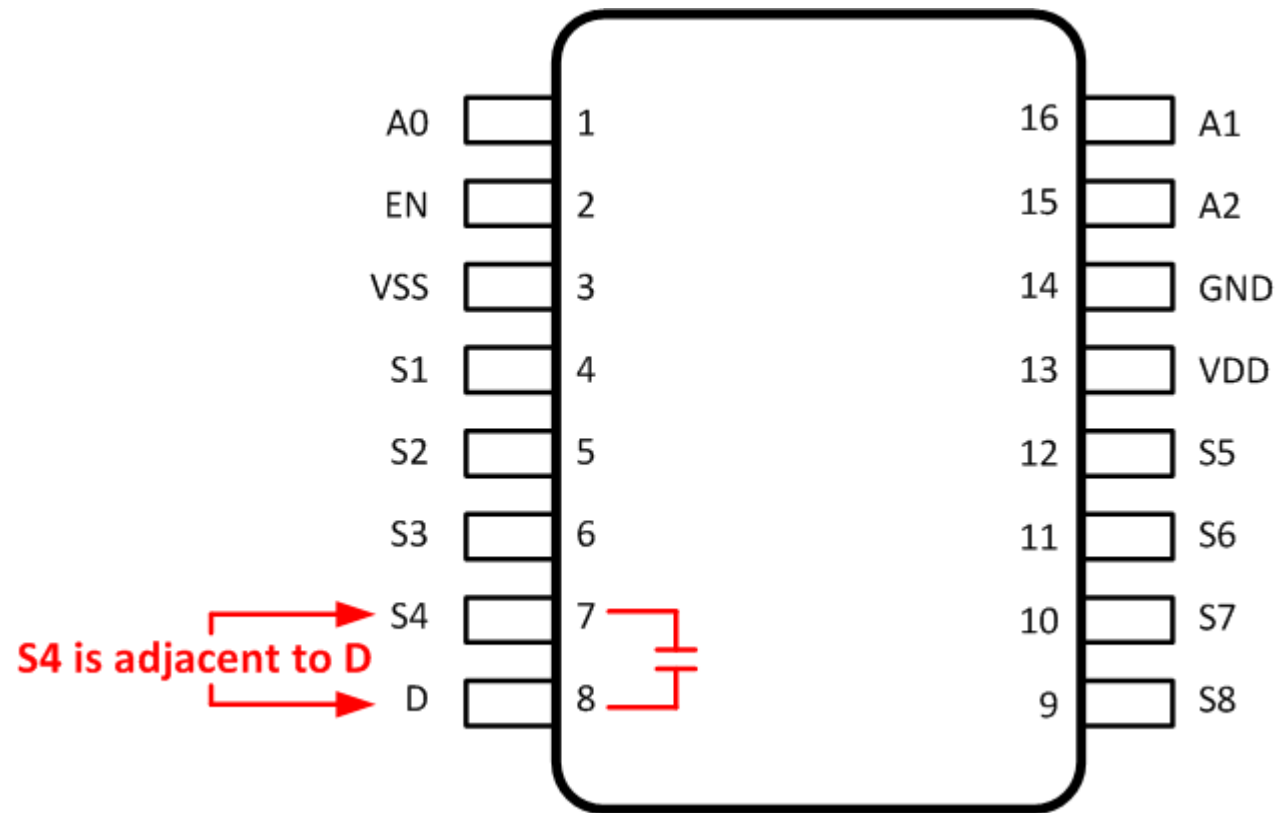


Off Isolation: Example Calculation

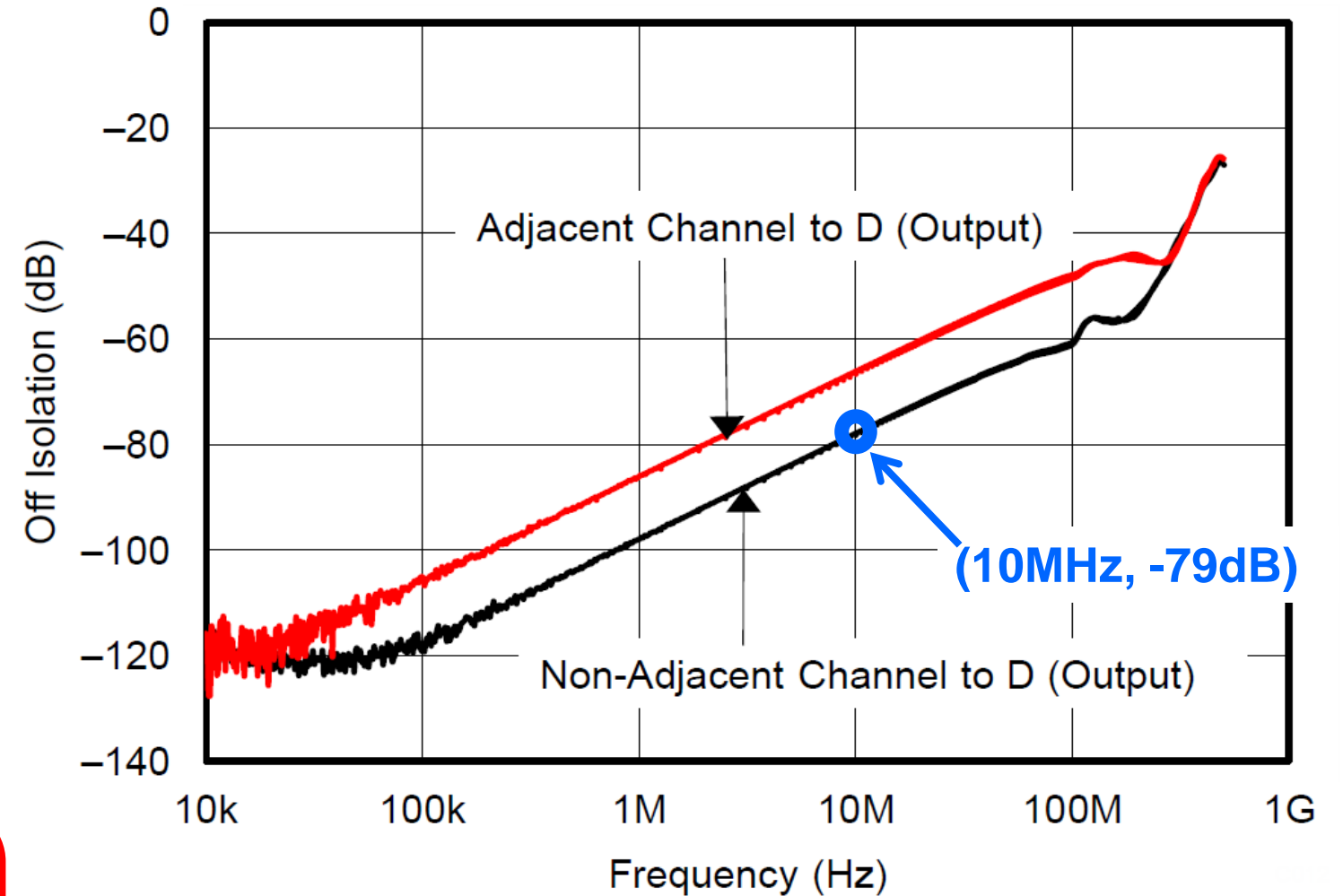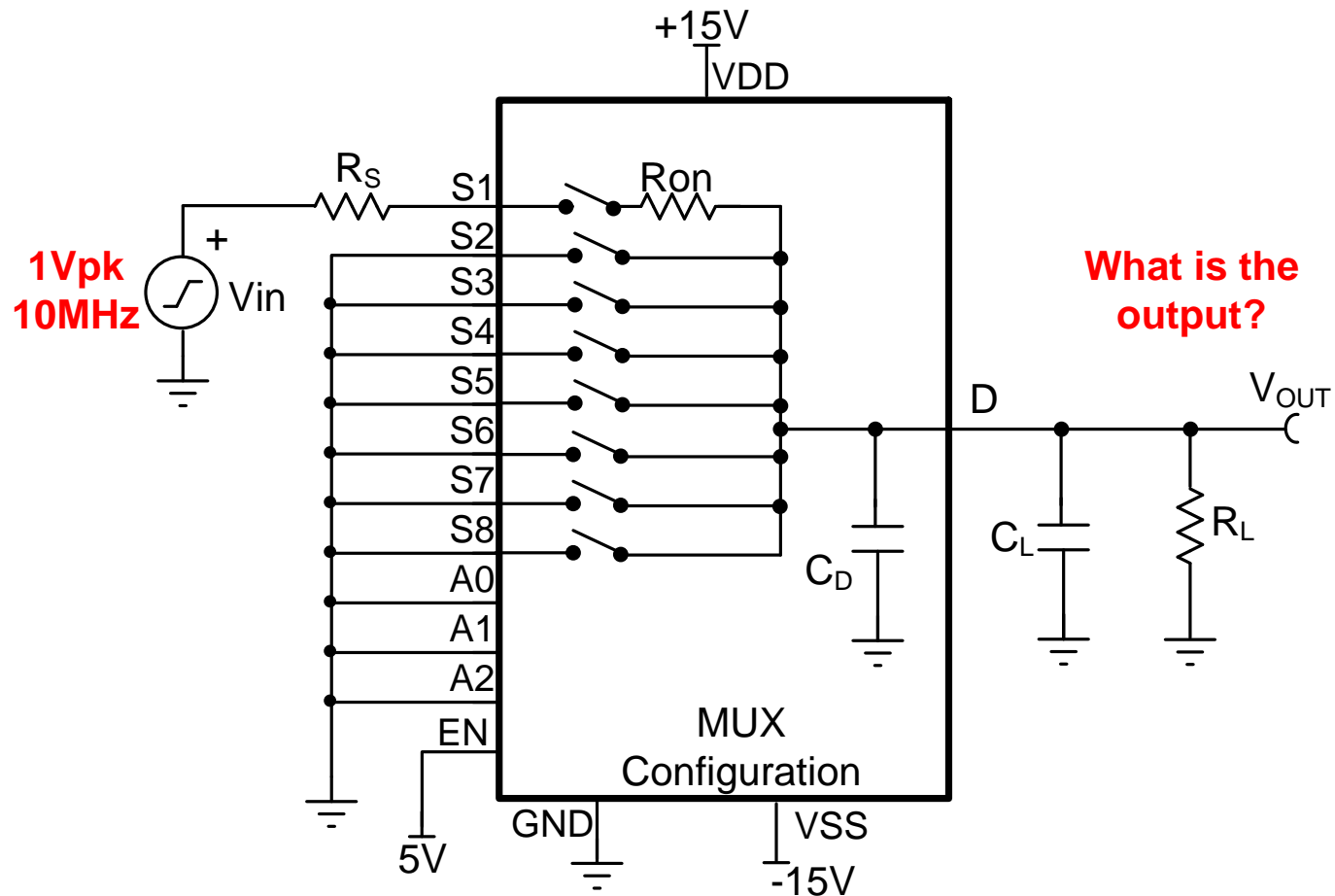

$$V_{OUT} = 1Vpk \cdot 10^{\left(\frac{-79dB}{20}\right)} = 112\mu Vpk$$


Total Harmonic Distortion + Noise: THD+N

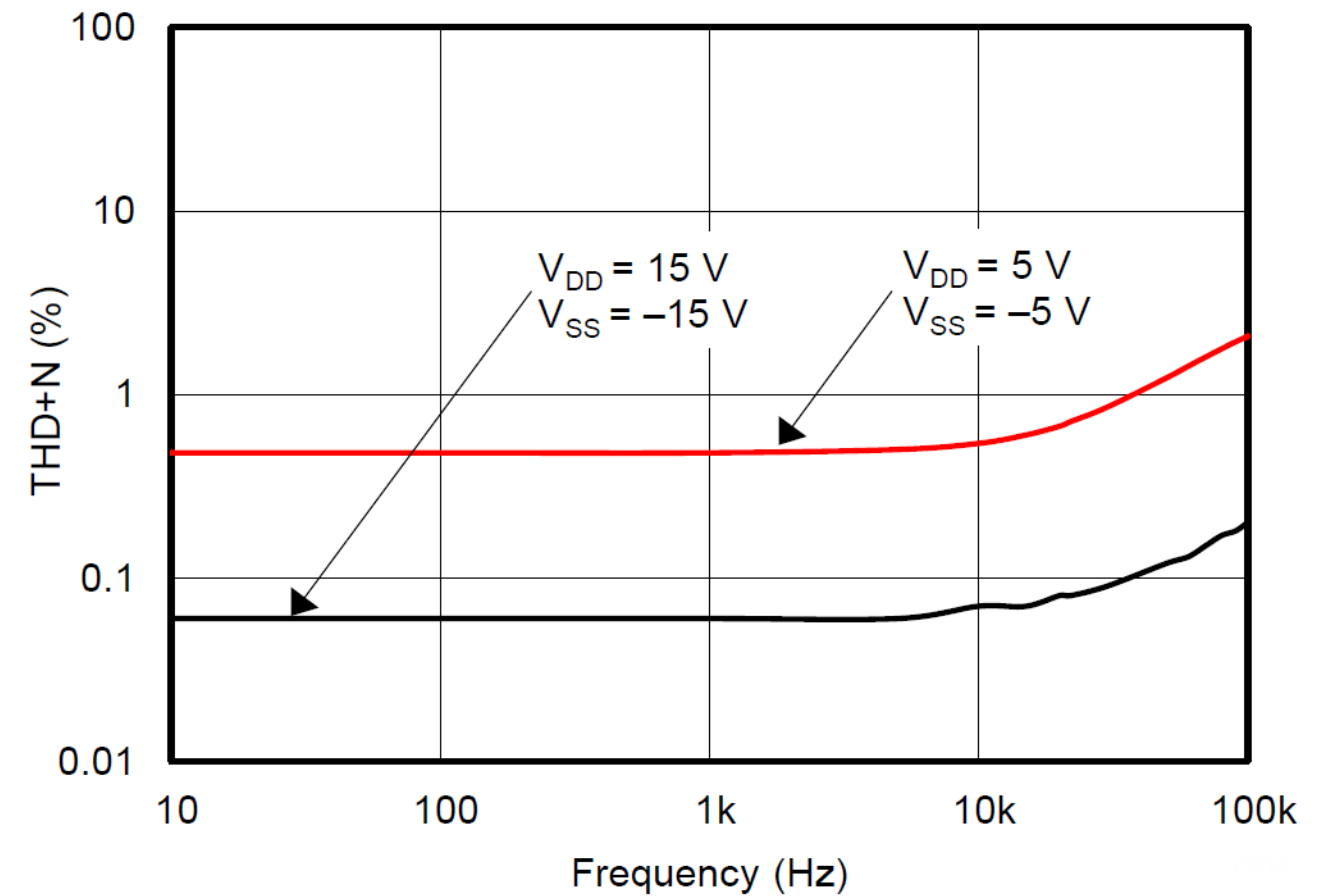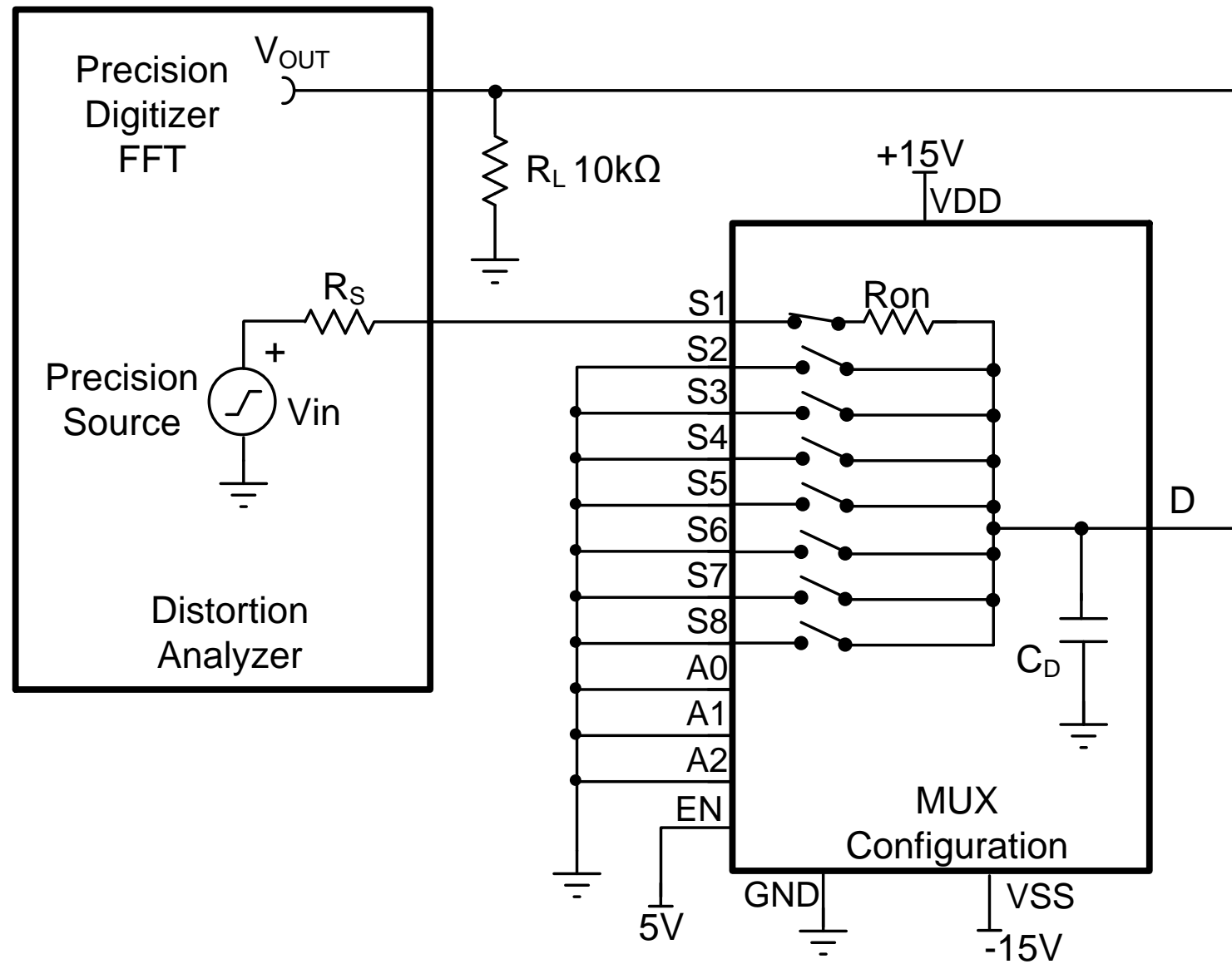

Total Harmonic Distortion + Noise




$$(THD + N)(\%) = 100 \left(\sqrt{\frac{\sum_{i=2}^{\infty} (V_i^2) + V_n^2}{V_f^2}} \right)$$

THD+Noise

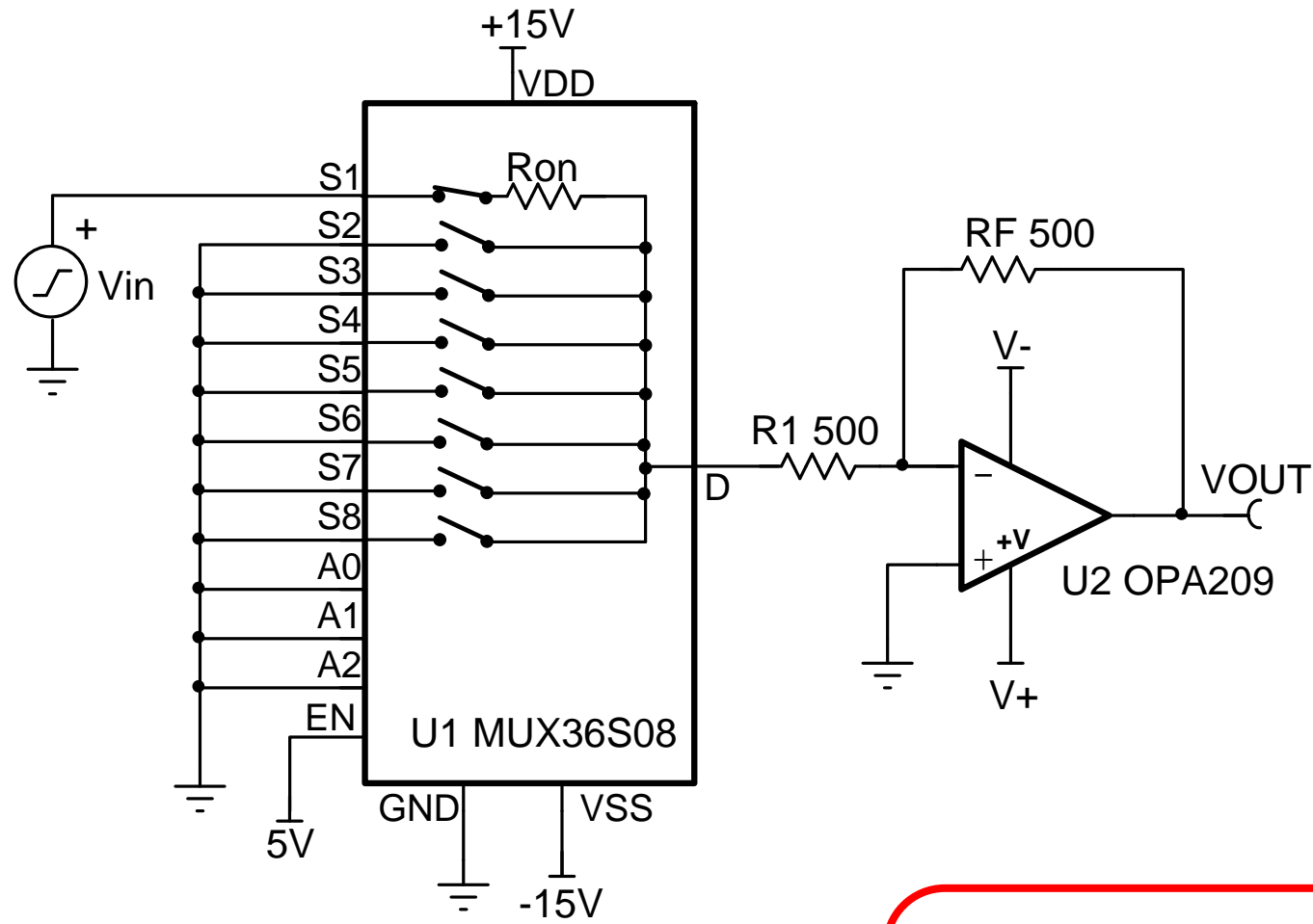

Effective Gain with MUX R_{ON} is:

$$AG = -RF / (R1 + R_{ON})$$

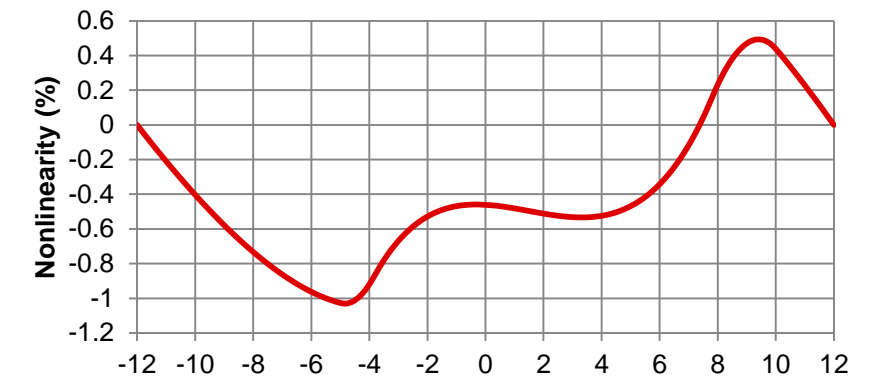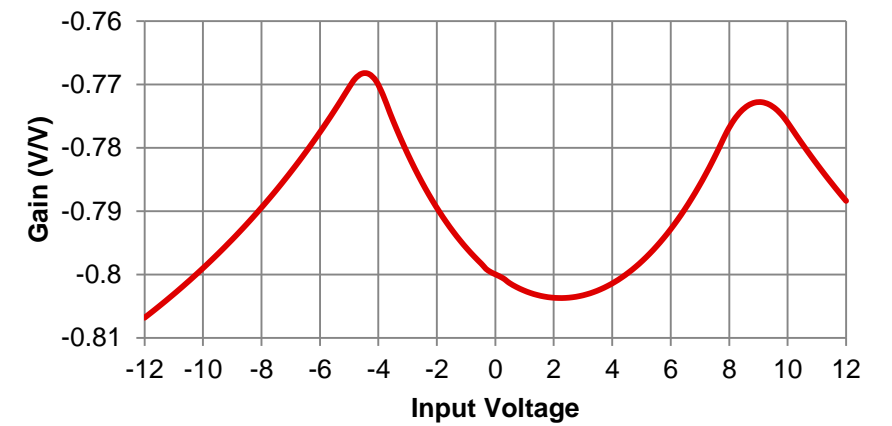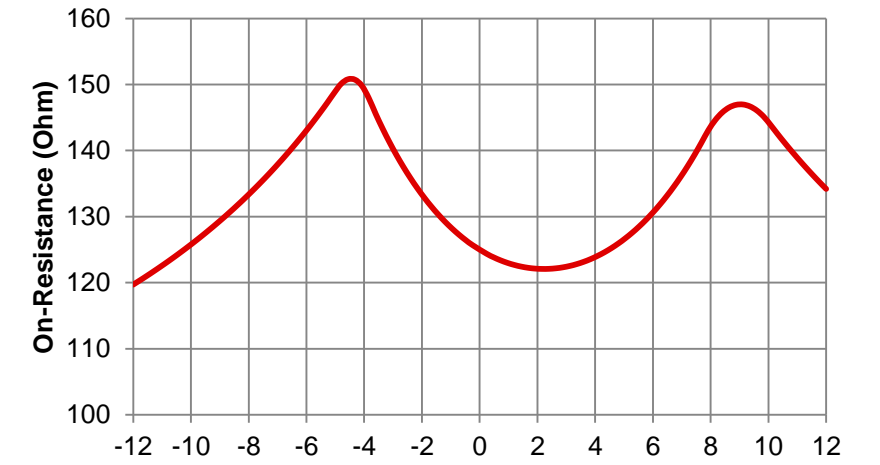

Thanks for your time!
Please try the quiz.