

Basics of Analog Multiplexers 4

TIPL 2604


TI Precision Labs – Op Amps

Prepared by Abhijeet Godbole and Art Kay

Presented by Peggy Liska



Prerequisites: ESD & EOS (TIPL1401 – 1414)

Basic Construction of CMOS Switch

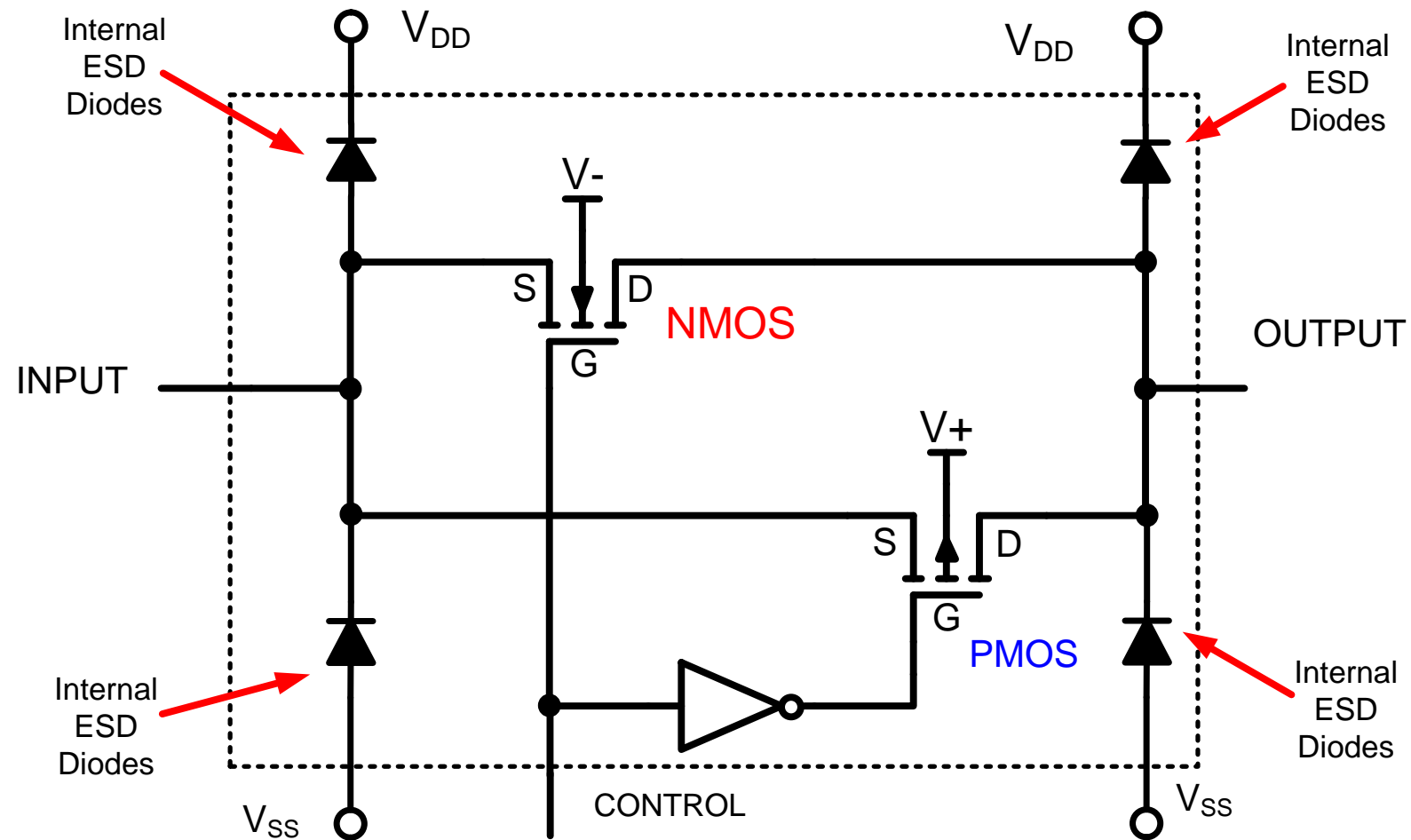


- Parallel combination of N and P channel FET
- Control Signal determines state of the switch
 - Logic High = On
- NMOS impedance = low for negative input
- PMOS impedance = low for positive input
- ESD diodes protect internal circuit from electrostatic discharge

Parasitic Latch-Up in CMOS Switches

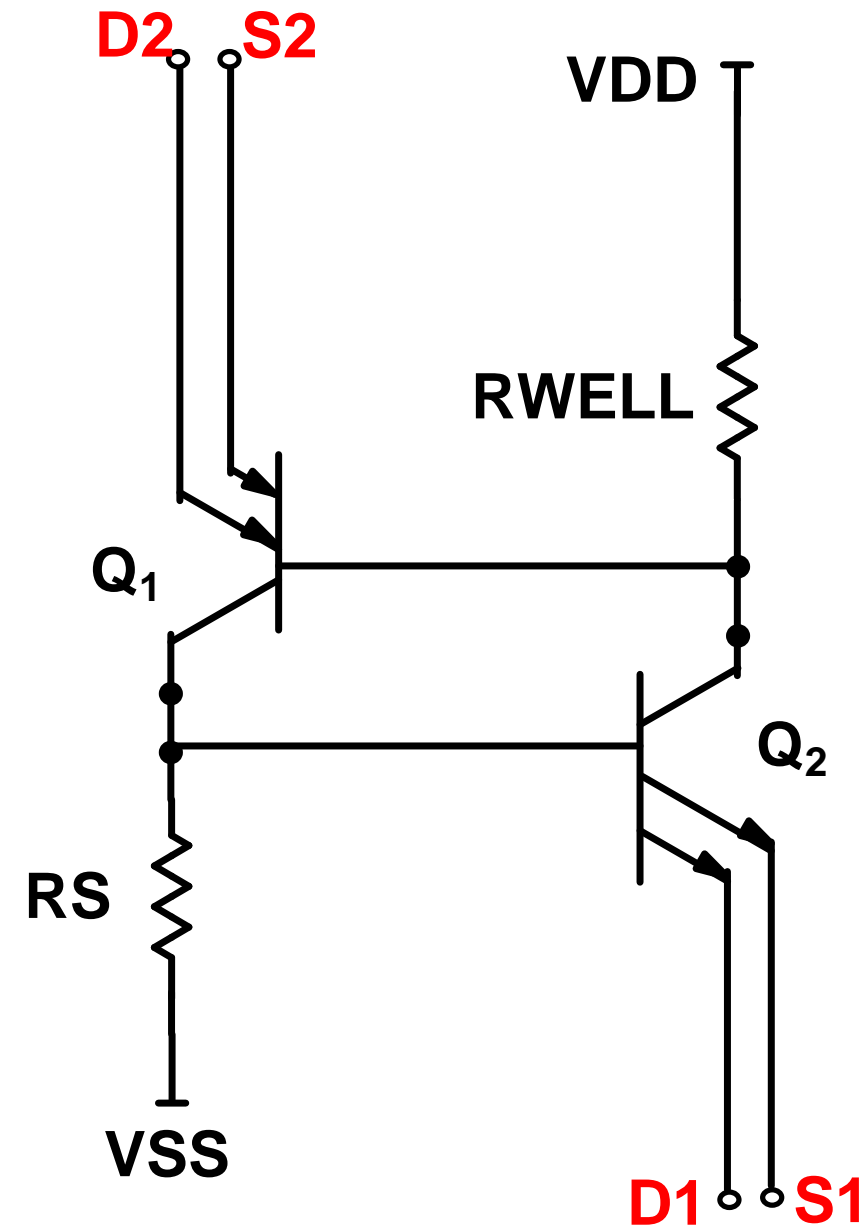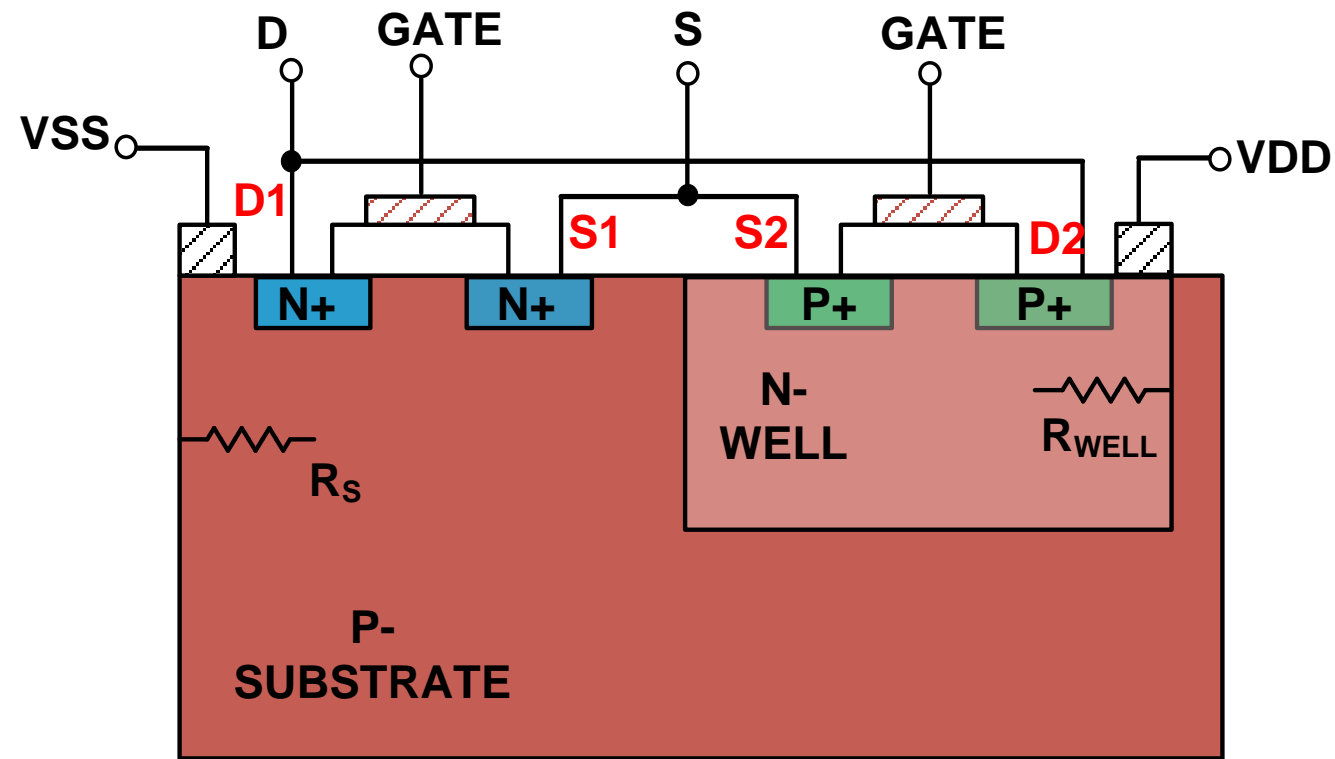


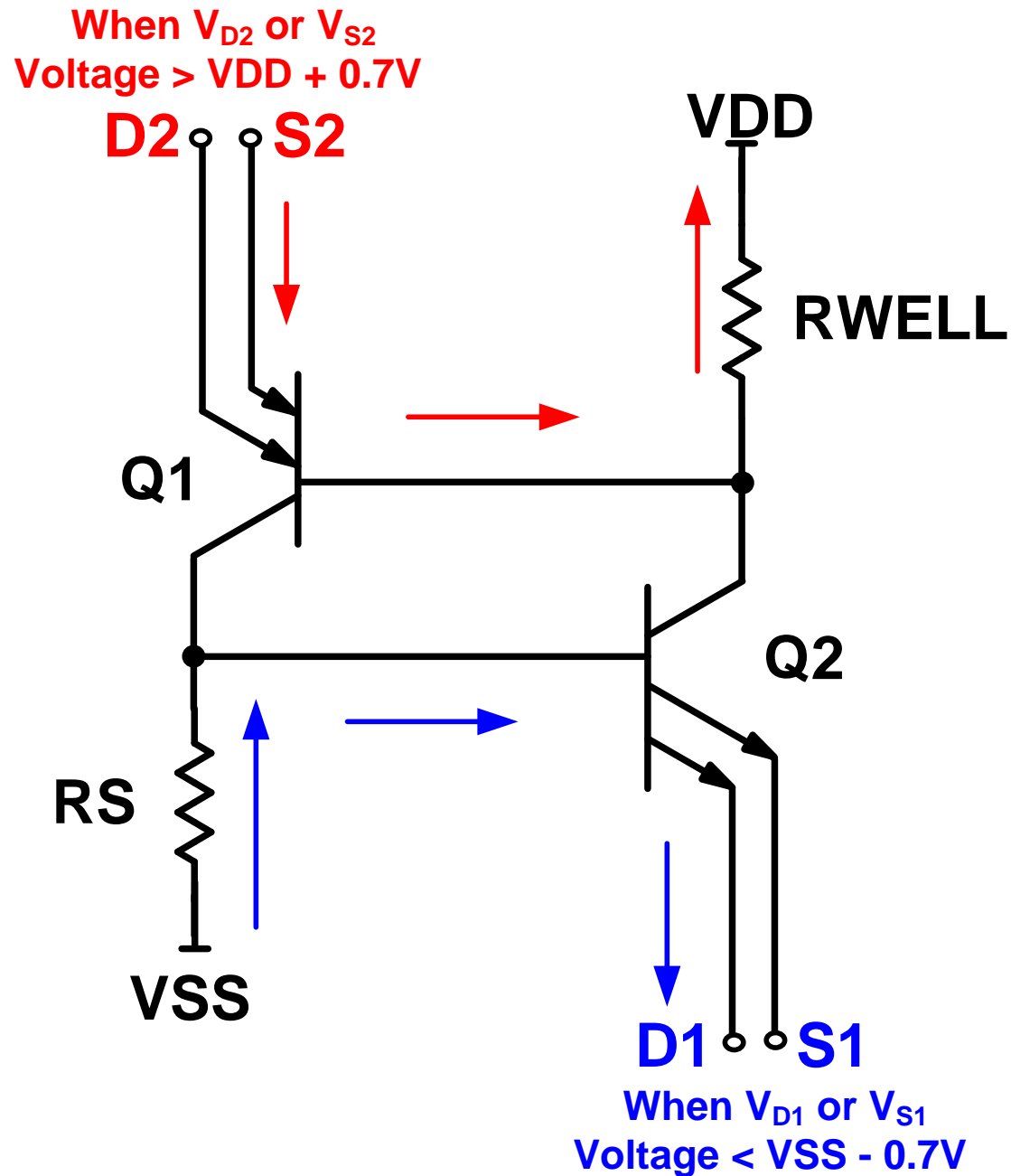Parasitic Latch-Up in CMOS Switches: SCR Latch



- The parasitic SCR mechanism is shown in here.
- SCR action takes place when either terminal of the switch (source or the drain) is either one diode drop more positive than V_{DD} or one diode drop more negative than V_{SS} .
- Once Triggered, high current will flow between the supplies.


Series Diode Protection Against Latch up

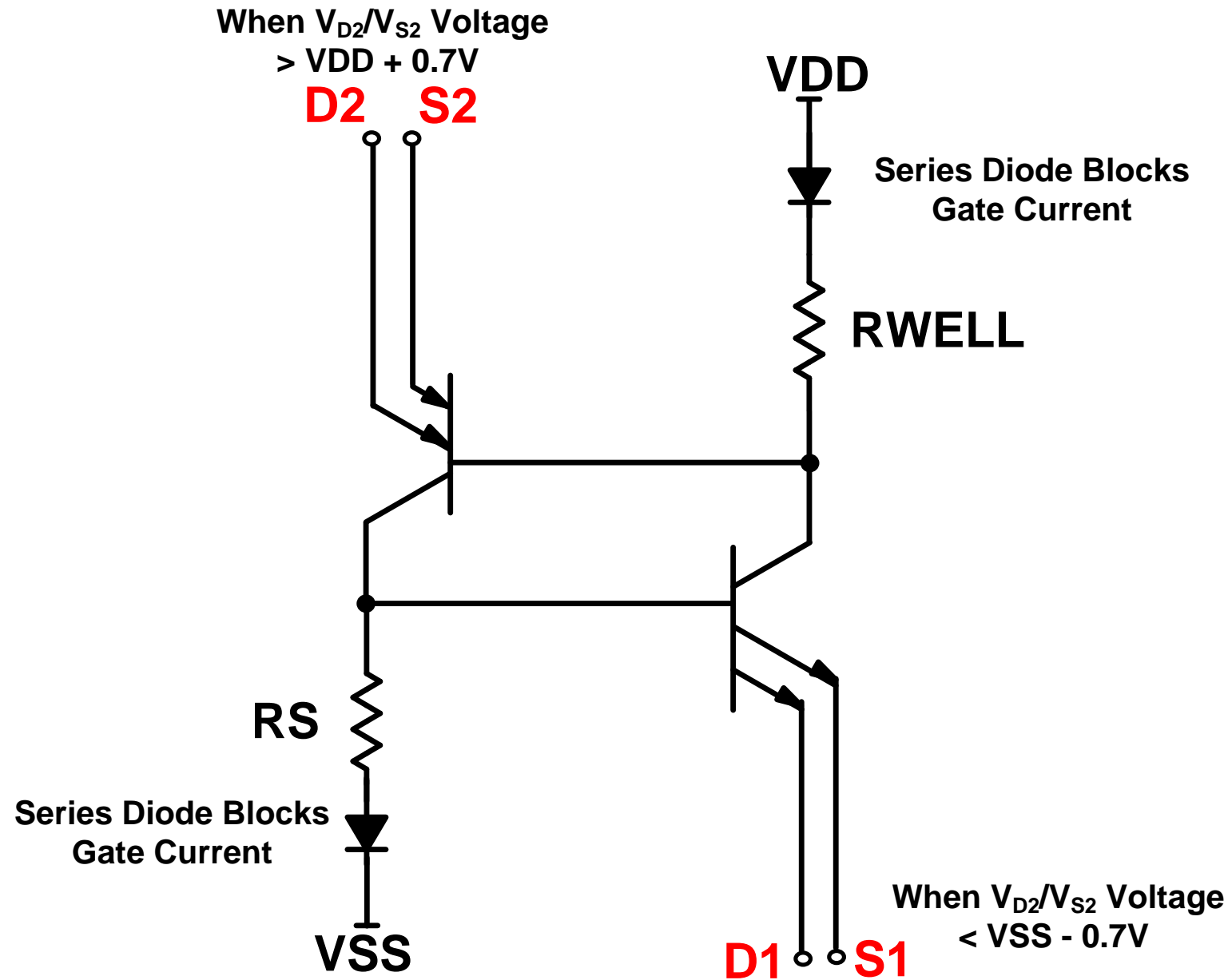


- Series diodes used in VDD and VSS path prevents latch up
- These diodes does not allow reverse gate current to flow in case of over voltage condition
- Input voltage swing limits to
$$V_{IN} \leq V_{DD} - 0.7V \text{ (Typical)}$$
$$V_{IN} \geq V_{SS} + 0.7V \text{ (Typical)}$$
- Reverse voltage of diodes should be greater than maximum over voltage input range

A short background on TVS diodes

Bidirectional

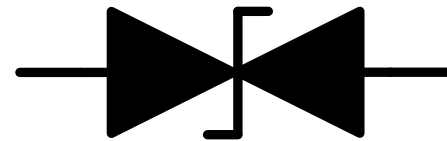

Unidirectional

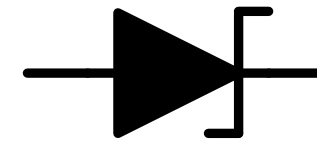

Symbol

V_{BR}

Parameter

Breakdown voltage

V_R

Stand-off voltage

V_C

Clamping voltage

V_F

Forward voltage drop

I_{BR}

Breakdown Current @ V_{BR}

I_R



Reverse Leakage @ V_R

I_F


Forward Current @ V_F

I_{PP}

Peak Pulse current @ V_C

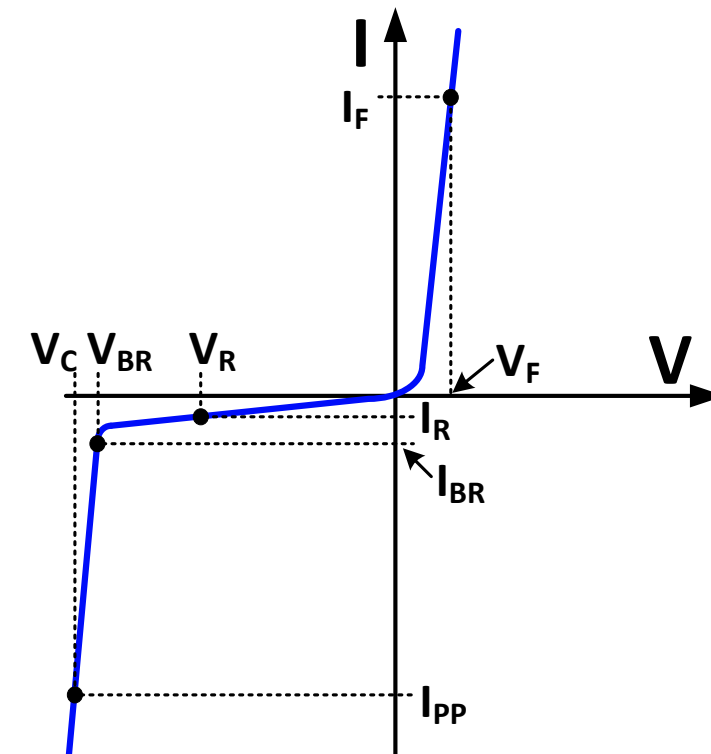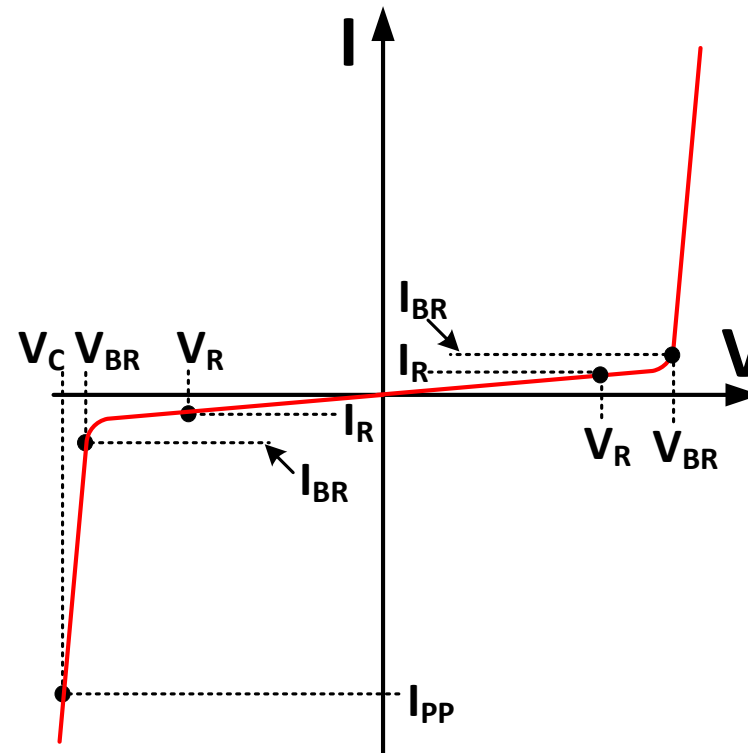

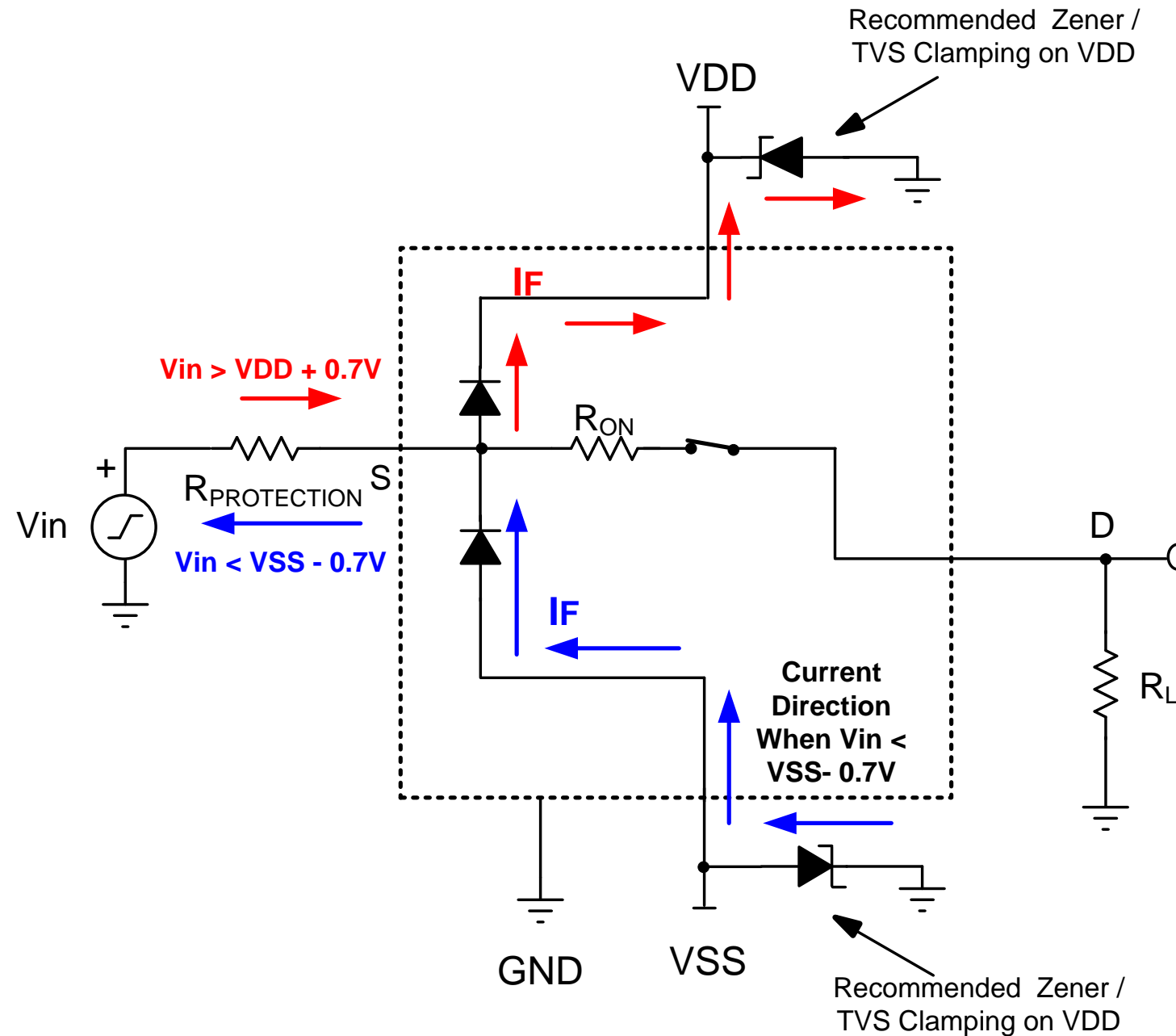Internal ESD Diode & Resistor as EOS Protection



$R_{PROTECTION}$ Example Calculation

$$V_{DD} = +15V \quad V_{SS} = -15V$$

$$V_{OVER \ VOLTAGE} \text{ at Input Channel} = (+/-) 20V$$

Let's say internal ESD diode current should not exceed 5mA.

$$I_{LIMIT} = 5mA$$



$$R_{PROTECTION} = \frac{V_{IN} - V_{DD} - V_{BE}}{I_{LIMIT}}$$

$$R_{PROTECTION} = \frac{20V - 15V - 0.7V}{5mA}$$



$$= 860 \text{ Ohm.}$$

Choose 910 Ohms - Standard Value


MUX36S08 Over voltage Fault Performance

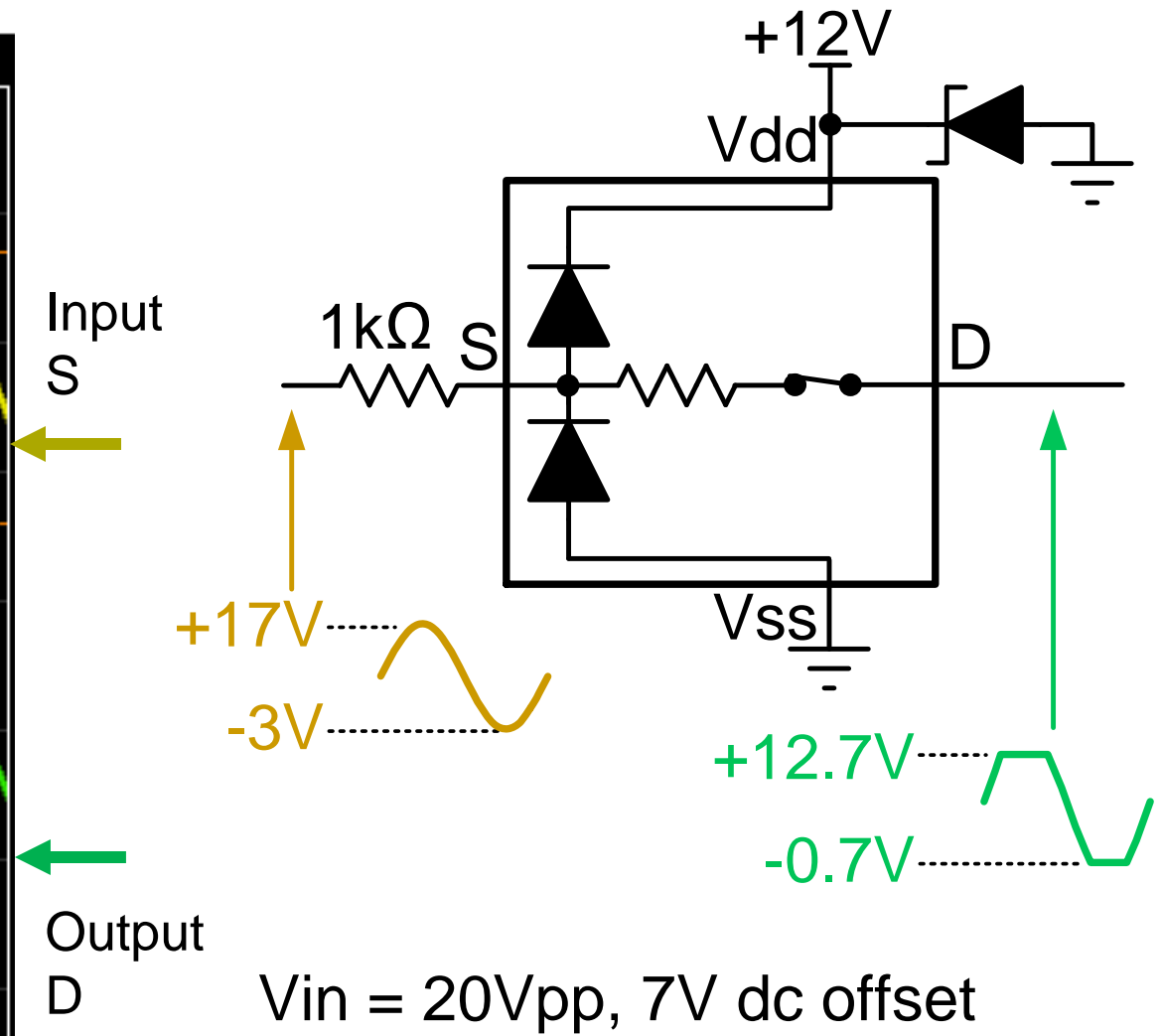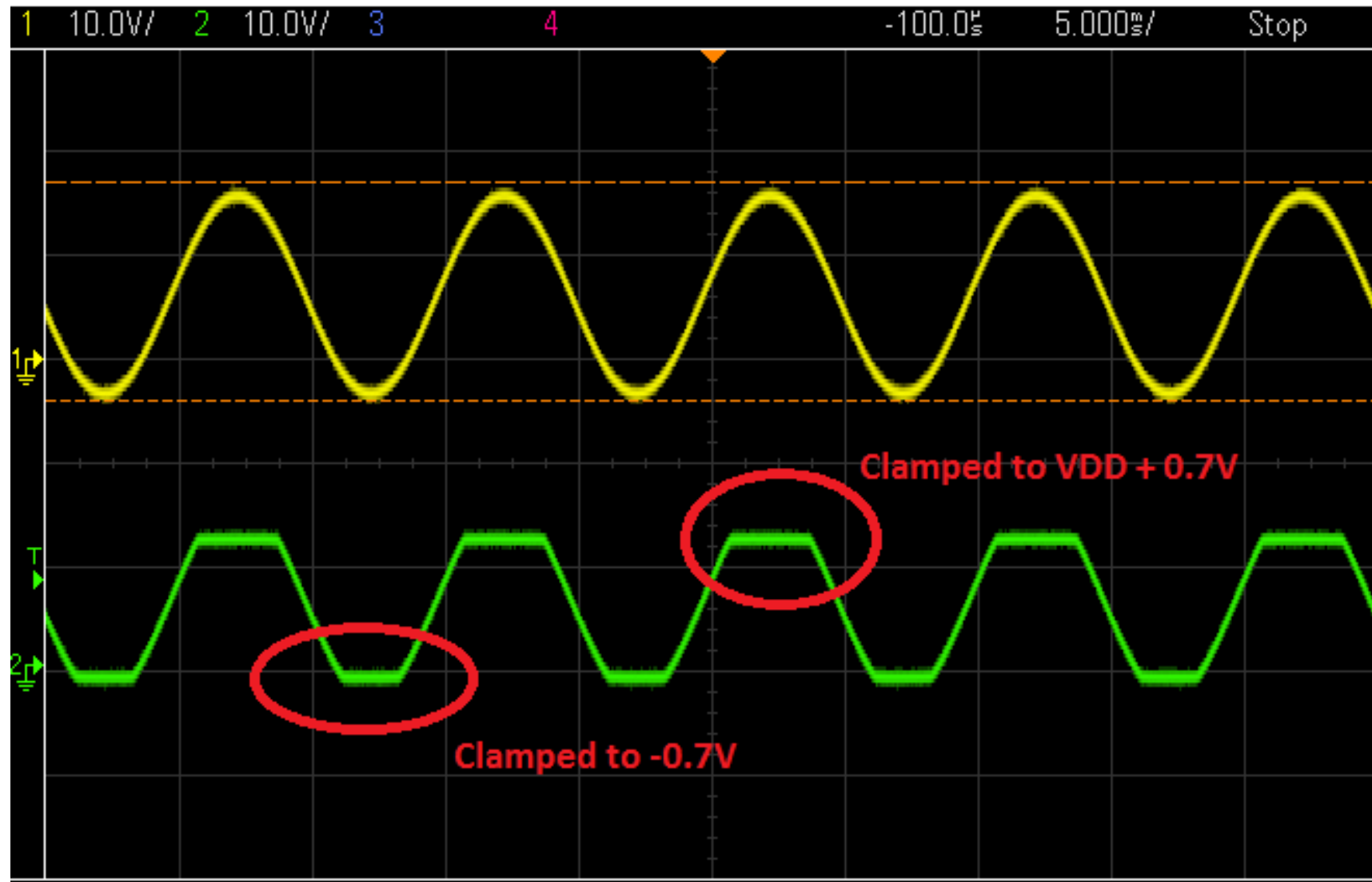


MUX36S08 Over voltage Fault Performance

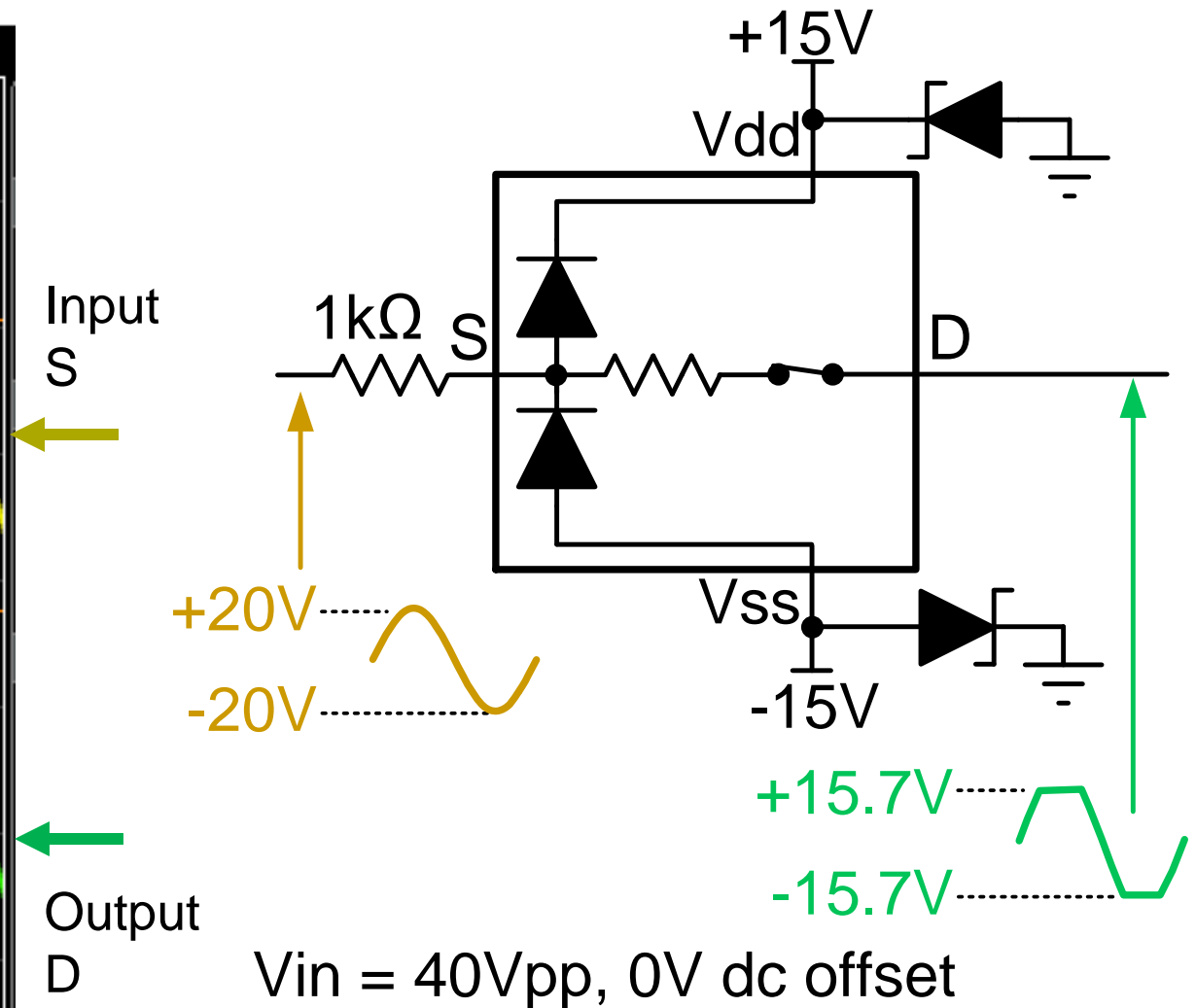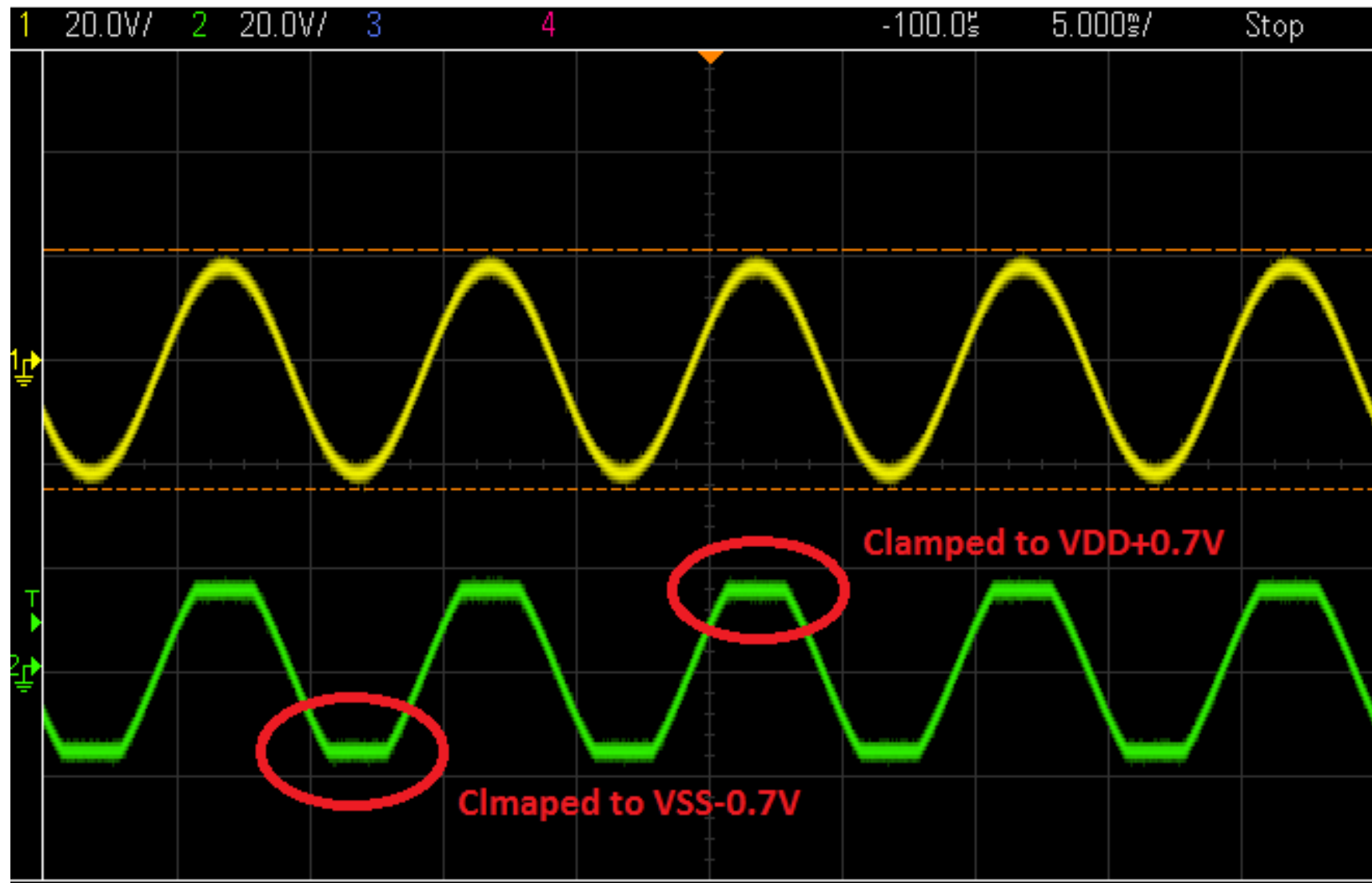


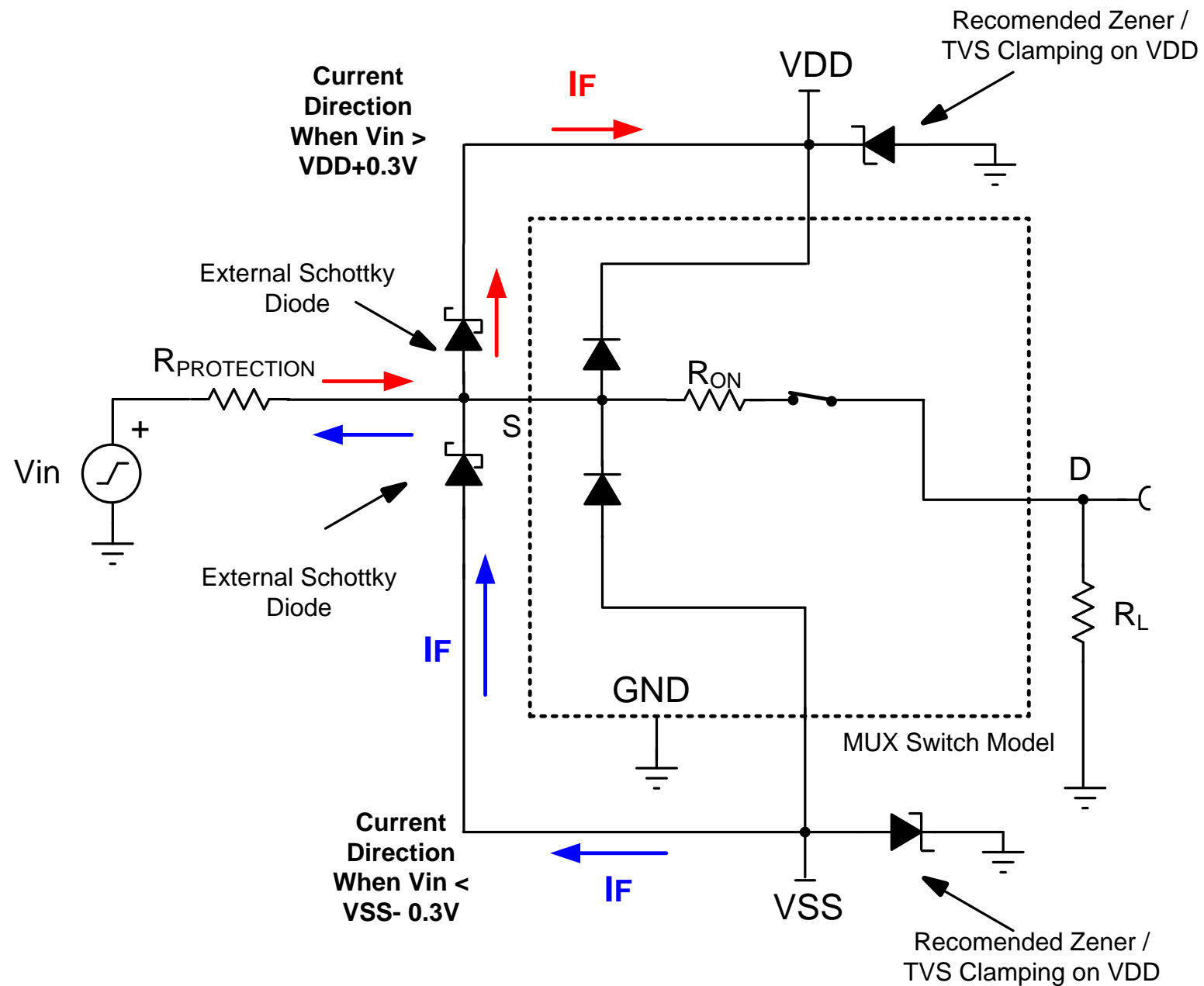
Using External Clamping Diode as EOS Protection




Over Voltage Applied on OFF Channel

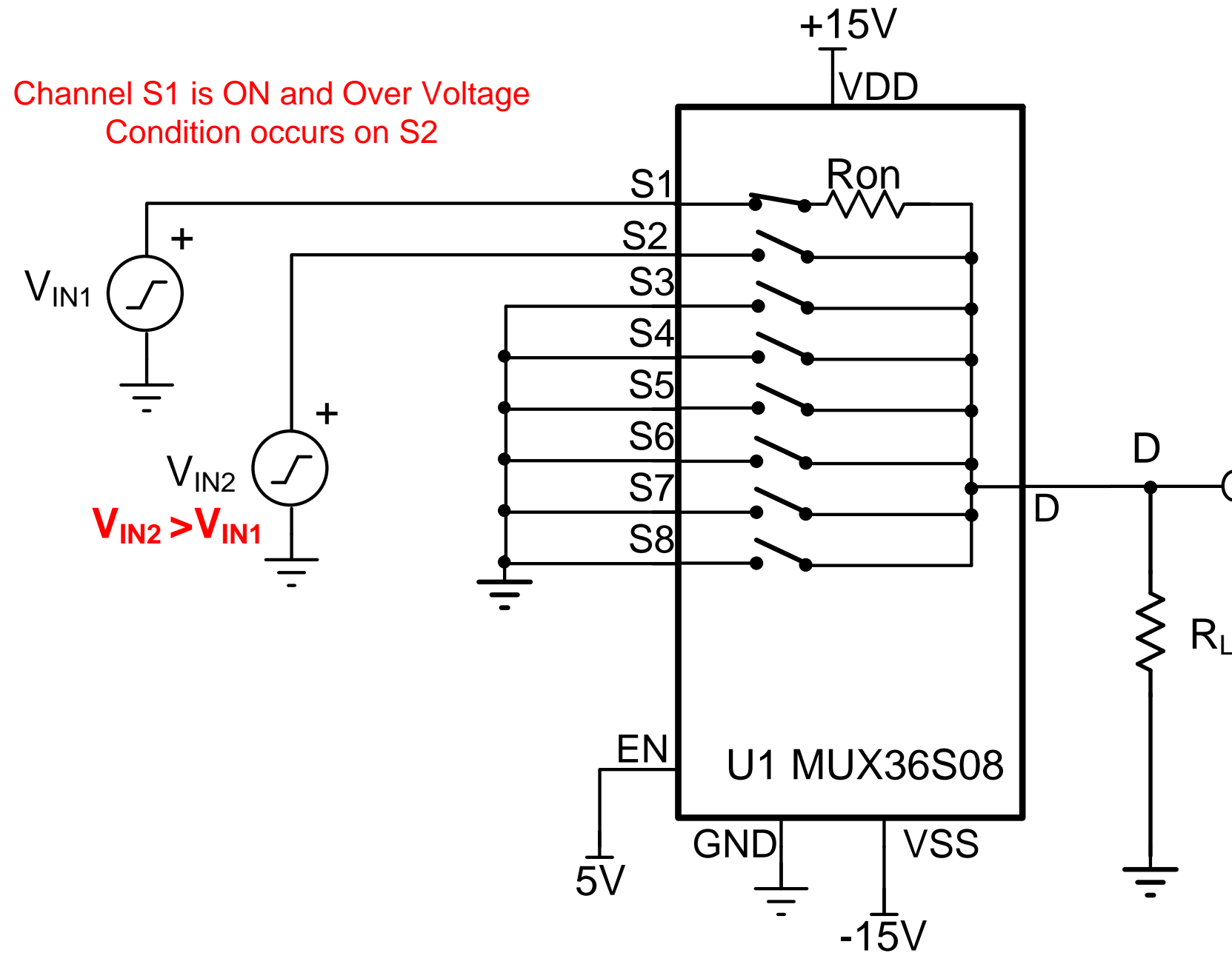

MUX36S08 Over voltage Fault Performance

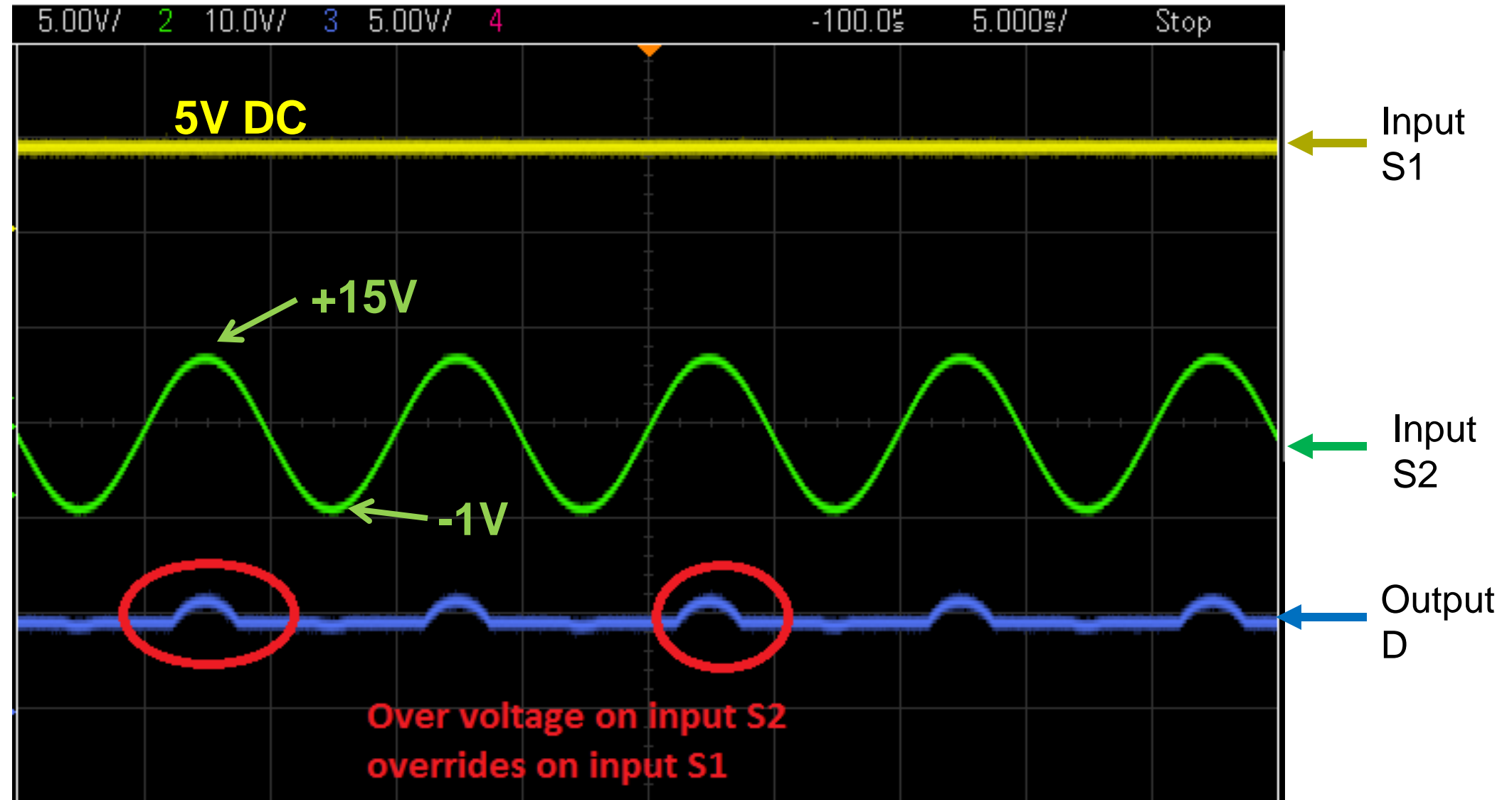
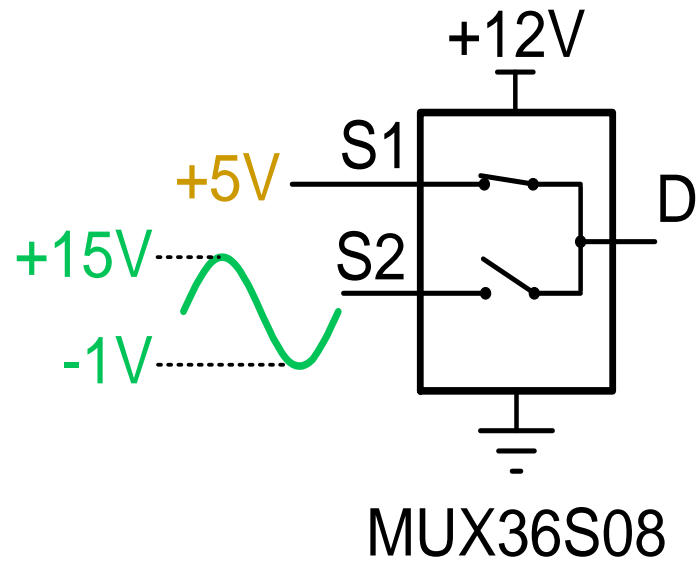


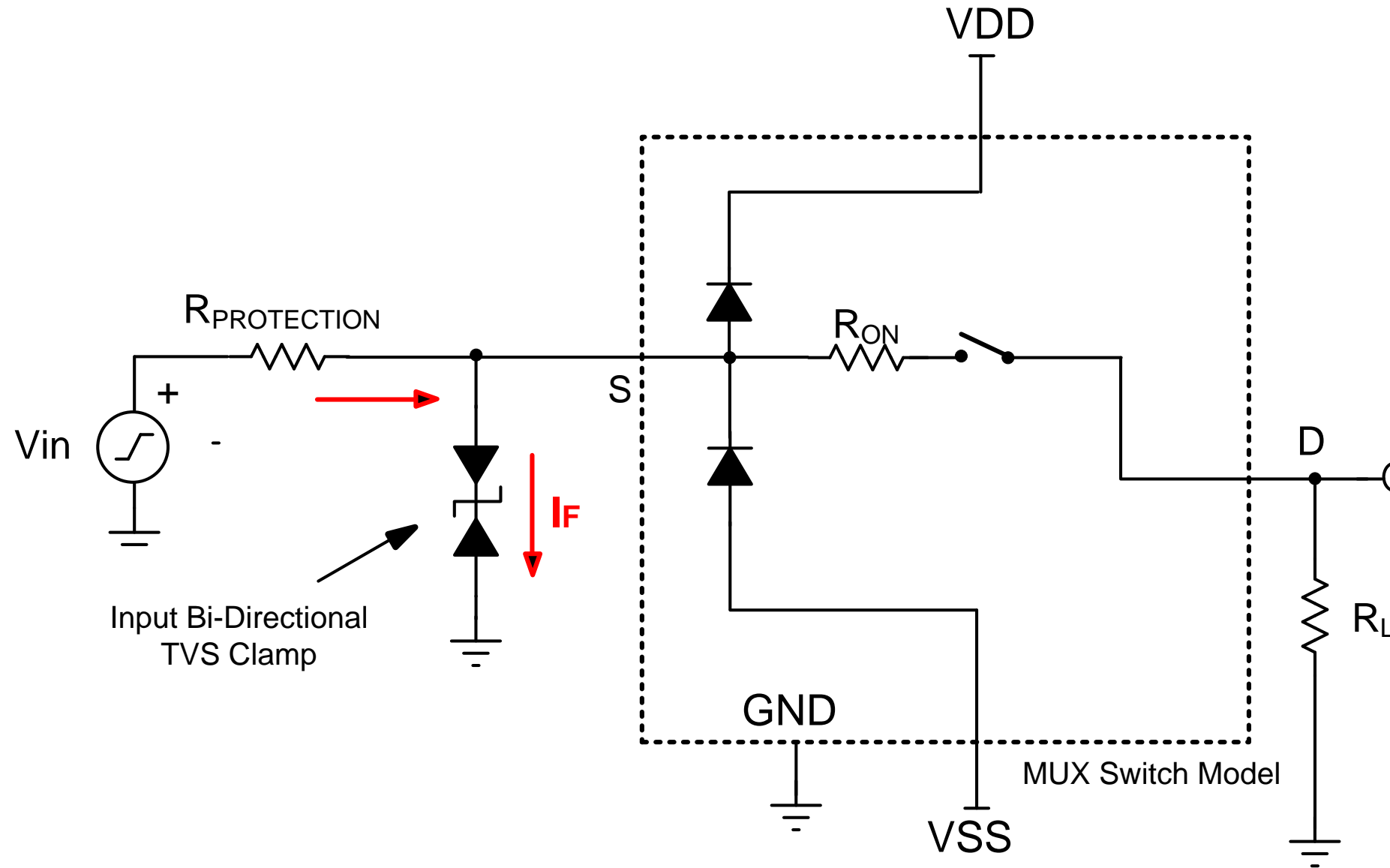Zener/TVS clamping at Input as EOS Protection



- Input voltage clamped using zener or TVS diode
- Series resistor acts as a current limiting resistor
- For Unipolar operation, Zener diode or unidirectional TVS diode can work
- For Bipolar operation Bi-directional TVS diode has to be selected

MUX36S08 Over voltage Fault Performance

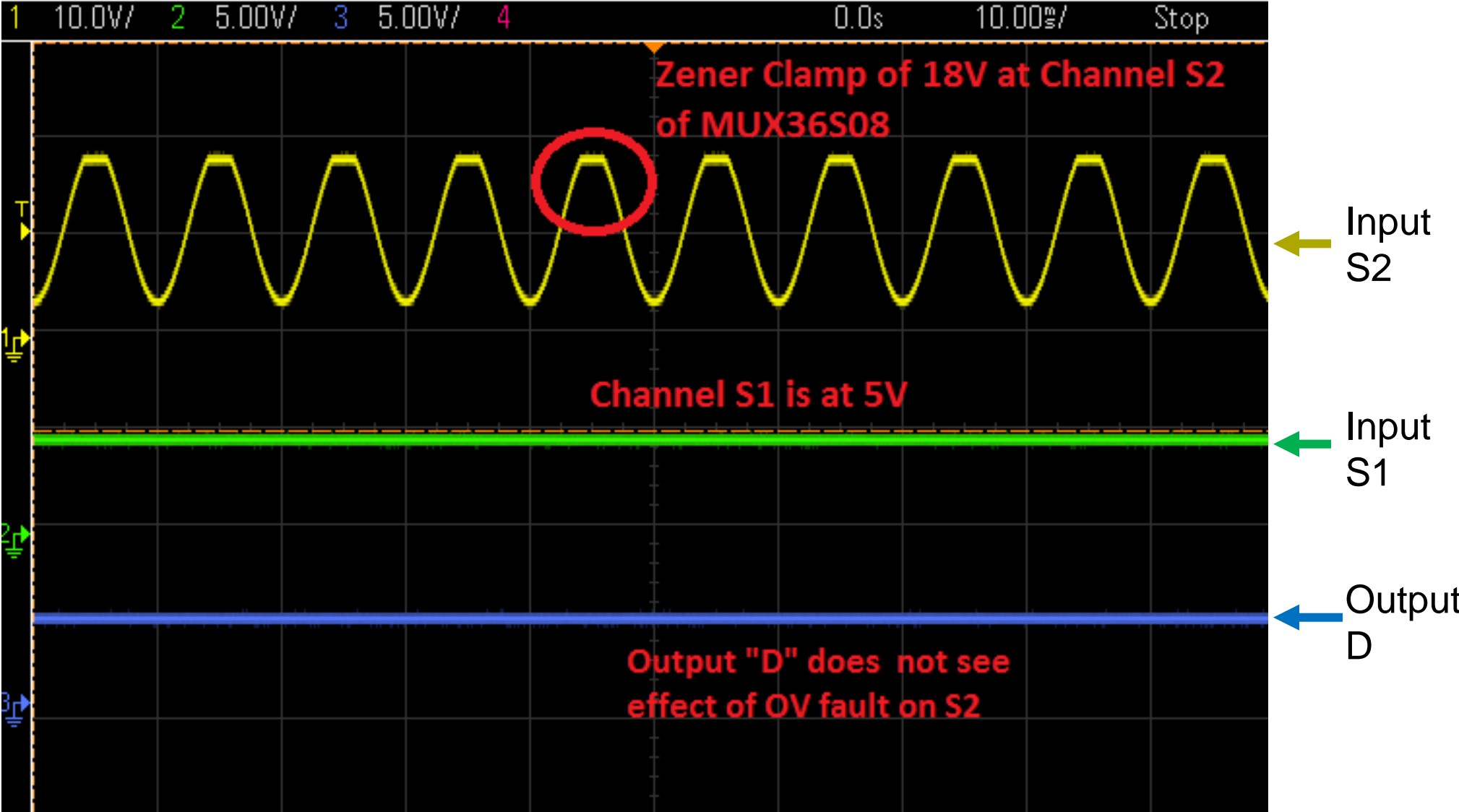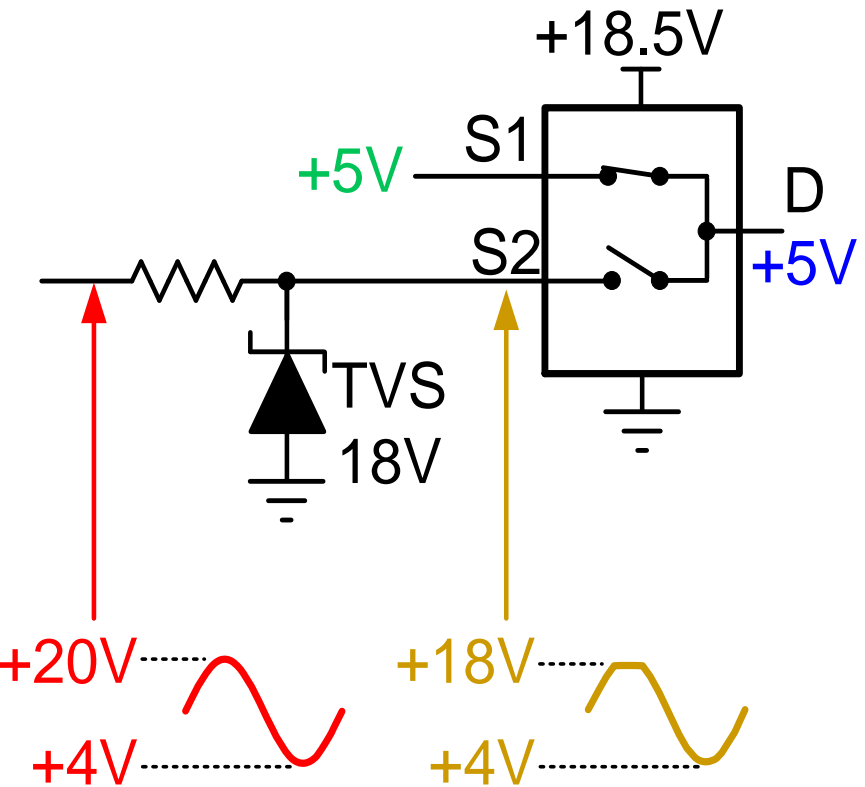

Thanks for your time!
Please try the quiz.