

# Quiz: Instrumentation Amplifier (IA) topologies: three-amp

TI Precision Labs – Instrumentation Amplifiers


Presented by Tamara Alani

Prepared by Tamara Alani

# Quiz: (IA) topologies: three-amp || Question

1. What are two challenges associated with the discrete one-amp IA topology?

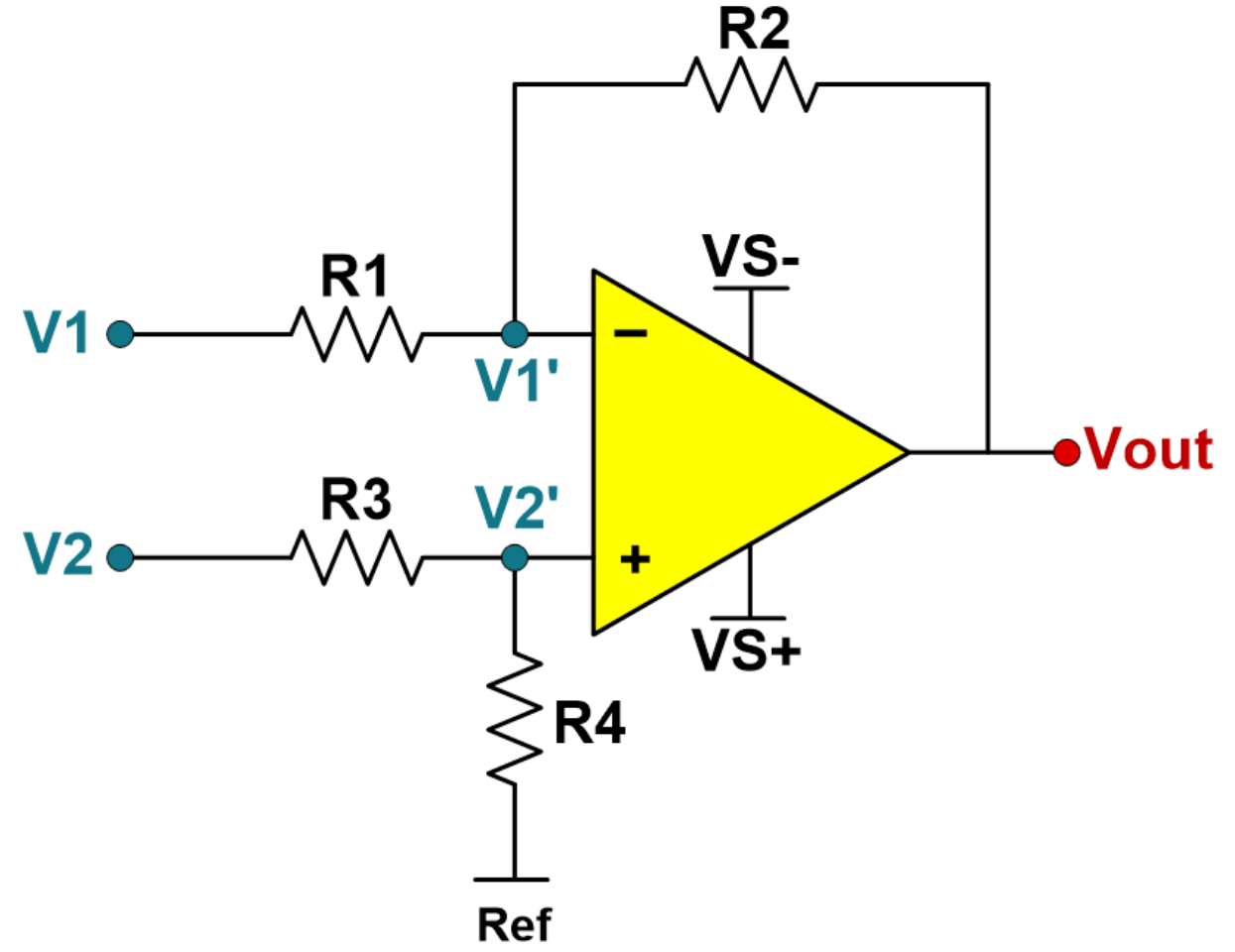
- a) The one-amp IA consumes more power
- b) The one-amp IA has low input impedance
- c) The one-amp IA must have precision-matched resistors for high accuracy
- d) The one-amp IA has fixed gain
- e) The one-amp IA can only be used for mV-level input signals
- f) b & e
- g) c & a
- h) b & c



# Quiz: (IA) topologies: three-amp || Answer

1. What are two challenges associated with the discrete one-amp IA topology?

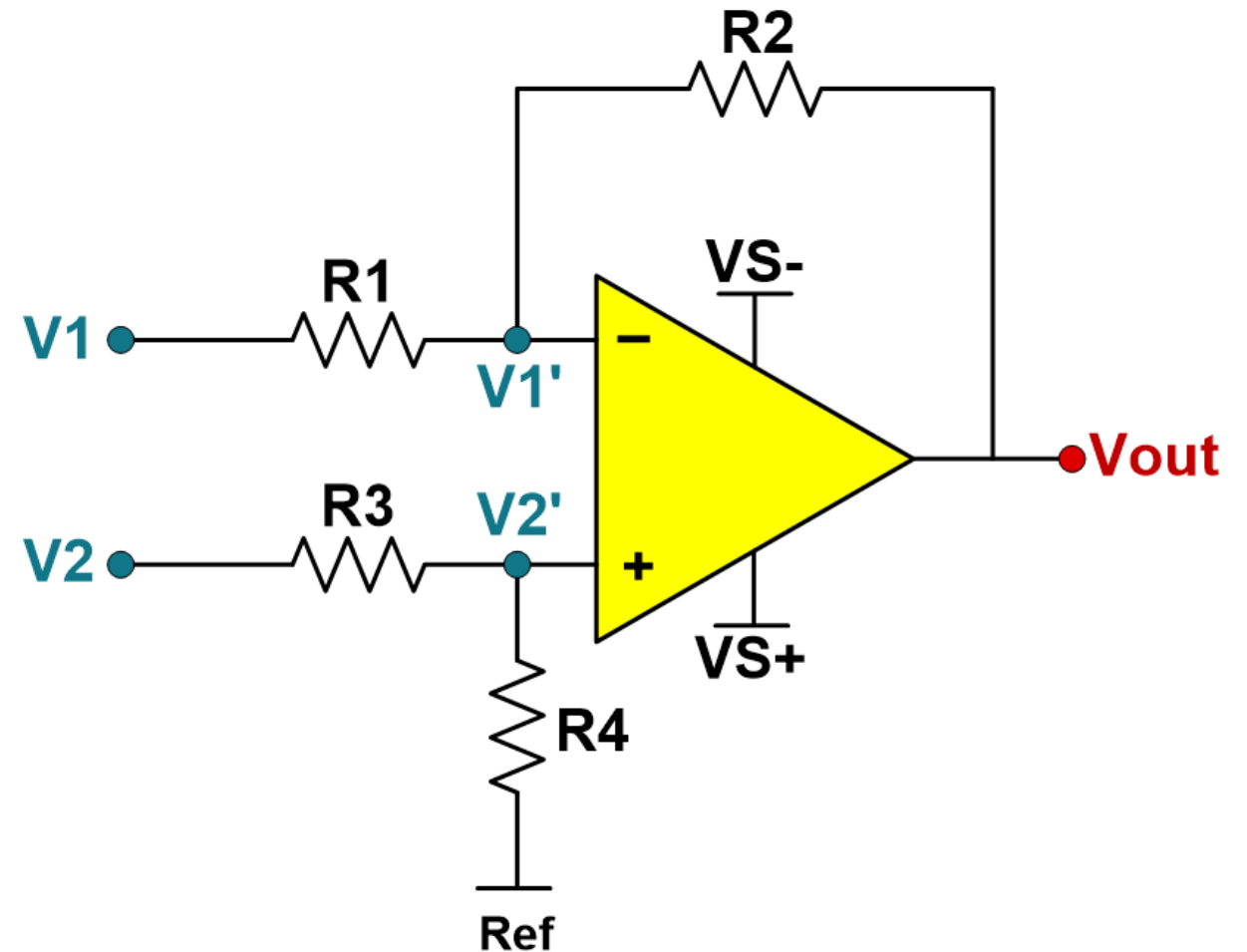
- a) The one-amp IA consumes more power
- b) The one-amp IA has low input impedance
- c) The one-amp IA must have precision-matched resistors for high accuracy
- d) The one-amp IA has fixed gain
- e) The one-amp IA can only be used for mV-level input signals
- f) b & e
- g) c & a
- h) b & c**



# Quiz: (IA) topologies: three-amp || Question

2. A one-amp IA has low input impedance. What is best way to resolve this?

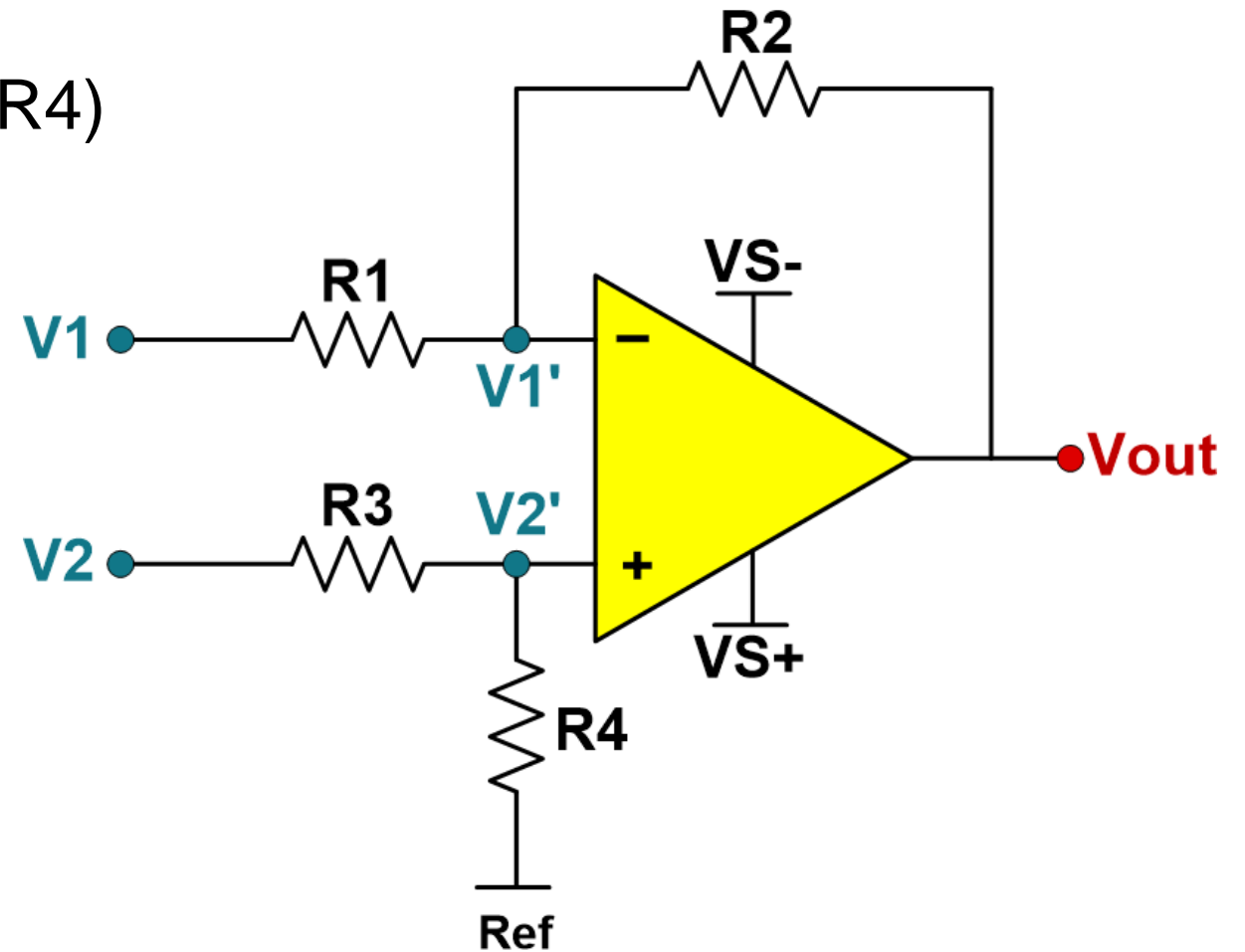
- a) Add really large input resistors (R1 through R4)
- b) Put the amplifier in high gain
- c) Add two buffers at the inputs (V1 and V2)
- d) Find an amplifier with high input impedance



# Quiz: (IA) topologies: three-amp || Answer

2. A one-amp IA has low input impedance. What is best way to resolve this?

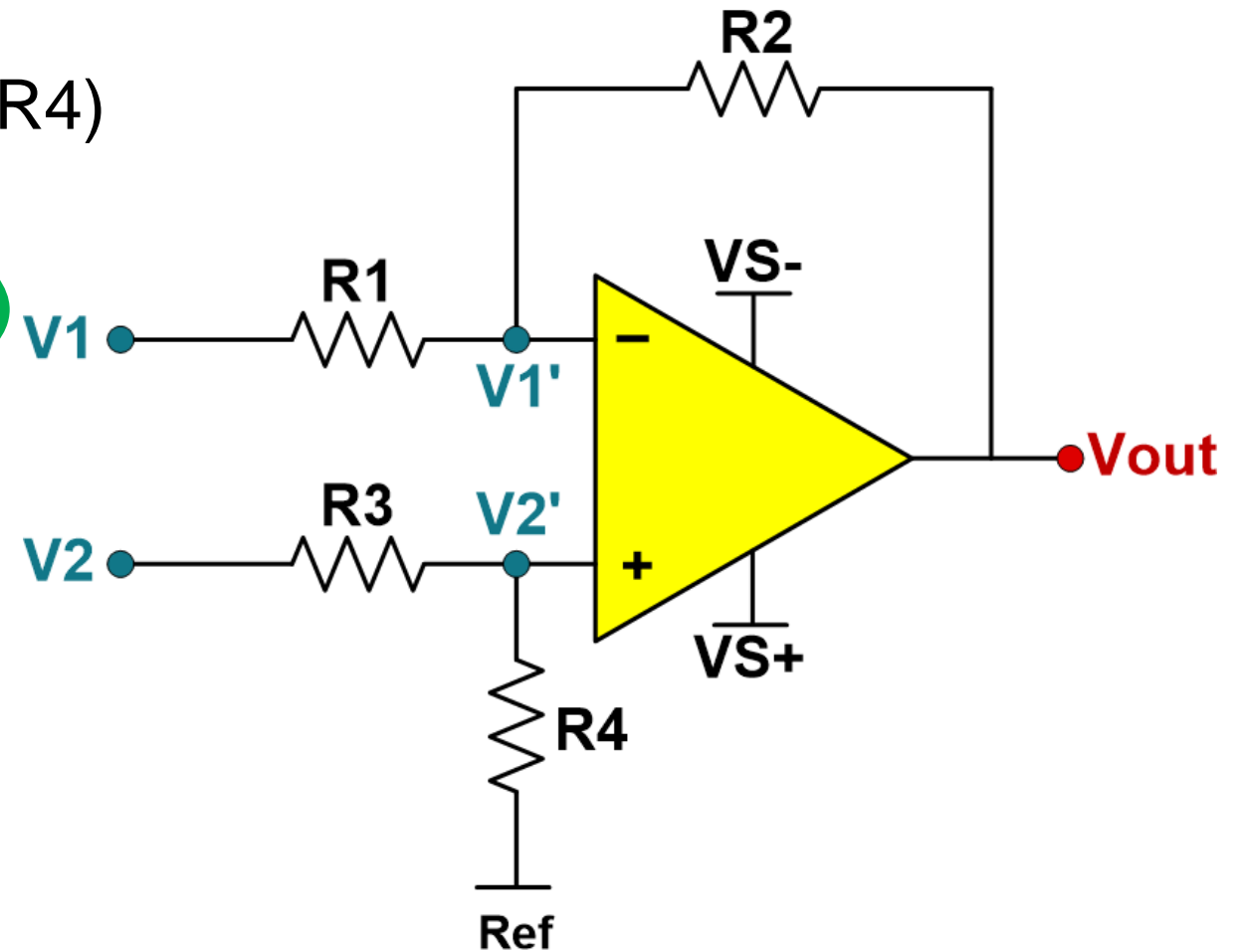
- a) Add really large input resistors (R1 through R4)
- b) Put the amplifier in high gain
- c) Add two buffers at the inputs (V1 and V2)**
- d) Find an amplifier with high input impedance



# Quiz: (IA) topologies: three-amp || Question

3. What is the gain equation for a three-amp IA?

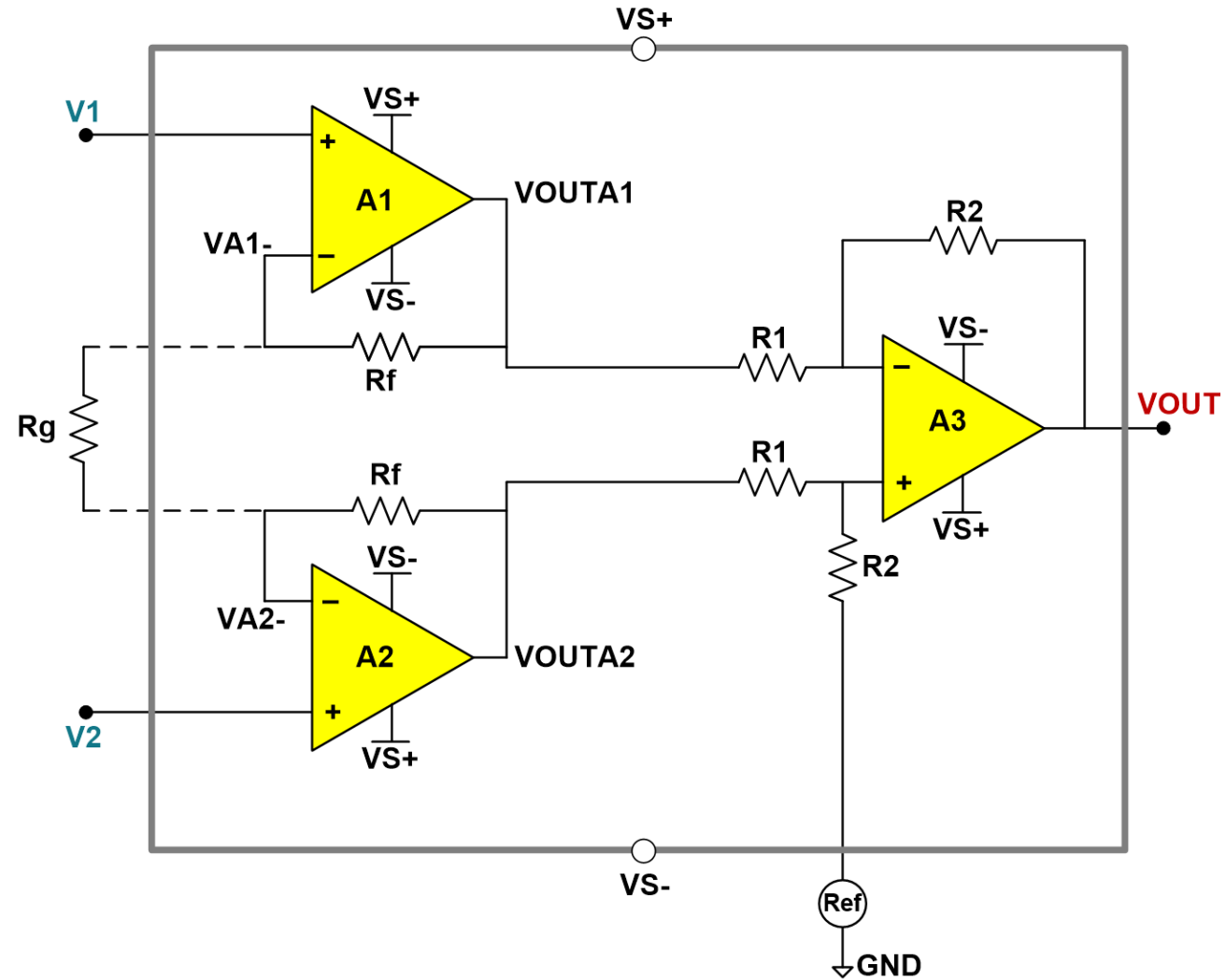
- a) Gain =  $\frac{R2}{R1}$
- b) Gain =  $Rg$
- c) Gain =  $\frac{R2}{R1} \times (Rg + 2 \times Rf)$
- d) Gain =  $\frac{R2}{R1} \times \left(1 + \frac{2 \times Rf}{Rg}\right)$



# Quiz: (IA) topologies: three-amp || Answer

3. What is the gain equation for a three-amp IA?

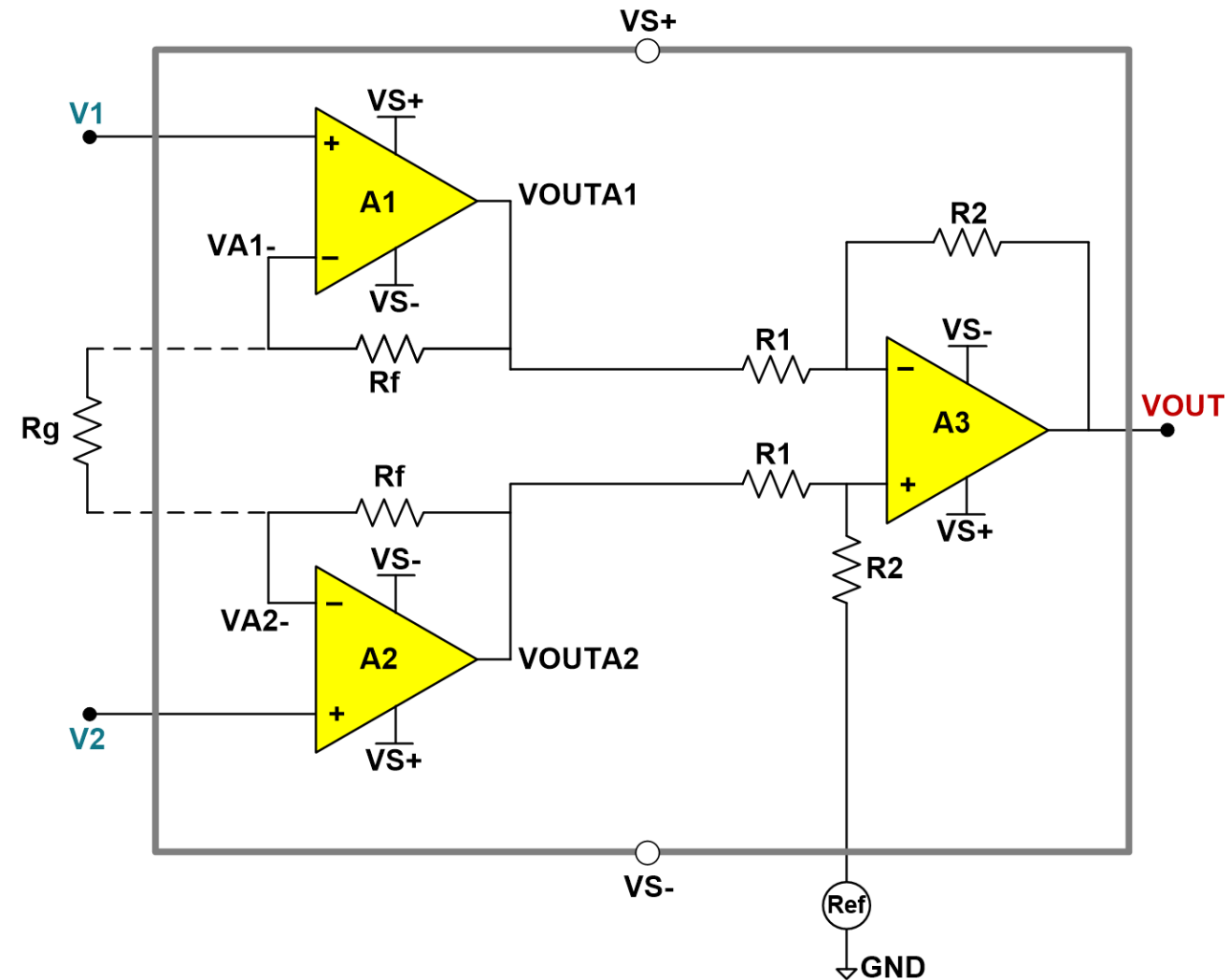- a) Gain =  $\frac{R2}{R1}$
- b) Gain =  $Rg$
- c) Gain =  $\frac{R2}{R1} \times (Rg + 2 \times Rf)$
- d) Gain =  $\frac{R2}{R1} \times \left(1 + \frac{2 \times Rf}{Rg}\right)$



## Quiz: (IA) topologies: three-amp || Question

4. Using the INA333-Q1 (TI's Automotive, Zero-drift, low power IA), what value of  $R_g$  do you need to achieve a signal gain of 501V/V?

- a)  $R_g = 100\Omega$
- b)  $R_g = 200\Omega$
- c)  $R_g = 200k\Omega$
- d)  $R_g = 501\Omega$

**HINT:**

Go to the product datasheet:

<https://www.ti.com/lit/ds/symlink/ina333-q1.pdf>



# Quiz: (IA) topologies: three-amp || Answer

4. Using the INA333-Q1 (TI's Automotive, Zero-drift, low power IA), what value of  $R_g$  do you need to achieve a signal gain of 501V/V?

- a)  $R_g = 100\Omega$
- b)  $R_g = 200\Omega$**
- c)  $R_g = 200k\Omega$
- d)  $R_g = 501\Omega$

**HINT:**

Go to the product datasheet:


<https://www.ti.com/lit/ds/symlink/ina333-q1.pdf>

$$\text{Gain} = \left( 1 + \frac{100k\Omega}{R_g} \right)$$

# Quiz: (IA) topologies: three-amp || Question

5. What is the differential gain of the following circuit?

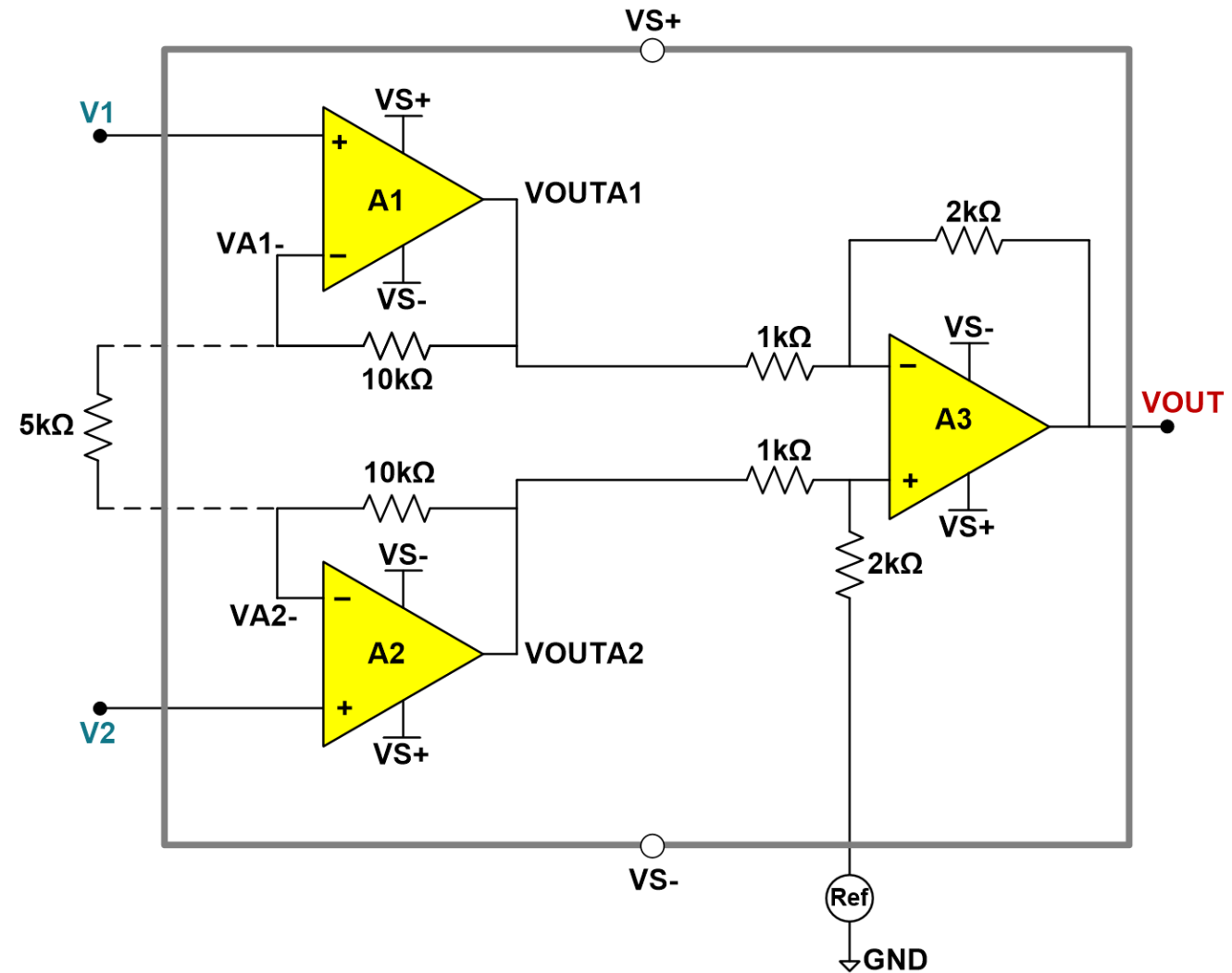
- a) Gain = 5V/V
- b) Gain = 2V/V
- c) Gain = 4V/V
- d) Gain = 10V/V



# Quiz: (IA) topologies: three-amp || Answer

5. What is the differential gain of the following circuit?

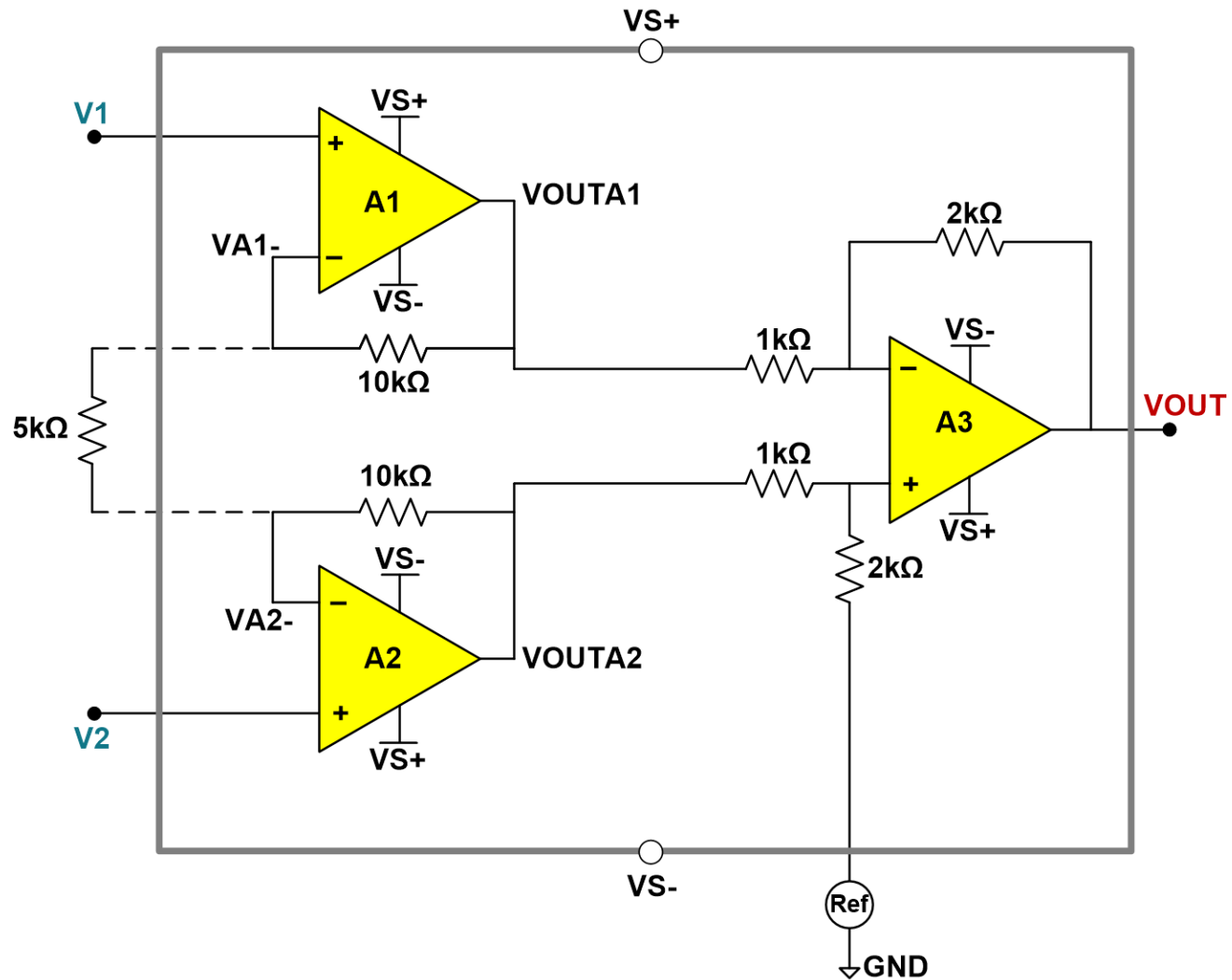- a) Gain = 5V/V
- b) Gain = 2V/V
- c) Gain = 4V/V
- d) **Gain = 10V/V**



**HINT:**

$$A_d = \frac{R_2}{R_1} \times \left( 1 + \frac{2R_f}{R_g} \right)$$

# Quiz: (IA) topologies: three-amp || Question

6. Using the INA818 (TI's high-precision, low-power IA with over-voltage protection), create a boundary plot for the following conditions:
- Voltage supply =  $\pm 15\text{V}$
  - Gain =  $100\text{V/V}$
  - Reference =  $0\text{V}$
  - Common mode voltage =  $8\text{V}$

**HINT:**

Use the INA Boundary Plot calculator in the **Analog Engineer's Calculator**:

<https://www.ti.com/tool/ANALOG-ENGINEER-CALC>

# Quiz: (IA) topologies: three-amp || Answer


6. Using the INA818 (TI's high-precision, low-power IA with over-voltage protection), create a boundary plot for the following conditions:

- Voltage supply =  $\pm 15V$
- Gain = 100V/V
- Reference = 0V
- Common mode voltage = 8V

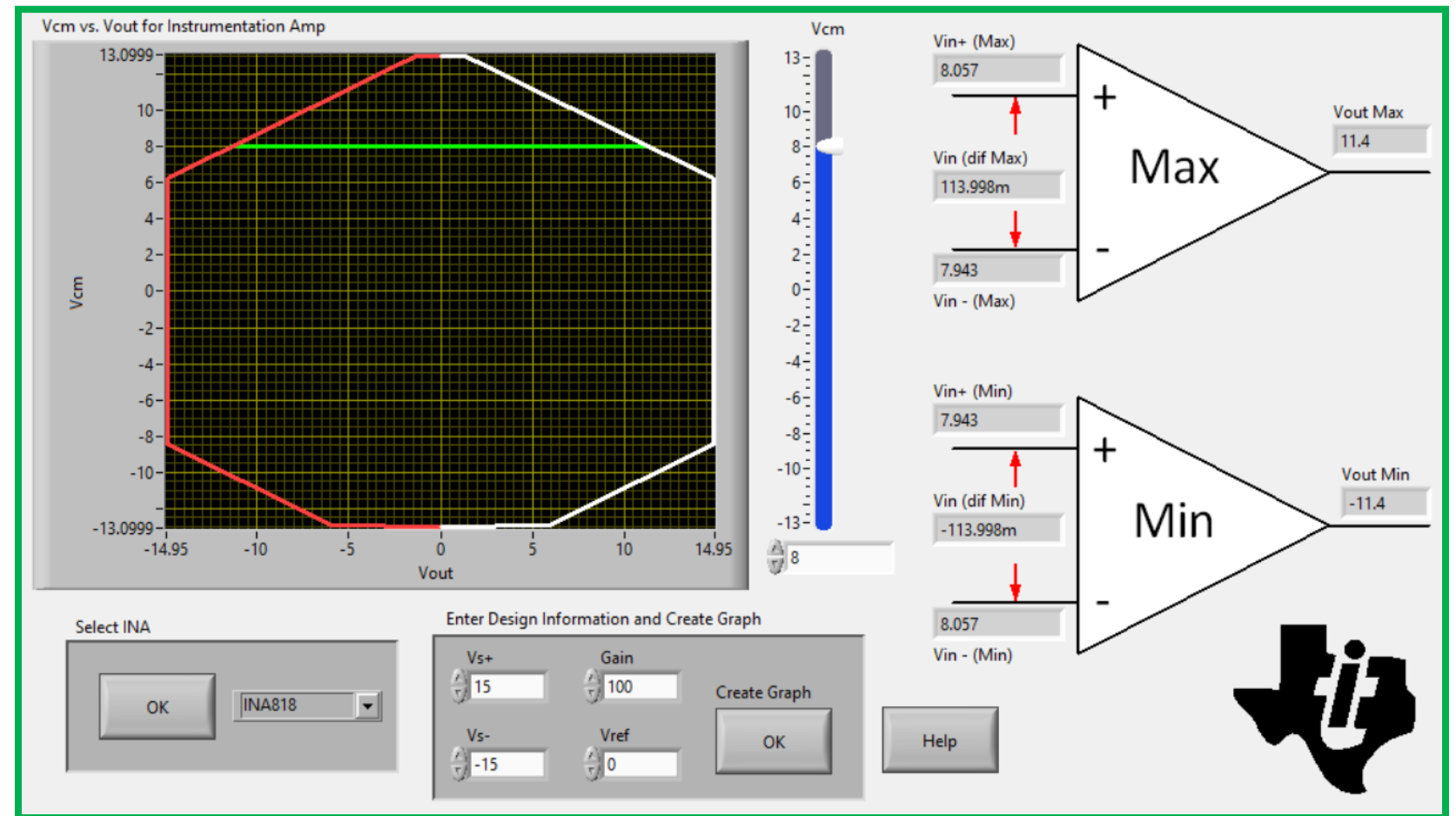**HINT:**

Use the INA Boundary Plot calculator in the **Analog Engineer's Calculator**:

<https://www.ti.com/tool/ANALOG-ENGINEER-CALC>



## Quiz: (IA) topologies: three-amp || Question

7. In theory, how does CMRR change with signal differential gain
- a) When signal gain is increased,  $ACM / Ad$  will increase so CMRR will double
  - b) When signal gain is decreased,  $ACM / Ad$  will increase so CMRR will increase in direct proportion to gain
  - c) When signal gain is increased,  $Ad / ACM$  will increase so CMRR will increase by a factor of  $1/2$
  - d) When signal gain is increased,  $Ad / ACM$  will increase so CMRR will increase in direction proportion to gain

# Quiz: (IA) topologies: three-amp || Answer

7. In theory, how does CMRR change with signal differential gain
- a) When signal gain is increased,  $A_{CM} / A_d$  will increase so CMRR will double
  - b) When signal gain is decreased,  $A_{CM} / A_d$  will increase so CMRR will increase in direct proportion to gain
  - c) When signal gain is increased,  $A_d / A_{CM}$  will increase so CMRR will increase by a factor of 1/2
  - d) **When signal gain is increased,  $A_d / A_{CM}$  will increase so CMRR will increase in direction proportion to gain**

**HINT:**

$$CMRR \left( \frac{V}{V} \right) = \frac{\text{differential gain}}{\text{common mode gain}} = \frac{A_d}{A_{CM}}$$

# Quiz: (IA) topologies: three-amp || Question

8. What are the typical magnitudes of input impedance for a 3 op amp IA?
- a)  $1\ \Omega$  to  $1\text{k}\ \Omega$
  - b)  $1\text{k}\ \Omega$  to  $100\text{k}\ \Omega$
  - c)  $100\text{k}\ \Omega$  to  $10\text{M}\ \Omega$
  - d)  $10^9\ \Omega$  to  $10^{12}\ \Omega$



# Quiz: (IA) topologies: three-amp || Answer

8. What are the typical magnitudes of input impedance for a 3 op amp IA?
- a) 1  $\Omega$  to 1k  $\Omega$
  - b) 1k  $\Omega$  to 100k  $\Omega$
  - c) 100k  $\Omega$  to 10M  $\Omega$
  - d) **10<sup>9</sup>  $\Omega$  to 10<sup>12</sup>  $\Omega$**

# Quiz: (IA) topologies: three-amp || Question

9. How do you determine the total current consumption of a 3 op amp IA?
- a) Look for the quiescent current specified in the datasheet and multiply it by 3
  - b) (Load currents ( $i_1$ ,  $I_2$ , and  $i_3$ ) + quiescent current) multiplied by 3
  - c) Load currents ( $i_1$ ,  $I_2$ , and  $i_3$ ) + quiescent current + any loading on  $V_{out}$
  - d) (Load currents ( $i_1$ ,  $I_2$ , and  $i_3$ ) + quiescent current)

## Quiz: (IA) topologies: three-amp || Answer

9. How do you determine the total current consumption of a 3 op amp IA?
- a) Look for the quiescent current specified in the datasheet and multiply it by 3
  - b) (Load currents ( $i_1$ ,  $I_2$ , and  $i_3$ ) + quiescent current) multiplied by 3
  - c) Load currents ( $i_1$ ,  $I_2$ , and  $i_3$ ) + quiescent current + any loading on  $V_{out}$**
  - d) (Load currents ( $i_1$ ,  $I_2$ , and  $i_3$ ) + quiescent current)

To find more Instrumentation Amplifier technical resources and search products, visit [ti.com/inas](https://www.ti.com/inas)