


Fully Differential Amplifiers - 2

Exercises

TI Precision Labs: Op Amps

Questions

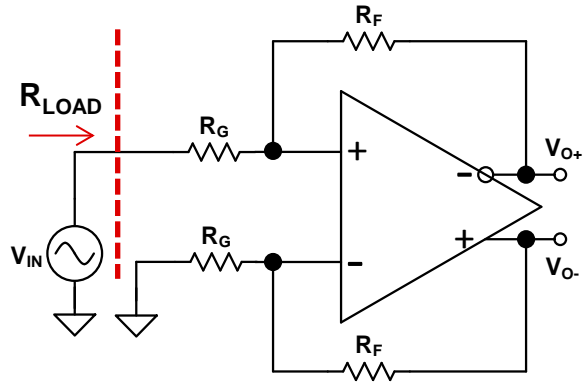
1. How would you AC couple a single-ended input source to an FDA?
2. What is the load seen by the single-ended input source? (HINT: It is not R_G). Assume that both the $V_{OCM} = 0V$ and the input signal common-mode is $0V$.



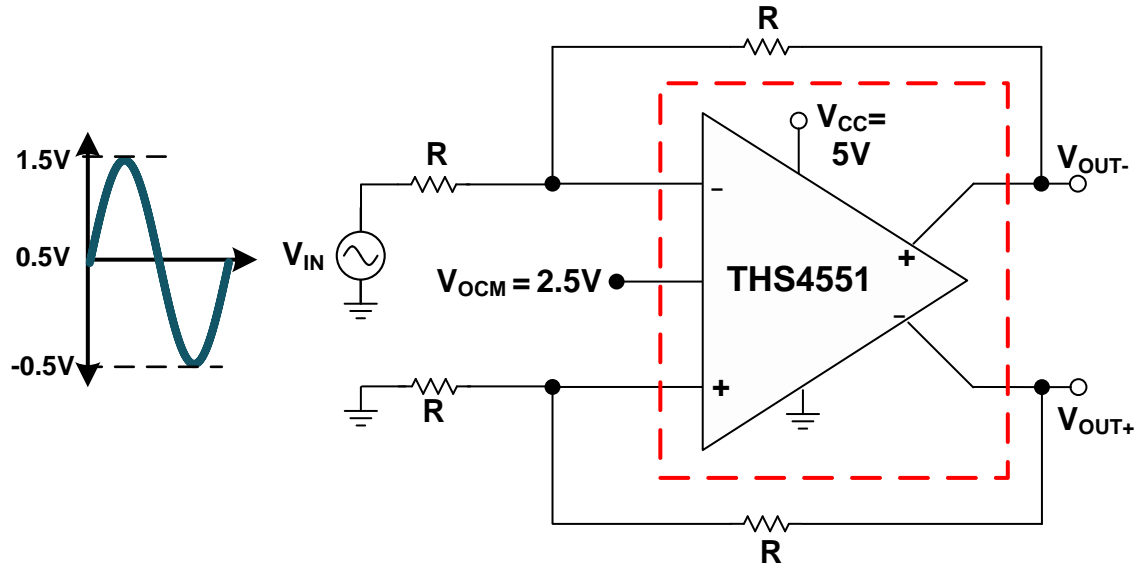
3. For the circuit shown below what is the,

- Output signal (differential and common-mode), and
- Input signal (differential and common-mode)

(HINT: The signal input common-mode is 0.5V while the non-driven input is at GND.)



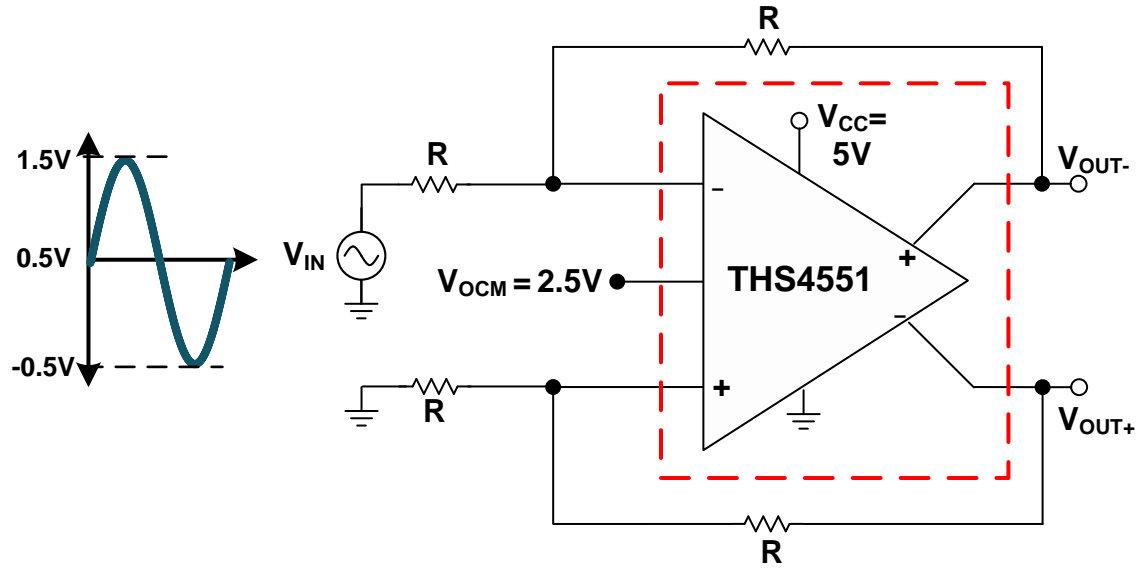
4. In the previous question how would you solve the problem of each output having a different common-mode (2.75V and 2.25V)



Answers

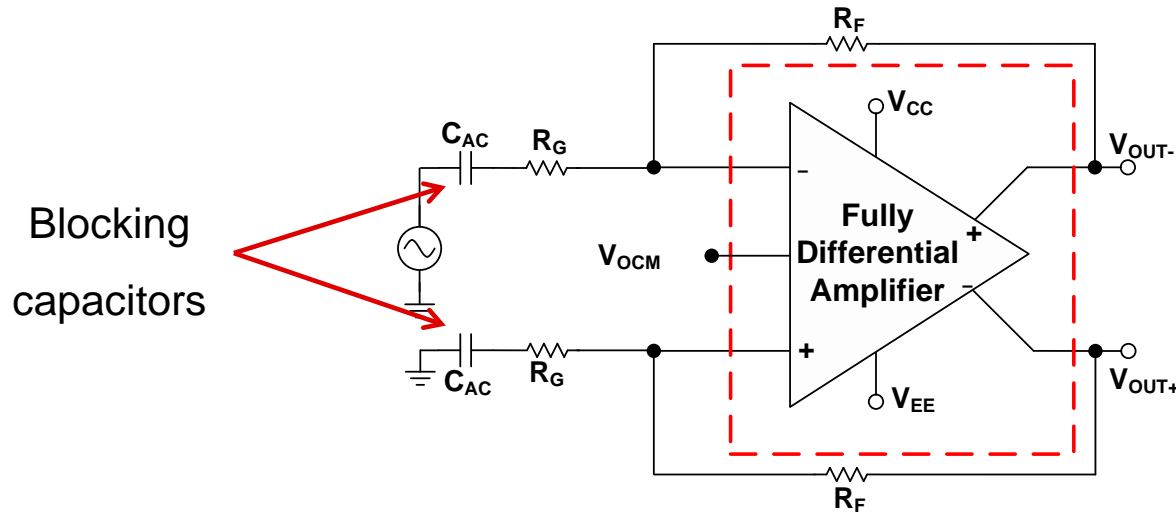1. How would you AC couple a single-ended input source to an FDA?

Answer: This circuit configuration is useful when the DC and low-frequency signal content can be ignored. If the single-ended input common-mode is not GND, then using this circuit configuration precludes the need for a 2nd opamp on the un-driven FDA side, to match the common-mode of the input signal.



2. What is the load seen by the single-ended input source? (HINT: It is not R_G). Assume that both the $V_{OCM} = 0V$ and the input signal common-mode is $0V$.

Answer: The load is not R_G because the amplifiers input common-mode is not fixed but is a function of the signal input and the feedback network.

$$V_{CM} = V_{O-} \left(\frac{R_G}{R_G + R_F} \right) \rightarrow (1) \text{ Using KCL on the bottom half of FDA}$$


$$\frac{V_{O-}}{V_{IN}} = \frac{1}{2} (\text{SignalGain}) = \frac{1}{2} \left(\frac{R_F}{R_G} \right) \rightarrow \text{By definition}$$

$$\Rightarrow V_{O-} = \frac{1}{2} \left(\frac{R_F}{R_G} \right) V_{IN} \rightarrow (2)$$

$$I_{LOAD} = \frac{V_{IN} - V_{CM}}{R_G} = \frac{V_{IN} - \frac{1}{2} \left(\frac{R_F}{R_G} \right) V_{IN} \left(\frac{R_G}{R_G + R_F} \right)}{R_G}$$

$$R_{LOAD} = \frac{V_{IN}}{I_{LOAD}} = \frac{R_G}{\left(1 - \frac{1}{2} \left(\frac{R_F}{R_G + R_F} \right) \right)}$$

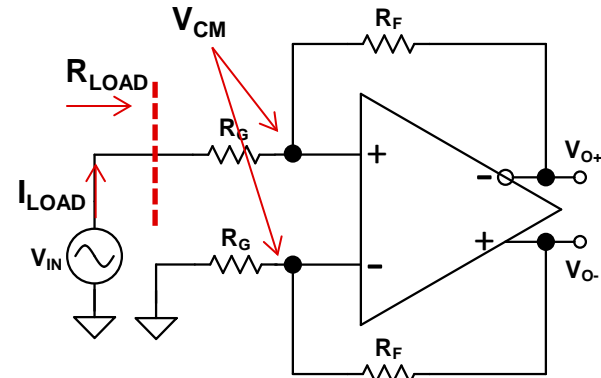Divide R_G by this factor to find the load seen by the signal source




3. For the circuit shown below what is the,
- Output signal (differential and common-mode), and
 - Input signal (differential and common-mode)

Answer: First lets start with the common-mode analysis

- The input common-mode is 0.5V and 0V respectively.
- The difference in common-mode is amplified by the signal gain and manifests itself as a differential signal centered on the output common-mode of 2.5V.
- The common-mode for V_{OUT-} is therefore equal to 2.25V and $V_{OUT+} = 2.75V$
- Also the input common-mode, $V_{CM} = \frac{1}{2} V_{OUT+} = 1.375V$
- The mathematical derivation for this is shown on the next slide.

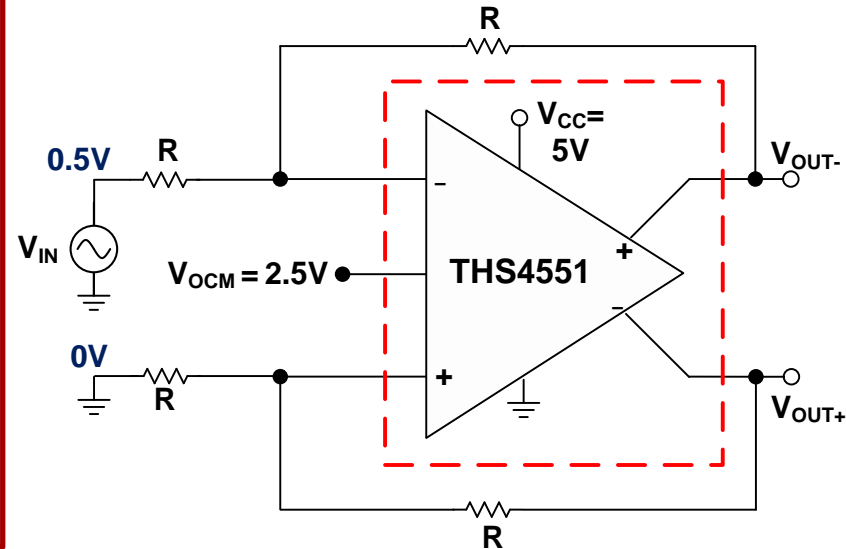**Intuitive derivation of
input and output
common-mode**



$$V_{CM} = \frac{1}{2}(V_{OUT+}) \rightarrow \text{Simple resistive divider on un-driven side} \quad \textcircled{1}$$

$$V_{OCM} = 2.5V = \left(\frac{V_{OUT+} + V_{OUT-}}{2} \right) \rightarrow \text{By definition} \Rightarrow V_{OUT-} = (2V_{OCM} - V_{OUT+}) \quad \textcircled{2}$$

$$\frac{0.5 - V_{CM}}{R} = \frac{V_{CM} - V_{OUT-}}{R} \rightarrow \text{Using KCL on the driven side}$$

$$\Rightarrow \frac{0.5V - \frac{1}{2}(V_{OUT+})}{R} = \frac{\frac{1}{2}(V_{OUT+}) - (2V_{OCM} - V_{OUT+})}{R}$$

$$\Rightarrow \left(\frac{1}{2} \right) V_{OUT+} + \left(\frac{1}{2} \right) V_{OUT+} + V_{OUT+} = 0.5V + 5V$$


$$\Rightarrow 2V_{OUT+} = 5.5V \Rightarrow V_{OUT+} = 2.75V$$

From $\textcircled{2}$ and $\textcircled{1}$ respectively -

$$V_{OUT-} = (2V_{OCM} - V_{OUT+}) = (5V - 2.75V) = 2.25V$$

$$V_{CM} = \frac{1}{2}(V_{OUT+}) = \frac{1}{2}(2.75) = 1.375V$$

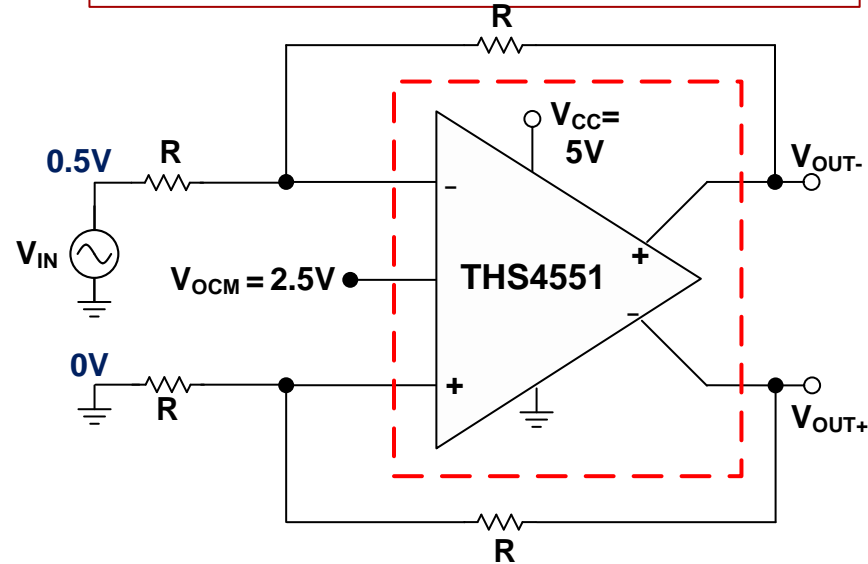
**Mathematical derivation of input
and output common-mode**



Answer: Now on to differential analysis

- Input sine-wave is $2V_{PP}$. FDA gain is $1V/V$. So each output will swing $1V_{PP}$ on each outputs common-mode of $2.75V$ and $2.25V$.
- The input common-mode will swing $0.5V_{PP}$ on the common-mode of $1.375V$.
- The results are shown below. Mathematical derivation is left as an exercise. Use similar concepts as shown for the common-mode.

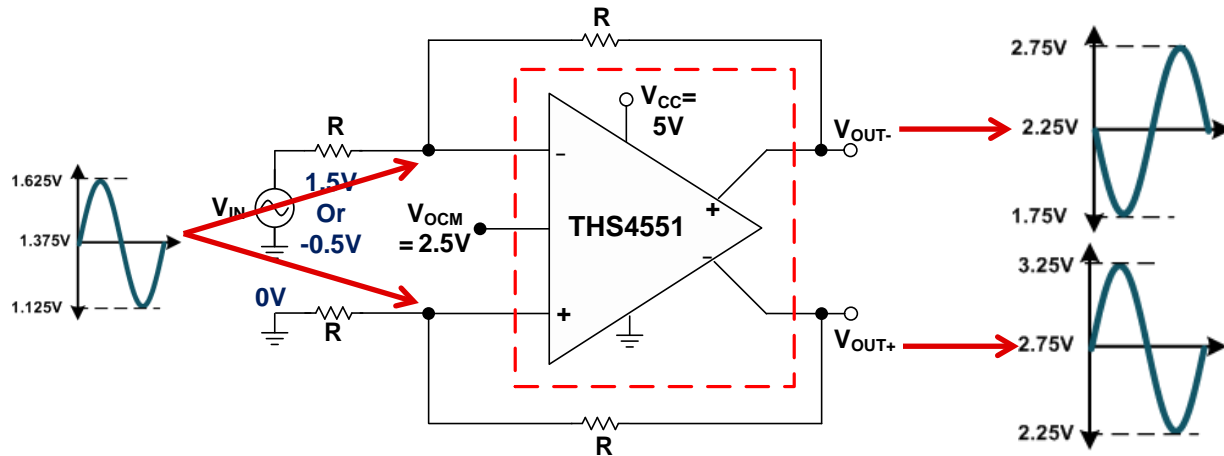**Intuitive derivation of input
and output differential-mode**



4. In the previous question how would you solve the problem of each output having a different common-mode (2.75V and 2.25V)

Answer: Use a 2nd single-ended opamp to drive 0.5V into the un-driven side. It is important to use a wideband amplifier that has a bandwidth on par with the FDA used. (Try the OPA836)

