





Fully Differential Amplifiers – 4


TIPL 2024

TI Precision Labs: Op Amps

Prepared and Presented by Samir Cherian

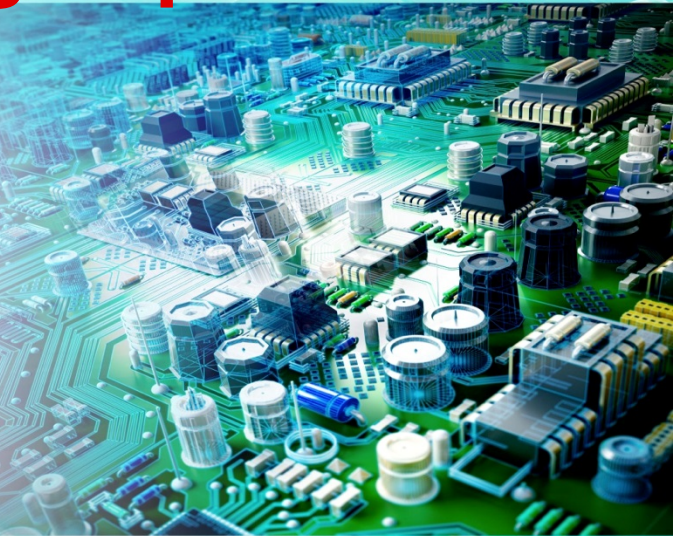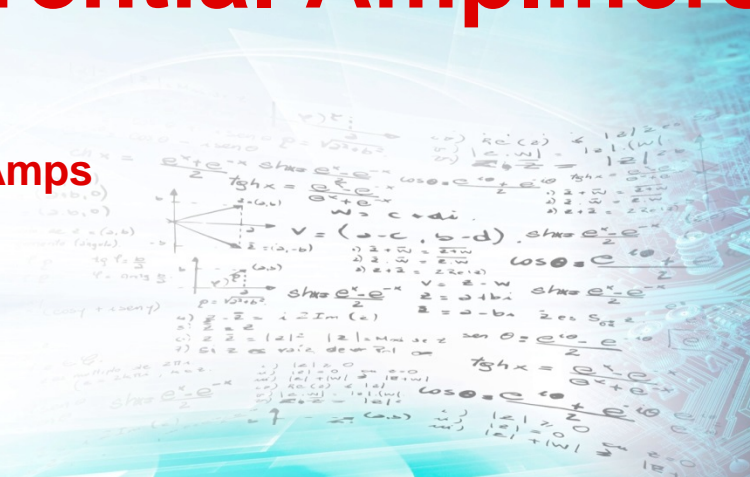

Noise Analysis

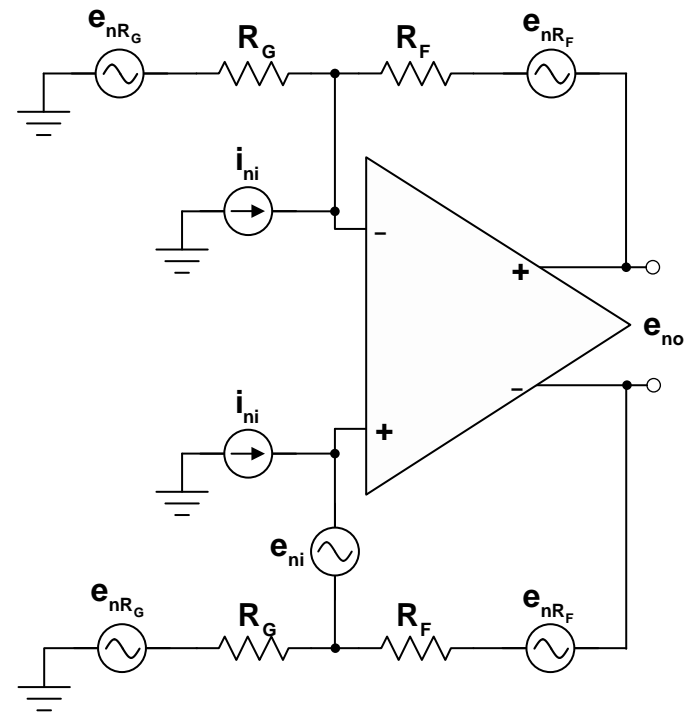


$$e_{no} = \sqrt{(e_{ni} \cdot NG)^2 + 2(i_{ni} \cdot R_F)^2 + 2(4kTR_F) + 2(4kTR_G \cdot (\frac{R_F}{R_G})^2)}$$

$$e_{no} = \sqrt{(e_{ni} \cdot NG)^2 + 2(i_{ni} \cdot R_F)^2 + 2(4kTR_F \cdot NG)}$$

NG is the Noise Gain

Resistor Noise Power = $4kTR$

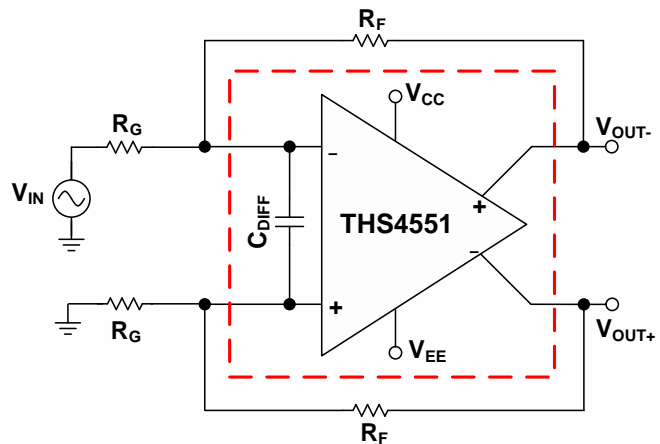Using large resistors with high-speed amplifiers



Recommended $R_F = 402 \Omega$



Voltage noise, $E_N = 2.2 \text{ nV}/\sqrt{\text{Hz}}$

Current noise, $I_{BN} = 1.9 \text{ pA}/\sqrt{\text{Hz}}$

Input offset current, $I_{BOS} = 150 \text{ nA}$


- Increasing R_F and R_G will result in larger noise contributions from the resistors compared to the amplifier.
- The current noise will be multiplied by R_F and will increase the overall system noise.
- Increased output offset voltage due to I_{BOS} .
- C_{DIFF} will introduce a noise gain zero which will reduce the phase margin and could cause oscillation. Large resistors lower the frequency of the zero within the amplifiers bandwidth

Effect of the noise gain zero

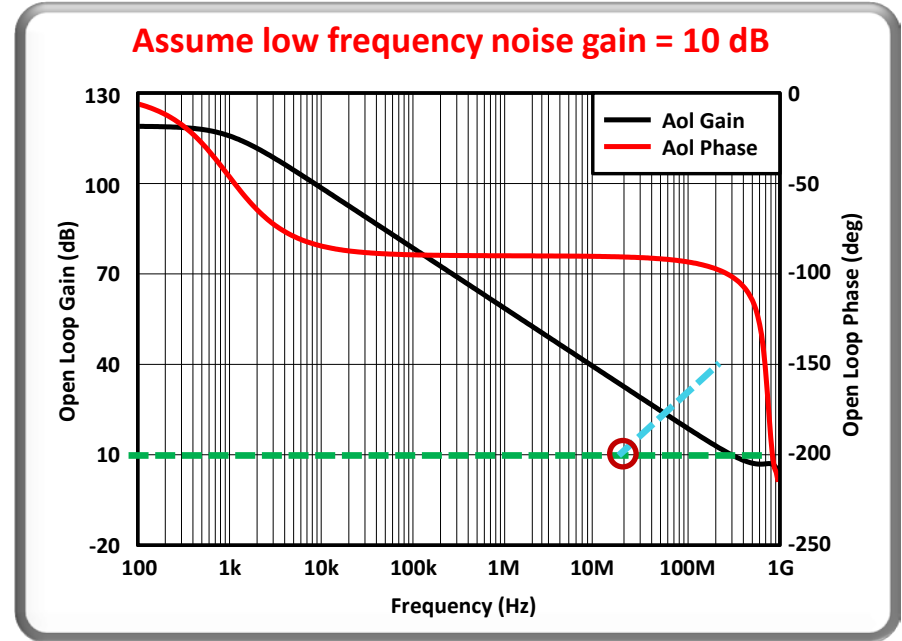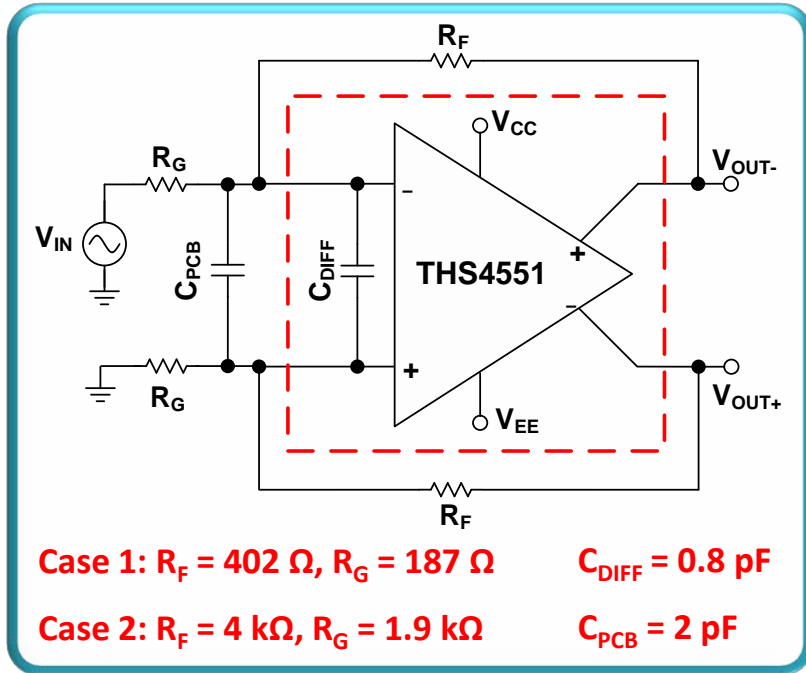


- The noise gain zero will occur at:
$$\frac{1}{2\pi(R_F \parallel R_G)(2C_{DIFF_IN} + C_{CM_IN})}$$

Feedback compensation

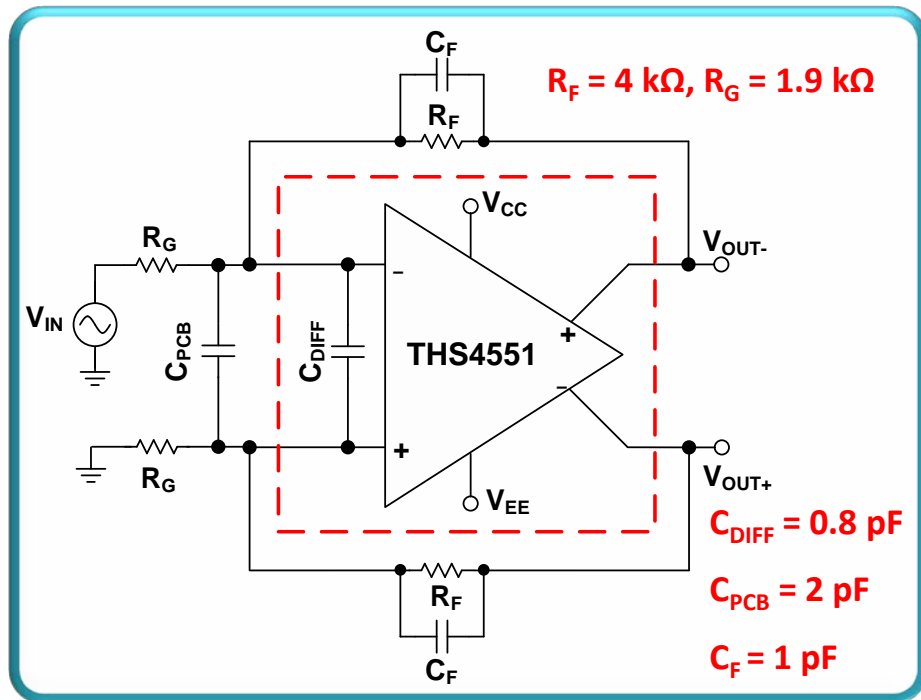


Assume low frequency noise gain = 10 dB

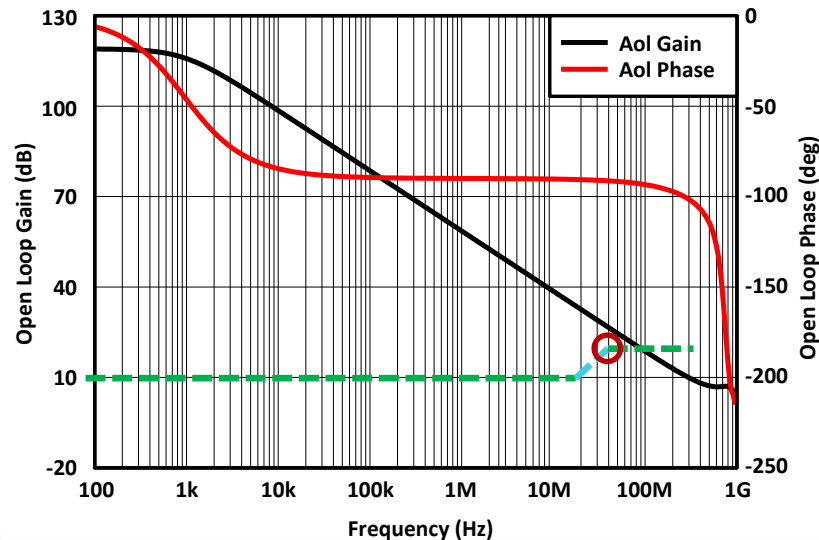

- Adding C_F introduces a pole in the noise-gain response which compensates for the zero. Pole is at: $\frac{1}{2\pi R_F C_F}$
- The high frequency noise gain is: $1 + \frac{(2C_{DIFF_IN} + C_{CM_IN})}{C_F}$

Input Terminations

Input Source

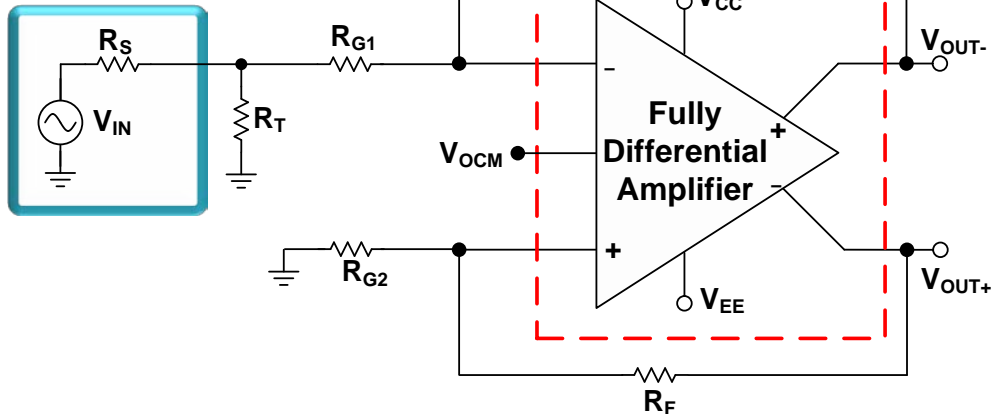

R_S is Source Resistance

R_T is Termination Resistance

$R_{G2} = R_{G1} + (R_S || R_T)$

- Matched termination is needed when the PCB trace $> \lambda/8$, where $\lambda = 300/f_{\text{MHZ}}$
- E.g., the wavelength of a 600-MHz signal is: $\lambda = 300/f_{\text{MHZ}} = 300/600 = 0.5 \text{ m} = 19.7 \text{ in.}$

A cable or PCB trace is a transmission line if it's longer than $0.5/8 = 0.0625\text{m}$ or 2.5 in.

$$R_T^2 - R_T * \frac{2R_S(2R_F + \frac{R_S}{2}A_V^2)}{2R_F(2 + A_V) - R_S A_V(4 + A_V)} - \frac{2R_F R_S^2 A_V}{2R_F(2 + A_V) - R_S A_V(4 + A_V)} = 0$$

Excel calculator for single-ended to differential matched termination configuration

Solving for R_t and then R_{g1} and R_{g2} in the single to differential FDA configuration with input impedance matching.

ENTER ONLY THE RED BOLD FIELDS							
MAIN RESULTS IN BLUE BOLD FIELDS							
Enter Source R_s	50	Ω	<i>This is single ended input to differential output design with R_f selected and other elements solved for.</i>				
Enter Feedback R_f	402	Ω					
Maximum gain	14.32502263	V/V					
Must enter a gain < this for valid solution							
Enter Target Gain	5	V/V	13.9794	dB			

<i>Now get standard 1% values</i>			
Required R_t value	79.65389444	Ω	78.7
Closest 1% value	80.6	Ω	80.6
Required R_{g1} value	68.07085543	Ω	66.5
Closest 1% value	68.1	Ω	68.1
Required R_{g2} value	98.78875048	Ω	97.6
Closest 1% value	97.6	Ω	100
Snapping R_f to closest 1%	402	Ω	402
Closest 1%	402	Ω	412

Some example FDAs from Texas Instruments

Product Name	I_Q (mA)	GBP (MHz)	Slew-Rate (V/ μ s)	Voltage Noise (nV/ \sqrt Hz)	Key Features
THS4531A	0.25	27	190	10	Low Power.
THS4551	1.35	135	220	3.3	Low Noise and High Precision.
THS4541	10.1	850	1500	2.2	Wide Bandwidth with Precision.
THS4509	37.7	3000	6600	1.9	
LMH5401	55	6200	17500	1.25	Ultra-wide bandwidth.
LMH3401	55	7000	18000	1.4	Fixed Gain with integrated resistors.
LMH6552	20.4	1500	3800	1.1	$\pm 10V$ supplies. Current Feedback topology.
OPA1632	14	180	50	1.3	$\pm 30V$ supplies and low-noise. Optimized for audio.

<http://www.ti.com/lscs/ti/amplifiers/op-amps/fully-differential-amplifiers-overview.page>

Digital Variable-Gain Amplifiers (DVGA)

- Wide gain range can be programmed through SPI or parallel-mode.
- Single-ended OR Differential Input to Differential Output.
- Input signals can be AC or DC coupled.
- Commonly used in Test & Measurement and Communications.

Product Name	I_Q (mA)	Gain Range	Noise Figure	Key Features
LMH6401	69	-6dB to 26dB	7.7 dB @ 100 Ω	4.5 GHz BW @ $A_V= 26$ dB
LMH6881	100	6dB to 26dB	9.7 dB @ 100 Ω	2.4 GHz BW @ $A_V= 26$ dB. SE or DIFF I/P
LMH6517	80	-9.5dB to 22dB	5.5 dB @ 100 Ω	1.2 GHz BW @ $A_V= 22$ dB
LMH6521	112.5	-5.5dB to 26dB	7.3 dB @ 200 Ω	1.2 GHz @ 0dB Gain. AC Coupled Only



©Copyright 2017 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.
Use of this material is subject to TI’s **Terms of Use**, viewable at TI.com