

# Isolated Power Supplies for PLC I/O Modules

**Industrial Systems - Factory Automation and Control**

# Agenda


- Where and why?
- What are my choices?
- Fly-Buck - How does it work, what is important?
  - Working principle
  - Why duty cycles of 40-60% should be chosen
  - Effects of leakage inductance

# Where and why?

- Where: PLC modules where only limited power is required (1-4 W)
- Why: Isolated supplies for Multiplexer, Amplifier, ADC, Reference, Isolator

## Example

### Group Isolated Analog Input Module

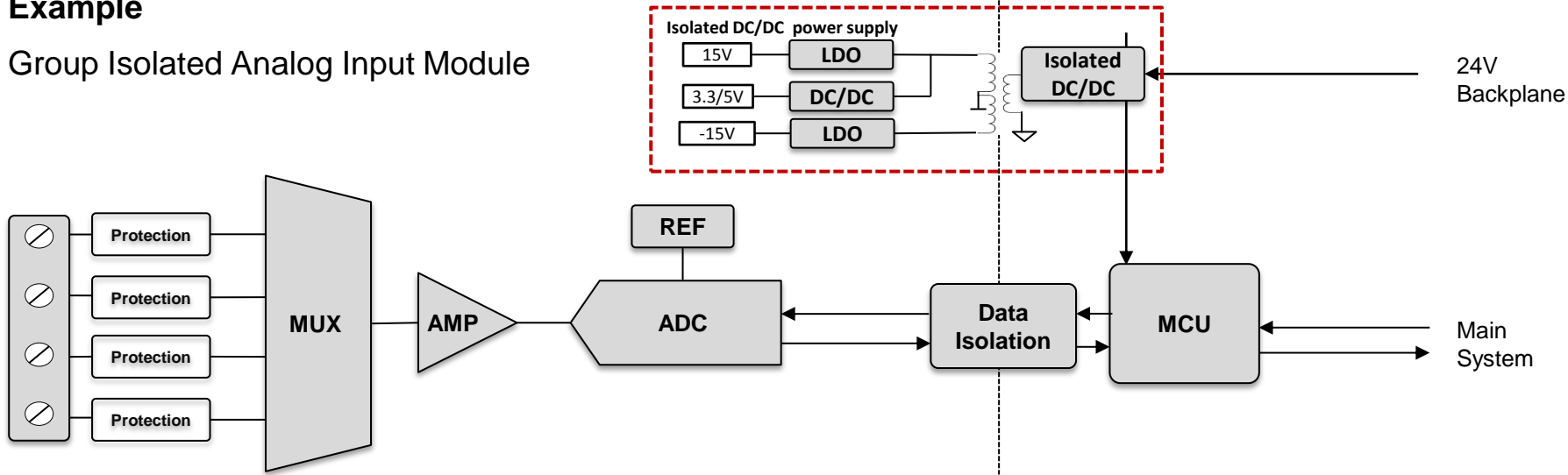


# What are my choices?

- Push-Pull (SN650x)
  - + Simple to use
  - + Low cost
  - No regulation (especially critical for transformers with high turn ratios)
- Flyback (UCC28xxx)
  - + Mid power (5W-100W)
  - + Single primary switch
  - + Wide  $V_{in}$  range
  - + Good regulation (if secondary side regulated)
  - Needs optocoupler
- Fly-Buck (LM5xxx, TPS55010)
  - + Low power (<10W)
  - + Primary side regulation (no optocoupler)
  - + Non-isolated + isolated outputs
  - + Wide input range
  - Bad regulation

Active Clamp, Half & Full Bridge oversized for power requirements (mostly used for >50W)


# Fly-Buck – How does it work, what is important?

# Topology

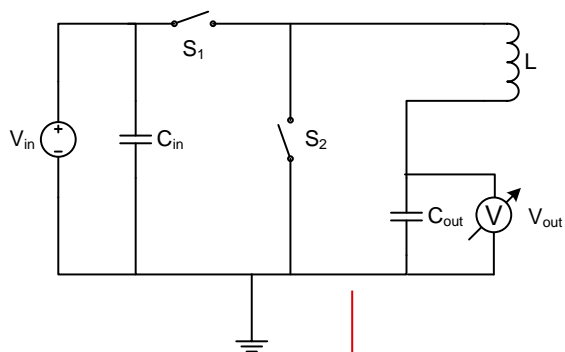


$$V_{out} = V_{in} \cdot D = V_{in} \cdot \frac{t_{on}}{t_{on} + t_{off}}$$

+

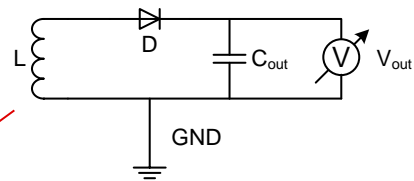

$$N = \frac{N_{sec}}{N_{pri}}$$



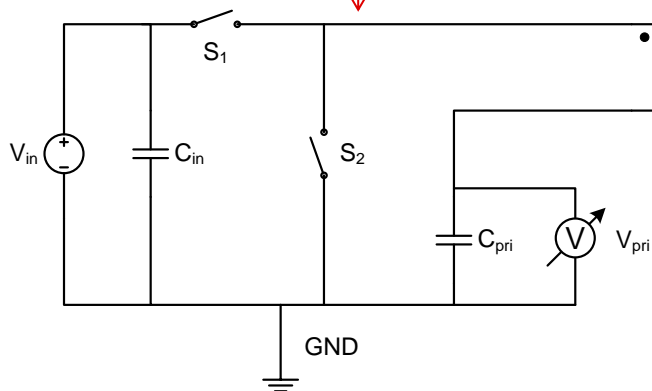


$$V_{pri} = V_{in} \cdot D = V_{in} \cdot \frac{t_{on}}{t_{on} + t_{off}}$$


$$\Rightarrow V_{sec} = V_{pri} \cdot N - V_{D1}$$
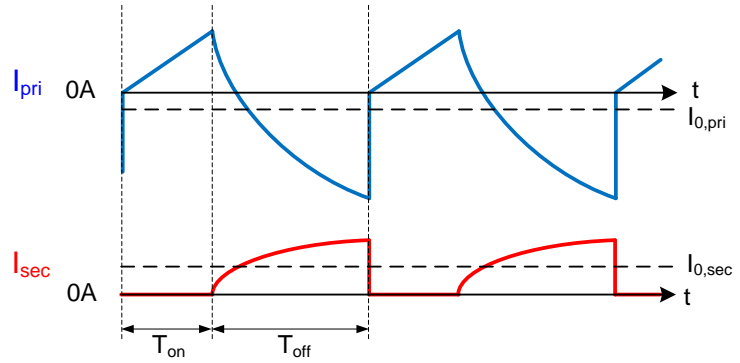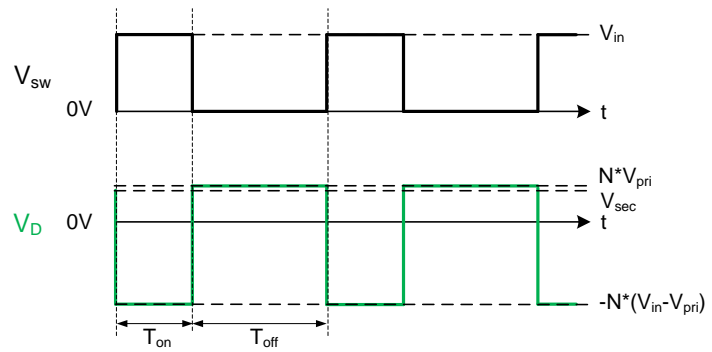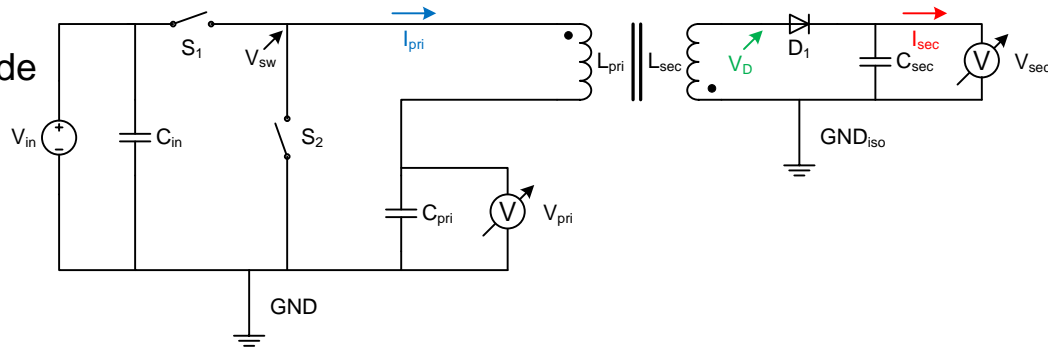
# Working Principle

- $t_{on}$  -  $S_1$  closed,  $S_2$  open:
  - Current flows through  $L_{pri}$ , secondary side voltage /  $D_1$  is reversed biased
  - No current flowing
- $t_{off}$  -  $S_1$  open,  $S_2$  closed:
  - Voltage across  $L_{pri}$  and  $L_{sec}$  reverses
  - Current flowing


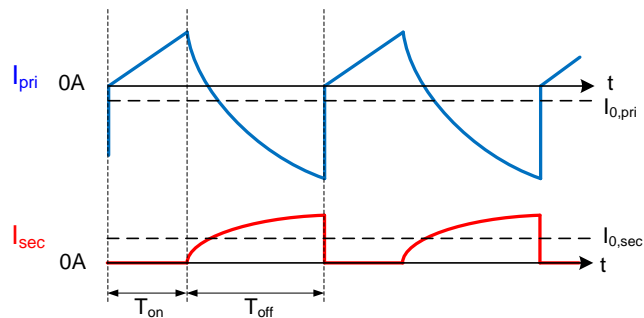
# Why duty cycles of 40-60% should be chosen



$$D = \frac{t_{on}}{t_{on} + t_{off}}$$



$$I_{pri} \cdot t_{on} = I_{sec} \cdot t_{off} \cdot N$$

$$I_{pri} = I_{sec} \cdot N \cdot \frac{1 - D}{D}$$

Too low or too high duty cycles lead to short energy charge or energy transfer times.


=> High peak currents on primary or secondary side

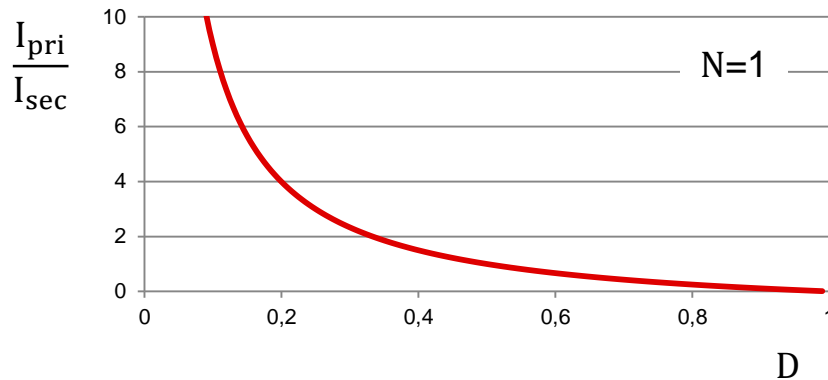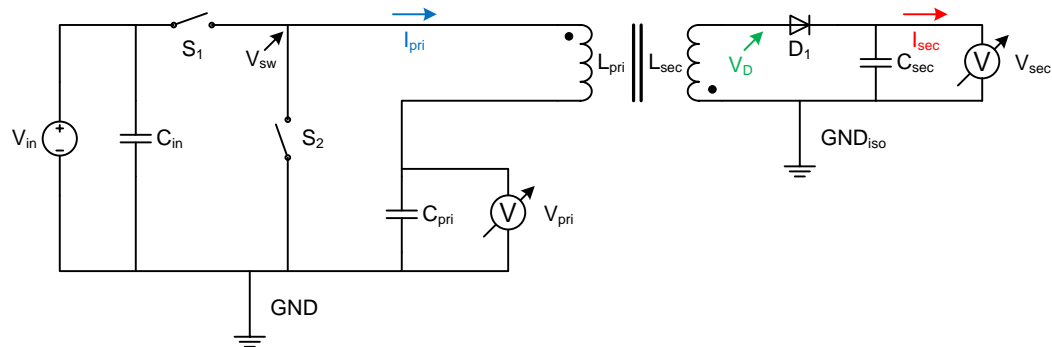=> Transformer needs high saturation current rating






# Effects of Leakage Inductance

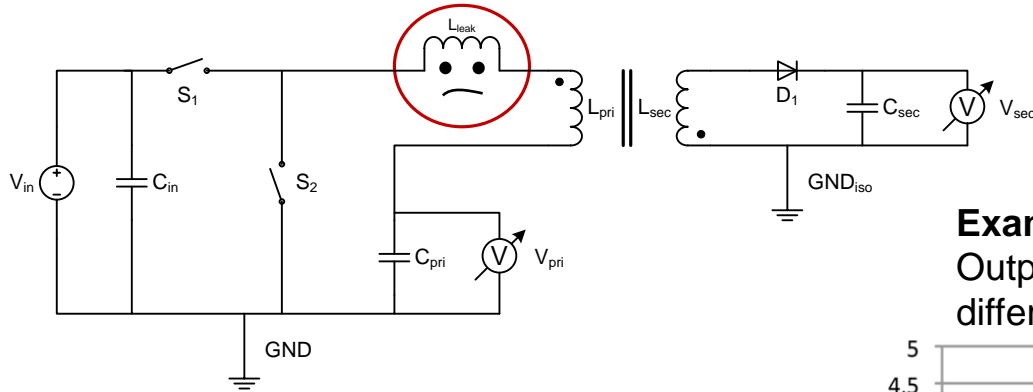

- Lower leakage inductance
  - ⇒ Higher peak currents
  - ⇒ Higher voltage drop across  $D_1$
- Higher leakage inductance
  - ⇒ High currents increase effect of already high leakage inductance
  - ⇒ Bad regulation
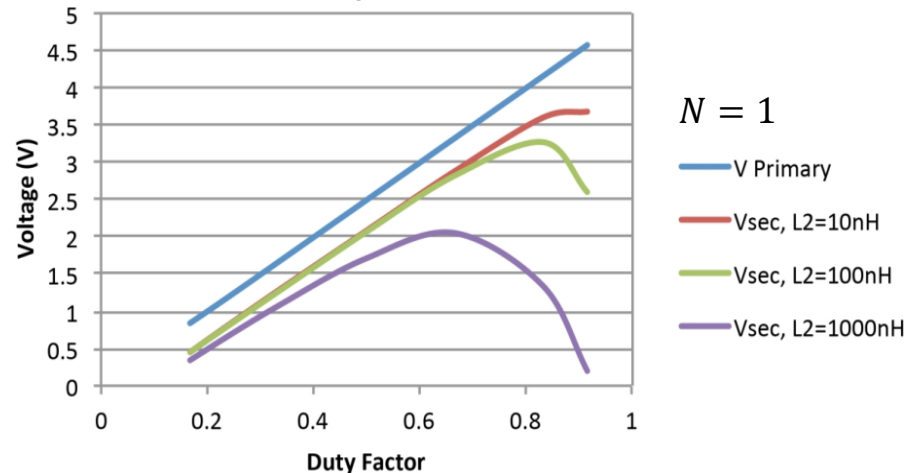
## Example 1:

Output voltage over duty factor for different leakage inductance




Robert Kollman, [http://www.eetimes.com/author.asp?section\\_id=183&doc\\_id=1321055](http://www.eetimes.com/author.asp?section_id=183&doc_id=1321055)

# Effects of Leakage Inductance
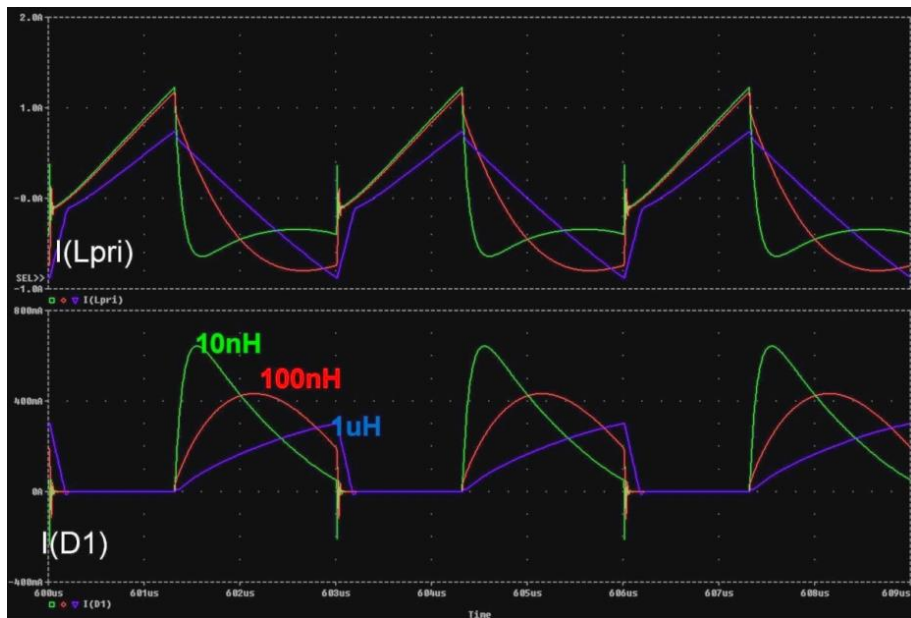
## Example 2:

Peak currents for increasing leakage inductance


⇒ High leakage inductance leads to “too slow” system



Robert Kollman, [http://www.eetimes.com/author.asp?section\\_id=183&doc\\_id=1321055](http://www.eetimes.com/author.asp?section_id=183&doc_id=1321055)
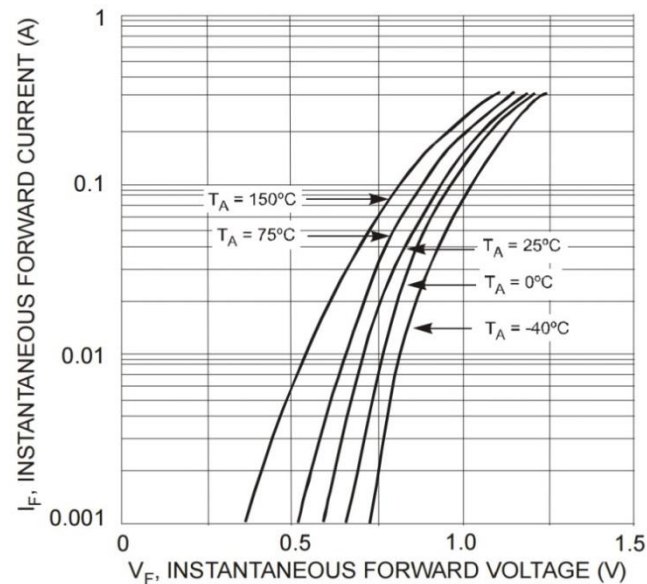
## Example 3:

Voltage drop across diode for increasing forward current



<http://www.diodes.com/files/datasheets/ds30086.pdf>, Fig. 2

# Resources

# LM5017 Fly-Buck: Top Industrial Applications

## Factory Automation PLCs and Motor Drives



- Bias power from main bus
- +/- bias voltage rails
- Analog/digital I/O isolation

**TI Designs**

- **PMP7993.1:**  $\pm 5V$  &  $\pm 15V$  outputs
- **PMP10535.1:**  $\pm 5V$  &  $\pm 12V$ , low profile
- **TIDA-00174:** IGBT driver bias for AC motor drive

## Smart Grid E-meters & Solar Inverters



- Bias power for RS485
- Bias power for PLC/Relay
- Inverter system bias supply

**TI Designs**

- **PMP9461:** Microinverter Gate Drive and System Bias
- **PMP9310:** Non-isolated offline power supply for E-meter

## Other Industrial Power Supplies & E-bikes



- Power Modules: Digital PWM controller bias (UCD3k)
- eBikes: system bias supply

**TI Designs**

- **PMP4394:** 1W isolated SIP module
- **PMP8581:** 48Vin, synchronous buck power supply in TO-220 footprint

## Further TI Designs

- Ultra-Small 1W, 12V-36V Iso Power Supply for Analog Prog Logic Controller Modules Reference Design (TIDA-00237)
- 1W Isolated Power Supply with Planar Transformer Reference Design (TIDA-00688)
- Small Footprint Isolated Analog DC/DC Converter Reference Design (TIDA-00689)

# LM5160A Fly-Buck Application-based TI Designs

## Industrial PLCs



### Application Needs

- 24V input bus typical
- 18-32V Vin range
- Isolated multiple outputs
- Up to 15W total output

### Reference Design

- Isolated triple output 5V@1A, +/-15V@200mA



PMP10532

## Industrial AC Motor Drive IGBT Bias



### Application Needs

- 24V input bus typical
- 18-32V Vin range
- Isolated multiple outputs
- Up to 15W total output

### Reference Design

- Isolated 8 outputs 15V/-8V@150mA for



PMP10531

## EV/HEV Bias



### Application Needs

- 12V battery, 6-16Vin range
- Isolated single or multiple outputs
- Up to 6W total output

### Reference Design

- 3 designs: Isolated +15V@150mA, -9V/150mA, and 5V/200mA for CAN bus



PMP10588

## POE Powered IP Camera/IP Phone



### Application Needs

- 48Vin typical
- 36-57V Vin range
- Isolated or non isolated 12V or 5V output
- Up to 12W output power

### Reference Design

- 12W POE solution LM5160+TPS2378



PMP10572

**[www.ti.com/automation](http://www.ti.com/automation)**

**[www.ti.com/flybuck](http://www.ti.com/flybuck)**