

SAR ADC Power Scaling



TIPL 4601

TI Precision Labs – ADCs

Created by Reed Kaczmarek and Peggy Liska



Presented by Peggy Liska

Acquisition Phase vs. Conversion Phase

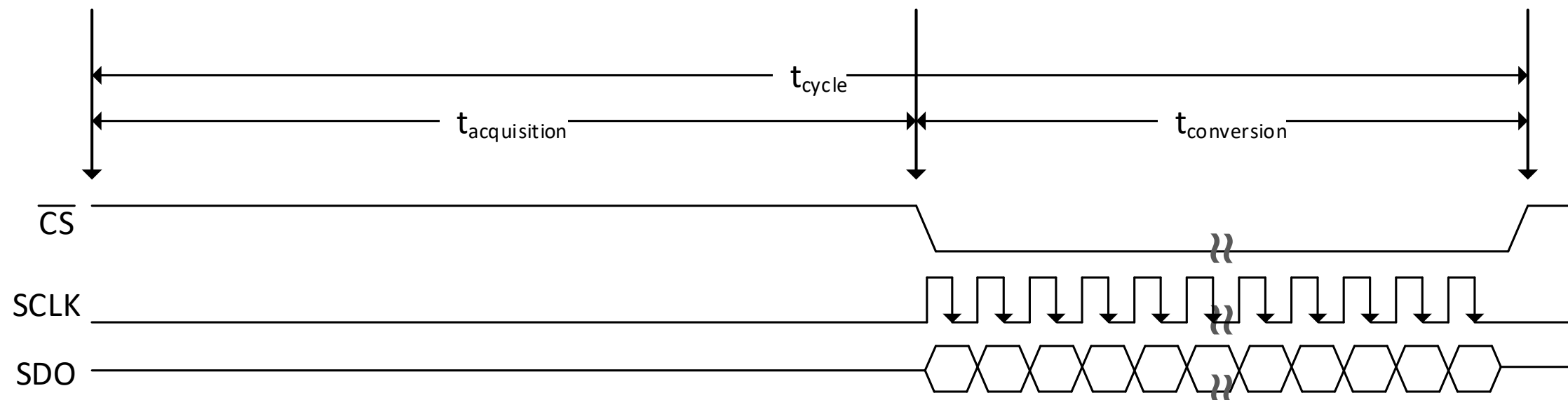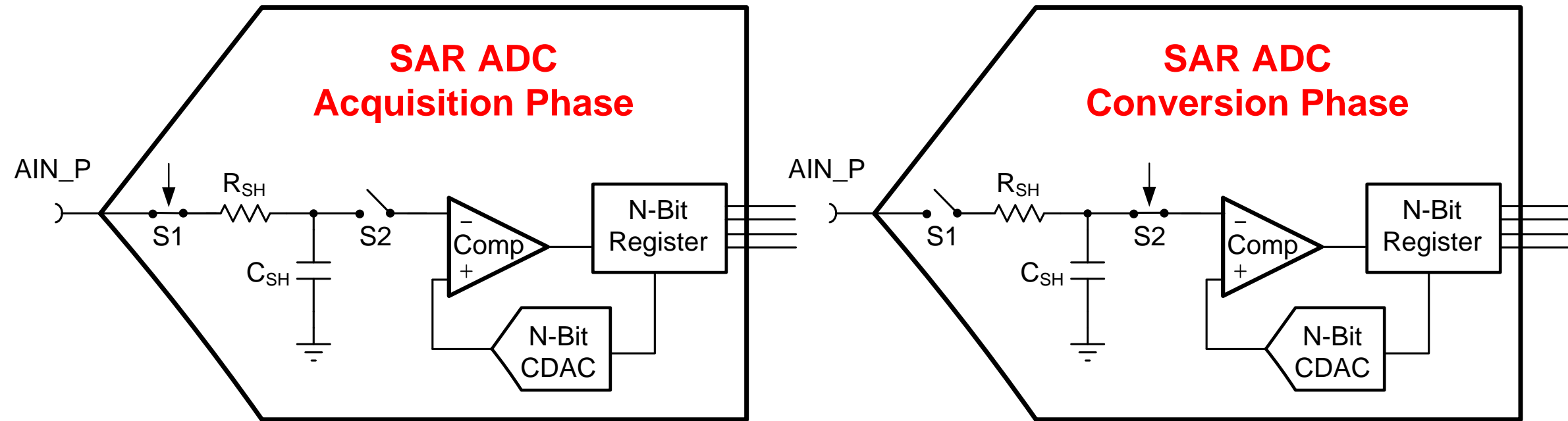



Power: Acquisition Phase vs. Conversion Phase

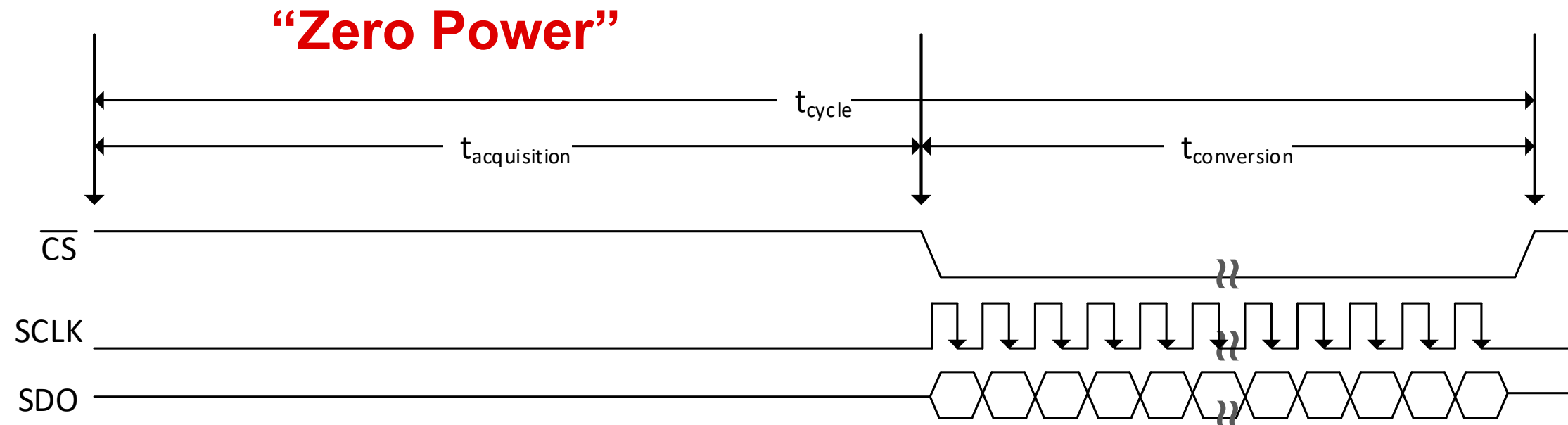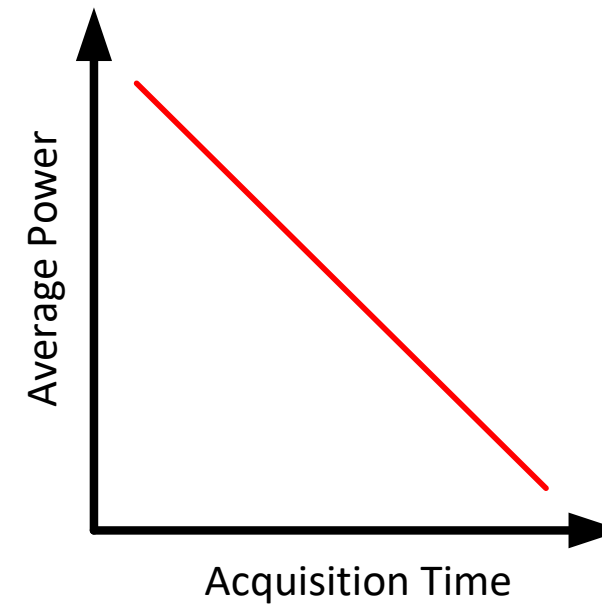- The majority of the power is consumed during the conversion phase
- Note that not all SAR ADCs will support power scaling



Acquisition Time: Internal Conversion Clock

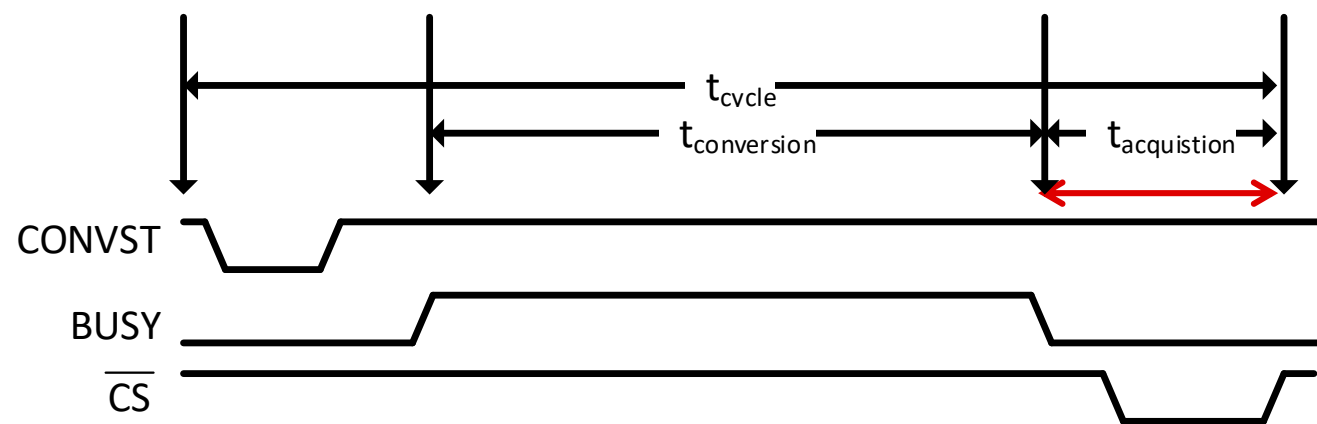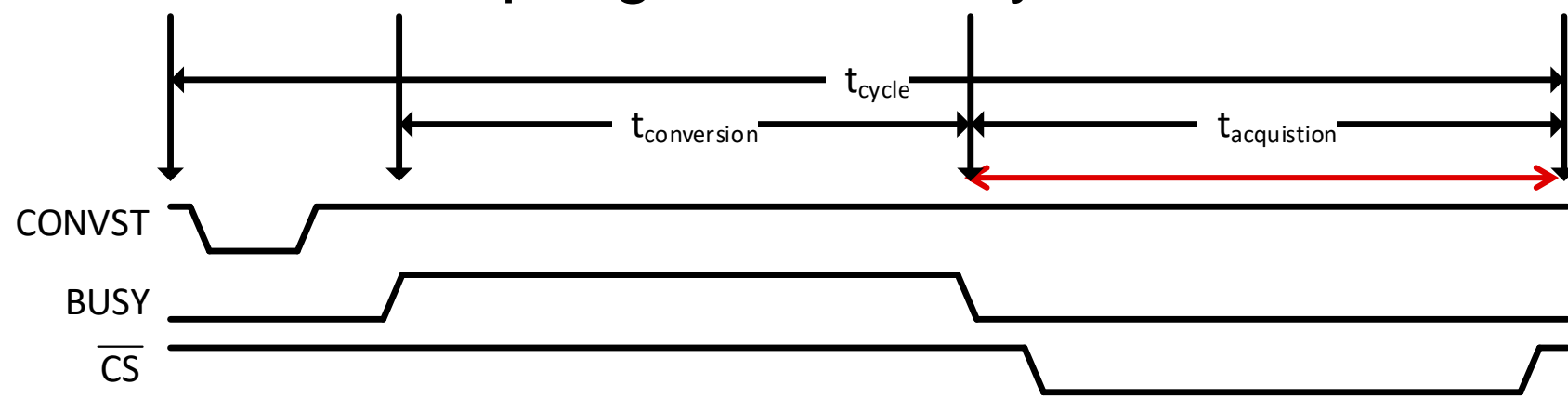- Conversion time is fixed due to internal conversion clock
- SCLK sets data output speed only, doesn't effect conversion / acquisition time
- Slower sampling rate directly adds more time for acquisition




Examples:

ADS8881

ADS8332

Acquisition Time: External Conversion Clock

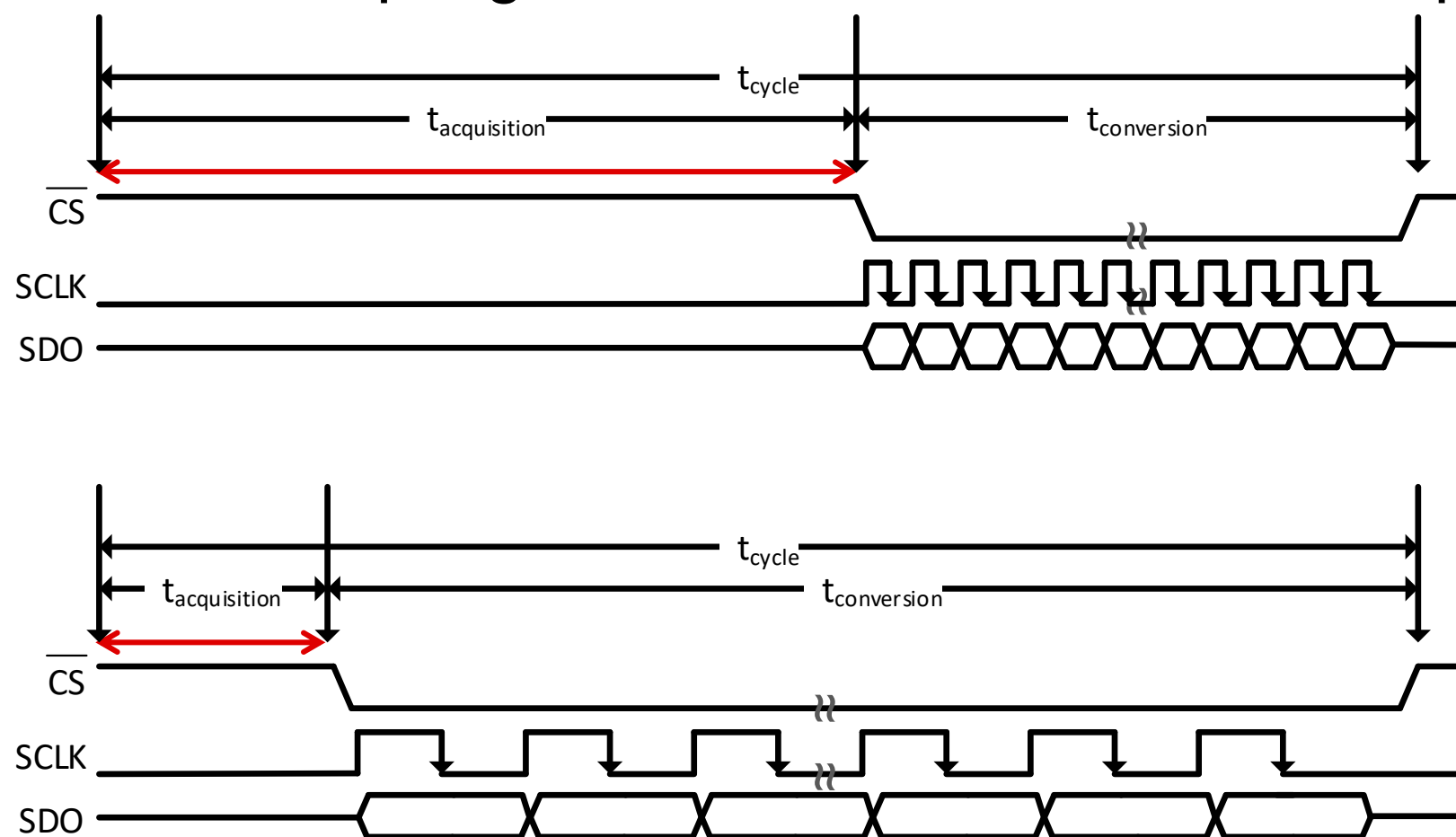- SCLK sets data output speed and conversion time
- Increasing SCLK frequency increases acquisition time for same sampling rate
- Slower sampling rate with the same SCLK frequency increases acquisition time




Examples:

ADS7042

ADS7056

Acquisition Time: Other

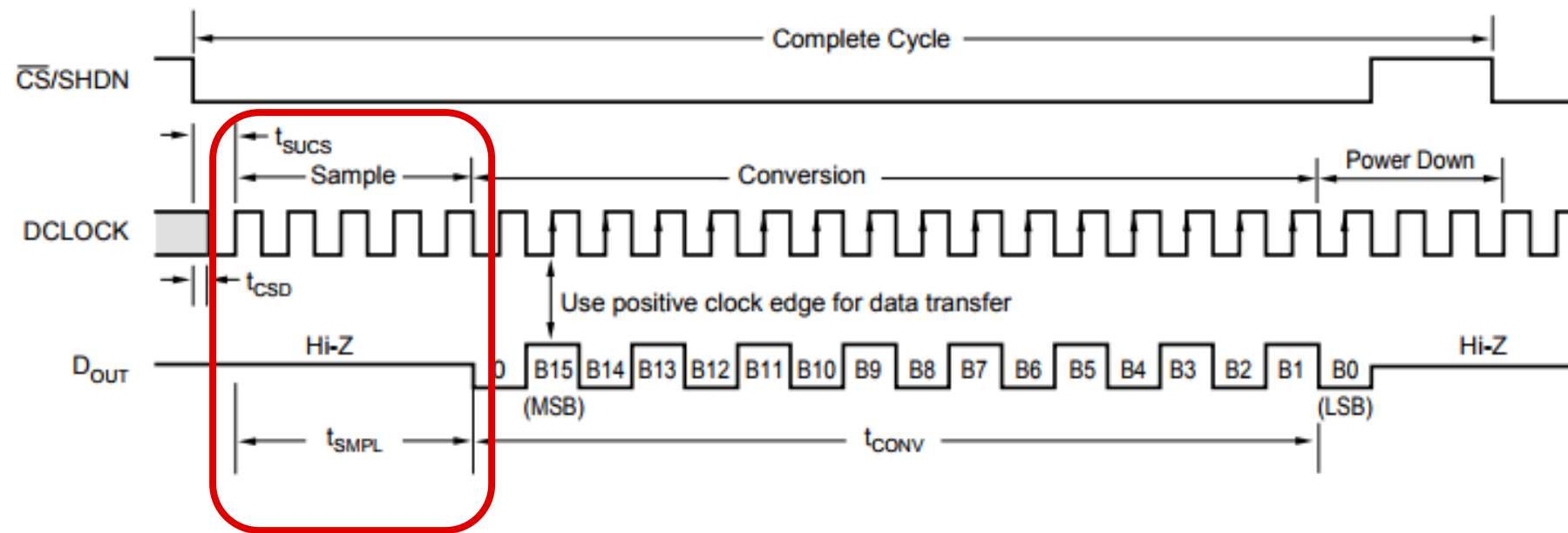
- I2C
- Fixed Acquisition
- Always check the datasheet for timing diagram






Fixed Acquisition Time

Examples:
ADS7924 – I2C
ADS8321 – Fixed Acquisition

Power of a SAR ADC

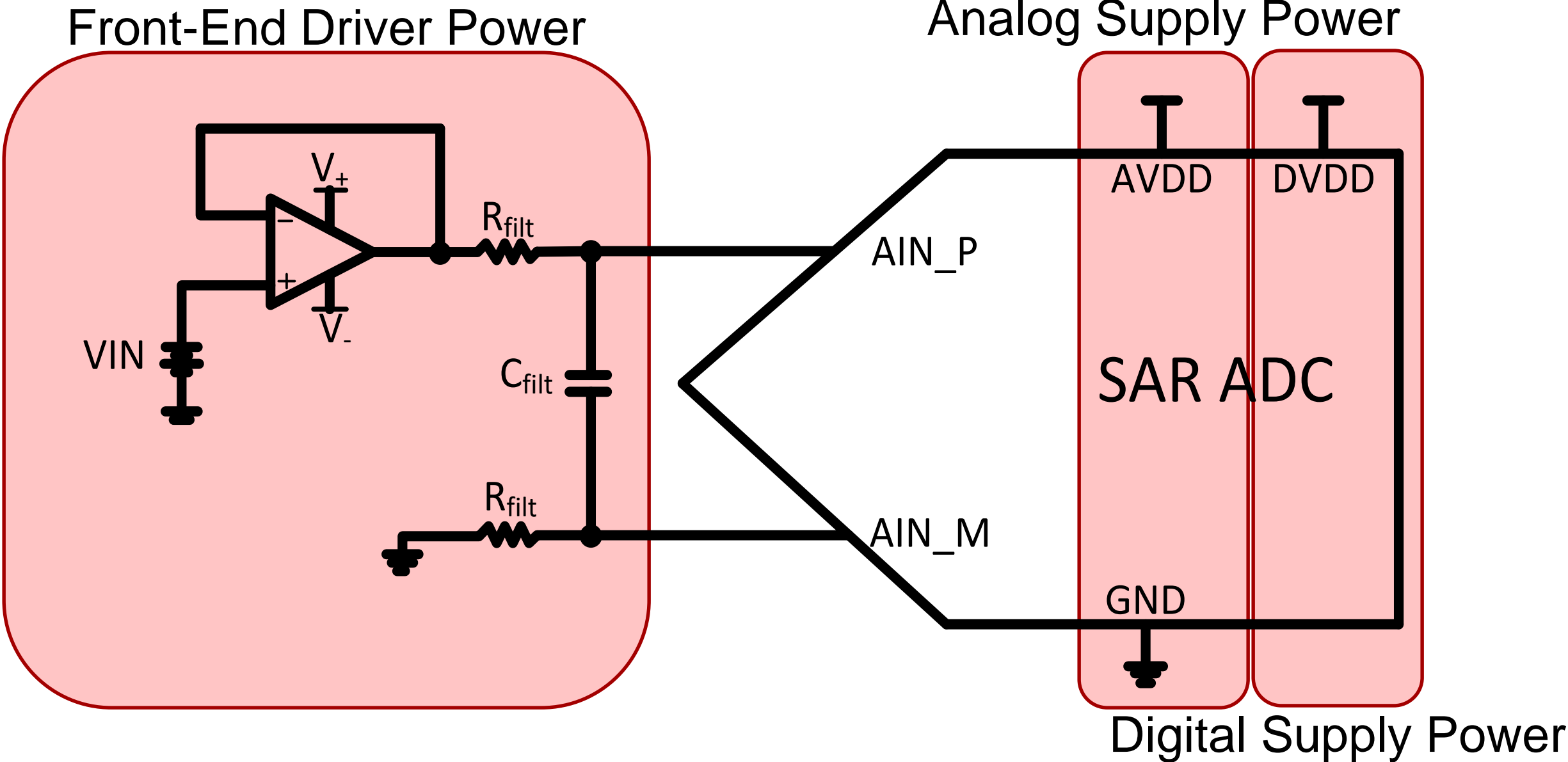

Analog Supply (AVDD) Power Consumption

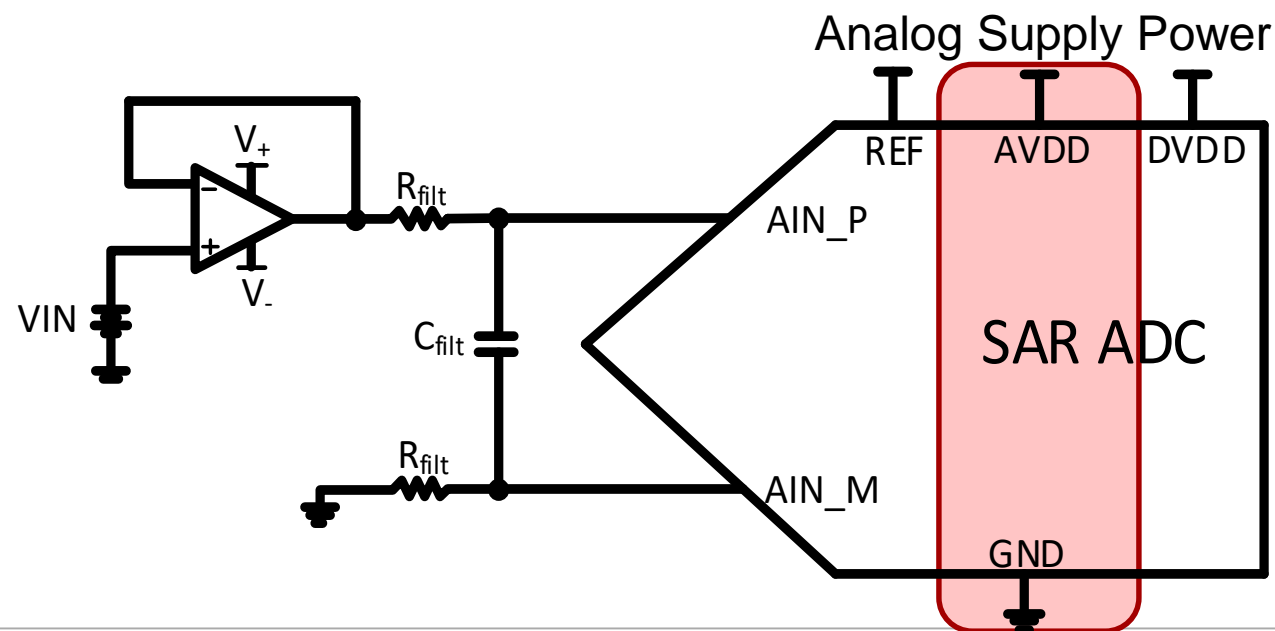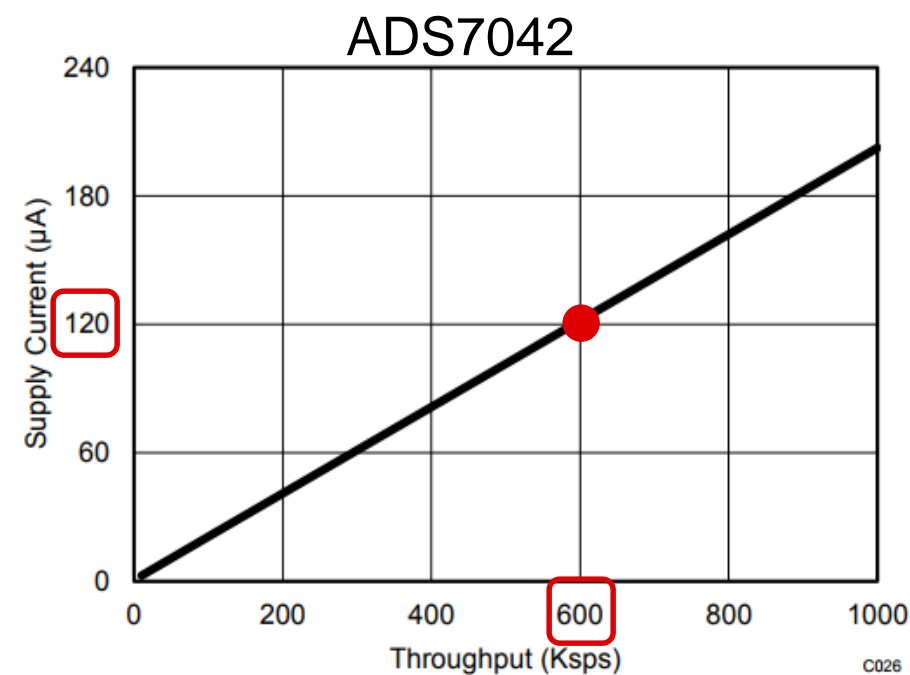 


AVDD Example Calculation:

$$P = AVDD \cdot I_{AVDD}$$

$$P = 3.3V \cdot 120\mu A = 396\mu W$$

Digital Supply (DVDD) Power Consumption

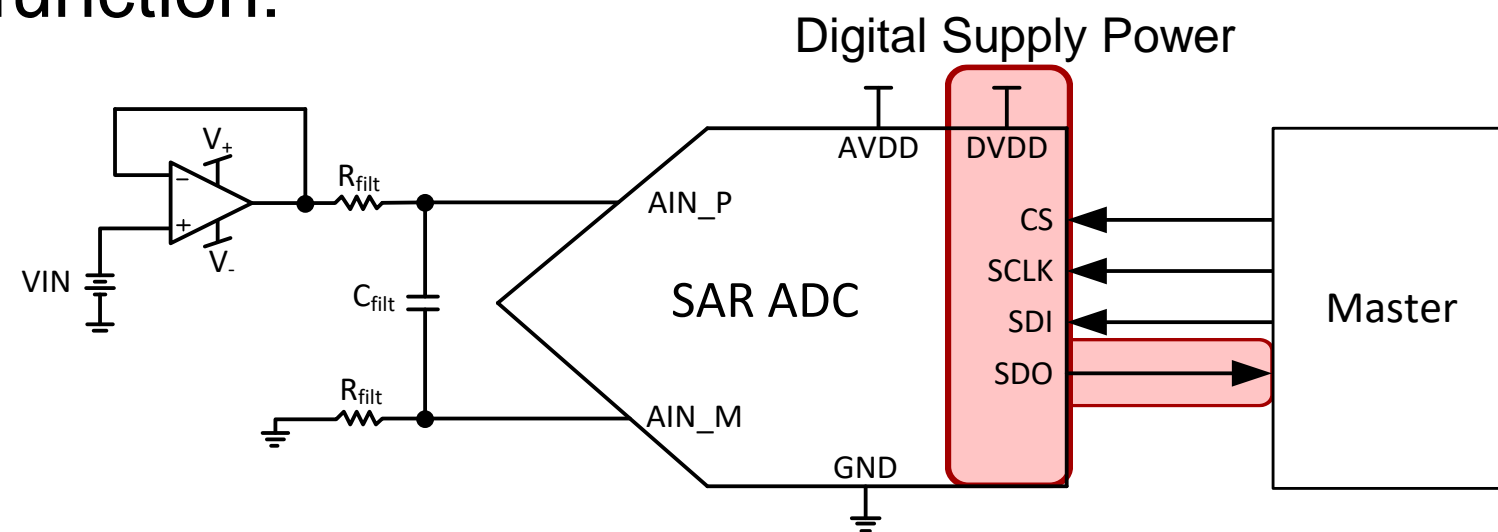- Digital supply power consumption is a function:
 - DVDD Voltage
 - Sampling rate
 - Digital output code
 - Capacitance
 - Trace + Pin + External



$$I_{DVDD} = C_{SDO} \cdot DVDD \cdot f$$

Where


I_{DVDD} is the DVDD supply current

C_{SDO} is the load capacitance on SDO

$DVDD$ is the digital supply voltage


f is the frequency of transitions on the SDO output

Maximum SDO Transitions for 12-bit SAR

 

Minimizing Digital Supply Power Consumption

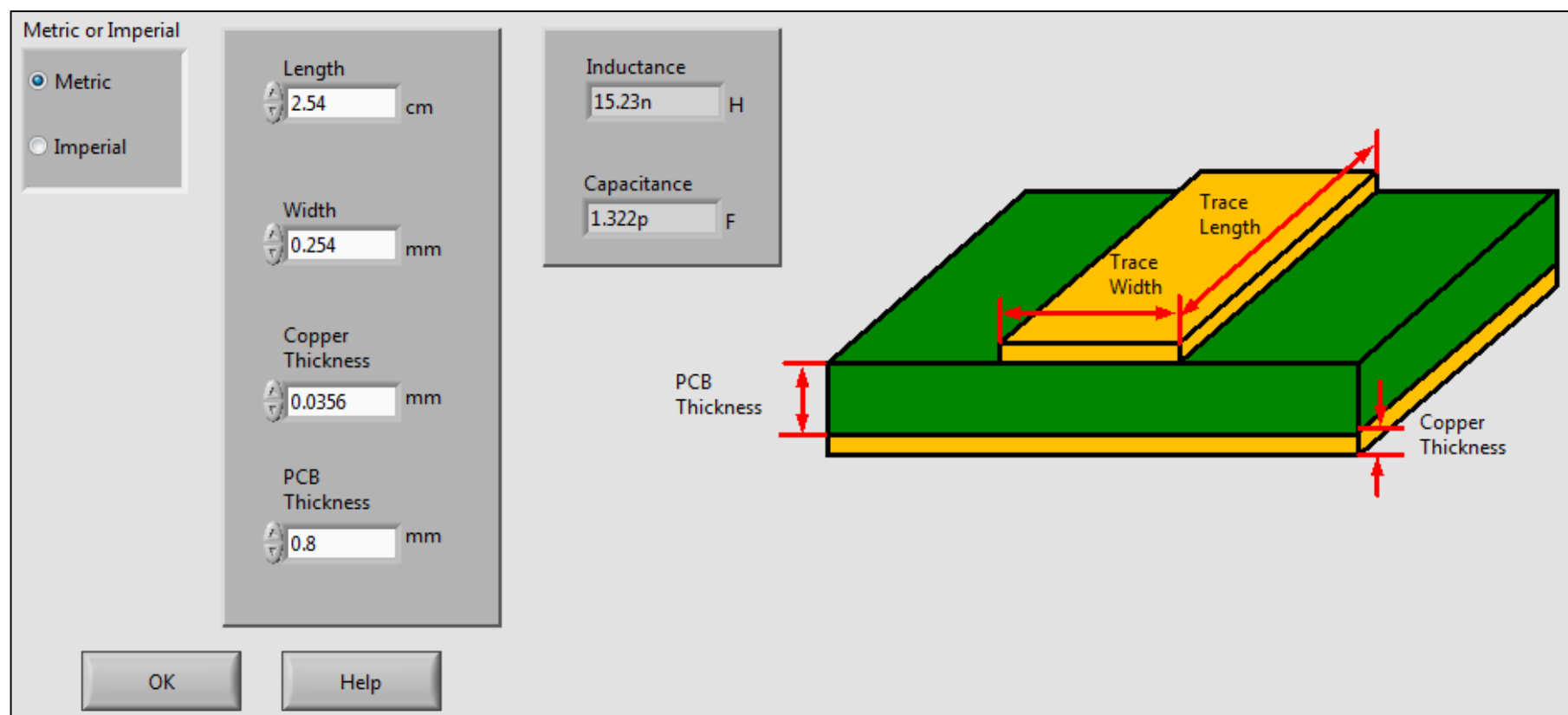- Use a lower digital voltage (ex. use 1.8V logic instead of 3.3V logic)
- Run the device at lowest applicable throughput
- Reduce the trace capacitance of SDO line
 - Analog Engineer's Calculator can be used to determine PCB capacitance



DVDD Supply Power: Example Calculation

- DVDD Voltage = 3.3V
- Pin Capacitance = 3 pF for both ADC and Master
- SDO Trace Capacitance (2.54 cm long, 0.254 mm wide) = 1.322 pF
- Sampling rate = 1 MSPS
- Frequency of SDO Transitions (12 bit transitions, 1 μs cycle time)

$$\begin{aligned} P_{DVDD} &= DVDD \cdot I_{DVDD} = DVDD \cdot (C_{SDO} \cdot DVDD \cdot f) \\ &= 3.3V \cdot \left((1.322pF + 3pF + 3pF) \cdot 3.3V \cdot \frac{12 \text{ bit}}{1\mu s} \right) = 956.8\mu W \end{aligned}$$

Where

P_{DVDD} is the total DVDD supply power



I_{DVDD} is the DVDD supply current

C_{SDO} is the load capacitance on SDO

DVDD is the digital supply voltage

f is the frequency of transitions on the SDO output

Front-End Driver Power Consumption

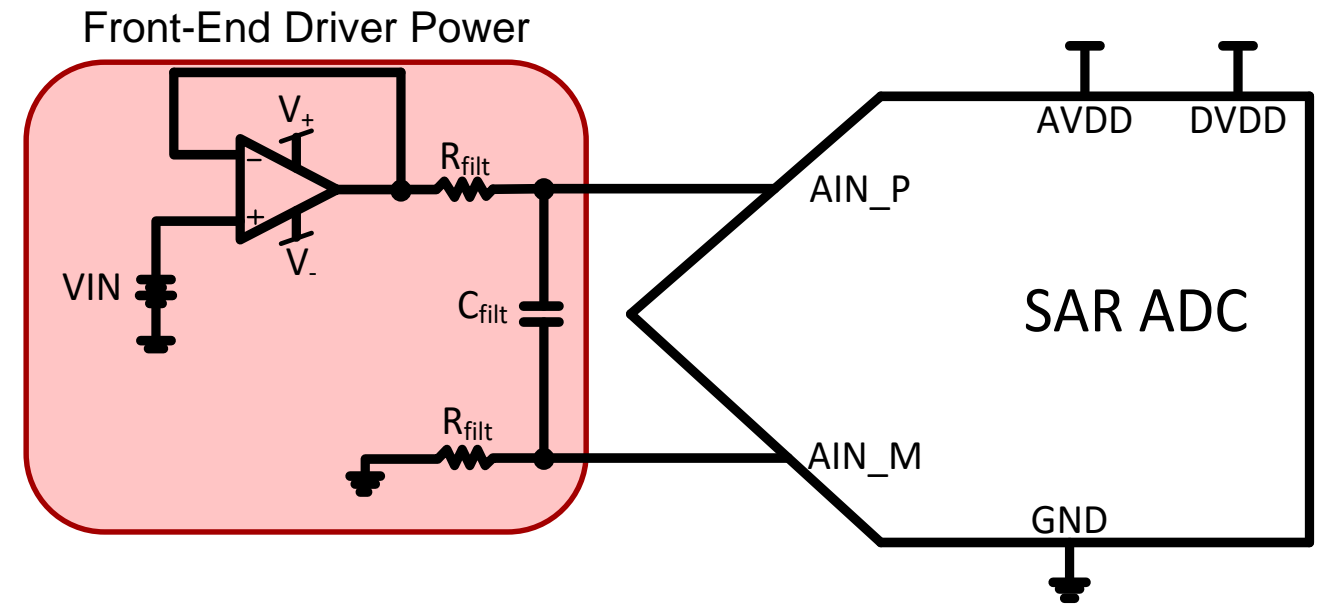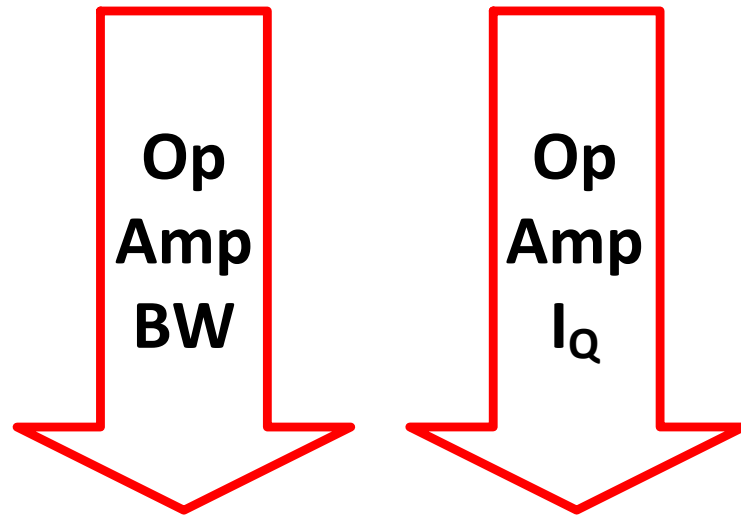

Amplifier	Bandwidth	I_Q
OPA365	50 MHz	5 mA
OPA211	45 MHz	3.6 mA
OPA320	20 MHz	1.45 mA
TLV313	1 MHz	65 μ A
LPV811	8 kHz	450 nA

$$P = I_Q \cdot ((V_+) - (V_-))$$

Where



P is the amplifier power consumption

I_Q is opamp quiescent current

V_+ is positive opamp power supply

V_- is negative opamp power supply

Front-End Driver Tradeoffs

 
 


$$e_n \propto 1/\sqrt{I_Q}$$

Where

e_n is opamp noise density

I_Q is opamp quiescent current

  

- Large feedback resistors will act as a small load and result in less power consumption but add more noise
- A good rule of thumb is to keep the Op Amp noise dominant

$$e_{n_{opa}} \geq 3 \cdot e_{n_{res}}$$



Where

$e_{n_{opa}}$ is opamp noise density

$e_{n_{res}}$ is resistor noise density

Driving a SAR ADC without a Driver Amplifier

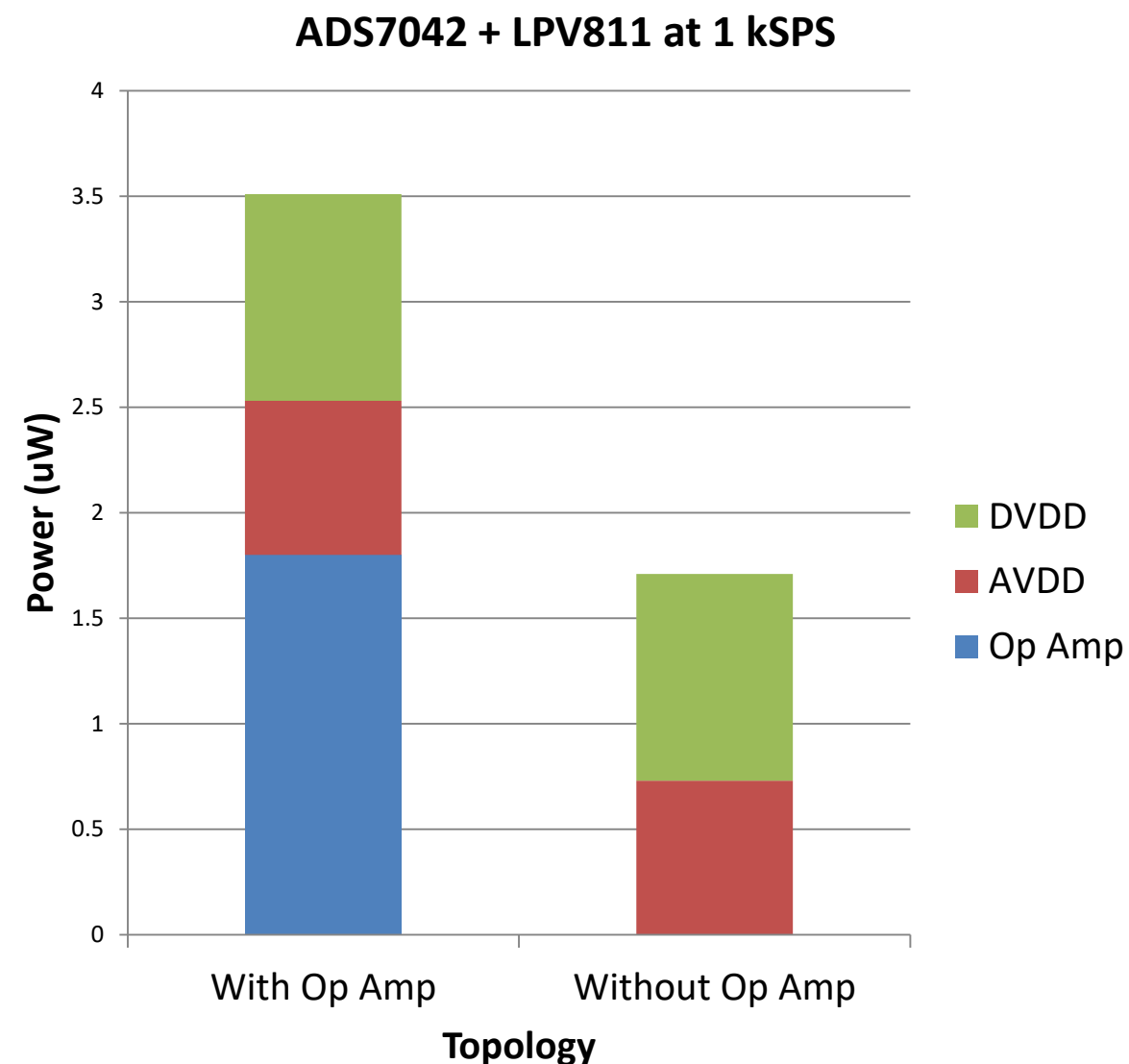 - Low frequency voltage inputs can be connected directly to the SAR ADC
- Applicable for low sampling rates (<20 kSPS)





Power Scaling Example

ADS7042

AVDD = 3.3V, DVDD = 3.3V, Op Amp Supply = 4.5V

Power Level	Amplifier	Sampling Rate	Measured Amplifier Power	Measured Analog Power	Measured Digital Power	Total System Power
Low	LPV811	1 kSPS	1.8 μ W	0.737 μ W	0.988 μ W	3.5 μ W
Medium	TLV313	100 kSPS	192.7 μ W	73.1 μ W	135.8 μ W	401.7 μ W
High	OPA320	1 MSPS	6386 μ W	708.3 μ W	655.2 μ W	7750 μ W

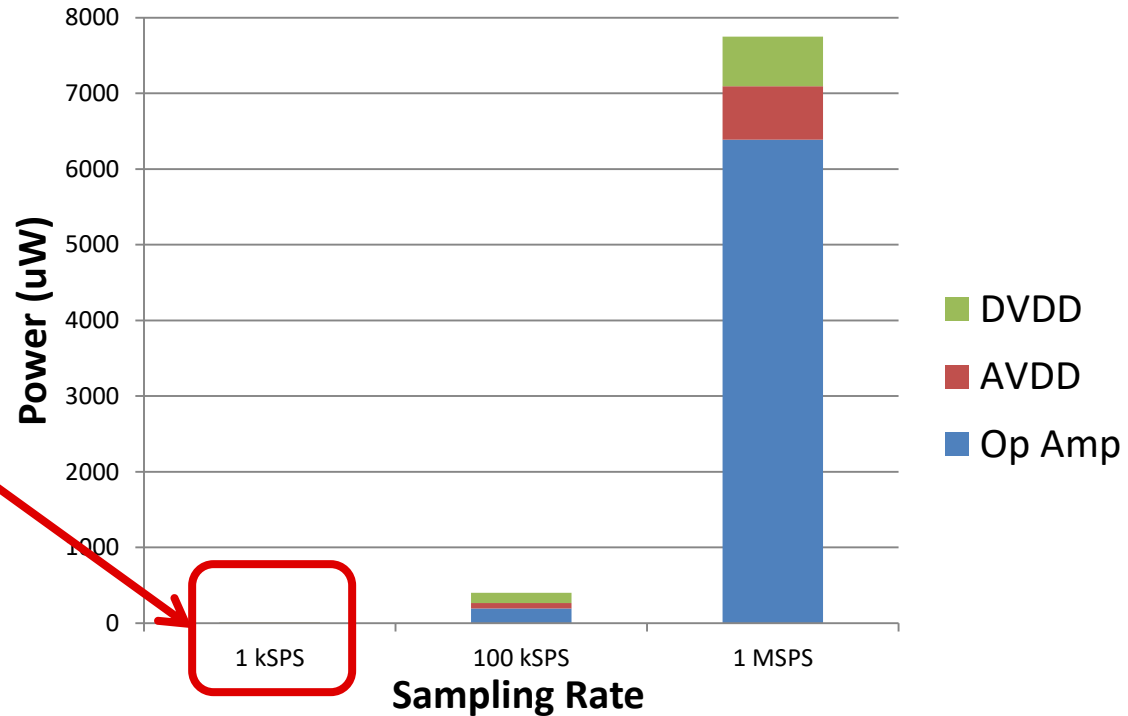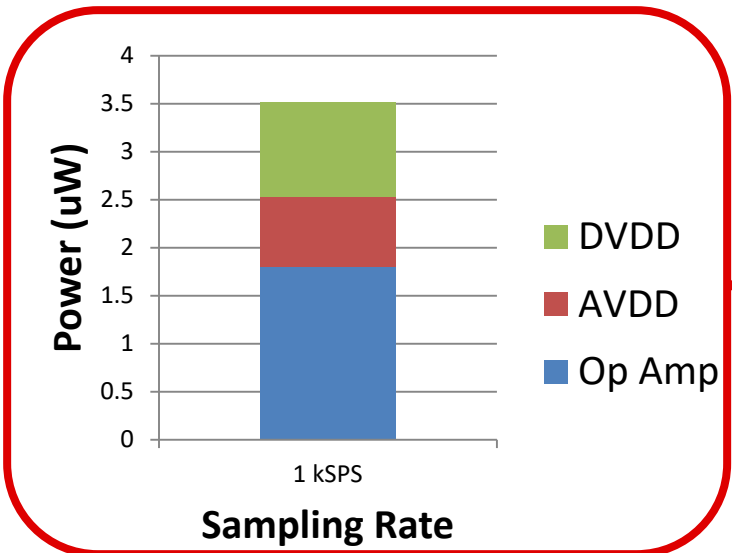

Thanks for your time!
Please try the quiz.

SAR ADC Power Scaling

TIPL 4601

TI Precision Labs – ADCs

Created by Peggy Liska

SAR ADC Power Scaling

1. (T/F) Most of the power is consumed by the SAR ADC during the acquisition phase.
 - a. True
 - b. False

2. You can always reduce the overall power consumption of a SAR ADC by _____.
 - a. Decreasing the acquisition time
 - b. Increasing the acquisition time
 - c. Decreasing the SCLK speed
 - d. Increasing the SCLK speed

SAR ADC Power Scaling

3. Which of the following is NOT a way to reduce digital supply (DVDD) power consumption?
 - a. Decrease the digital logic voltage level
 - b. Increase the throughput of the ADC
 - c. Reduce the trace capacitance of the SDI line
 - d. Both a & c
 - e. Both b & c

4. (T/F) Large feedback resistors on the front-end driver reduce power consumption but add noise.
 - a. True
 - b. False

SAR ADC Power Scaling

5. Calculate the digital supply power consumption using the following values:

HINT: Use the [Analog Engineer's Calculator](#).

- DVDD Voltage = 1.8 V
- SDO Trace Dimensions = 1000 mils long, 10 mils wide
- Copper Thickness = 1 oz
- PCB Thickness = 31 mils
- Sampling rate = 1 MSPS
- ADC Resolution = 12-bit

Solutions

SAR ADC Power Scaling

1. (T/F) Most of the power is consumed by the SAR ADC during the acquisition phase.
 - a. True
 - b. False**

2. You can always reduce the overall power consumption of a SAR ADC by _____.
 - a. Decreasing the acquisition time
 - b. Increasing the acquisition time**
 - c. Decreasing the SCLK speed
 - d. Increasing the SCLK speed

SAR ADC Power Scaling

3. Which of the following is NOT a way to reduce digital supply (DVDD) power consumption?
- a. Decrease the digital logic voltage level
 - b. Increase the throughput of the ADC
 - c. Reduce the trace capacitance of the SDI line
 - d. Both a & c
 - e. **Both b & c**
4. (T/F) Large feedback resistors on the front-end driver reduce power consumption but add noise.
- a. **True**
 - b. False

SAR ADC Power Scaling

5. Calculate the digital supply power consumption using the following values:

HINT: Use the [Analog Engineer's Calculator](#).

- DVDD Voltage = 1.8 V
- SDO Trace Dimensions = 1000 mils long, 10 mils wide
- Copper Thickness = 1 oz
- PCB Thickness = 31 mils
- Sampling rate = 1 MSPS
- ADC Resolution = 12-bit

$$L = 15.14\text{nH}$$
$$C = 1.328\text{pF}$$

$$P = DVDD \cdot (C \cdot DVDD \cdot f)$$
$$P = 1.8V \cdot \left(1.33\text{pF} \cdot 1.8V \cdot \frac{12}{1\mu\text{s}} \right)$$
$$P = 51.7\mu\text{W}$$

