



# Control of SMPS – a Refresher

## Part 1

Colin Gillmor (APP, HPC)



# Control of SMPS – a Refresher:

## Agenda

- Part 1 {
    - 1. Concepts
    - 2. Transfer Functions
    - 3. Control Systems
  - Part 2 {
    - 4. Loop Transfer Functions
      - Control to Output:  $G(s)$
      - Output to Control:  $H(s)$
    - 5. Loop Compensation
  - Part 3 {
    - 6. Measuring the Control Loop
    - 7. Summary and other issues
    - 8. References
- Power Stage (Plant)  
Feedback (Control)



# Control of SMPS – a Refresher:

## 1. Concepts

2. Transfer Functions

3. Control Systems

4. Loop Transfer Functions

Control to Output:  $G(s)$

Output to Control:  $H(s)$

5. Loop Compensation

6. Loop Compensation

7. Measuring the Control Loop

8. Summary and other issues

9. References



Power Stage (Plant)

Feedback (Control)

# Concepts:

## Controllability:

- What variables can we use to control the system's state
- Eg: **Switching Frequency, Duty Cycle, Handlebars**

## Observability:


- How can we determine the system's state
- Eg: **Measure  $V_{out}$ ,  $V_{in}$ ,  $I_{out}$ , Inductor Current, Eyes**

## Reachability:

- Does the control system have enough authority to do what we want it to do?
- Eg: **Transient response, Trim range, Current limit  
Start-up time, Lean limits (aka, training wheels)**
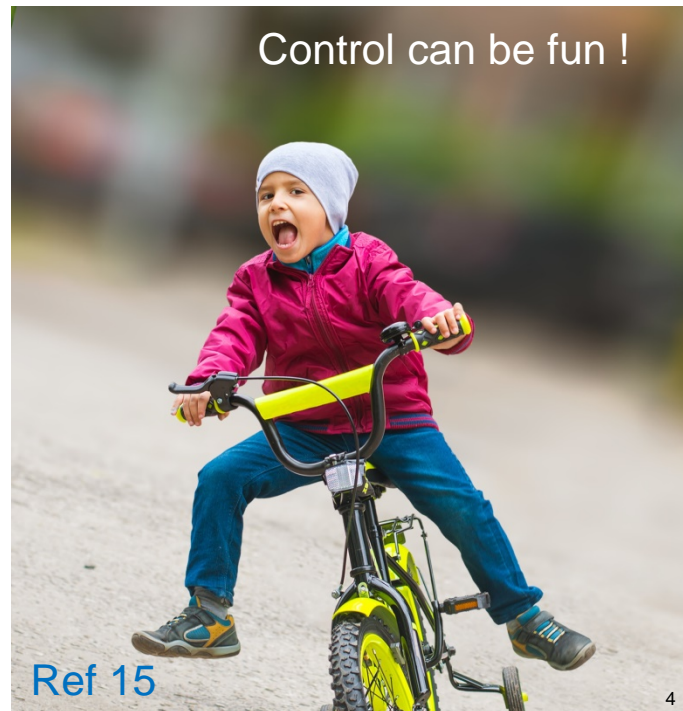
## Control:

- Measure the system
- Compare to reference
- Adjust appropriately



# Concepts: LTI, Linear Time-Invariant

Linearity  $f(a+b) = f(a) + f(b)$  ,  $f(k*a) = k*f(a)$

- System response doesn't depend on the load power or current
- Non-Linear at OCP, OVP, Enhanced Dynamic Response etc

Time Invariance


- System does not change with time
- Exceptions at power up, power down, OCP etc
- Switching action in power stage must be averaged

Continuous time assumed

- Time variable is continuous and can take up any value
- Assumption is valid up to about 20% of switching frequency

Switching frequency does not appear in the transfer function !

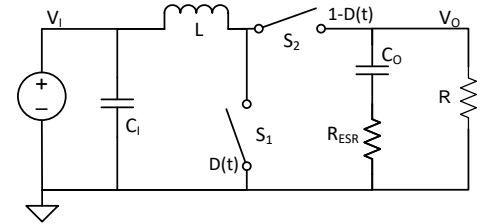SMPS are not linear and are not time invariant !



So we 'cheat' and build a model which is LTI 😊

- Linearisation
- State Space Averaging

$$G(s) = A_{VC} \cdot \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{Q_0 \cdot \omega_0} + \frac{s^2}{\omega_0^2}}$$

Typical Buck Converter model

# Concepts: Complex Frequency (s)

Complex Frequency:  $s = \sigma + j\omega$

$\sigma$  sets decay rate,


- $\sigma > 0$ , increasing:  $\sigma < 0$ , decaying:  $\sigma = 0$ , steady state
- We set  $\sigma$  to 0 and so that  $s = j\omega$
- $\omega$  is the frequency of the underlying sine wave

$$V_i(t) = \text{Re}\left(V_m \cdot e^{\sigma \cdot t} \cdot \cos(\omega \cdot t + \varphi)\right)$$

$y(s)$  contains Magnitude and Phase information.

Really useful property – a single calculation gives

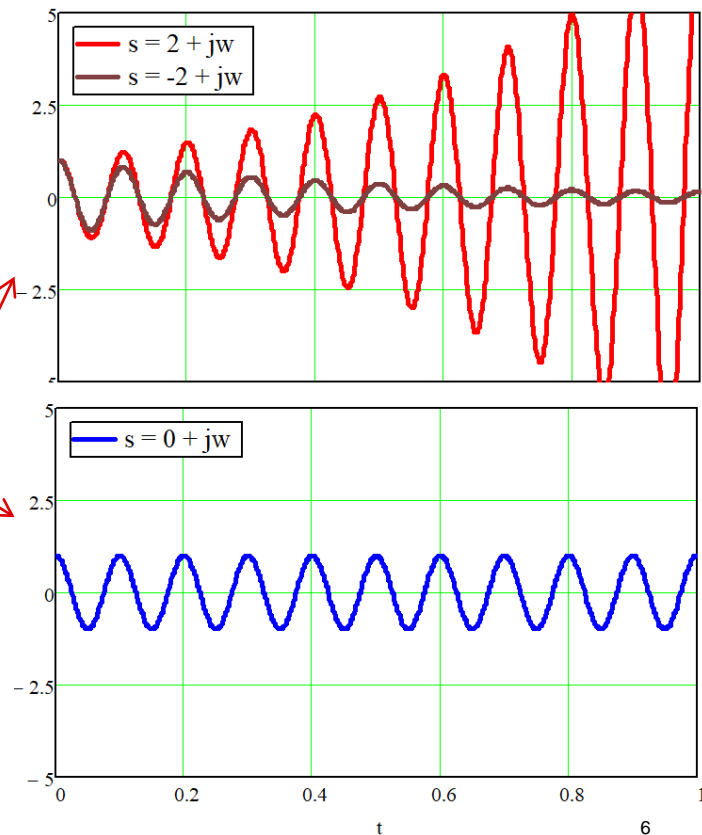
- Magnitude =  $\text{Mag}[y(s)]$ ,
- Phase =  $\text{arg}[y(s)]$  (radians !)





# Control of SMPS – a Refresher:

1. Concepts
- 2. Transfer Functions**
3. Control Systems
4. Loop Transfer Functions
  - Control to Output:  $G(s)$
  - Output to Control:  $H(s)$
5. Loop Compensation
6. Measuring the Control Loop
7. Summary and other issues
8. References



Power Stage (Plant)  
Feedback (Control)

# Transfer Functions: Bode Plots

The transfer function is basically  $V_o(s) / V_i(s)$


- $H(s)$ ,  $G(s)$ ,  $Y(s)$  etc, etc,
- Calculated or Measured
- A function frequency
- Complex frequency gives Magnitude and Phase

Bode Plot, Magnitude and Phase versus frequency


- Frequency is on a Log scale
- Magnitude in dB:  $20 \log (V_o/V_i)$
- Phase in deg:  $\theta_{IN} - \theta_O$
- Can use straight line approximations (dotted)

Note

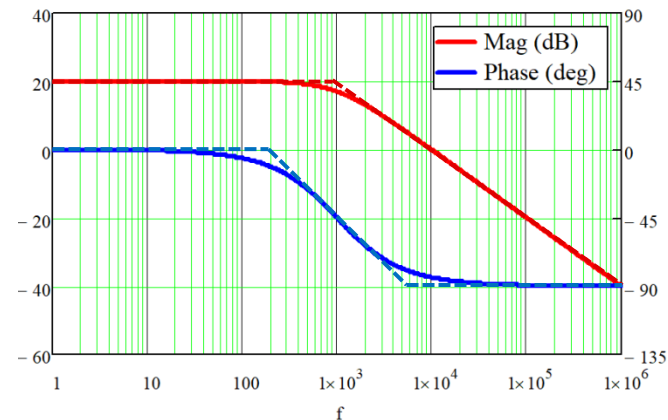- Magnitude, Amplitude, Gain are equivalent


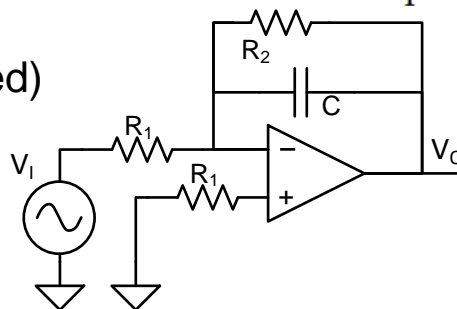
$$G(s) = \frac{-R_2}{R_1} \cdot \frac{1}{1 + \frac{s}{\omega_p}} \quad \text{where} \quad \omega_p = \frac{1}{R_2 \cdot C}$$





# Transfer Functions: Poles

$$G(s) = \frac{-R_2}{R_1 \cdot (R_2 \cdot sC + 1)} = \frac{-R_2}{R_2} \cdot \frac{1}{1 + sCR_2} = \frac{-R_2}{R_1} \cdot \frac{1}{1 + \frac{s}{\omega_0}}$$

$$G(s) = \frac{-R_2}{R_1} \cdot \frac{1}{1 + \frac{s}{\omega_0}}$$

where  $\omega_0 = \frac{1}{R_2 \cdot C}$

LF gain is  $-R_2/R_1$

Gain rolls off at  $-20\text{dB per decade}$  above  $\omega_0$


Gain is flat below  $\omega_0$

Phase flat below  $\omega_0 / 10$  and above  $10 \omega_0$


**Phase is:**

- $0^\circ$  at LF
- $-45^\circ$  at  $\omega_0$
- $-90^\circ$  at HF

Pole  
-3dB  
-45°

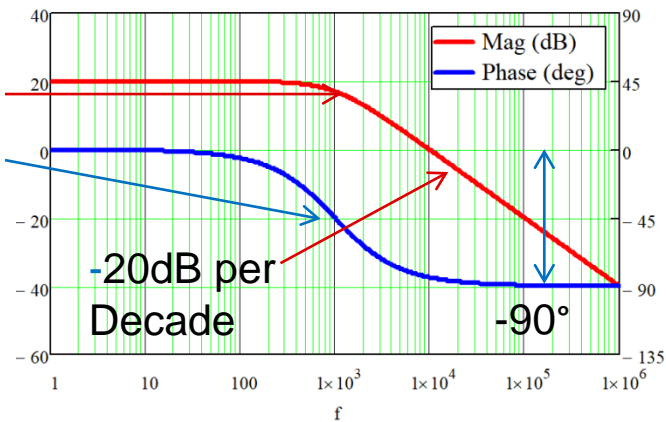

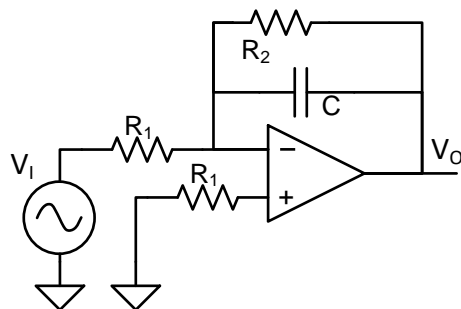
Gain is  $-3\text{dB}$  at  $\omega_0$       $f_p = \frac{1}{2\pi R_2 C}$


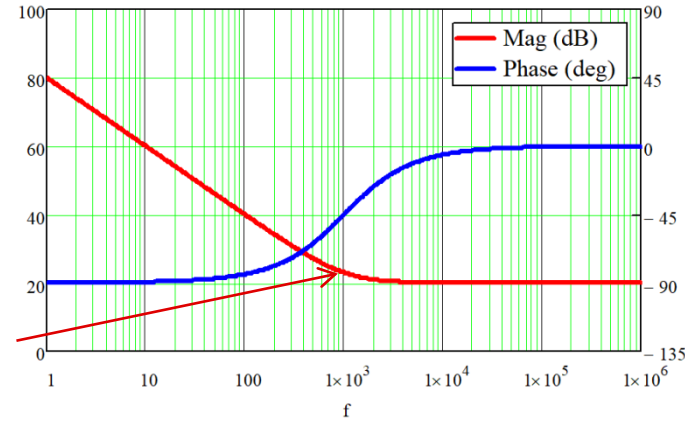
# Transfer Functions: Zeros


$$G(s) = \frac{-z_1}{z_2} = \frac{-\left(R_2 + \frac{1}{sC_1}\right)}{R_1} = \frac{-R_2}{R_1} \left(1 + \frac{1}{sCR_2}\right) = \frac{-R_2}{R_1} \left(1 + \frac{\omega_Z}{s}\right)$$

$$G(s) = \frac{-R_2}{R_1} \left(1 + \frac{\omega_Z}{s}\right) \quad \text{where} \quad \omega_Z = \frac{1}{R_2 \cdot C} \quad \leftarrow \text{Zero}$$




Used in Type 2 compensator to add some phase boost and so increase the phase margin

+3dB at  $f_z = \frac{1}{2\pi R_2 C}$

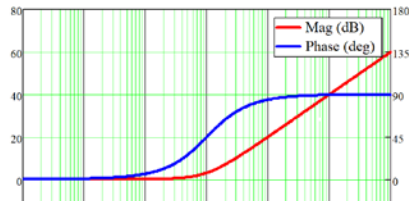

Alternative form

$$G(s) = 1 + \frac{s}{\omega_Z}$$

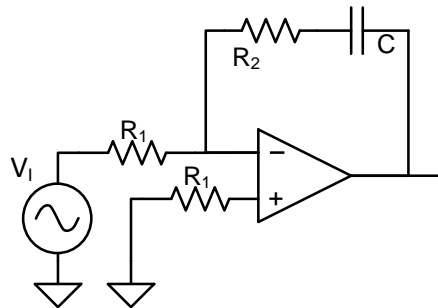


# Transfer Functions: Complex Conjugate Poles

Complex Conjugate Poles: Resonance,  
Phase decreasing to  $-180^\circ$   
Q determines peak response

Gain rolls off at  $-40\text{dB}$  per decade above  $\omega_0$


Phase is:

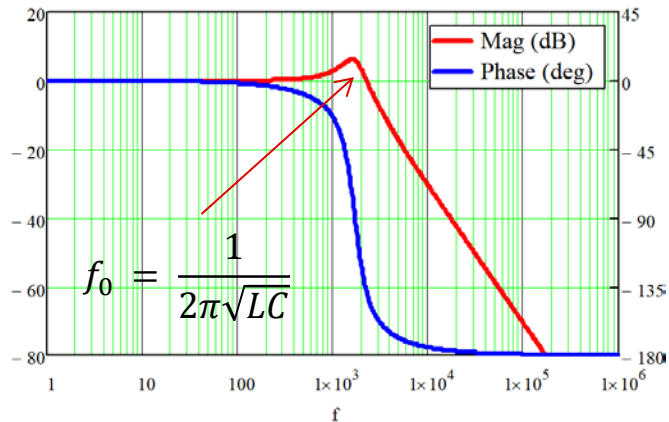- $0^\circ$  at LF
- $-90^\circ$  at  $\omega_0$
- $-180^\circ$  at HF



$$G(s) = \frac{1}{1 + \frac{s}{Q \cdot \omega_0} + \frac{s^2}{\omega_0^2}}$$

$$Q = \frac{R}{\sqrt{L/C}}$$

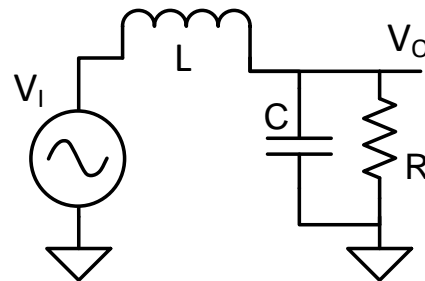

# Transfer Functions: Right Half Plane Zero

RHPZ:

- A characteristic of topologies which deliver energy to the output  $180^\circ$  out of phase with the energy taken from the input Flyback, Boost, Cuk, (CCM only).

RHPZ: (Right Half Plane Zero)



- Gain increasing Phase decreasing
- Almost impossible to compensate for this
- Must close the loop at frequencies  $\ll \omega_z$

RHPZ is not an issue in Boost PFC

- They must close the loop at very low frequencies for other reasons,  $\text{typ} < 10 \text{ Hz}$ .
- Controlled quantity is input current, not output current

Ref 1


$$G(s) = 1 - \frac{s}{\omega_z}$$

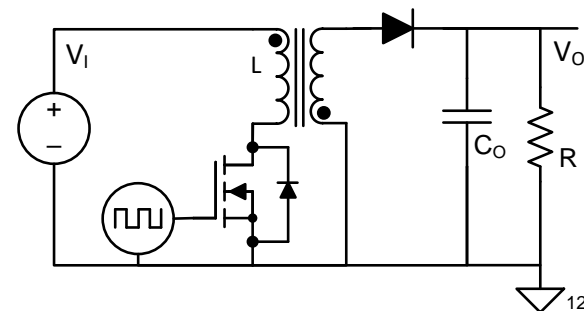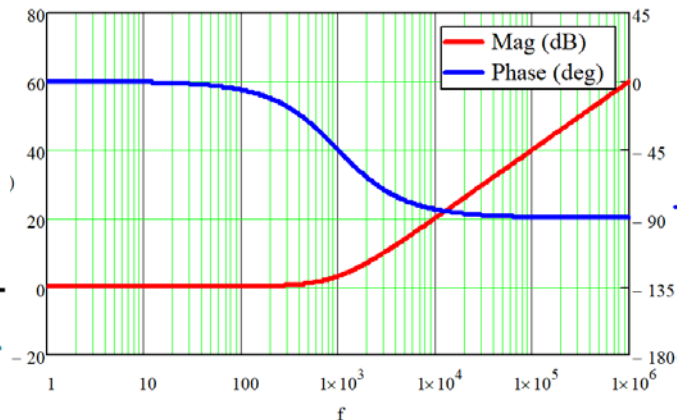



# Control of SMPS – a Refresher:

1. Concepts
2. Transfer Functions
- 3. Control Systems**
4. Loop Transfer Functions
  - Control to Output:  $G(s)$
  - Output to Control:  $H(s)$
5. Loop Compensation
6. Measuring the Control Loop
7. Summary and other issues
8. References



Power Stage (Plant)  
Feedback (Control)

# Control Systems: Variables

Many SMPS use Duty Cycle (D) as the control variable

- CCM, PSFB, Push-Pull

Sometimes D and  $F_{SW}$  are both used

- Mainly to improve efficiency
- Quasi Resonant, DCM converters
- Conversion ratios are unchanged

$$V_{OUT} = D \cdot V_{IN}$$

Buck Converter

$$V_{OUT} = \frac{1}{1 - D} \cdot V_{IN}$$

Boost Converter

$$V_{OUT} = \frac{D}{1 - D} \cdot V_{IN}$$

Flyback Converter

Conversion factor is a function of D, not of  $F_{SW}$

LLC uses  $F_{sw}$  as the control variable

- One of a large class of resonant converters

Gain(f, Q) =

$$\left| \frac{L_N \cdot f^2}{L_N \cdot f^2 + (f^2 - 1)(1 + j \cdot f \cdot L_N \cdot Q)} \right|$$



Conversion factor is a function of  $F_{SW}$  not of D


Hysteretic SMPS use Upper and Lower limits on VOUT

# A Typical Control System:

A typical analog SMPS control system looks something like this [Ref 2: Ch6](#)

- $K_{EA}(s)$ \* Error Amplifier (transfer function as function of complex frequency)
- $K_{PWM}$  Pulse Width Modulator (A Constant)
- $K_{LC}(s)$  Output Filter
- $K_{FB}$  Feedback Potential Divider

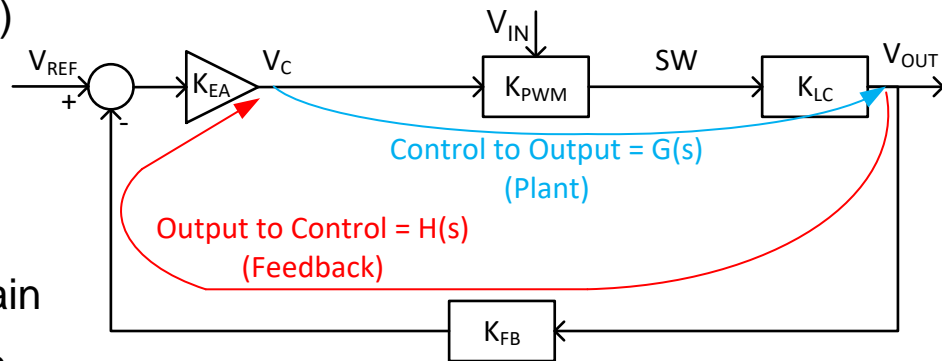- $G(s) = K_{PWM} * K_{LC}(s) =$  Control to Output gain
- $H(s) = K_{FB} * K_{EA}(s) =$  Output to Control gain
- Total loop response  $T(s) = G(s) * H(s)$



System measures the output, compares to the reference, makes an adjustment

# Two Control Systems: VMC and CMC


## VMC:

- Error Amplifier controls Duty Cycle (D) directly

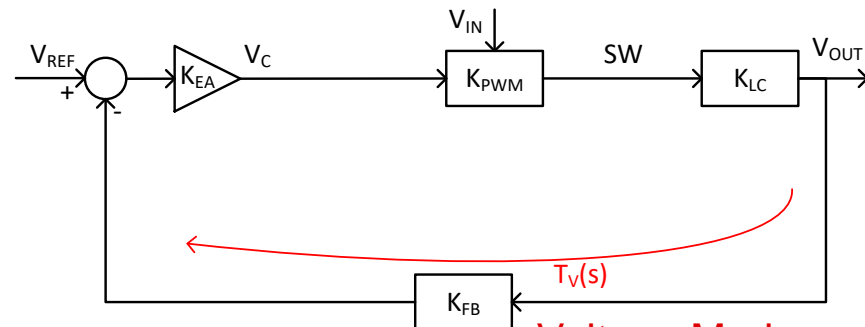
## CMC:

- PCM (Peak Current Mode)
- ACM (Average Current Mode)
- Error Amplifier sets  $I_{DEM}$  (Current Demand) for inner loop. sometimes called 'COMP'
- Inner loop regulates the output current

Other control methods do exist – not covered here



Voltage Mode Control (VMC)

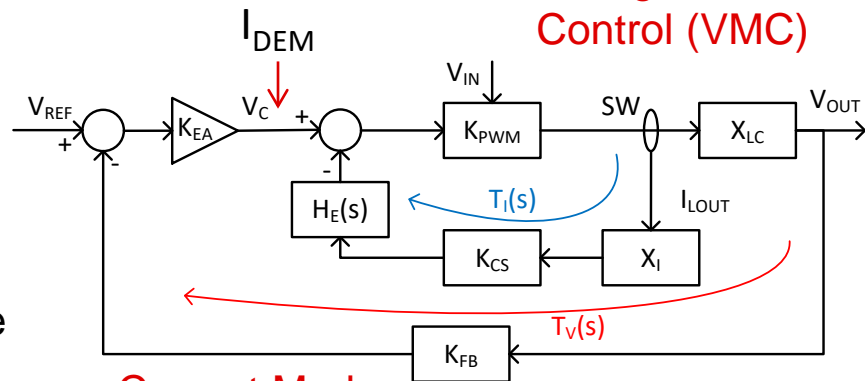

Current Mode Control (CMC)



# Control Systems: Voltage Mode Control

Error amplifier output  $V_C$  controls  $D$  directly

$V_{OUT}$  drops  $\rightarrow V_C$  increases  $\rightarrow D$  increases  $\rightarrow V_{OUT}$  increases



Less noise sensitive than PCM – larger ramp

Easy to implement Voltage Feed Forward

Output Filter appears in the transfer function so

- Control loop bandwidth is lower than with CMC
- More difficult to stabilise than CMC
- Type 3 Compensation (more on this later)

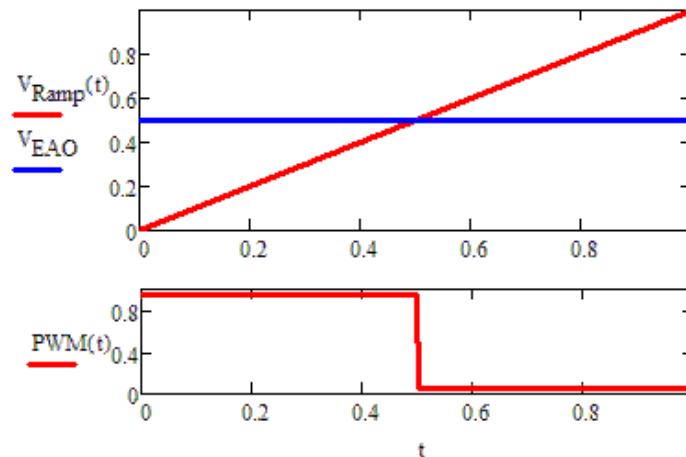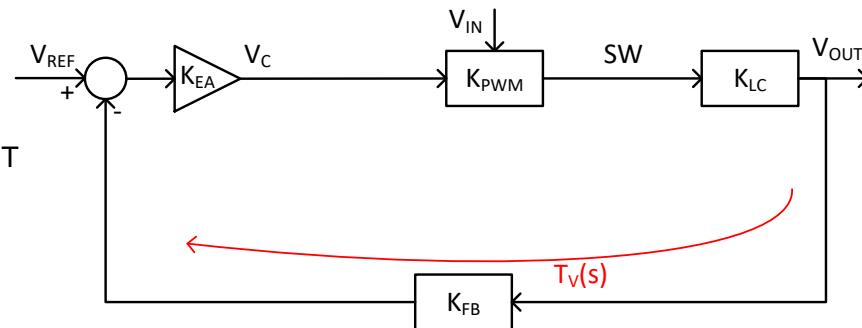Just because it's more difficult to stabilise doesn't mean that it is impossible to stabilise.



# Control Systems: Current Mode Control

Peak Current Mode – most common

Average Current Mode – used in some PFC stages

Error amplifier output  $V_C$  sets a current demand

Inner current loop forces the output current to equal the current demand.



$V_{OUT}$  drops  $\rightarrow V_C$  ( $I_{DEM}$ ) increases,  $I_{OUT}$  increases  $\rightarrow V_{OUT}$  increases

Wider loop bandwidth and easier to stabilise than VMC

Cycle-by-Cycle over current protection

Sub-Harmonic instability, (PCM in CCM)

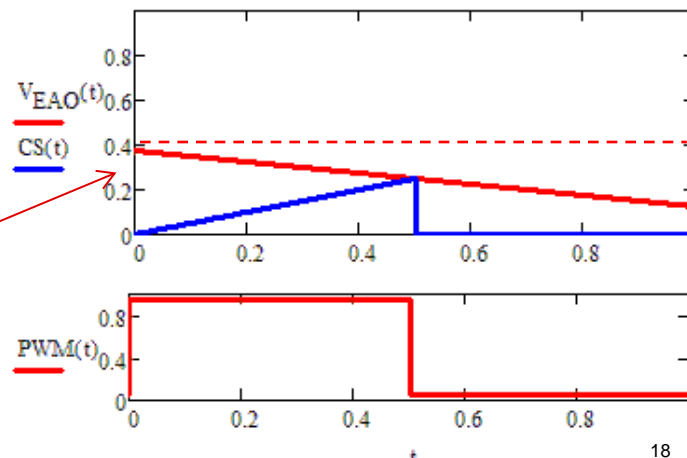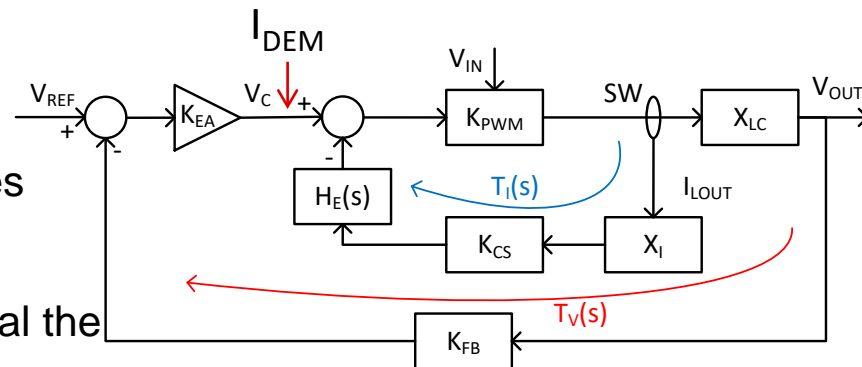- Slope Compensation (added to  $V_{EAO}$ )
- Peak-to-Average ratio not constant – distortion in PFC



# Control Systems: PCM Half Bridge instability

Peak Current Mode control of half bridge is unstable


Described in [Ref 13](#)

Voltage at centre point of  $C_1$  and  $C_2$  diverges from  $V_{IN}/2$

- This is an inherent instability

Solutions

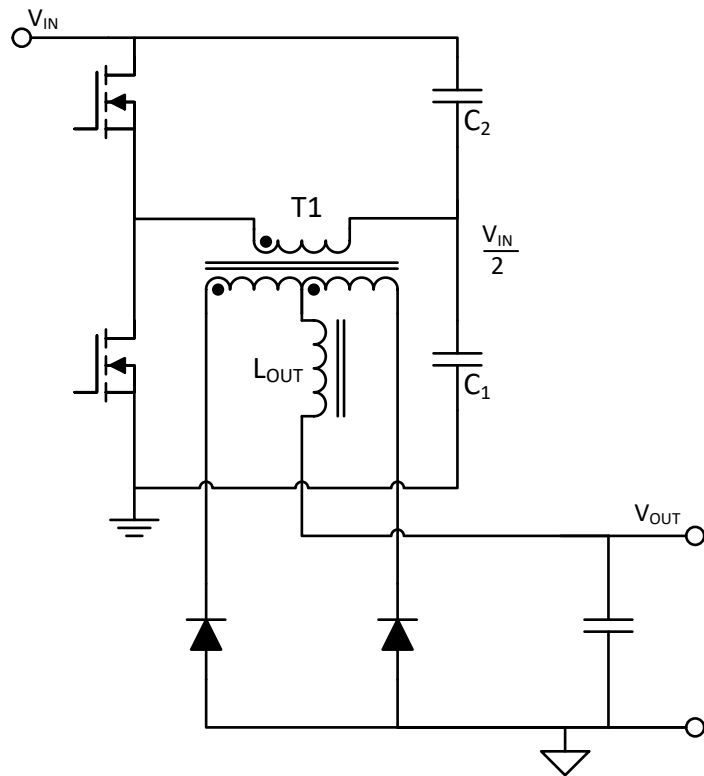- Use VMC – any half bridge controller
- Use duty cycle copy – UCC28251
- Use Average current limit - LM5039
- Modified CT circuit – see article above





# References

- 1/ The Right Half plane Zero, A Simplified Explanation, Dixon: <https://www.ti.com/seclit/ml/slup084/slup084.pdf>
- 2/ Fundamentals of Power Supply Design: Mammano: Texas Instruments, 2017
- 3/ SMPS compensation made easy, Sheehan: <https://www.ti.com/seclit/ml/slup340/slup340.pdf>
- 4/ Control Loop Cookbook, Dixon: <https://www.ti.com/seclit/ml/slup113/slup113.pdf>
- 5/ Compensation Design with TL431 for UCC28600: <http://www.ti.com/lit/an/slua671/.pdf>
- 6/ Designing with the TL431, Ridley: [https://www.researchgate.net/publication/280308828\\_Designing\\_with\\_the\\_TL431\\_-\\_the\\_first\\_complete\\_analysis](https://www.researchgate.net/publication/280308828_Designing_with_the_TL431_-_the_first_complete_analysis)
- 7/ A more Accurate Current-Mode Control Model, Ridley: <https://www.ti.com/seclit/ml/slup122/slup122.pdf>
- 8/ Modelling, Analysis and Compensation of the Current Mode Converter: <http://www.ti.com/lit/an/slua101/slua101.pdf>
- 9/ Average Current Mode Control of Switching Power Supplies, Dixon: <https://www.ti.com/seclit/ml/slup091/slup091.pdf>
- 10/ Considerations for measuring loop gain in power supplies: <https://www.ti.com/seclit/ml/slup386/slup386.pdf>
- 11/ Fundamentals of Power Electronics: Erickson and Maksimovic, ISBN 0-7923-7270-0
- 12/ Modern Control Systems: Dorf, Addison Wesley, ISBN: 0-201-51713-2
- 13/ [http://www.how2power.com/pdf\\_view.php?url=/newsletters/1204/articles/H2PToday1204\\_design\\_TexasInstruments.pdf](http://www.how2power.com/pdf_view.php?url=/newsletters/1204/articles/H2PToday1204_design_TexasInstruments.pdf)
- 14/ <http://venable.biz/uploads/files/01-Technical-Paper-Testing-Power-Sources-for-Stability.pdf>
- 15/ [https://en.wikipedia.org/wiki/Bicycle\\_and\\_motorcycle\\_dynamics](https://en.wikipedia.org/wiki/Bicycle_and_motorcycle_dynamics)



# Control of SMPS – a Refresher

End of Part 1

**Colin Gillmor (APP, HPC)**

**colingillmor@ti.com**