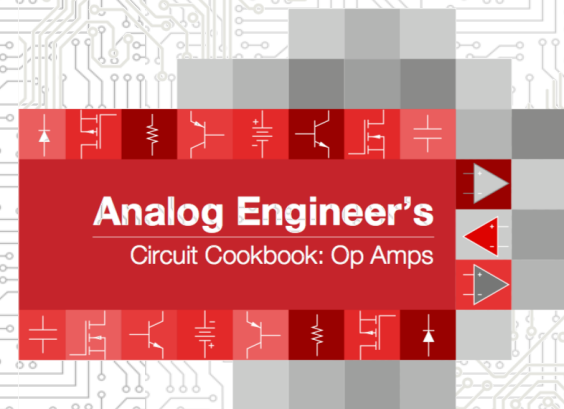


How to Design Dual-Supply, Discrete, Programmable Gain Amplifier Circuit


General Purpose Amplifiers

www.ti.com/general-amps

www.ti.com/circuitcookbooks




Circuit Description

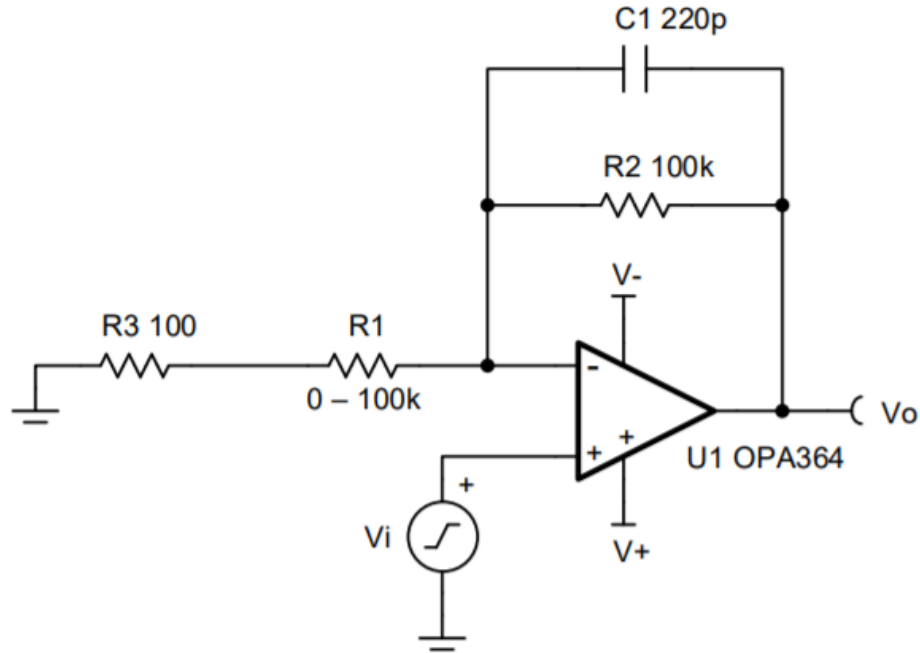

$$V_o = V_i \times \left(\frac{R_2}{R_1 + R_3} + 1 \right)$$

Design Steps

| Input | | Output | | Supply | | Gain |
|------------|------------|------------|------------|----------|----------|-------------|
| V_{iMin} | V_{iMax} | V_{oMin} | V_{oMax} | V_{dd} | V_{ee} | 6db to 60db |
| -1.25V | 1.25V | -2.4V | 2.4V | 2.5V | -2.5V | |

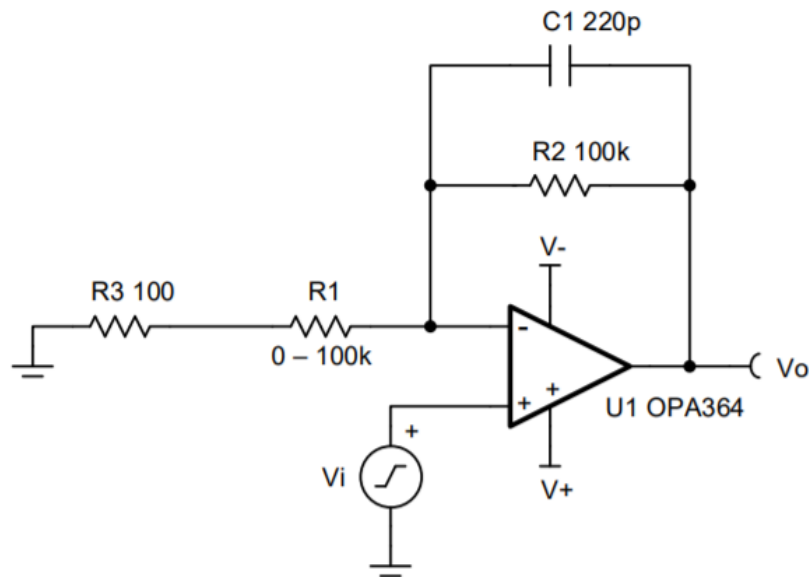


Non-Inverting
Gain

$$V_o = V_i \times \left(1 + \frac{R_2}{R_1 + R_3} \right)$$

Variable Resistor

Design Steps

| Input | | Output | | Supply | | Gain |
|------------|------------|------------|------------|----------|----------|-------------|
| V_{iMin} | V_{iMax} | V_{oMin} | V_{oMax} | V_{dd} | V_{ee} | 6db to 60db |
| -1.25V | 1.25V | -2.4V | 2.4V | 2.5V | -2.5V | |

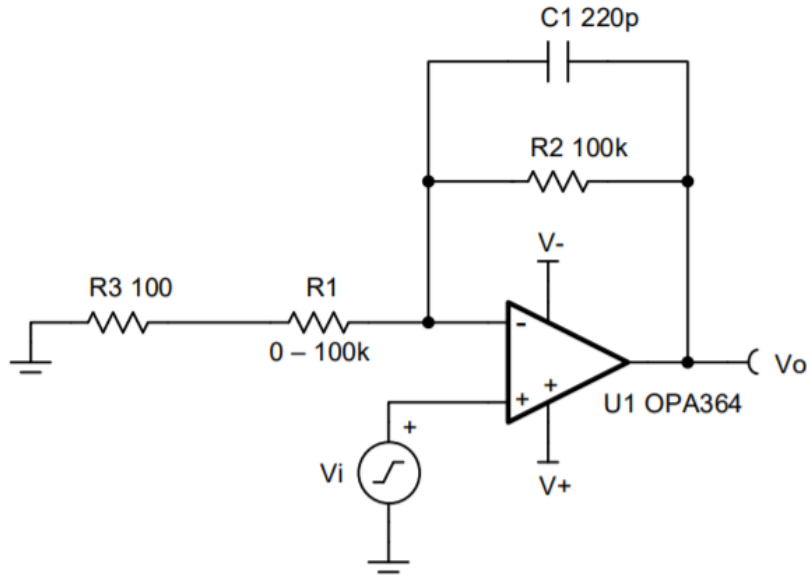

$$G_{Max} = \frac{R_2}{R_3} + 1$$


$$R_2 = (G_{Max} - 1) \times R_3$$

$$R_3 = 100\Omega$$

$$R_2 = 99k\Omega \rightarrow 100k\Omega$$

Design Steps

| Input | | Output | | Supply | | Gain |
|------------|------------|------------|------------|----------|----------|-------------|
| V_{iMin} | V_{iMax} | V_{oMin} | V_{oMax} | V_{dd} | V_{ee} | 6db to 60db |
| -1.25V | 1.25V | -2.4V | 2.4V | 2.5V | -2.5V | |

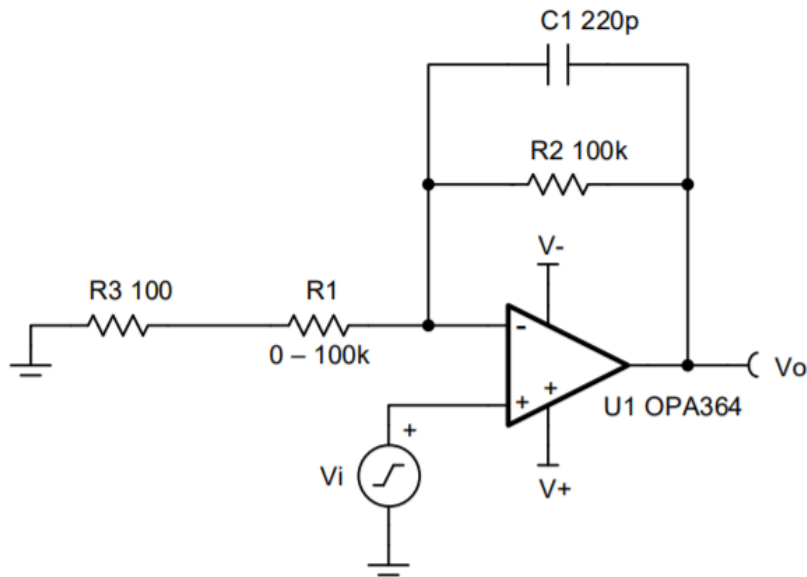


$$G_{Min} = \frac{R_2}{R_{1Max} + R_3} + 1$$

$$R_{1Max} = \frac{R_2}{G_{Min} - 1} - R_3$$

$$R_{1Max} = 99.9k\Omega \rightarrow 100k\Omega$$

Design Steps

| Input | | Output | | Supply | | Gain |
|------------|------------|------------|------------|----------|----------|-------------|
| V_{iMin} | V_{iMax} | V_{oMin} | V_{oMax} | V_{dd} | V_{ee} | 6db to 60db |
| -1.25V | 1.25V | -2.4V | 2.4V | 2.5V | -2.5V | |

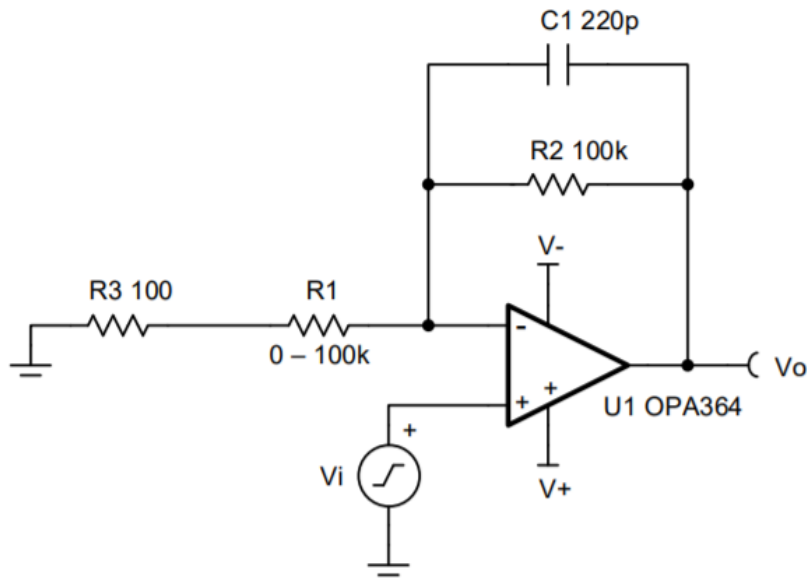


$$f_c = \frac{GBW}{G_{Max}} = \frac{7MHz}{1000V/V} = 7kHz$$

$$C_1 = \frac{1}{2 \times \pi \times R_2 \times f_c} = 227pF \rightarrow 220pF$$

Design Steps

| Input | | Output | | Supply | | Gain |
|------------|------------|------------|------------|----------|----------|-------------|
| V_{iMin} | V_{iMax} | V_{oMin} | V_{oMax} | V_{dd} | V_{ee} | 6db to 60db |
| -1.25V | 1.25V | -2.4V | 2.4V | 2.5V | -2.5V | |

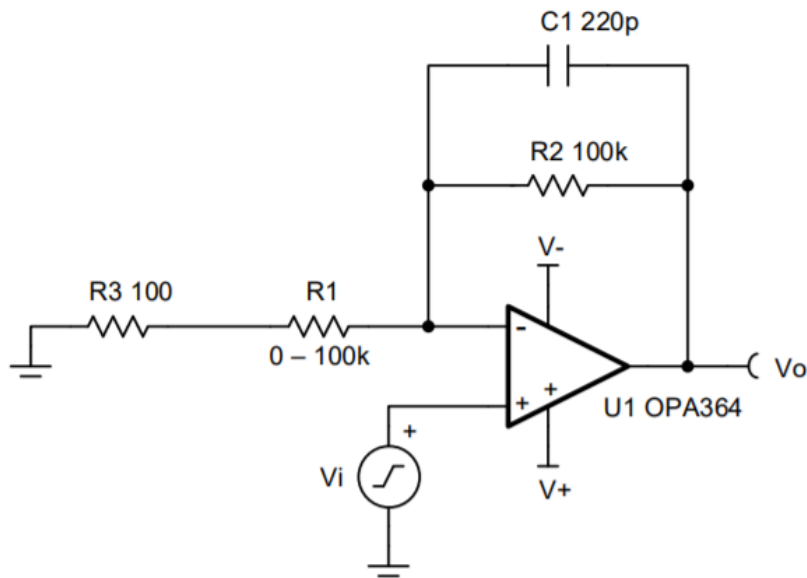



$$f_{zero} = \frac{1}{2 \times \pi \times (C_{cm} + C_{diff}) \times (R_2 || R_1)}$$

$$f_{zero} = 637\text{kHz}$$

$$7\text{kHz} < 637\text{kHz} \rightarrow f_c < f_{zero}$$


AC Results

| Input | | Output | | Supply | | Gain |
|------------|------------|------------|------------|----------|----------|-------------|
| V_{iMin} | V_{iMax} | V_{oMin} | V_{oMax} | V_{dd} | V_{ee} | 6db to 60db |
| -1.25V | 1.25V | -2.4V | 2.4V | 2.5V | -2.5V | |

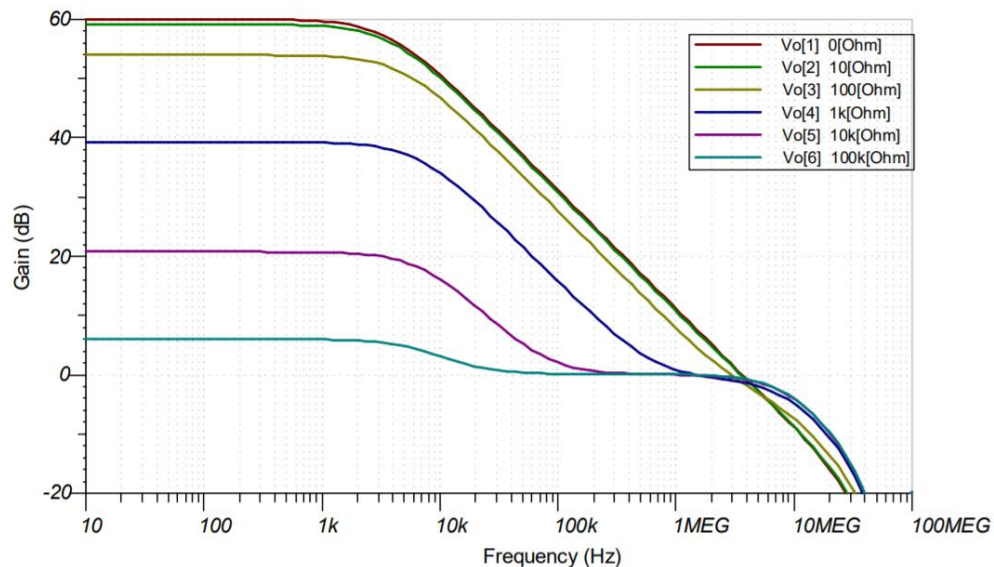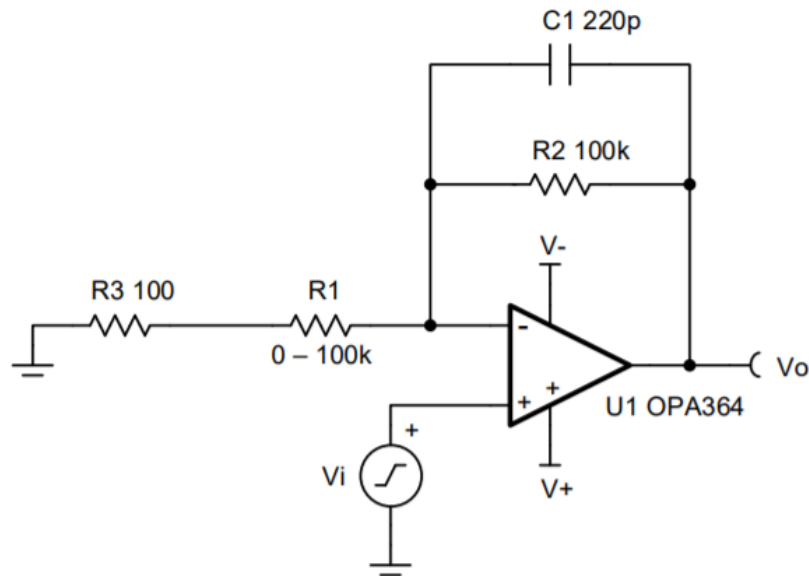

Design Notes

| Input | | Output | | Supply | | Gain |
|------------|------------|------------|------------|----------|----------|-------------|
| V_{iMin} | V_{iMax} | V_{oMin} | V_{oMax} | V_{dd} | V_{ee} | 6db to 60db |
| -1.25V | 1.25V | -2.4V | 2.4V | 2.5V | -2.5V | |

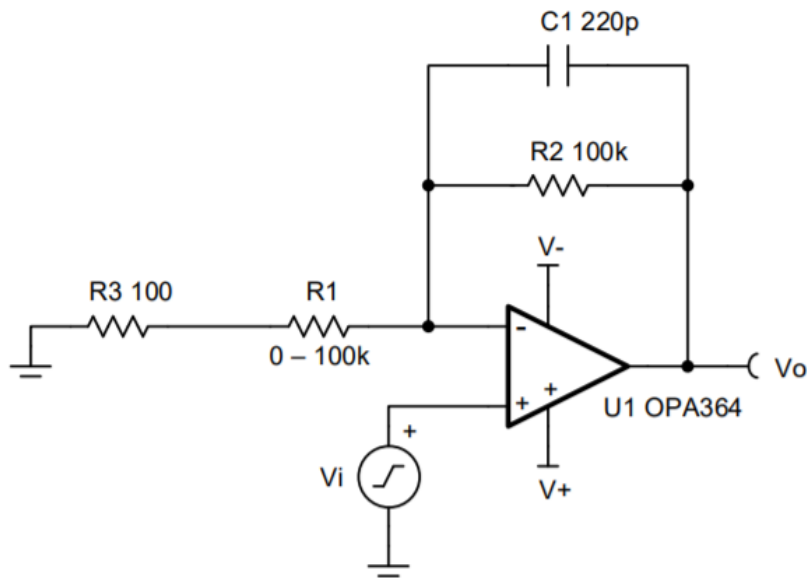

Design Notes:

1. R_3 sets the maximum gain when R_1 approaches 0Ω .
2. Stability should be evaluated across the selected gain range. The minimum gain setting will likely be most sensitive to stability issues.
3. Choose a digital potentiometer, such as TPL0102 for R_1 to design a low-cost digital programmable gain amplifier.

Design Resources

EE Cookbook: Op Amp

www.ti.com/circuitcookbooks

Step-by-step circuit design of common op amp building block circuits.

TI Designs

www.TI.com/tidesigns

Ready-to-use reference designs with theory, calculations, simulations schematics, PCB files, bench test results

Analog Engineer's Pocket Reference

www.TI.com/analogrefguide

PDF, iTunes app and hardcopy available
PCB, analog, mixed signal design formulae
Conversions, tables, equations

TI Precision Labs

www.TI.com/precisionlabs

Quiz questions, problems, solutions
Labs and evaluation module (EVM) available

TINA-TI™ simulation software

www.TI.com/tool/tina-ti

Complete SPICE simulator DC, AC, transient, noise analysis
Schematic entry and post-processor for waveform math

DIYAMP-EVM

www.TI.com/DIYAMP-EVM

Evaluation module providing engineers with SC70, SOT23, SOIC packaging and 12 popular amplifier configurations

The Signal

www.TI.com/thesignal

PDF, iTunes app and hardcopy available
A compendium of blog posts on op amp design topics including offset voltage, input bias current, stability, noise and more

Analog Wire Blog

www.TI.com/analogwire

Technical blogs written by analog experts
Tips, tricks, and design techniques

TI E2E™ Community

www.TI.com/e2e

Support forums for all TI products

Op Amp Parametric Quick Search

www.TI.com/amplifiers

Search for precision, high-speed, general-purpose, ultra-low-power, audio and power op amps

Op Amp Parametric Cross-Reference

www.TI.com/opampcrossreference

Find similar TI op amps using competitive part numbers

www.ti.com/circuitcookbooks



© Copyright 2021 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)