

How to Design Multi-kW Converters for Electric Vehicles

- Part 1: Electric Vehicle power systems
- Part 2: Introduction to Battery Charging**
- Part 3: Power Factor and Harmonic Currents
- Part 4: Power Factor Correction
- Part 5: The Phase Shifted Full Bridge
- Part 6: How the PSFB works
- Part 7: A High Power On Board Charger Design
- Part 8: MOSFET gate driver considerations and References

Colin Gillmor: (HPC), email: colingillmor@ti.com

Batteries

Li-Ion:



- Charged to 4.2V/cell, discharged to 2.5V/cell
- 400V battery discharged to 230V,
- 1.75:1 ratio

Lead Acid:

- Charged to 2.35V/cell, discharged to 1.9V/cell
- 12V battery, 14.1V charged, fully discharged to 11.4V
- 1.25:1 ratio

Considerations:

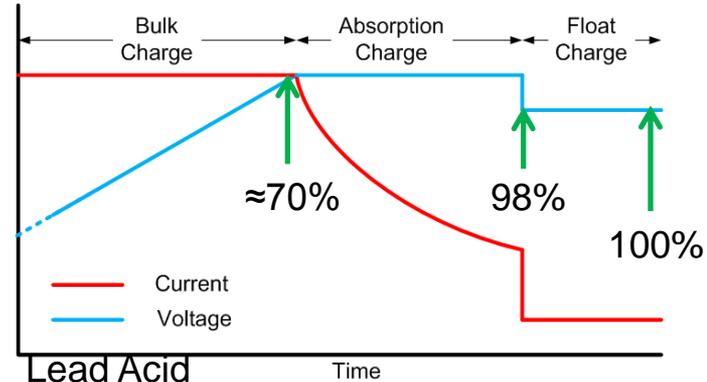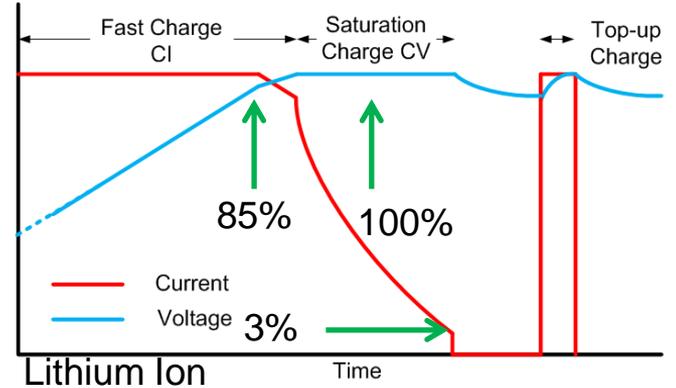- Tight voltage tolerances and maintaining charged state
- Temperature rise during charging → OTP
- Battery pack cell balancing – not considered here
- Charge Rate vs Charge Time vs Battery Life
- Charger must operate in CI and CV modes



Batteries

Volt/Time characteristic is approximately Linear

- Power delivered is therefore a linear function of time during CI phase



Charging time is long compared to thermal time constants in charger – typ 8 hour charge cycle

Power dissipated in charger is as important as efficiency

Good efficiency needed over wide V_{out}/I_{out} range

Not Considered here:

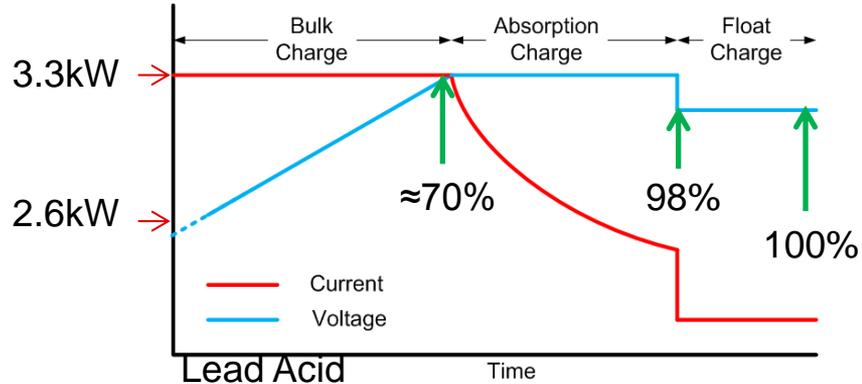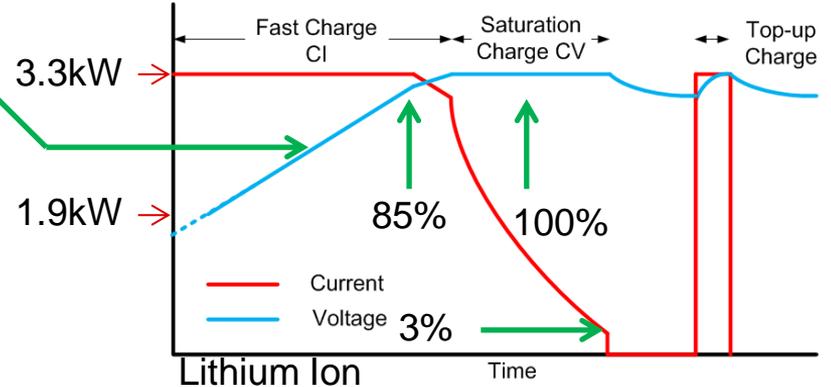- Initial charging, battery stack management, thermal issues, battery lifetime



Typical Battery Charger Specifications

Input: Universal Single Phase Line with PFC

Output Voltage:

- 1.75:1 range (Li-Ion), 400V/230V
- 1.25:1 range (Lead Acid), 14.1V/11.4V

Output Power



- Pout: 3.3kW (typ), increases during charging

CI and CV modes

- 'Normal' protections (OCP, OTP etc...)

Topologies


- AC/DC: Boost PFC
- DC/DC: PSFB

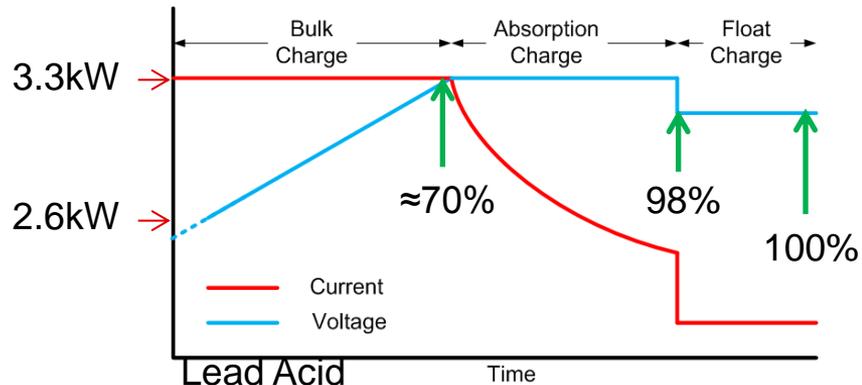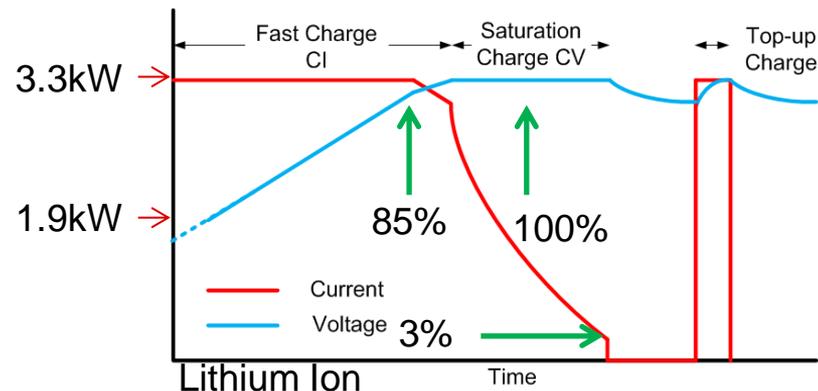

CI / CV operation

Two feedback paths

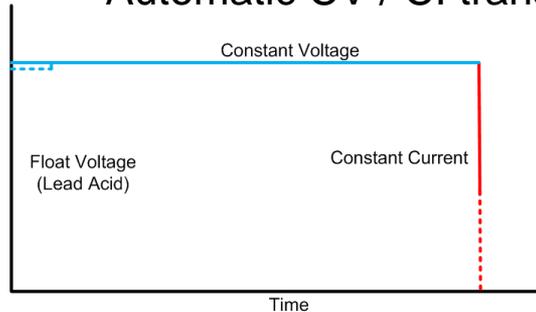
- One measures output current
 - Compare to reference
 - Output error signal (power demand)
- One measures output voltage
 - Compare to reference
 - Output error signal (power demand)
- Diode 'or' errors – lowest error 'wins'
 - Automatic CV / CI transition



Low side sense at $400V_{out}$
 High side sense at $12V_{out}$ is possible

Lowest error 'wins'

& Controls the output

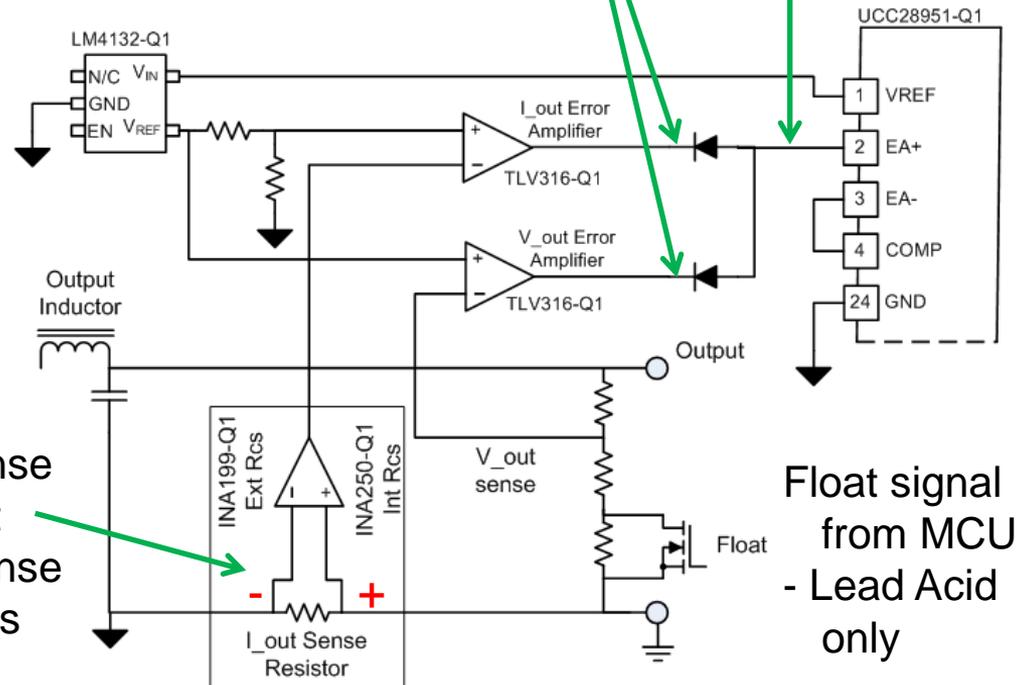

Float signal from MCU - Lead Acid only

How to Design Multi-kW Converters for Electric Vehicles

Thank You

- Part 1: Electric Vehicle power systems
- Part 2: Introduction to Battery Charging**
- Part 3: Power Factor and Harmonic Currents
- Part 4: Power Factor Correction
- Part 5: The Phase Shifted Full Bridge
- Part 6: How the PSFB works
- Part 7: A High Power On Board Charger Design
- Part 8: MOSFET gate driver considerations and References

Colin Gillmor: (HPC), email: colingillmor@ti.com



© Copyright 2018 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)