

Linear OPAMP Characterization: Power Supply Rejection Ratio


Presented by: Joseph Serritella

Prepared by: Joseph Serritella, Daryl Hiser, Ray Ochotorena, Mark Irwin

OPAMP verification

OPAMP Electrical Characterization:

- Characterizing the electrical behavior of an integrated circuit is critical during application troubleshooting
 - Non-conformances can be identified by comprehending device level characteristics in addition to system performance
- OPAMP electrical characterization series will review following topics:
 - Voltage offset (V_{OS})
 - V_{CM} / Common mode rejection ratio (CMRR)
 - **Power supply rejection ratio (PSRR)**
 - Output swing
 - Quiescent current
 - Open loop gain (A_{OL})

 

Prerequisites

Electrical characterization: PSRR

- Power supply rejection ratio measurements methods are reviewed
- Following prerequisites are recommended prior to proceeding though the handbook

Prerequisites:

TI-Precision Labs (TIPL) courses:

PSRR: TIPL - Op Amps: Power Supply Rejection

ti.com/training-power-supply-rejection

Pocket Reference:

Training: Analog Engineer's Pocket Reference

ti.com/analogrefguide

Application handbook:

A-B-A: Board Level Troubleshooting

ti.com/board-level-troubleshooting

Simulation tools:

Simulations are presented within the handbook. It is recommended to install TINA-TI

TINA-TI can be downloaded for free on ti.com: <http://www.ti.com/tool/tina-ti>

OPAMP test loops

Overview:

- Analyzing datasheet parameters may appear a challenging task!
- Multiple parameters can be derived easily from offset (V_{OS}).
 - PSRR, CMRR, and AOL can be calculated by monitoring shifts


False Summing Junction (FSJ):

- Accurate VOS measurements can be obtained through test loops
 - **Benefits:**
 - Simplistic
 - Stable
 - Small
 - **Disadvantages:**
 - Feedback resistor load in parallel with other added loads
 - Loop drive function of DUT V_{OS}
- Majority of DC parameters determined with 4 resistors!

Measuring VOS:

- **VOS:** differential input voltage required to force output to mid-supply
 - best measured at the summing junction (V_{SJ})
- **Output control voltage (VOC):** Calibrate the out voltage to zero volts
 - Know as offset correction factor (derived from Kirchhoff's Voltage Law):
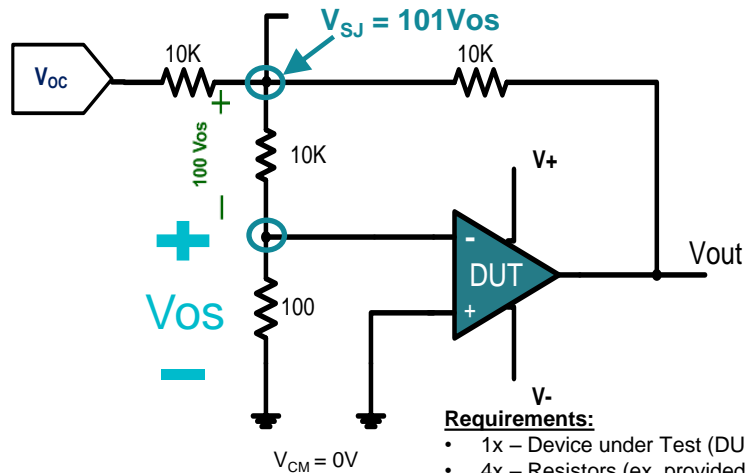
$$V_{OC} = -(V_{OUT} + VOS(302)) + 2V_{CM}$$



Requirements:

- 1x – Device under Test (DUT)
- 4x – Resistors (ex. provided)
 - Resistor values can be varied depending on device

Example:

- $V_+ = +10V$
- $V_- = -10V$
- $V_{OUT} = 0V$
- $V_{OC} = 0V$ (ideal opamp)

Results:

- $V_{SJ} = 1.01mV$
- $1.01mV = (101)V_{OS} = V_{SJ}$
 $10\mu V = V_{OS}$

Power supply rejection ratio – OPA192

Bench setup and measurements:

- **PSRR:** Change in V_{OS} divided by the change in V_{Supply}
 - Consider the transition region for rail to rail amps
 - The nMos active region remains constant as supply delta varies
- Refer to data sheet for PSRR test conditions versus supply range

$$PSRR\left(\frac{V}{V}\right) = \left(\left|\frac{\Delta V_{OS}}{\Delta V_{Supply}}\right|\right)$$

$$PSRR(dB) = -20 \times LOG\left(PSRR\left(\frac{V}{V}\right)\right)$$


 


Figure: representative V_{CM} versus V_{OS} graph. The red line represents the common voltage range of a decreased supply voltage

PARAMETER	TEST CONDITIONS	MIN	TYP	MAX	UNIT
PSRR Power-supply rejection ratio	$T_A = -40^\circ\text{C to } +125^\circ\text{C}$		± 0.3	± 1.0	$\mu\text{V/V}$

Power supply rejection ratio

Bench Setup and Measurements:

 

Offset Voltage (1):

- DUT: OPA192IDGK
- V+ = +15V
- V- = -15V
- V_{OUT1} = 0V

Offset Voltage (2):

- DUT: OPA192IDGK
- V+ = +6V
- V- = -6V
- V_{OUT2} = 0V

Use the offset correction factor equation to accurately set V_{out}