

Quiz: Instrumentation Amplifier (IA) topologies: one-amp

TI Precision Labs – Instrumentation Amplifiers


Presented by Tamara Alani

Prepared by Tamara Alani

Quiz: (IA) topologies: one-amp || Question

1. What is the simplified output equation of a one-amp IA assuming $R2 = R4$ and $R1 = R3$?

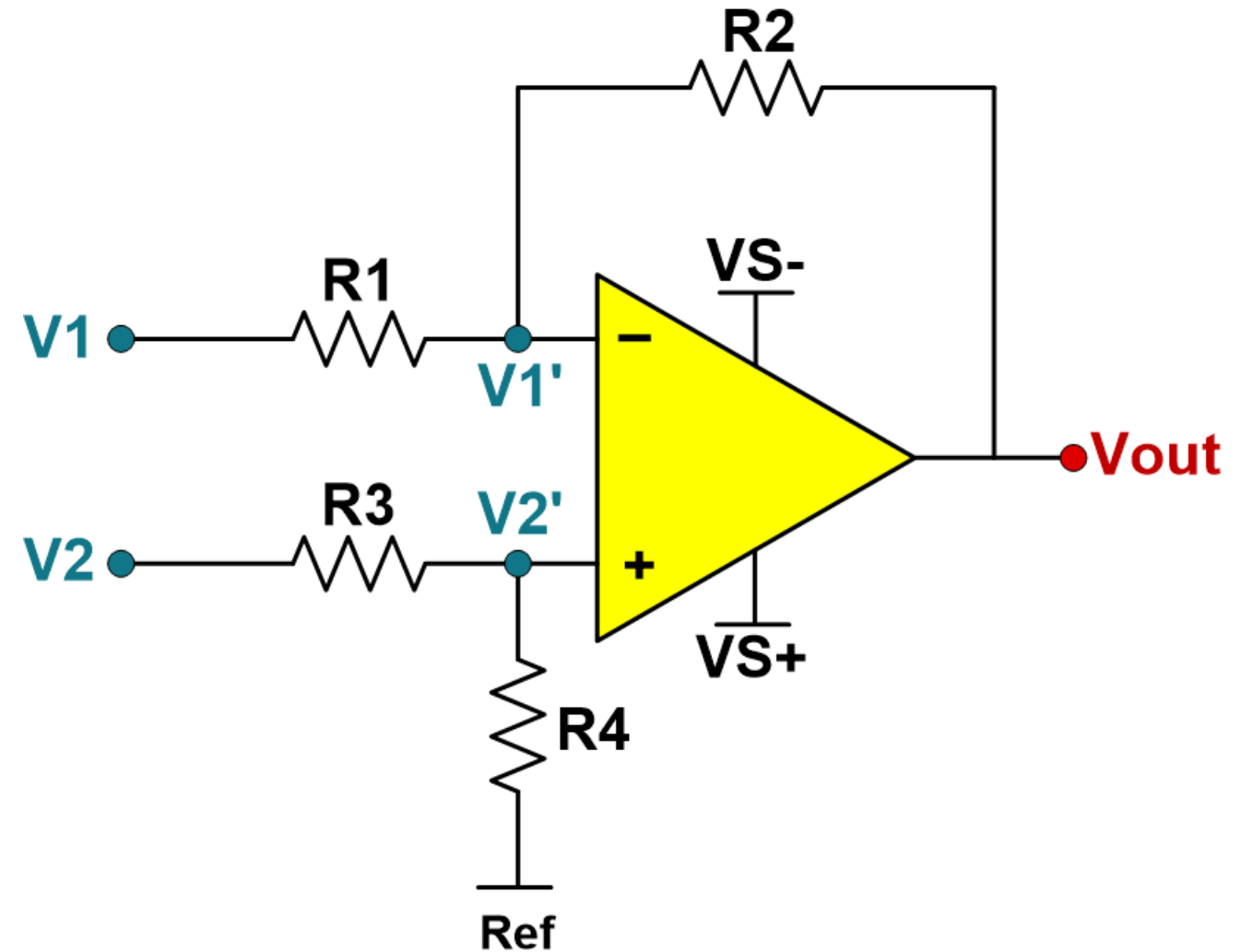- a) $V_{out} = V2 \times V1$
- b) $V_{out} = R2/R1 \times (V2 - V1) + Ref$
- c) $V_{out} = Ref \times (V2 - V1)$
- d) $V_{out} = V1 \times V2 \times Ref$



Quiz: (IA) topologies: one-amp || Answer


1. What is the simplified output equation of a one-amp IA assuming $R2 = R4$ and $R1 = R3$?

a) $V_{out} = V2 \times V1$

b) $V_{out} = R2/R1 \times (V2 - V1) + Ref$

c) $V_{out} = Ref \times (V2 - V1)$


d) $V_{out} = V1 \times V2 \times Ref$

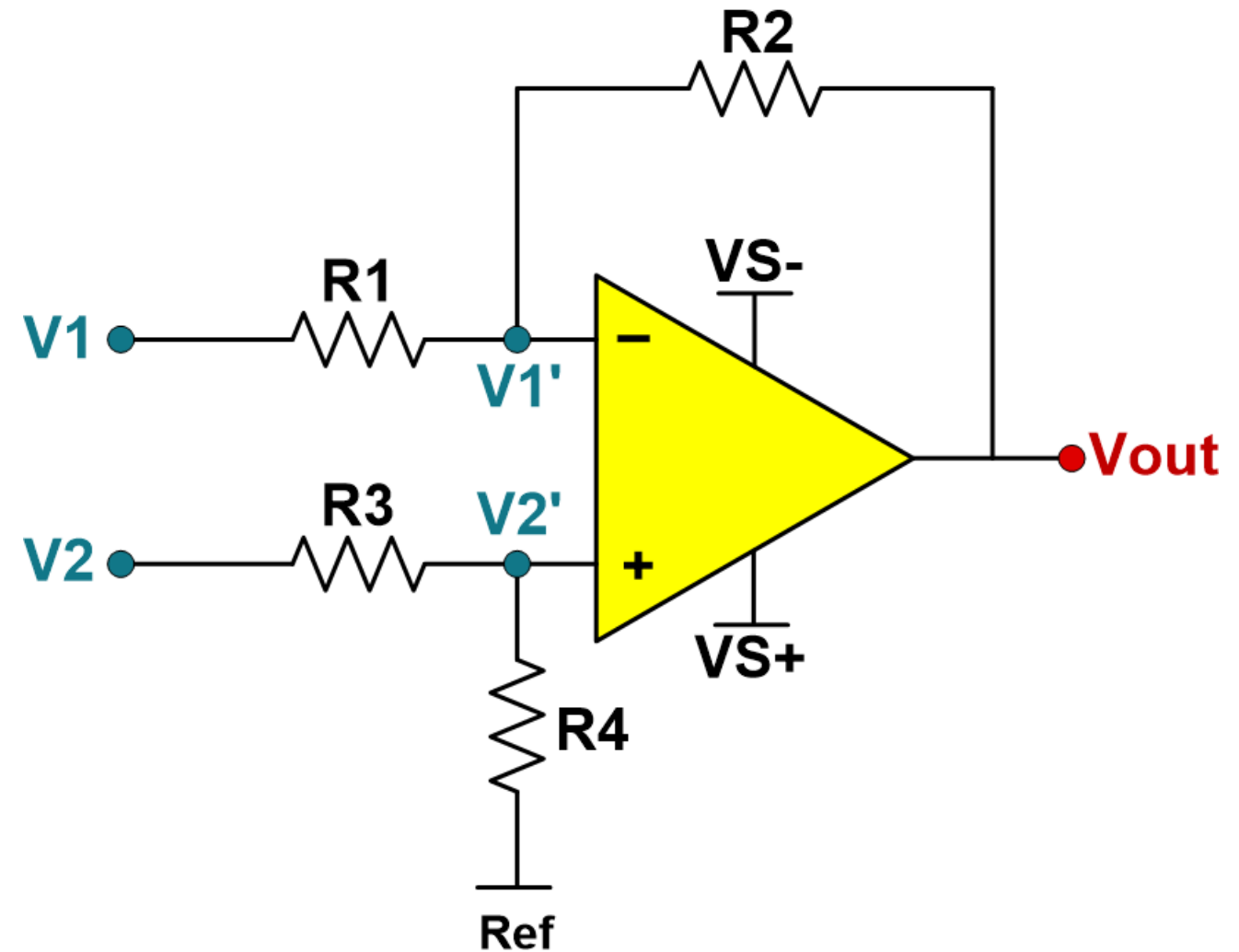

Quiz: (IA) topologies: one-amp || Question

2. In the circuit shown below, what is the maximum voltage you are able to place on V_2 and still maintain linear input operation, assuming rail-to-rail input operation?

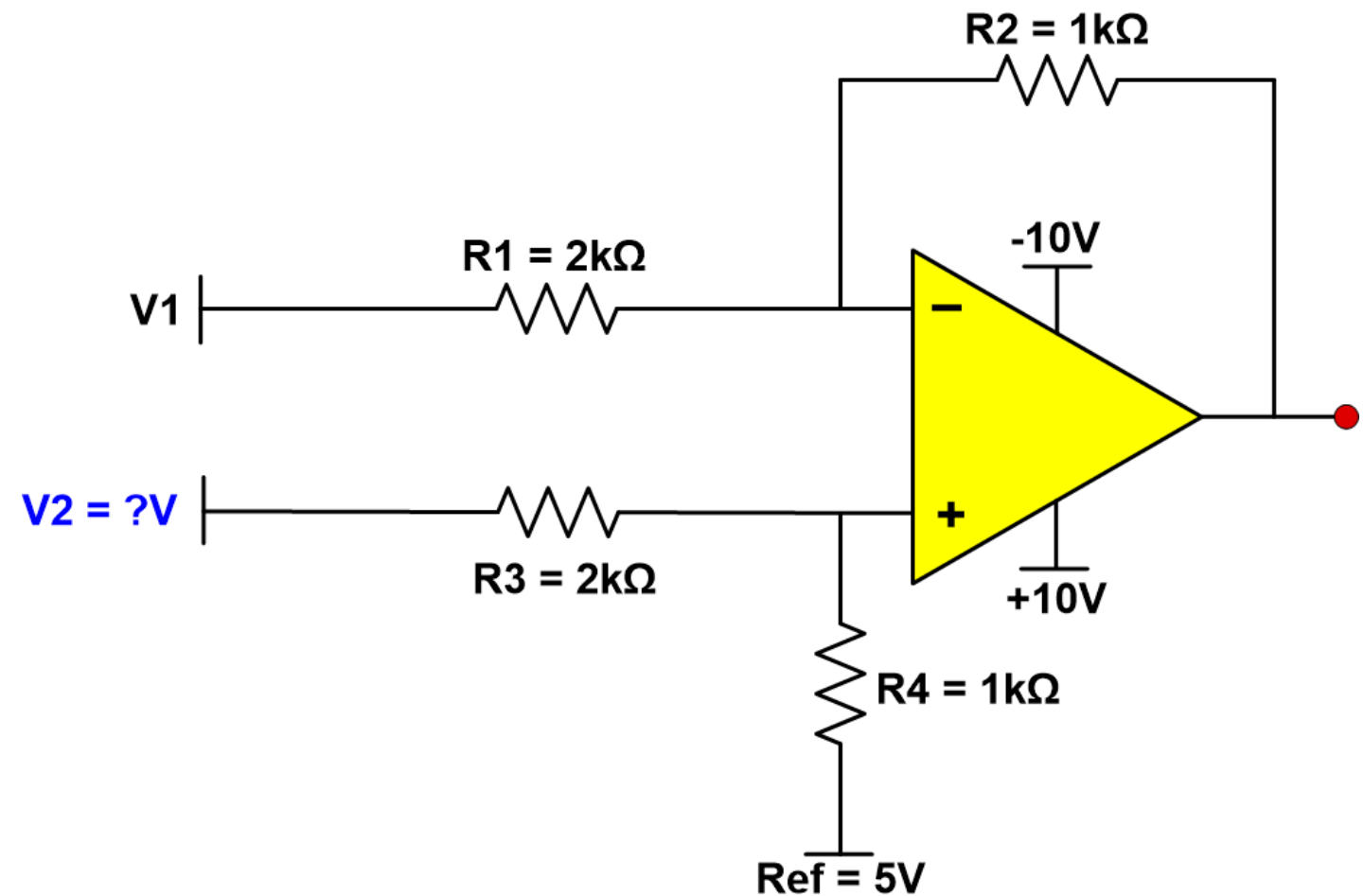- a) $V_2 = 10V$
- b) $V_2 = 15V$
- c) $V_2 = 5V$
- d) $V_2 = 20V$




Quiz: (IA) topologies: one-amp || Answer

2. In the circuit shown below, what is the maximum voltage you are able to place on V2 and still maintain linear input operation, assuming rail-to-rail input operation?

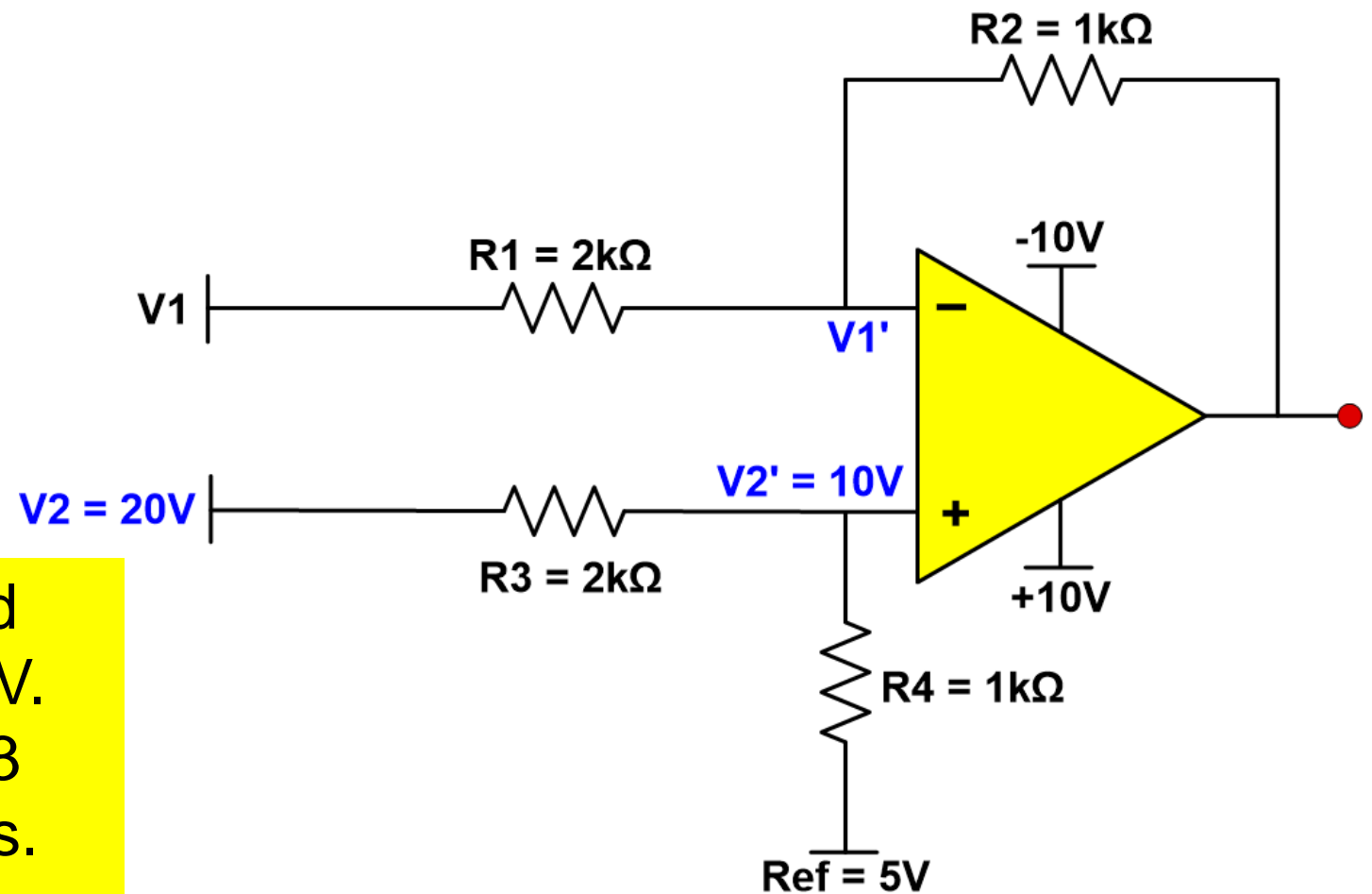- a) $V2 = 10V$
- b) $V2 = 15V$
- c) $V2 = 5V$
- d) $V2 = 20V$


Rail-to-rail input: the voltage seen at V2' and V1' need to be at most 10V and at least -10V. Because of the voltage divider formed by R3 and R4, V2 can be beyond than the supplies. Take caution, there is a 5V reference voltage.



Quiz: (IA) topologies: one-amp || Question

3. In the circuit shown below, what is the minimum voltage you are able to place on V_2 and still maintain linear input operation, assuming rail-to-rail input operation?

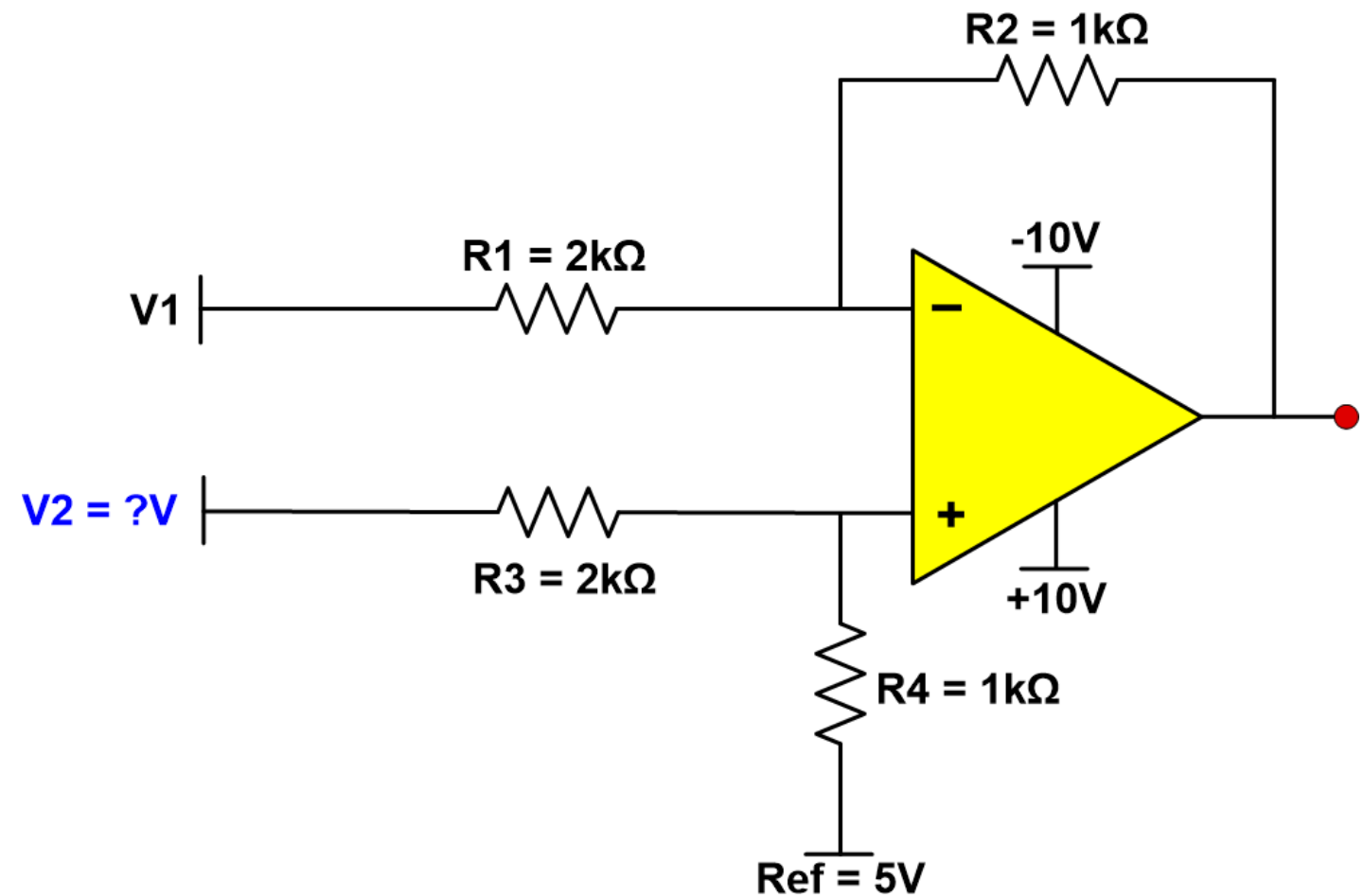- a) $V_2 = -10V$
- b) $V_2 = -40V$
- c) $V_2 = 0V$
- d) $V_2 = -20V$




Quiz: (IA) topologies: one-amp || Answer

3. In the circuit shown below, what is the minimum voltage you are able to place on V2 and still maintain linear input operation, assuming rail-to-rail input operation?

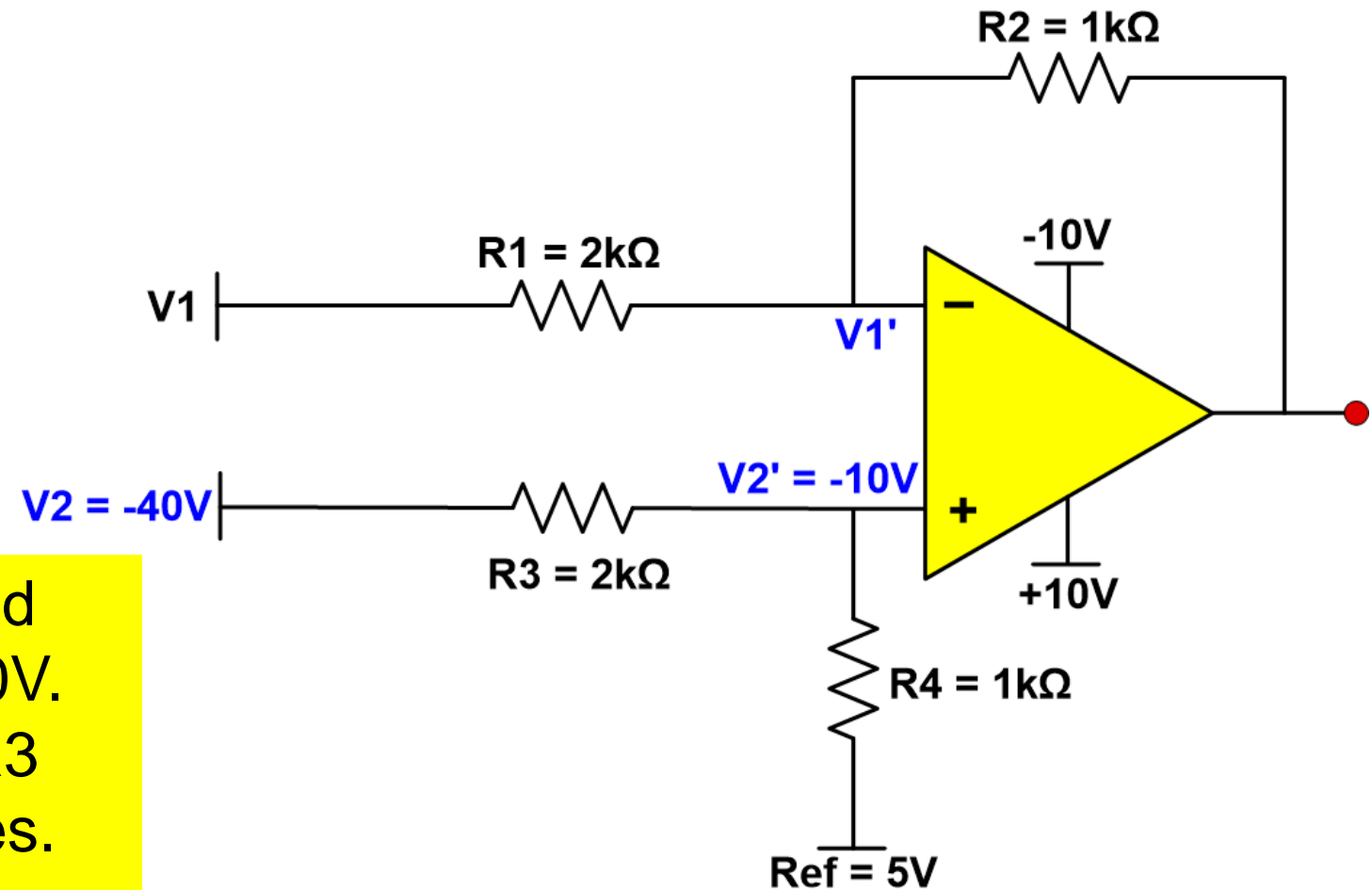
- a) $V2 = -10V$
- b) $V2 = -40V$**
- c) $V2 = 0V$
- d) $V2 = -20V$

Rail-to-rail input: the voltage seen at V2' and V1' need to be at most 10V and at least -10V. Because of the voltage divider formed by R3 and R4, V2 can be beyond than the supplies. Take caution, there is a 5V reference voltage.





Quiz: (IA) topologies: one-amp || Question

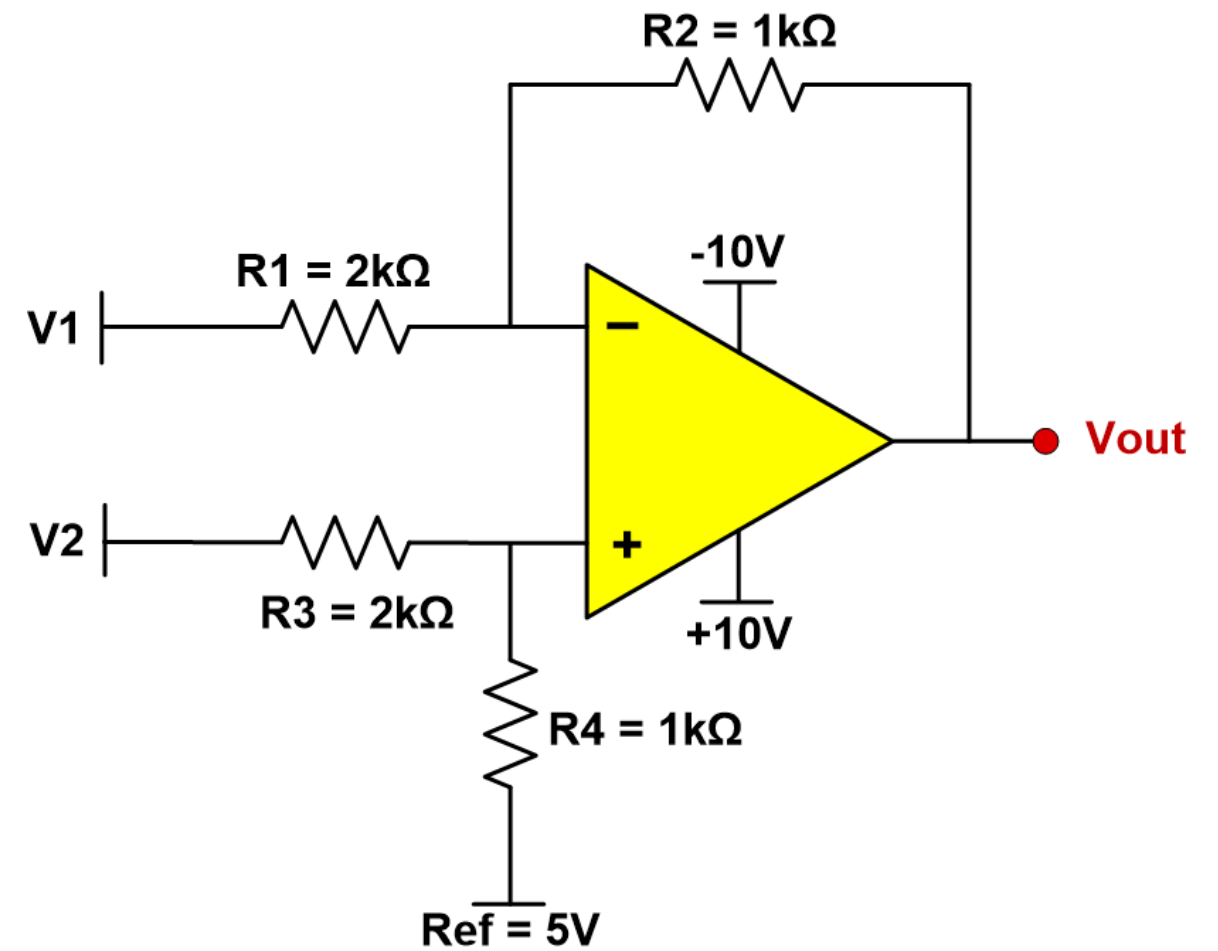4. Create a boundary plot to graphically show the usable range of this IA given that the supplies are $\pm 10\text{V}$ and the reference voltage is set to 5V .




Quiz: (IA) topologies: one-amp || Answer

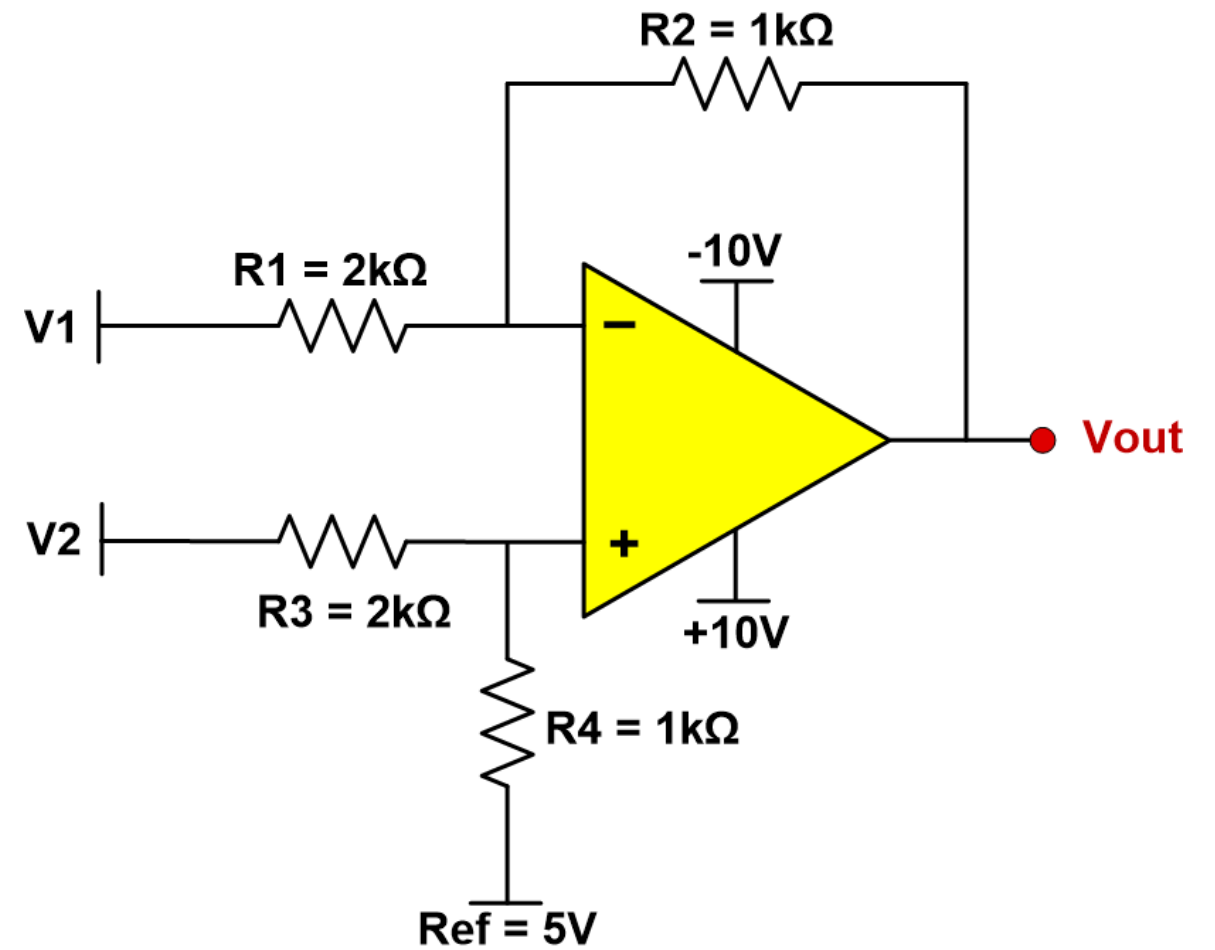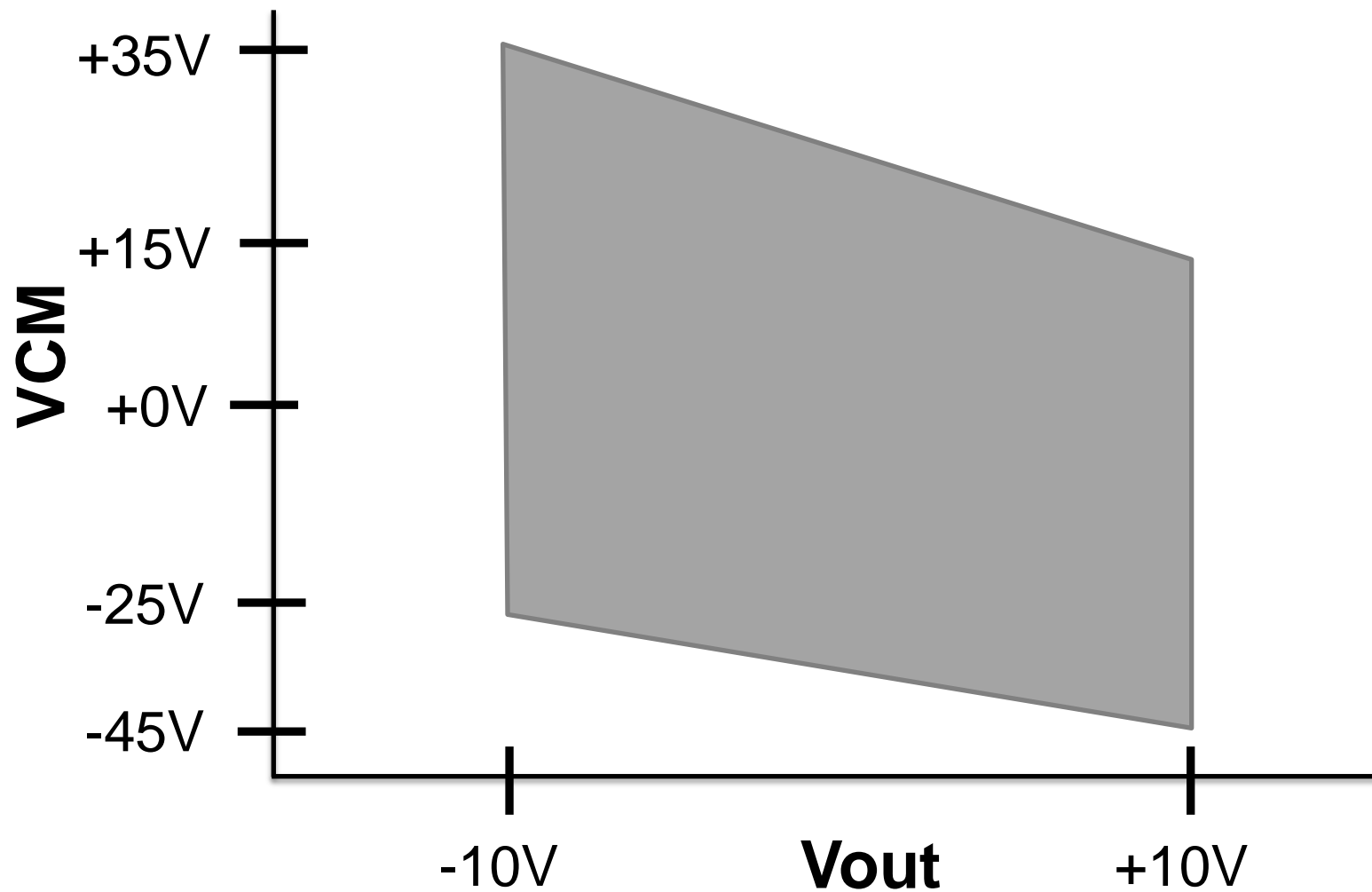4. Create a boundary plot to graphically show the usable range of this IA given that the supplies are $\pm 10V$ and the reference voltage is set to 5V.




Quiz: (IA) topologies: one-amp || Question

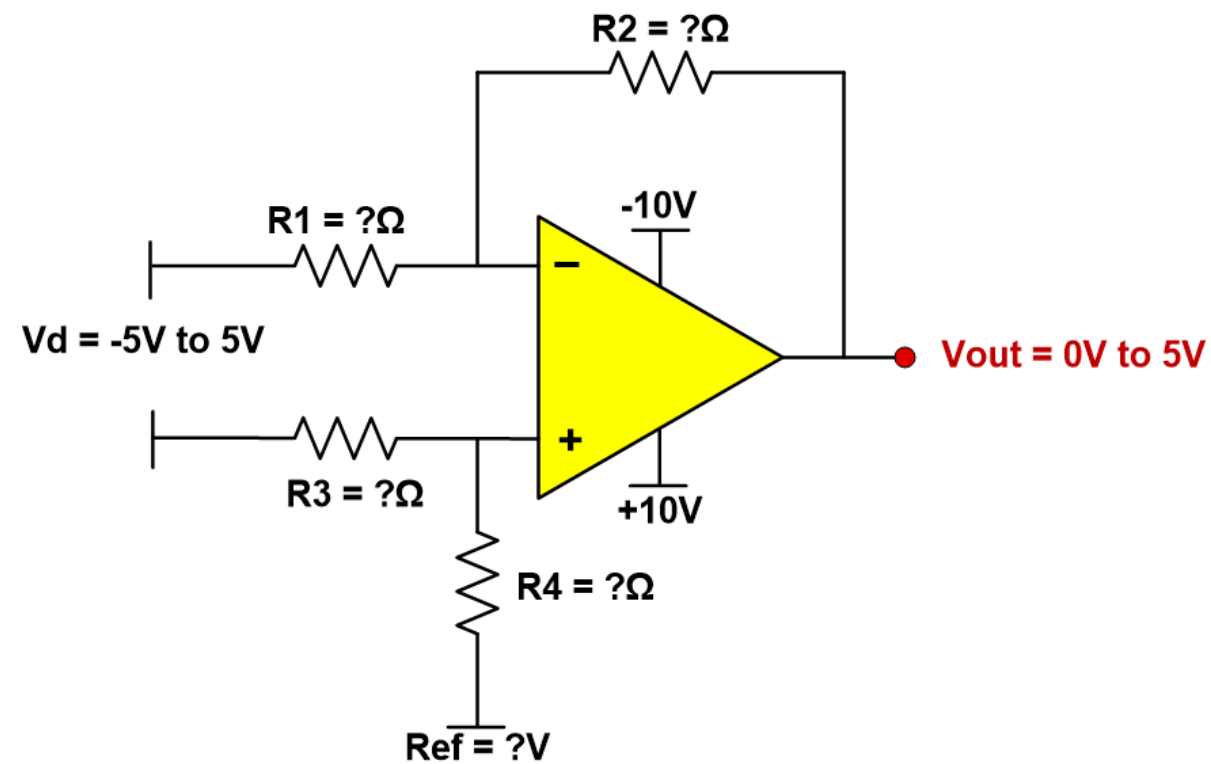5. Assume we have an input signal of $-5V$ to $+5V$. We would like to process this with a $5V$ ADC. So when V_{in} equals $-5V$, we want to see $0V$ at the output. And when the input is $+5V$, we want to see $+5V$ at the output. Determine the gain and reference voltage required to achieve this.



Quiz: (IA) topologies: one-amp || Answer

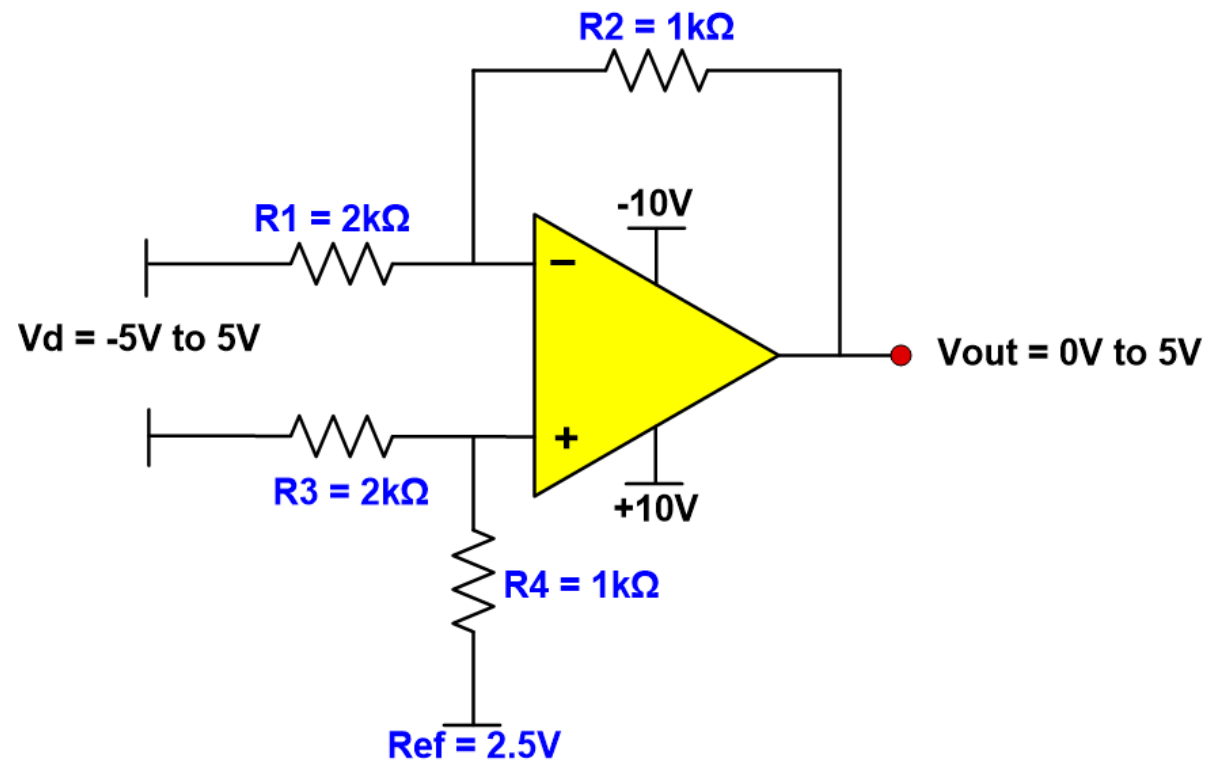5. Assume we have an input signal of -5V to +5V. We would like to process this with a 5V ADC. So when V_{in} equals -5V, we want to see 0V at the output. And when the input is +5V, we want to see +5V at the output. Determine the gain and reference voltage required to achieve this.



- Solve for Gain:

$$\text{Gain} = \frac{\Delta V_{out}}{\Delta V_d} = \frac{5}{10} = \frac{1}{2} = \frac{V_{outmax} - V_{outmin}}{V_{inmax} - V_{inmin}}$$

Choose $R_2 = R_4 = 1\text{k}\Omega$, $R_1 = R_3 = 2\text{k}\Omega$

- Solve for Ref:

$$V_{out} = A_d \times V_d + \text{Ref}$$
$$0 = \frac{1}{2} \times (-5) + \text{Ref} \rightarrow \text{Ref} = 2.5\text{V}$$

To find more Instrumentation Amplifier technical resources and search products, visit [ti.com/inas](https://www.ti.com/inas)