


Instrumentation Amplifier (IA) topologies: two-amp

TI Precision Labs – Instrumentation Amplifiers

Presented by Tamara Alani

Prepared by Tamara Alani

IA topologies – One amp recap

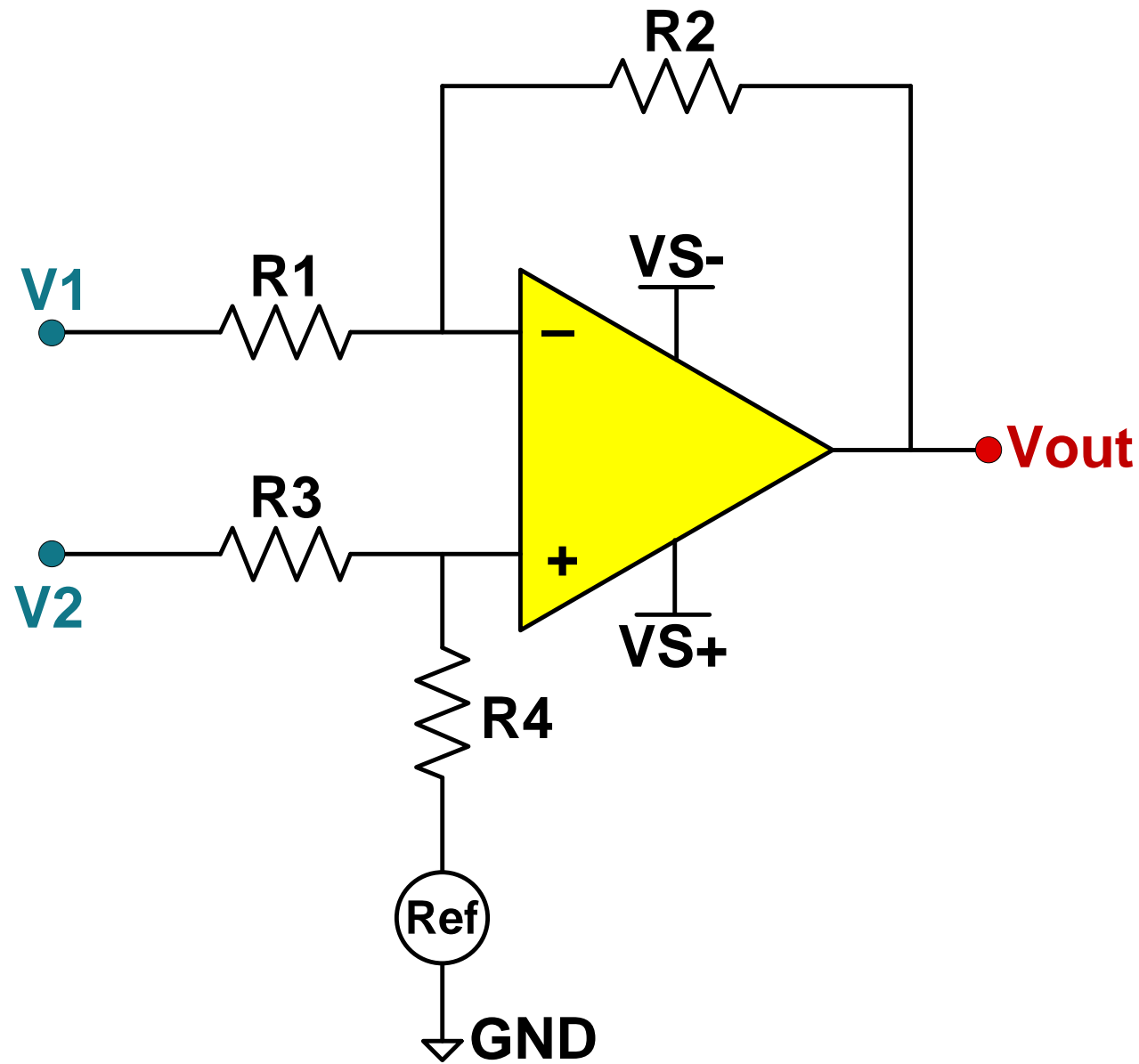

Difference amplifier output equation:

$$V_{out} = V_d \times A_d + Ref$$

Where A_d is the gain of the circuit

If $R_1 = R_3$, and $R_2 = R_4$, then $A_d = \frac{R_2}{R_1}$

Challenges:


1. Precision relies on matched resistors
2. Low input impedance

IA topologies – Three amp recap

Buffer stage with gain and high input impedance

Rf1 and Rf2 are absolutely matched for precise gain calculation:

$$A_d = 1 + \frac{2R_f}{R_g}$$

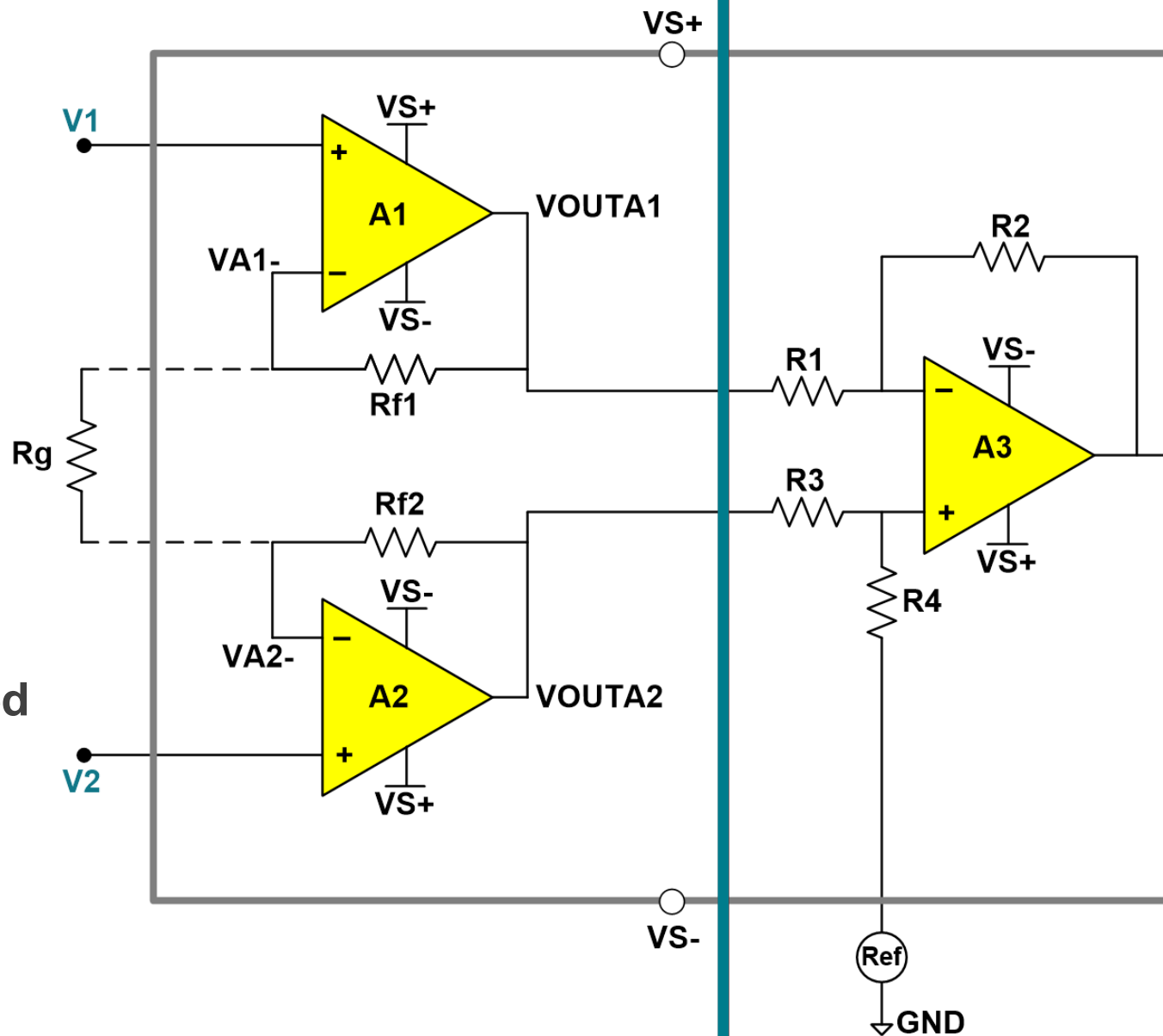


Difference amplifier output stage

$$V_{out} = V_d \times \frac{R_2}{R_1} \times \left(1 + \frac{2R_f}{R_g} \right) + Ref$$

R1, R2, R3 and R4 are ratiometrically matched in production to achieve the desired gain, commonly unity

$$A_d = \frac{R_2}{R_1} \text{ if } R_2=R_4 \text{ and } R_1=R_3$$


IA topologies – Three amp recap cont'd

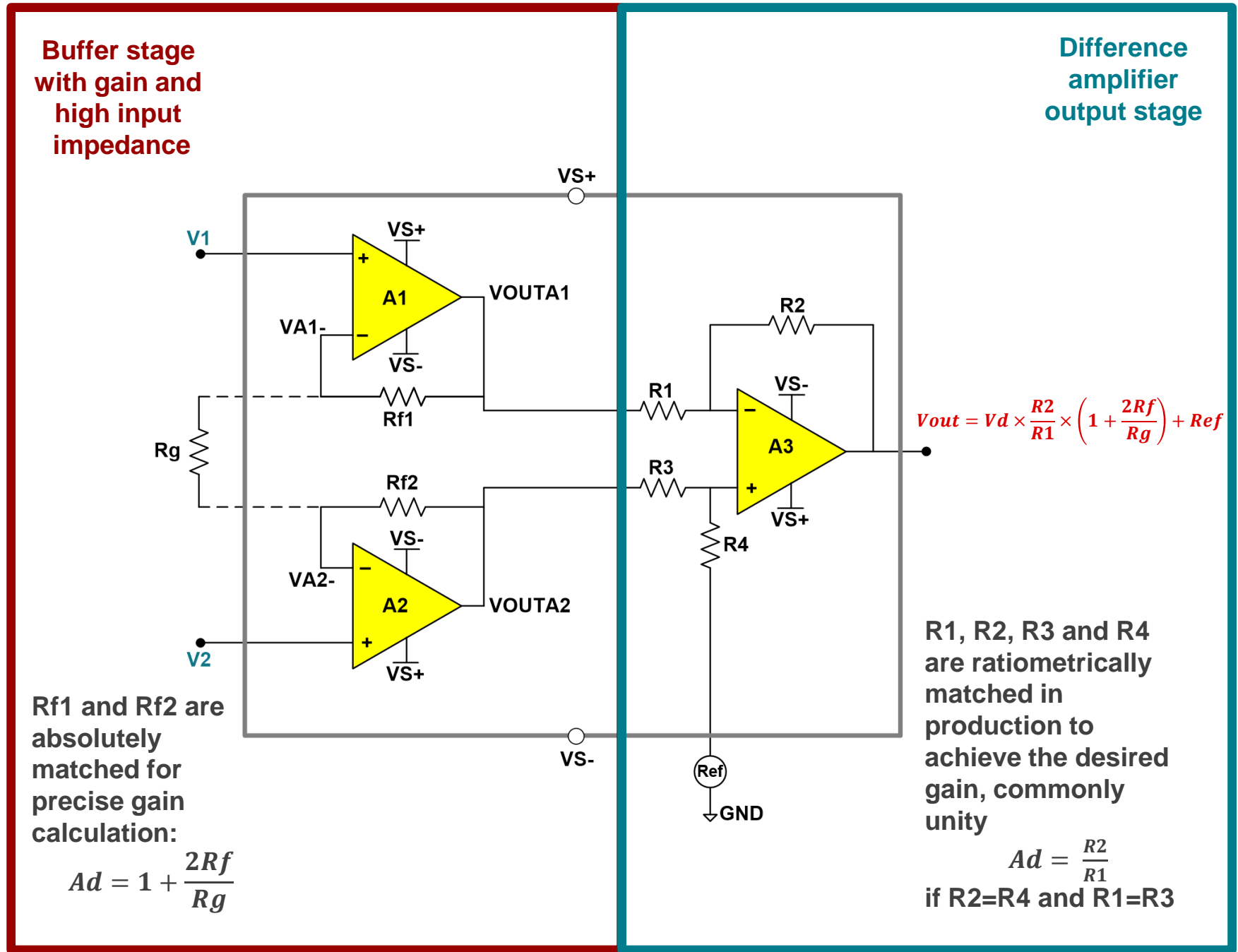

Drawbacks:

- Complex design: 3 amplifiers and 6 resistors.
- This complexity may result in:
- larger die size,
 - higher current consumption,
 - higher manufacturing cost.

IA topologies – Two amp IA introduction

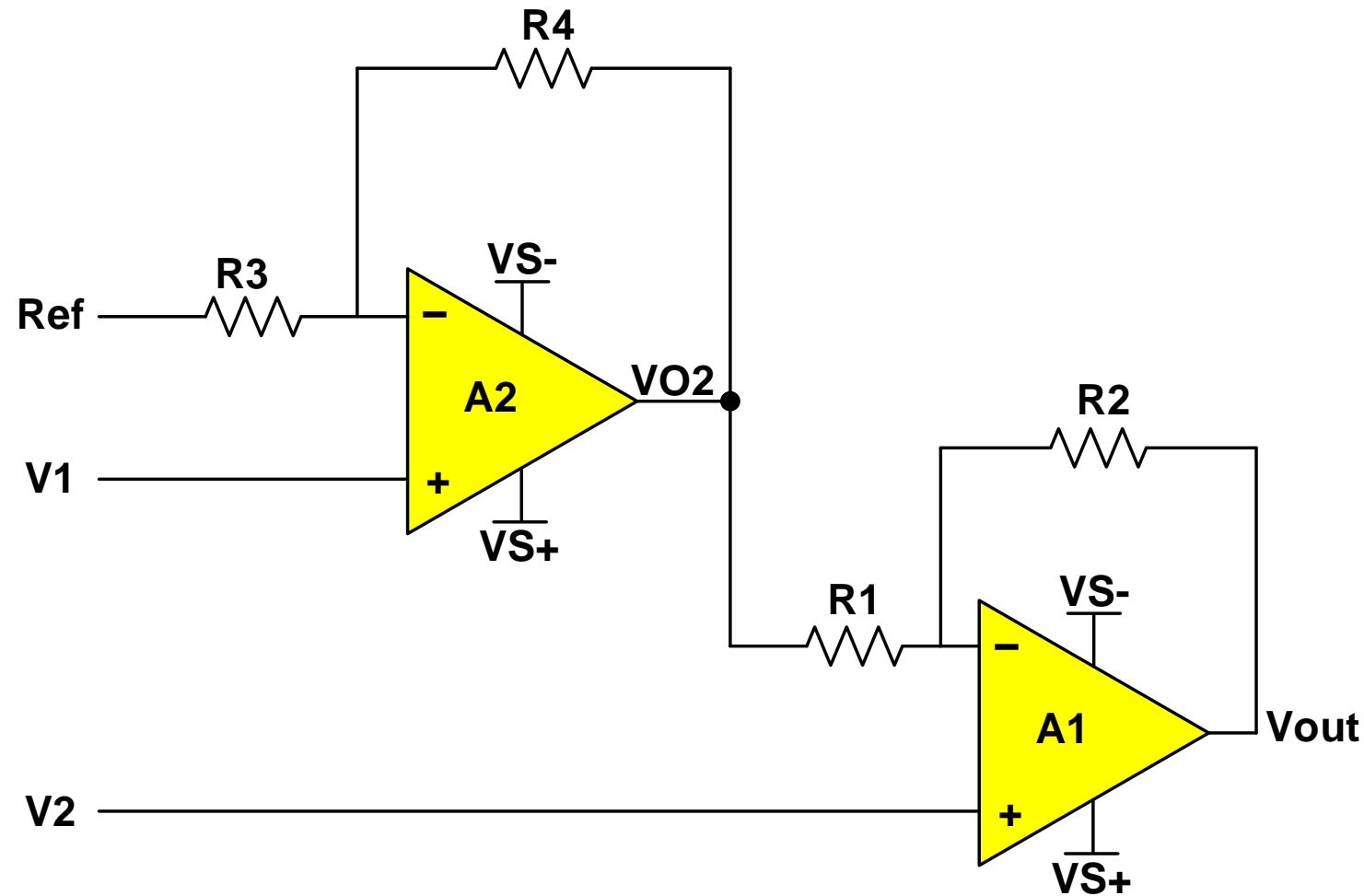


Design simplicity:

- 2 amps, 4 resistors →
 - smaller IC
 - lower current consumption
 - smaller manufacturing cost

Input impedance:

- High (typically $10^9 \Omega$)

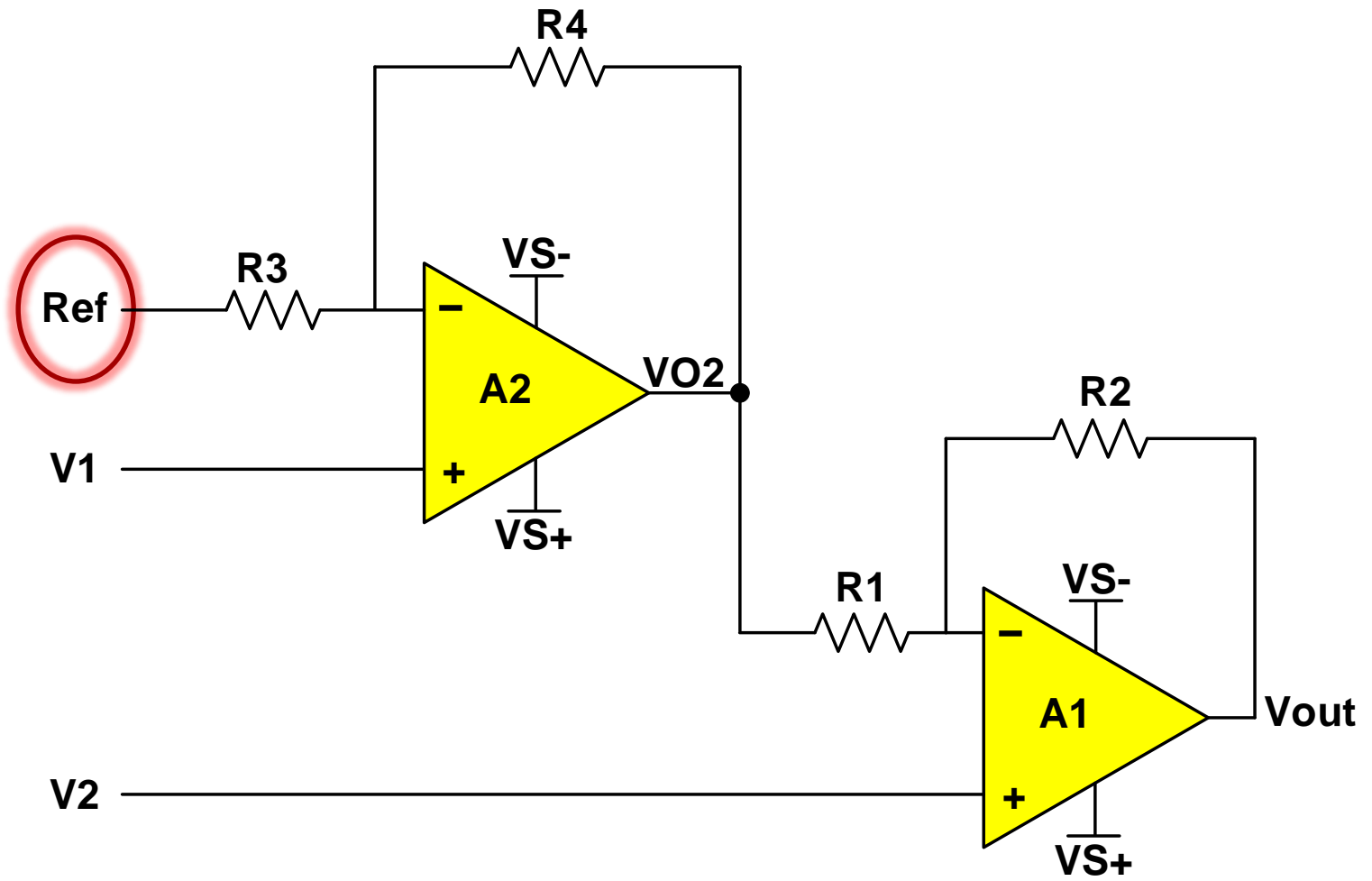IA topologies – 2 amp IA derivation; A2 derivation



Derive output of A2 using superposition theorem:

Equation	V1	Ref
V1*	Keep	Short
Ref*	Short	Keep
$VO2 = V2^* + Ref^*$		


Ground Ref:

A2 looks like non-inverting configuration:

$$VO2 = \left(1 + \frac{R4}{R3} \right) \times V1$$

Equation V1*

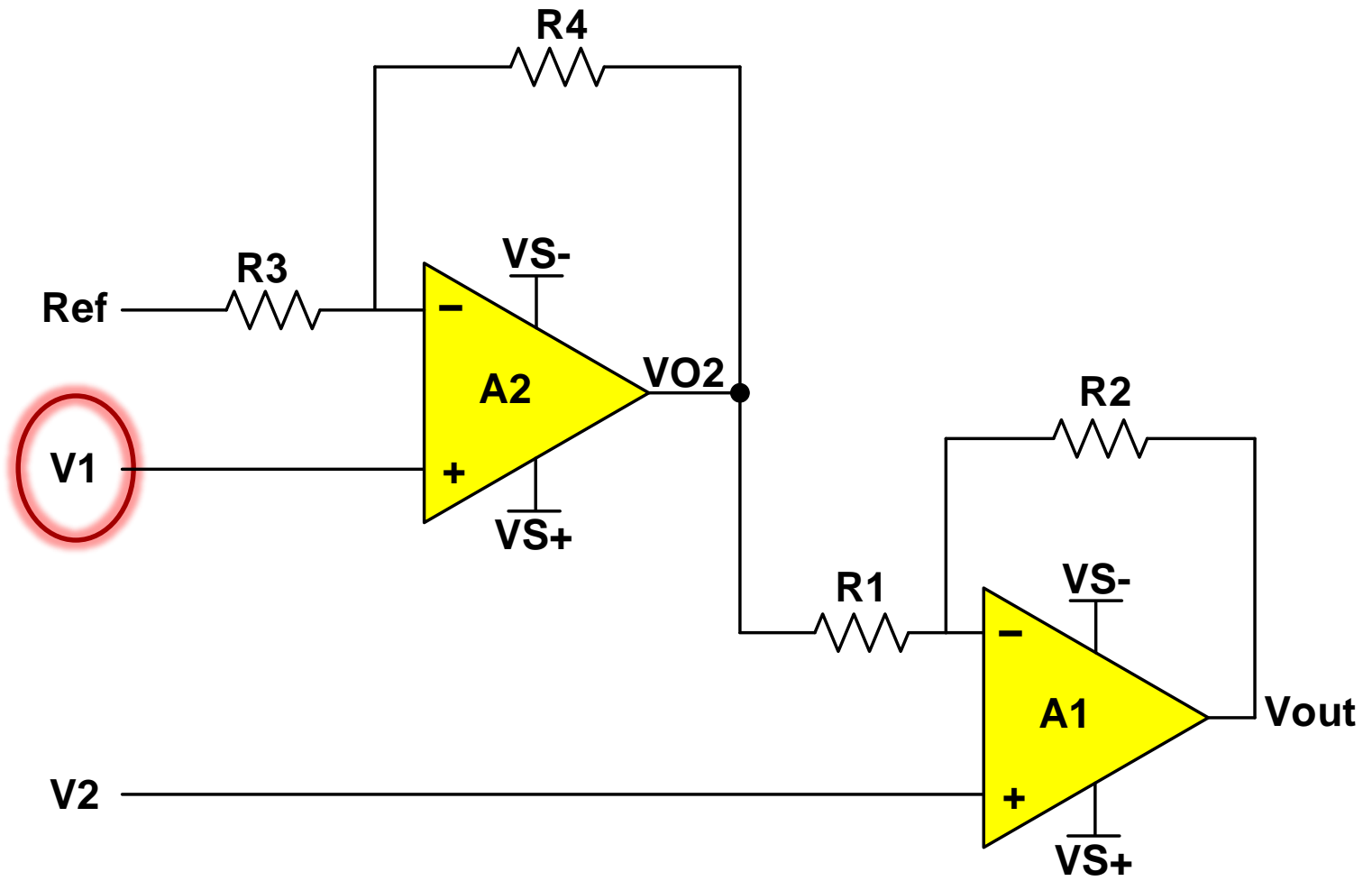IA topologies – 2 amp IA derivation; A2 derivation



Derive output of A2 using superposition theorem:

Equation	V1	Ref
V1*	Keep	Short
Ref*	Short	Keep
$VO2 = V2^* + Ref^*$		

Ground V1:


A2 looks like inverting configuration:

$$VO2 = \left(-\frac{R4}{R3} \right) \times Ref$$

Equation Ref*

IA topologies – 2 amp IA derivation; A2 derivation

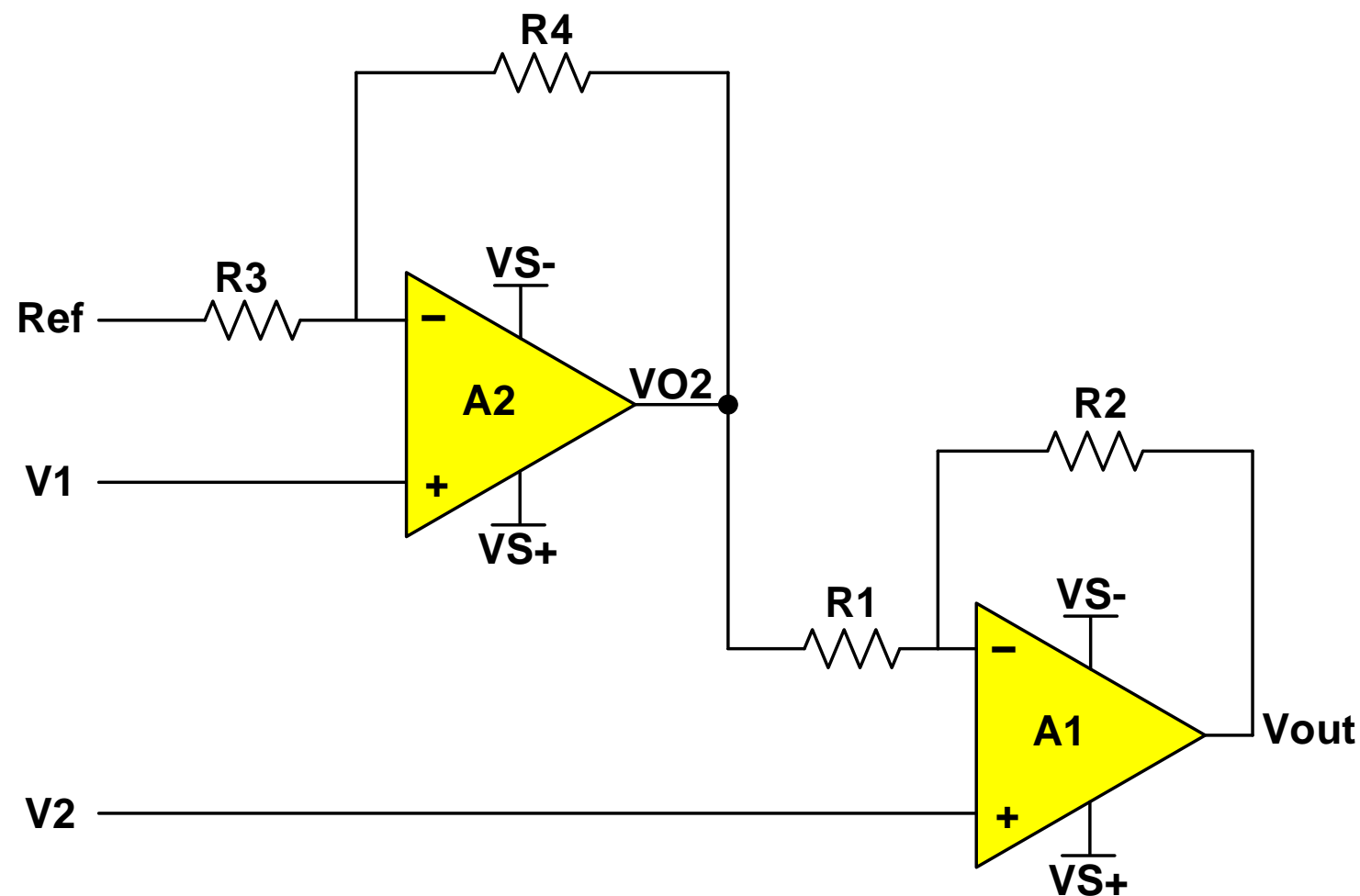Derive output of A2 using superposition theorem:




Equation	V1*	Ref	
V1*	Keep	Short	$V1^* = (1+R4/R3) \times V1$
Ref*	Short	Keep	$Ref^* = (-R4/R3) \times Ref$
$VO2 = V1^* + Ref^*$			

Combine equations $V1^*$ and Ref^* to yield VO2:

$$VO2 = \frac{-R4}{R3} \times Ref + \left(1 + \frac{R4}{R3}\right) \times V1$$

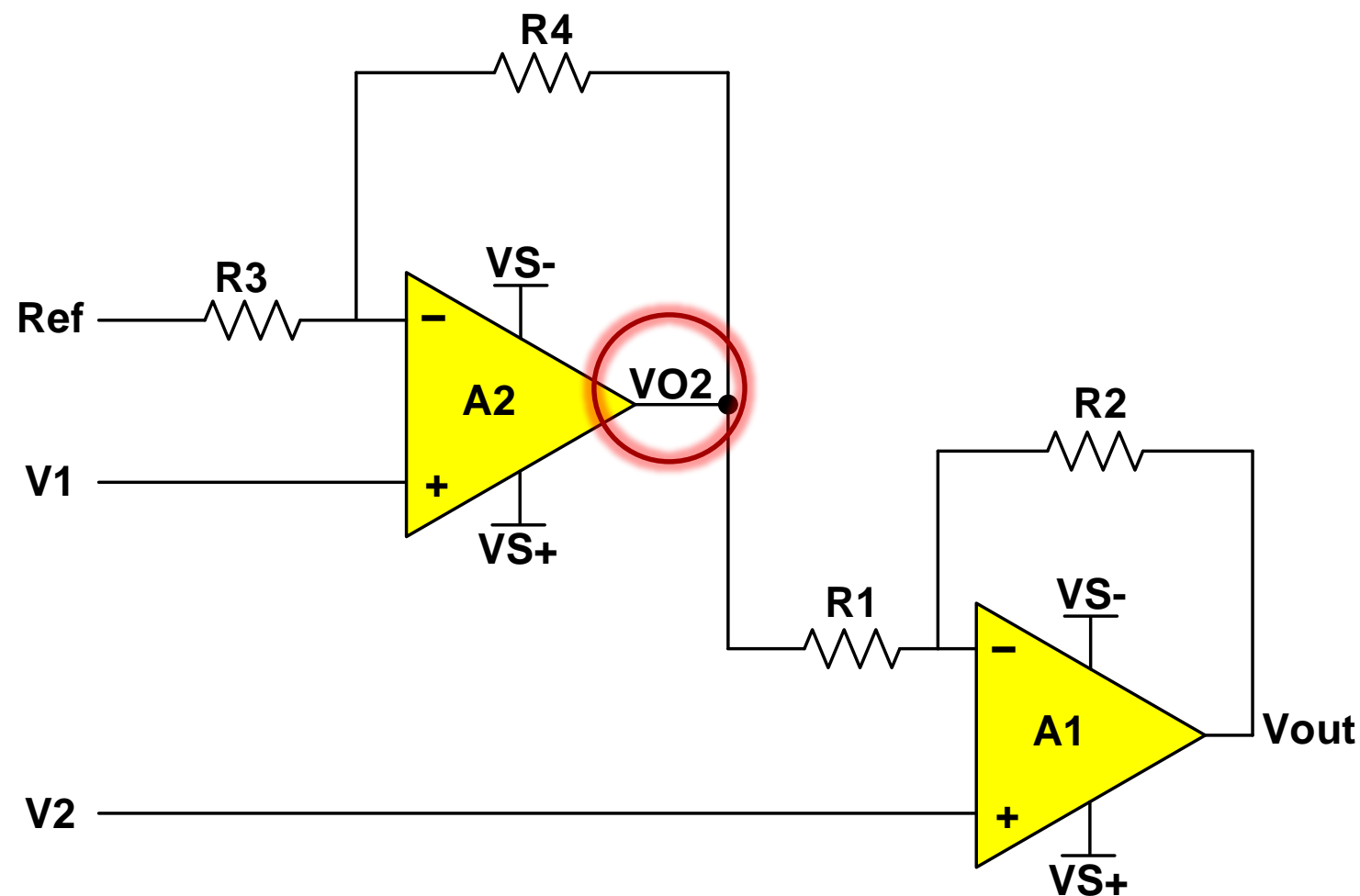IA topologies – 2 amp IA derivation; A1 derivation



Derive output of A1 using superposition theorem:

Equation	V2	VO2
V2*	Keep	Short
VO2*	Short	Keep
$V_{out} = V2^* + VO2^*$		


Ground VO2:

Looks like non-inverting configuration,

$$V_{out} = \left(1 + \frac{R2}{R1}\right) \times V2$$

Equation V2*

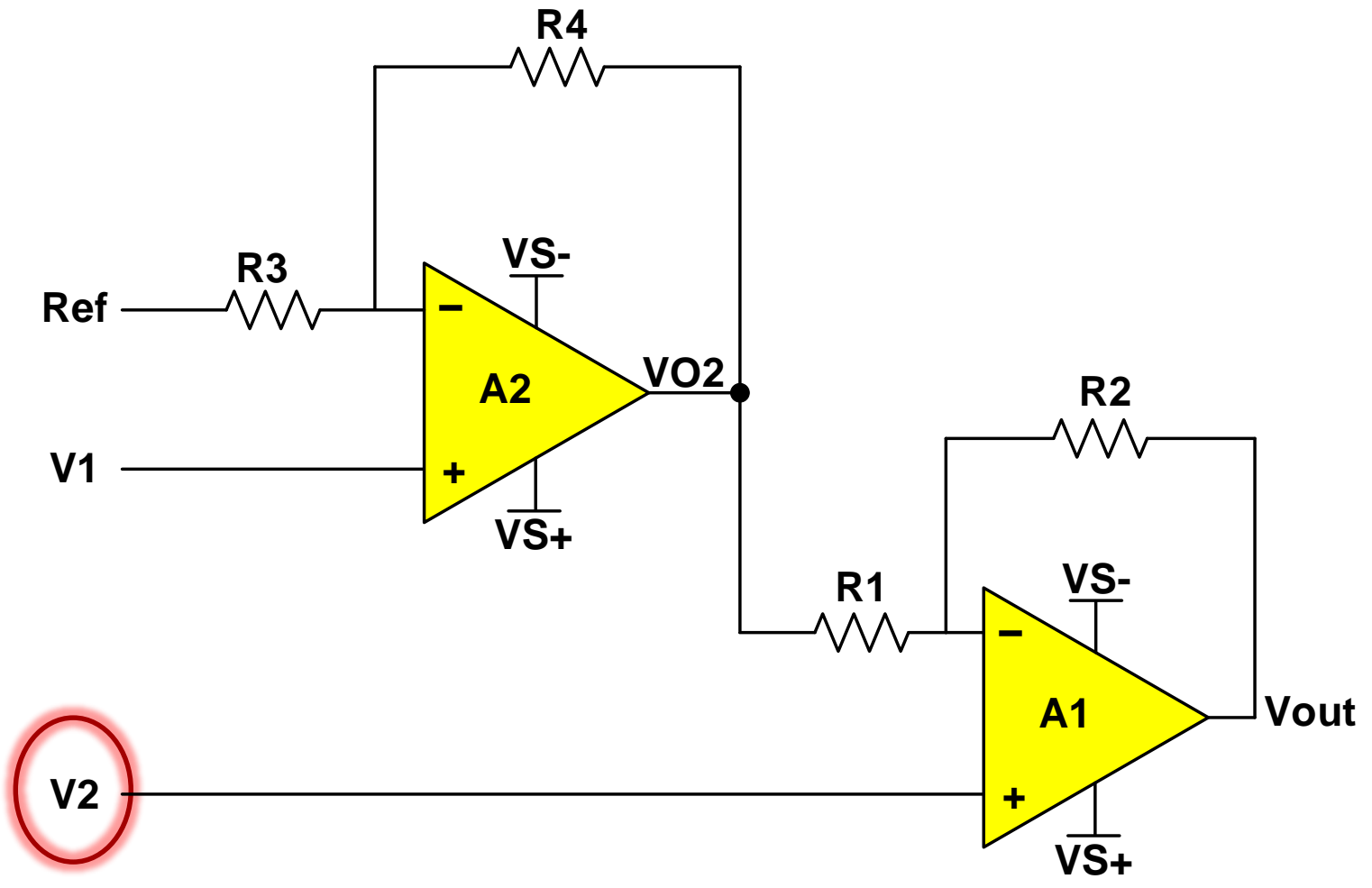IA topologies – 2 amp IA derivation; A1 derivation



Derive output of A1 using superposition theorem:

Equation	V2	VO2
V2*	Keep	Short
VO2*	Short	Keep
$V_{out} = V2^* + VO2^*$		


Ground V2:

Looks like an inverting configuration,

$$V_{out} = \frac{-R2}{R1} \times VO2$$

Equation VO2*

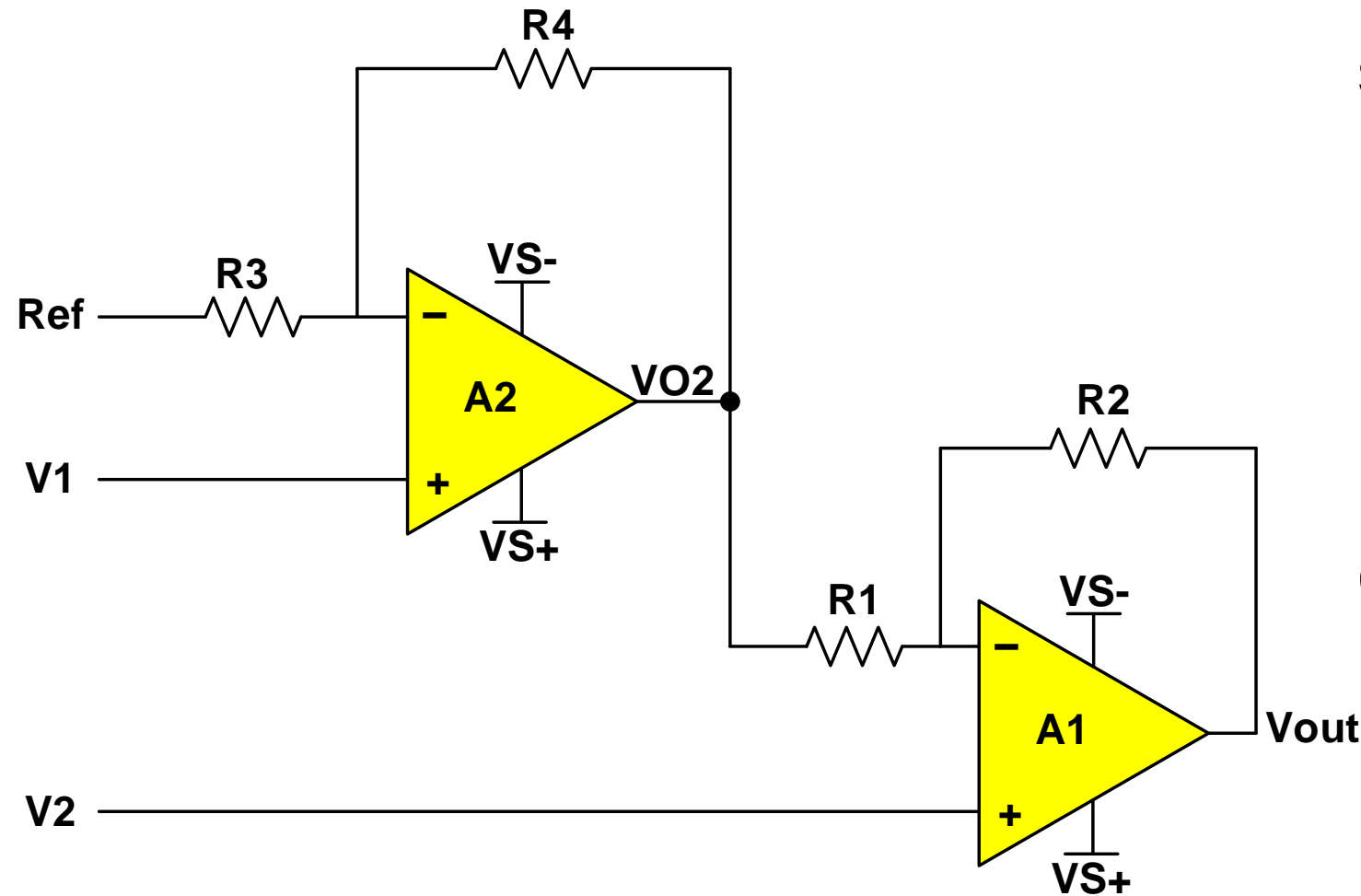IA topologies – 2 amp IA derivation; A1 derivation



Derive output of A1 using superposition:

Equation	V2	VO2	
V2*	Keep	Short	$V2^* = \left(1 + \frac{R2}{R1}\right) \times V2$
VO2*	Short	Keep	$VO2^* = \frac{-R2}{R1} \times VO2$
$Vout = V2^* + VO2^*$			

Combine V2* and VO2* to yield Vout:

$$Vout = \left(1 + \frac{R2}{R1}\right) \times V1 - \frac{R2}{R1} \times VO2 \text{ (eq1)}$$

$$VO2 = \frac{-R4}{R3} \times Ref + \left(1 + \frac{R4}{R3}\right) \times V1 \text{ (eq2)}$$

$$Vout = \left(1 + \frac{R2}{R1}\right) \times V2 - \frac{R2}{R1} \times \left[\frac{-R4}{R3} \times Ref + \left(1 + \frac{R4}{R3}\right) \times V1 \right]$$

IA topologies – 2 amp IA derivation; simplified

$$V_{out} = \left(1 + \frac{R2}{R1}\right) \times V2 - \frac{R2}{R1} \times \left[\frac{-R4}{R3} \times Ref + \left(1 + \frac{R4}{R3}\right) \times V1 \right]$$


Assuming $R4 = R1$ and $R3 = R2$:

$$V_{out} = \left(1 + \frac{R2}{R1}\right) \times V2 - \frac{R2}{R1} \times \left[\frac{-R1}{R2} \times Ref + \left(1 + \frac{R1}{R2}\right) \times V1 \right]$$

Simplify...

$$V_{out} = \underbrace{\left(1 + \frac{R2}{R1}\right)}_{Ad} \times \underbrace{(V2 - V1)}_{Vd} + Ref$$

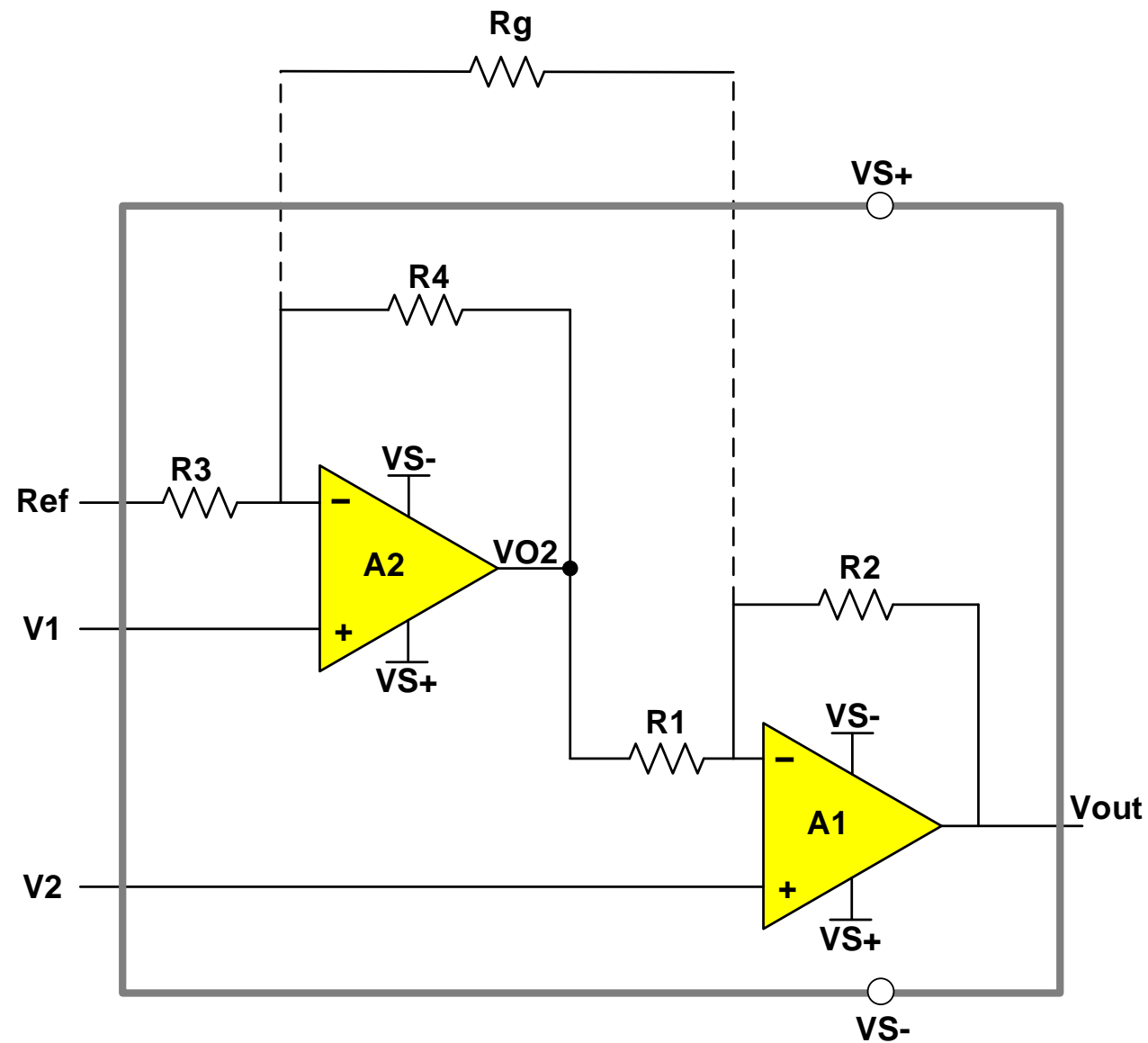2 amp IA – Gain control & driving the Ref pin



Goal: Set the gain of the entire circuit with one additional resistor

Adding resistor Rg yields the following output equation:

$$V_{out} = \left(1 + \frac{R2}{R1} + \frac{2 \times R2}{Rg} \right) \times (V2 - V1) + Ref$$

Resistor matching recap:

Aim for $R4 = R1$ and $R3 = R2$


In an integrated solution, R1, R2, R3, and R4 are absolutely matched in production.

Reference voltage recap:

Drive with low-impedance source, such as a buffer or voltage reference

2 amp IA – ACM analysis and performance
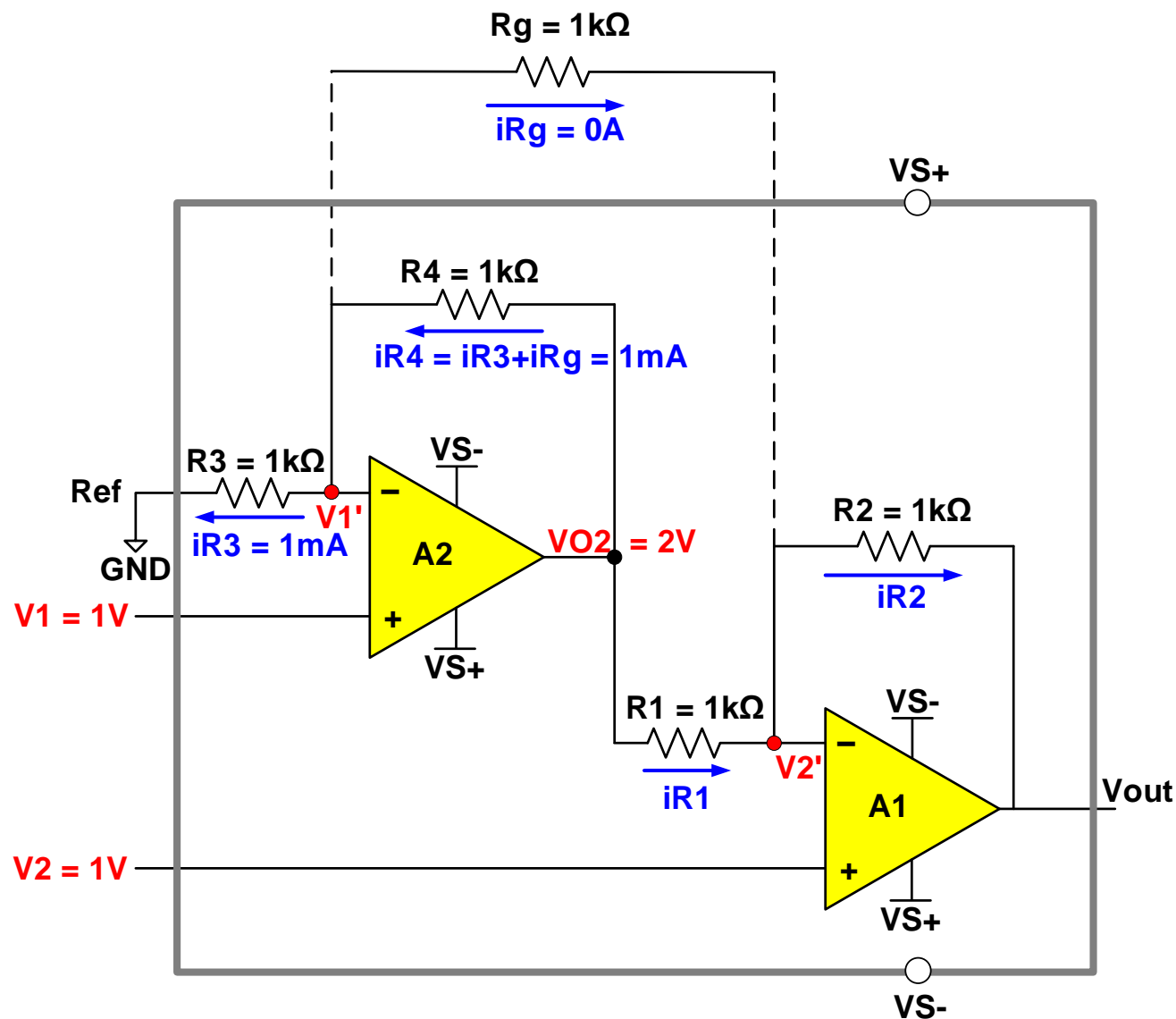
$$\text{Common mode gain} = A_{CM} = \frac{V_{OCM}}{V_{CM}} \ll 1$$



Apply a 1V VCM (1V at V1 and V2)

Assume:

- Ref is grounded
- R1, R2, R3, R4 and Rg = 1kΩ

If $V1 = 1V \rightarrow V1' = 1V$:


- Current flowing through R3 = $1V/1k\Omega = 1mA$

If $V2 = 1V \rightarrow V2' = 1V$:

- $V1' = V2' = 1V$, there is no current flowing through Rg, so $iRg = 0A$

- $iR4 = iR3 + iRg = 1mA$,
 - Voltage drop across R4 is 1V, so $VO2 = 2V$

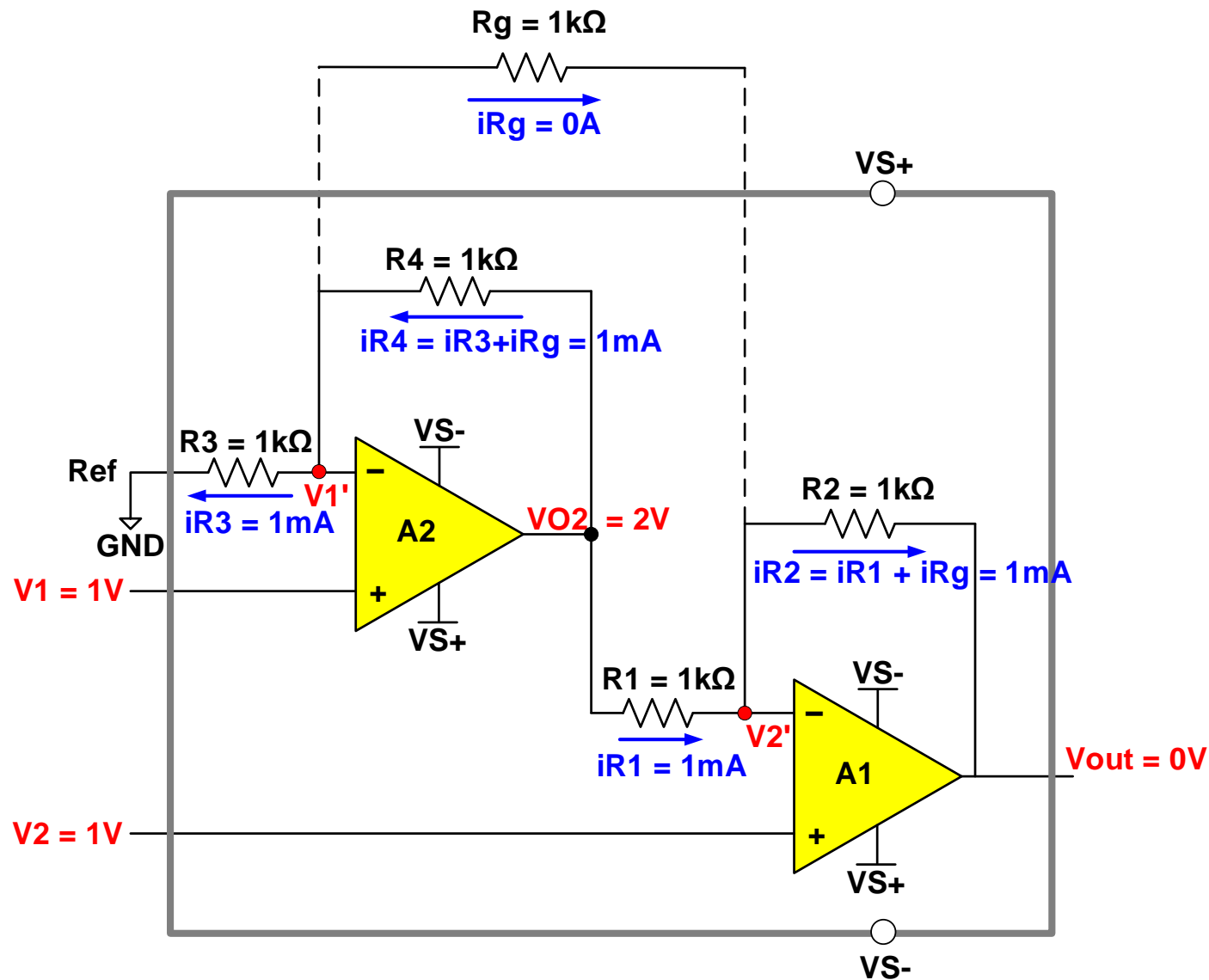2 amp IA – ACM analysis and performance cont'd



$V_{O2} = 2V$ and $V_{2'} = 1V$:


– current flowing through R_1 is $1V/1k\Omega = 1mA$

$i_{R2} = i_{Rg} + i_{R1} = 1mA$

Voltage drop across R_2 is $1V$, so $V_{out} = 0V$

The two-amp IA was able to reject the common mode voltage (VCM)

2 amp IA topology drawbacks – Gain

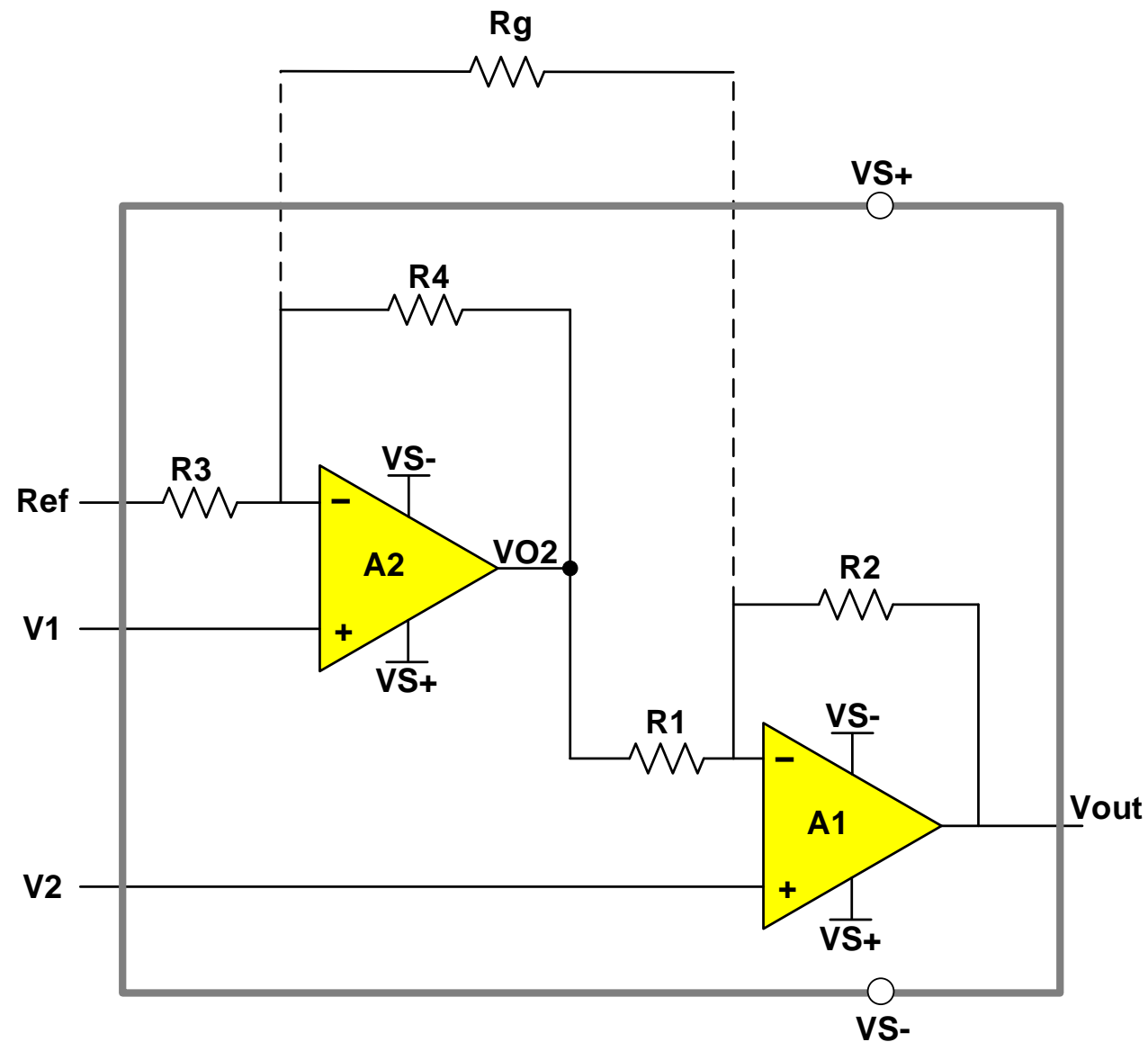

$$V_{out} = \left(1 + \frac{R2}{R1} + \frac{2 \times R2}{Rg} \right) \times (V2 - V1) + Ref$$

$$A_d = \text{differential gain} = 1 + \frac{R2}{R1} + \frac{2 \times R2}{Rg}$$


$$V_d = \text{differential voltage} = V2 - V1$$

Ref = reference voltage, level shifting term

Drawback:

- A_d cannot be 1V/V due to the addition of 1 in the gain equation: $1 + \frac{R2}{R1} + \frac{2 \times R2}{Rg}$

2 amp IA topology drawbacks – Headroom

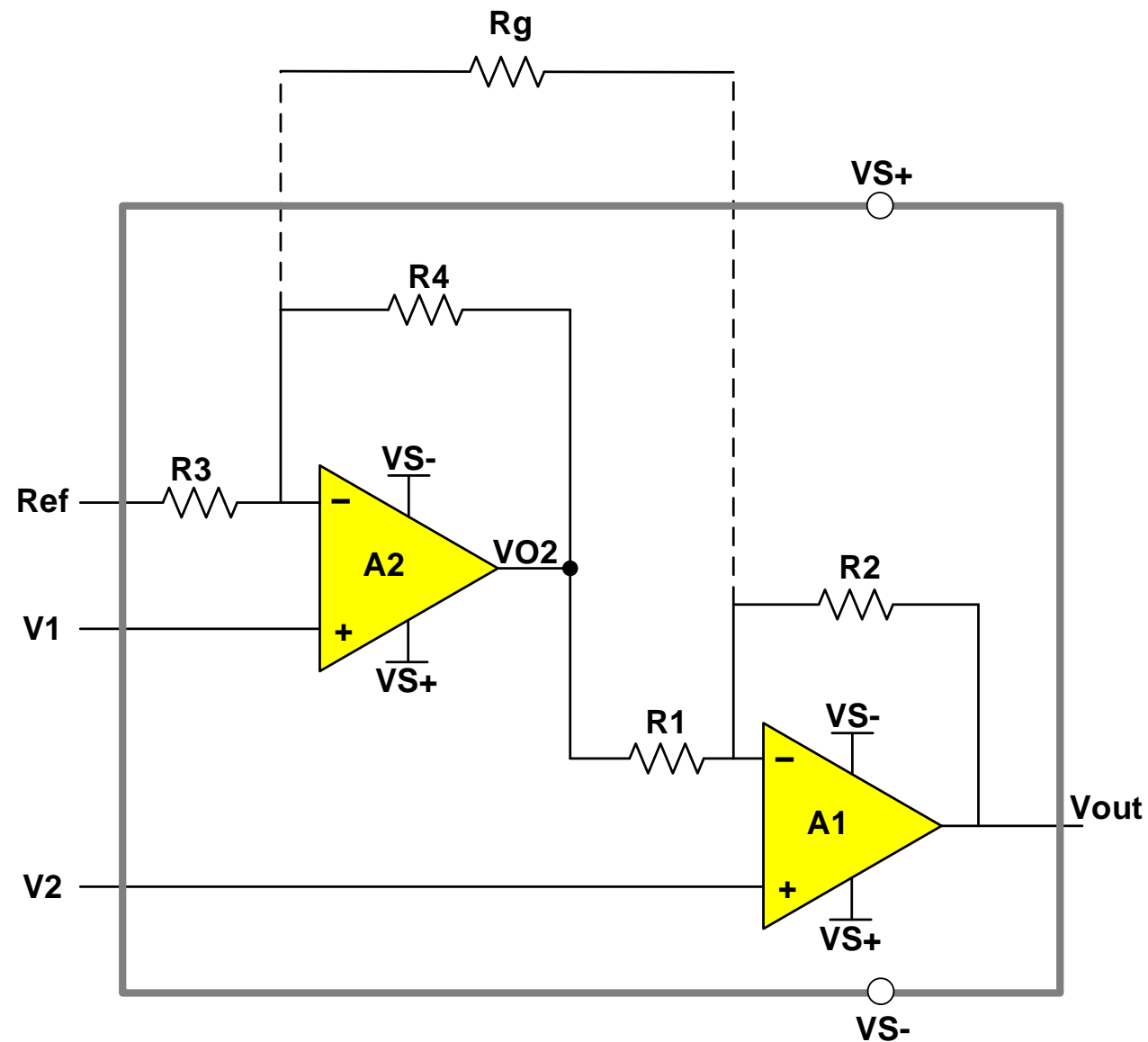

$$V_{out} = \left(1 + \frac{R2}{R1} + \frac{2 \times R2}{Rg} \right) \times (V1 - V2) + Ref$$


Drawback:

- Headroom:
 - Low gain: If $R4 \gg R3$, A2 will saturate if V1 VCM is too high, leaving no headroom for A2 to amplify the wanted signal
 - High gain: If $R4 \ll R3$, there is more headroom at VO2, allowing for higher VCM

*Note: Ref = 0V

2 amp IA topology drawbacks – Headroom cont'd
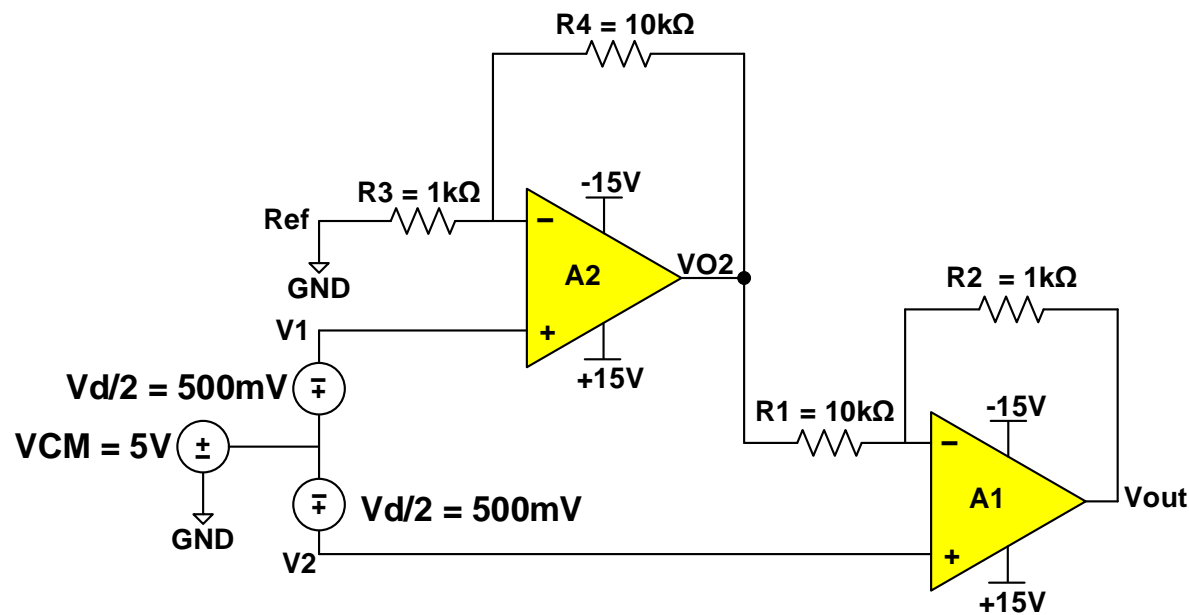
$$V_{out} = \left(1 + \frac{R_2}{R_1} + \frac{2 \times R_2}{R_g} \right) \times (V_d) + Ref$$




Low gain example: $R_4 \gg R_3$

Assume A1 and A2 are powered by $\pm 15V$ supplies

$A_d = 1.1 \text{ V/V}$, $V_d = 1V$

$V_{CM} = 5 \text{ V}$, $Ref = 0V$

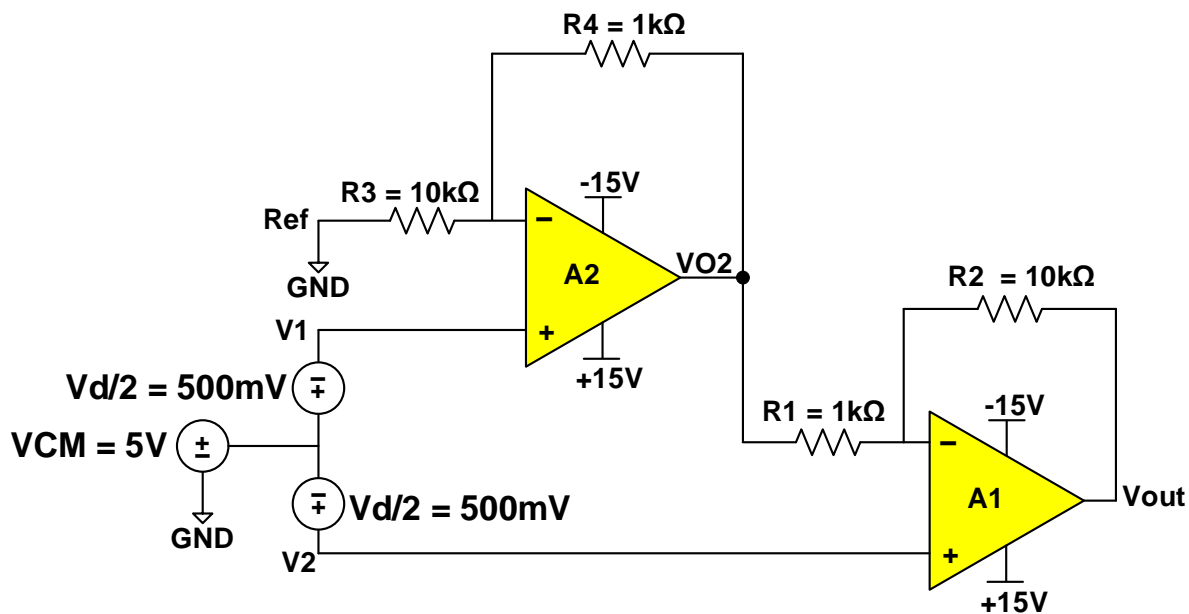Expected output $V_{out} = A_d \times V_d + Ref = 1.1 \text{ V}$



High gain example: $R_4 \ll R_3$

Assume A1 and A2 are powered by $\pm 15V$ supplies


$A_d = 11 \text{ V/V}$, $V_d = 1V$

$V_{CM} = 5 \text{ V}$, $Ref = 0V$

Expected output $V_{out} = A_d \times V_d + Ref = 11 \text{ V}$

2 amp IA topology drawbacks – Headroom cont'd
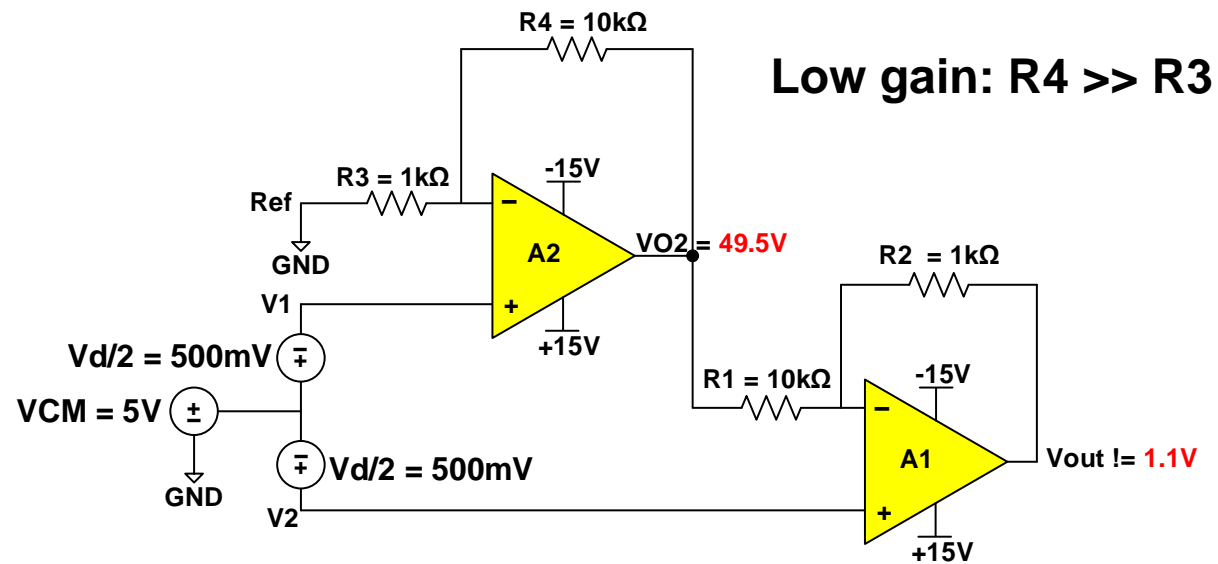
$$V_{out} = \left(1 + \frac{R_2}{R_1} + \frac{2 \times R_2}{R_g} \right) \times (V_d) + Ref$$




A1 and A2: $\pm 15V$ supplies, RRIO

Ad = 1.1 V/V, Vd = 1V, VCM = 5V, Ref = 0V

Expected output $V_{out} = A_d \times V_d + Ref = 1.1 V$

VO2 = **49.5V**

Vout != **1.1V**

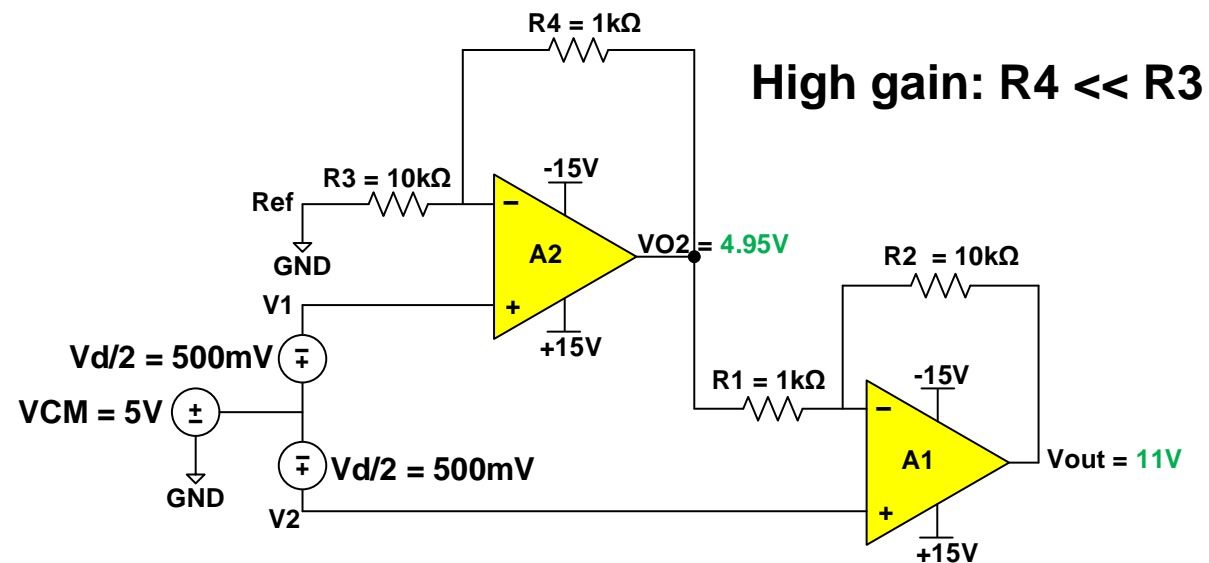

A1 and A2: $\pm 15V$ supplies, RRIO


Ad = 11 V/V, Vd = 1V, VCM = 5V, Ref = 0V

Expected output $V_{out} = A_d \times V_d + Ref = 11 V$

VO2 = **4.95V**

VOUT = **11V**

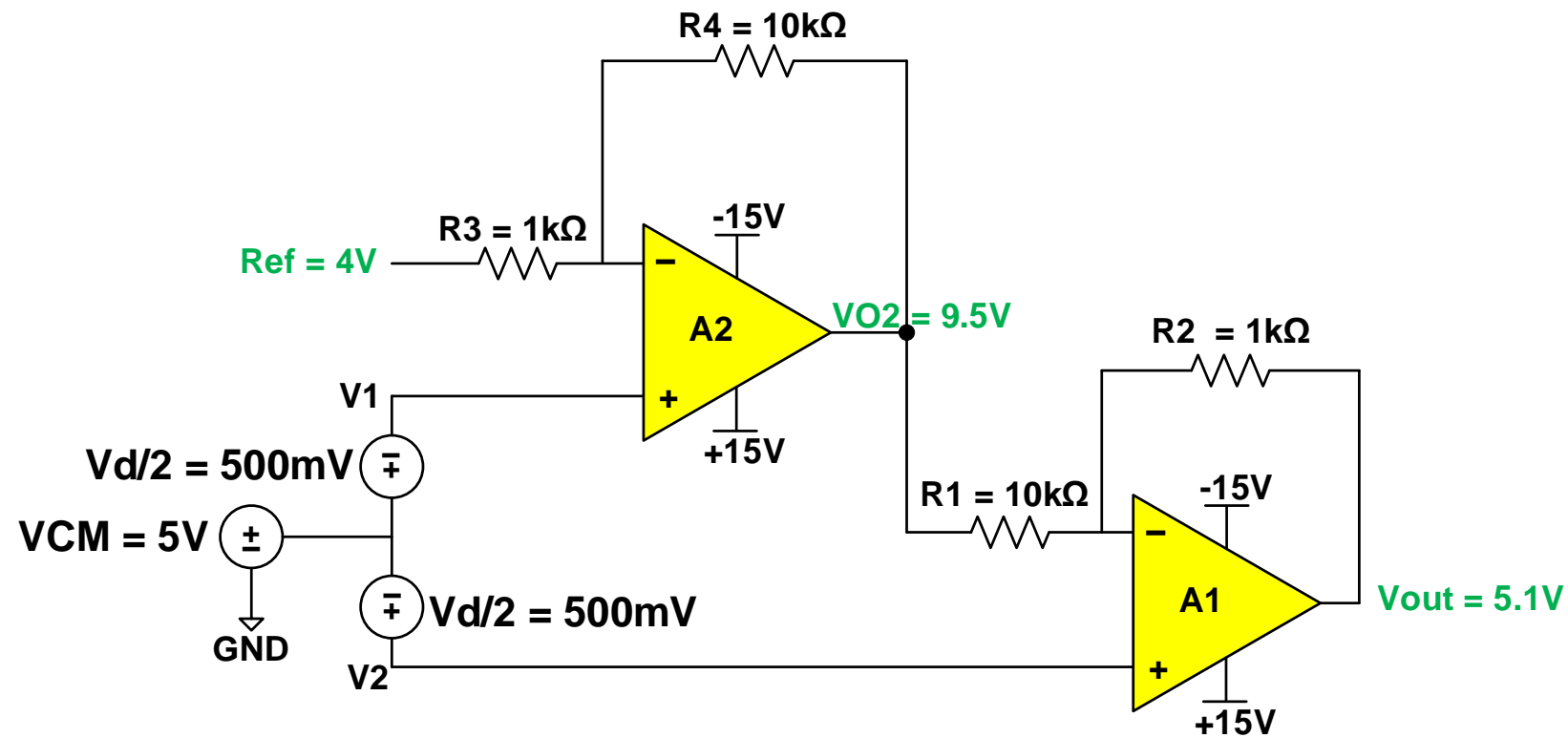2 amp IA topology drawbacks – Headroom cont'd



Low gain: $R4 \gg R3$

- A1 and A2: $\pm 15V$ supplies, RRIO
- Differential gain (A_d) = 1.1 V/V
- Differential voltage (V_d) = 1V
- Common mode voltage (V_{CM}) = 5V
- Reference voltage (Ref) = 4V

Expected output:

$$V_{out} = A_d \times V_d + Ref = 5.1 \text{ V}$$





$$VO_2 = 9.5V$$

$$V_{out} = 5.1V$$


$$V_{out} = \left(1 + \frac{R_2}{R_1} + \frac{2 \times R_2}{R_g} \right) \times (V_d) + Ref$$

2 amp IA vs 3 amp IA – Headroom

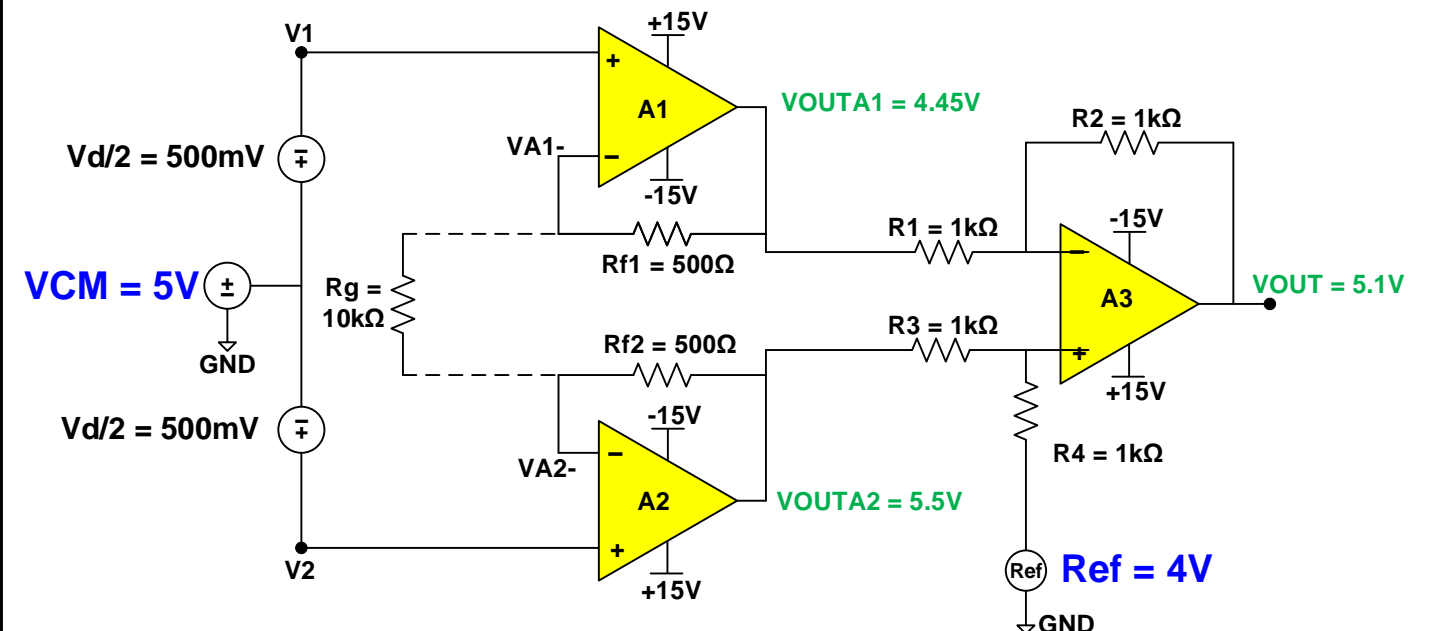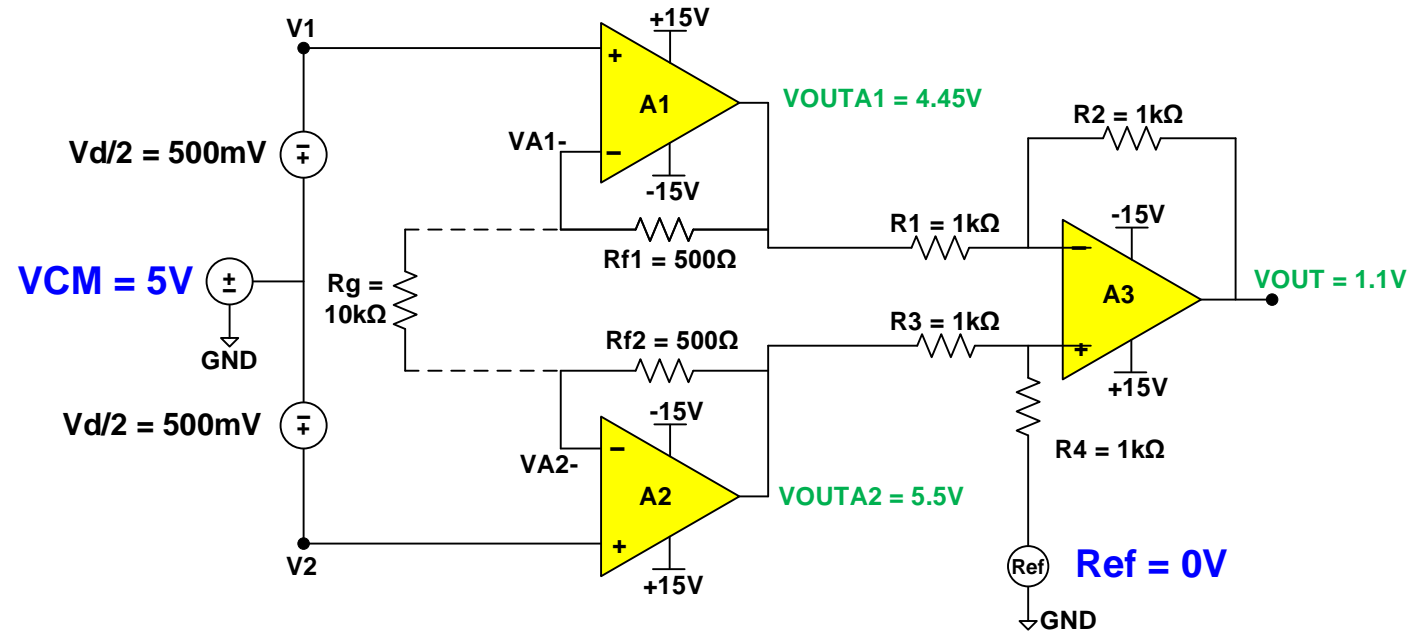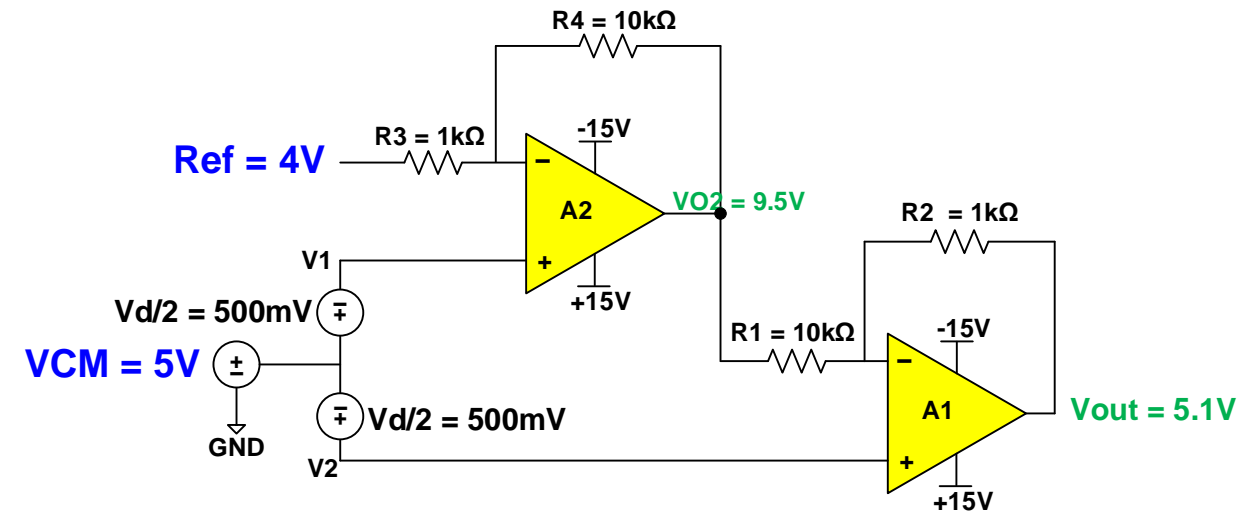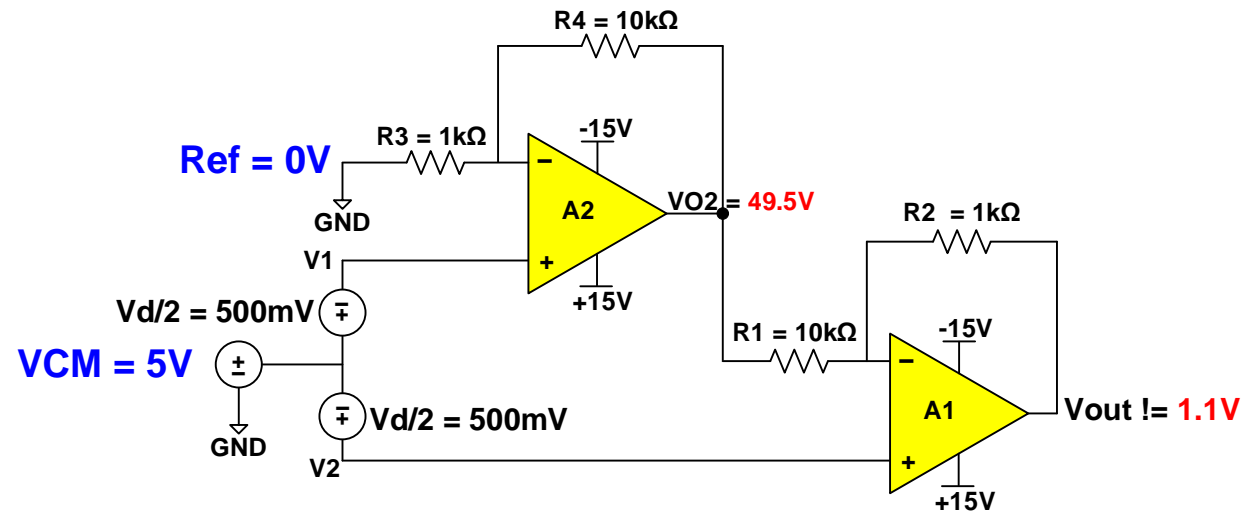$A_d = 1.1V/V$, $V_d = 1V$, $V_{CM} = 5V$
 $Ref = 0V$ or $4V$
 Expected $V_{out} = 1.1V$ or $5.1V$



2 amp IA topology drawbacks – AC CMRR

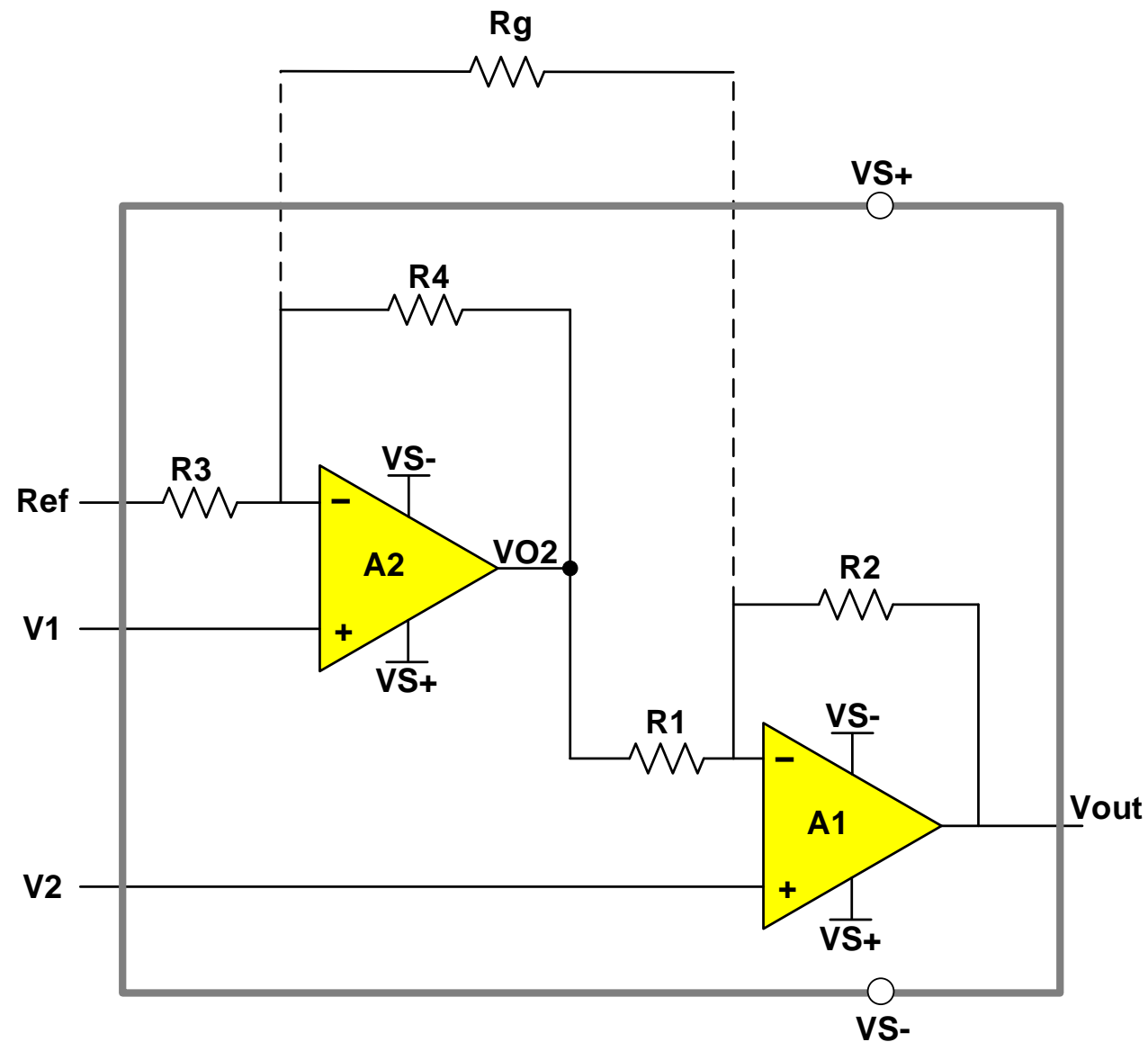

Drawback:

- AC CMRR:
 - Path from V1 to Vout has an additional phase shift of A2

Example:

Assume we apply VCM at FCM to V1 and V2. Expected common mode error = 0V which means A1 needs to see 0 difference between V2 and VO2.

Phase shift introduced by A2 causes the phase of VO2 to lag behind V2 → frequency-dependent common mode voltage error at Vout

2 amp IA – Example

Assume the following conditions:


Voltage supplies = $\pm 10V$, Ref = 0V

$V_d = 10mV$, $V_{CM} = 2V$

Expected $V_{out} = 3V$

4 design steps:

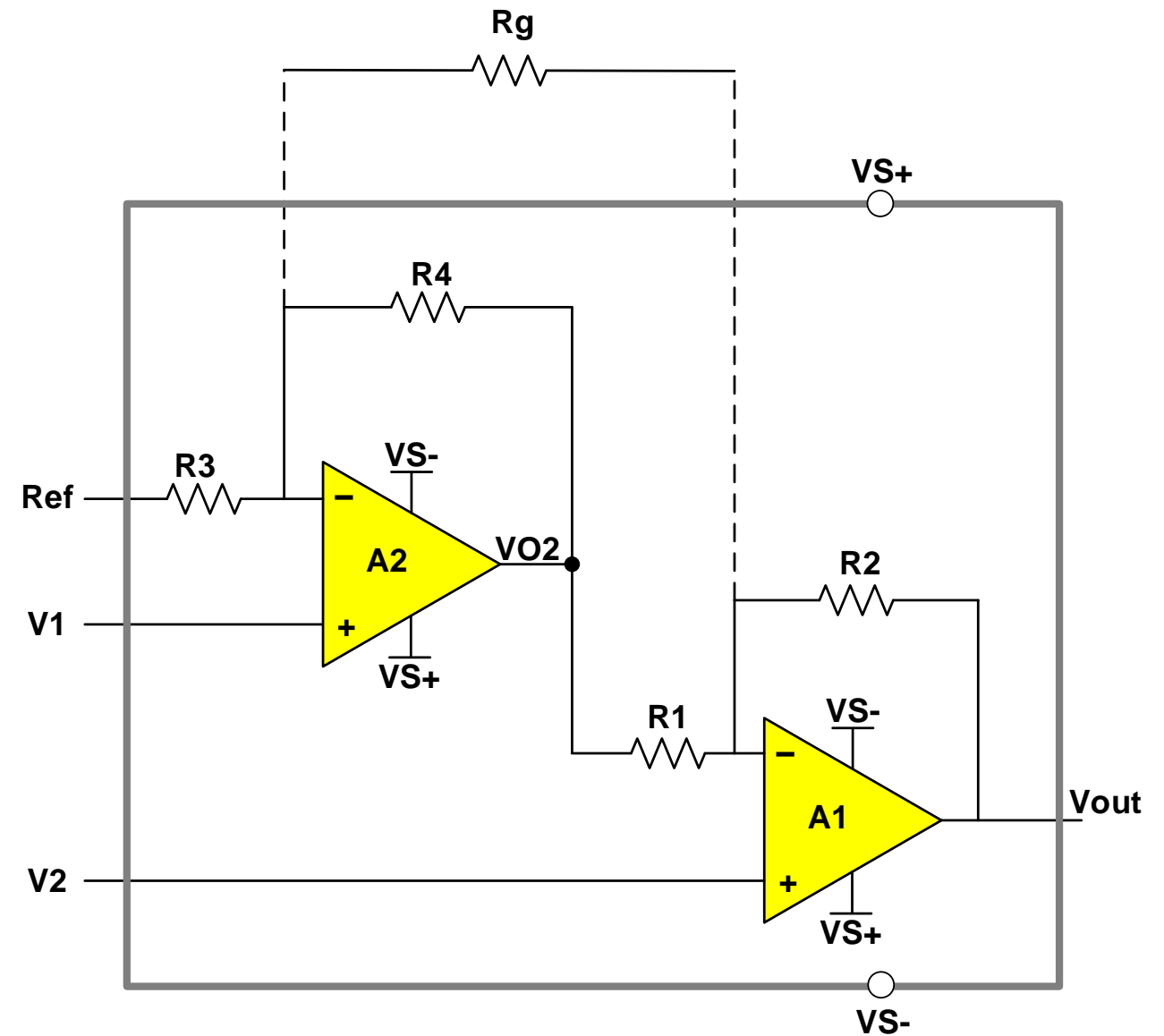1. Determine gain required
2. Find IA & check boundary plot
3. Determine R_g required
4. Build and simulate with confidence



2 Amp IA – Example cont'd

1. Determine gain required


$$\text{Gain} = \frac{\Delta V_{out}}{\Delta V_{in}} = \frac{3V}{10mV} = 300V/V$$

2. Find IA & check boundary plot

IA selected: INA126

Plug in supply, gain, ref and VCM

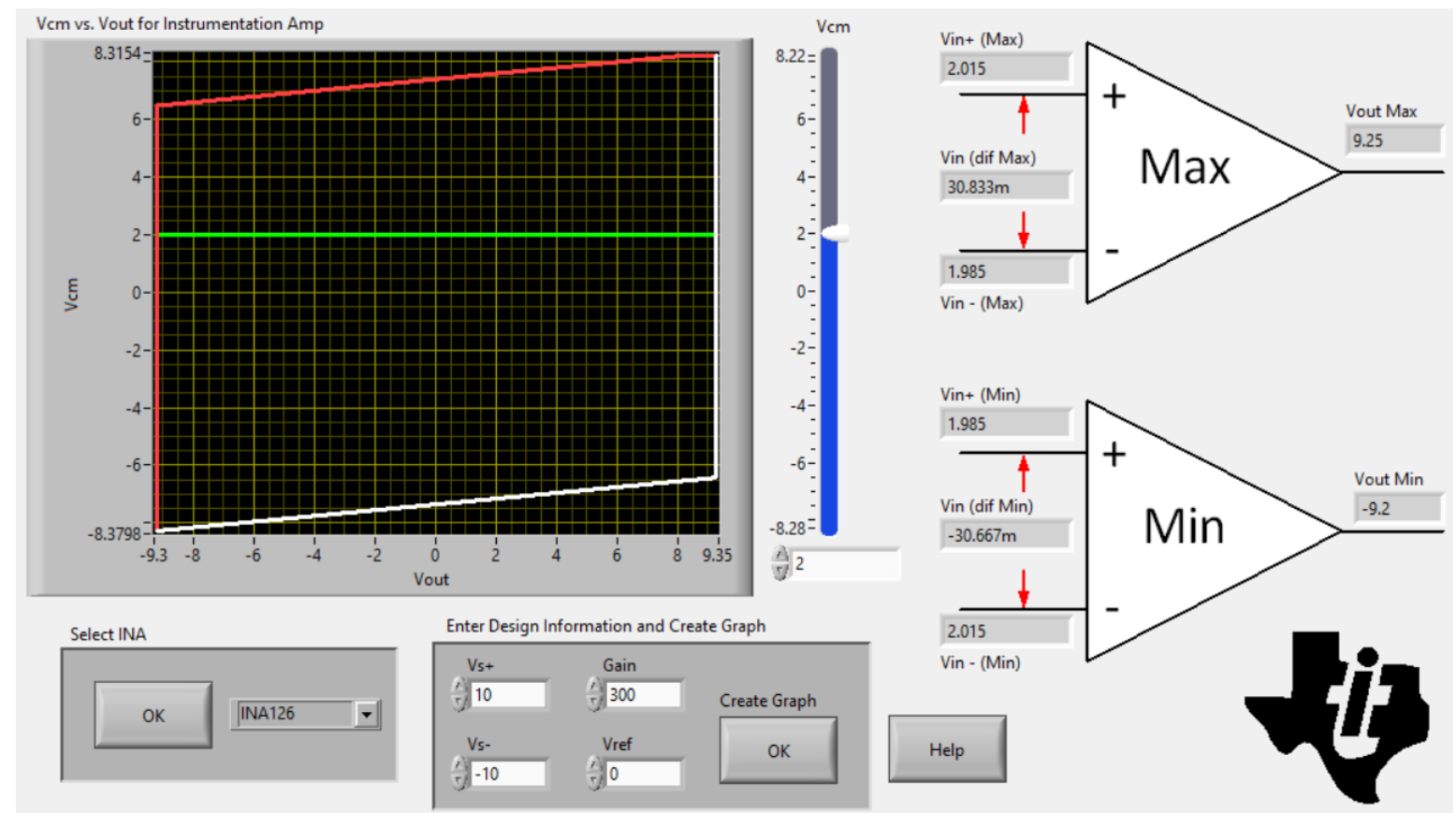Make sure our expected input & output voltages are within range




[Analog engineer's calculator → INA VCM vs Vout](#)

2 amp IA – Example cont'd


3. Determine R_g required

$$\text{INA126 datasheet} \rightarrow \text{Gain} = 5 + \frac{80k}{R_g} \rightarrow R_g = 271\Omega$$

4. Build and simulate with confidence

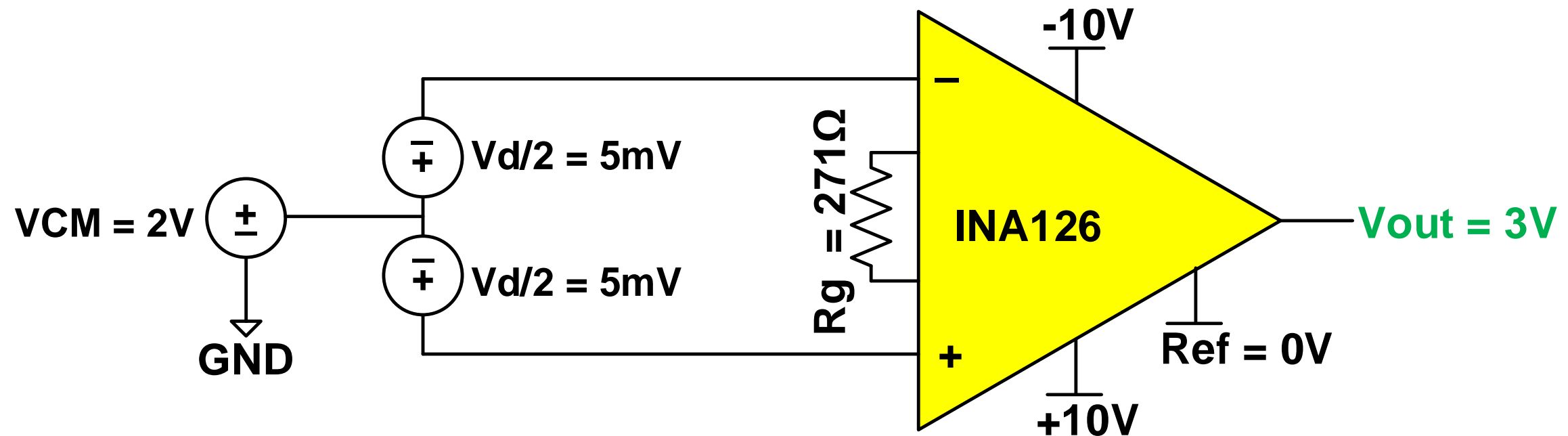

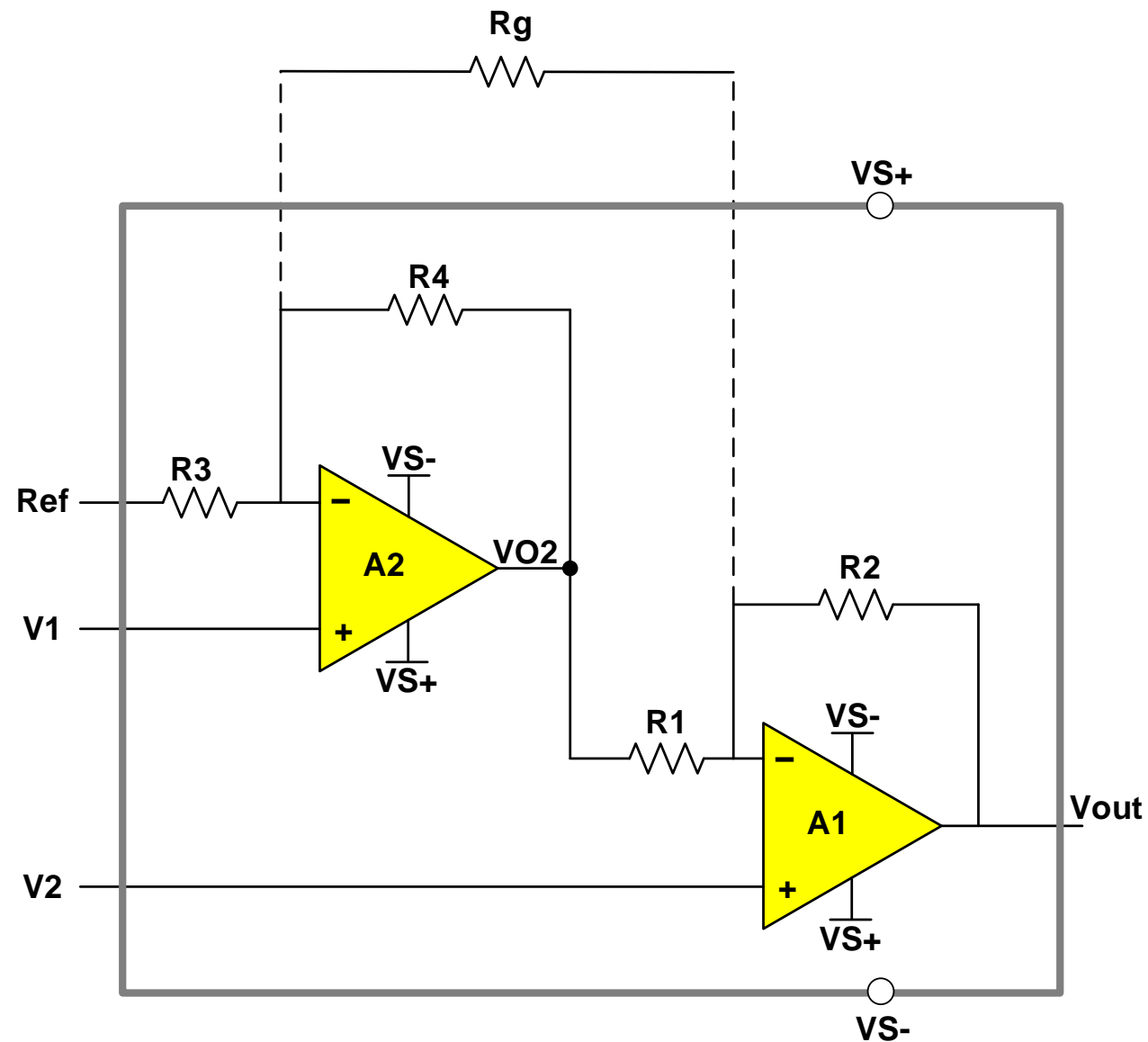2 amp IA – Summary of benefits and drawbacks



Benefits:

- Fewer resistors, must need to be well matched → pick an integrated IA
- Fewer amplifiers → lower cost
- High input impedance

Drawbacks:

- Minimum gain limitation ($> 1V/V$ minimum)
- Gain vs headroom
- CMRR vs frequency
- Common mode voltage must be within the power supply rails

Thanks for your time!
Please try the quiz.

To find more Instrumentation Amplifier technical resources and search products, visit [ti.com/inas](https://www.ti.com/inas)

Quiz: Instrumentation Amplifier (IA) topologies: two-amp

TI Precision Labs – Instrumentation Amplifiers


Presented by Tamara Alani

Prepared by Tamara Alani

Quiz: (IA) topologies: two-amp || Question

1. What are some challenges associated with the two-amp IA topology? Select all that apply.

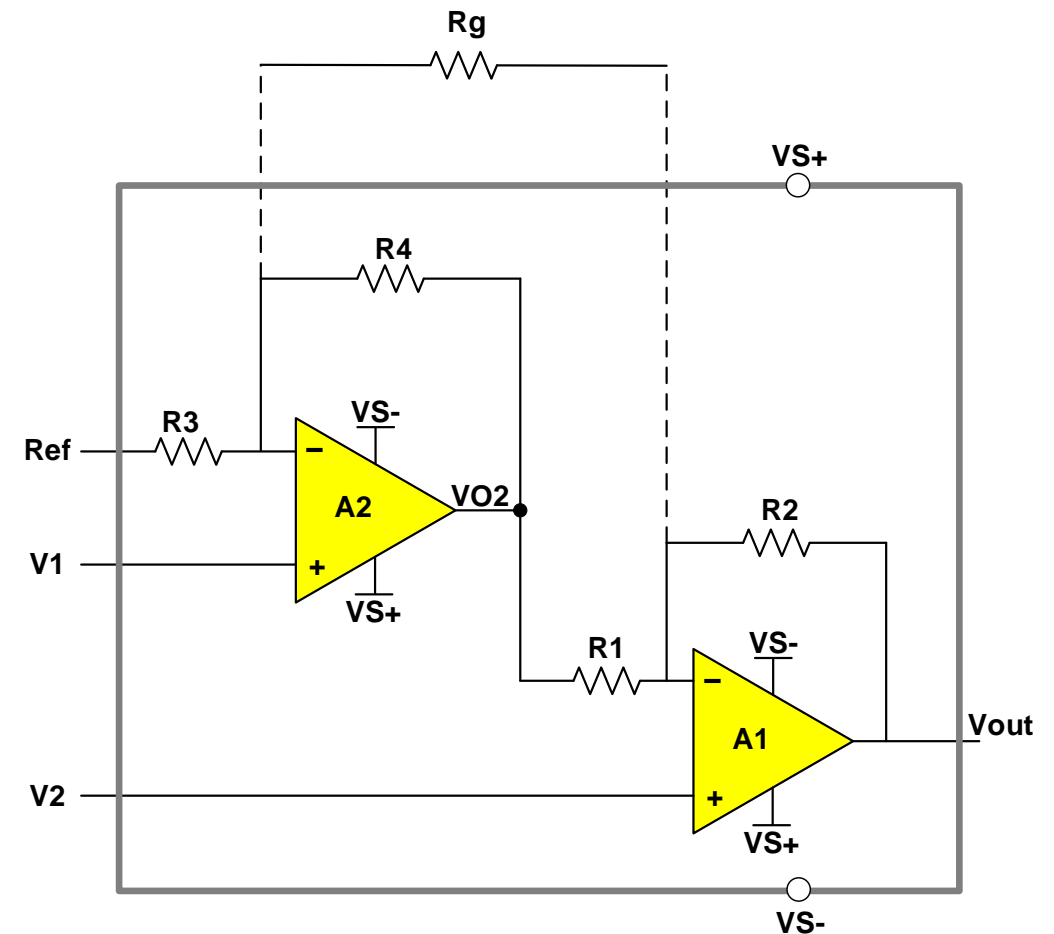
- a) The path from V1 to Vout has an additional phase shift of A2
- a) The two-amp IA must be configured in gains > 1 V/V
- a) The two-amp IA consumes more power
- b) There is trade-off between VCM and Ref to Gain



Quiz: (IA) topologies: two-amp || Answer

1. What are some challenges associated with the two-amp IA topology? Select all that apply.

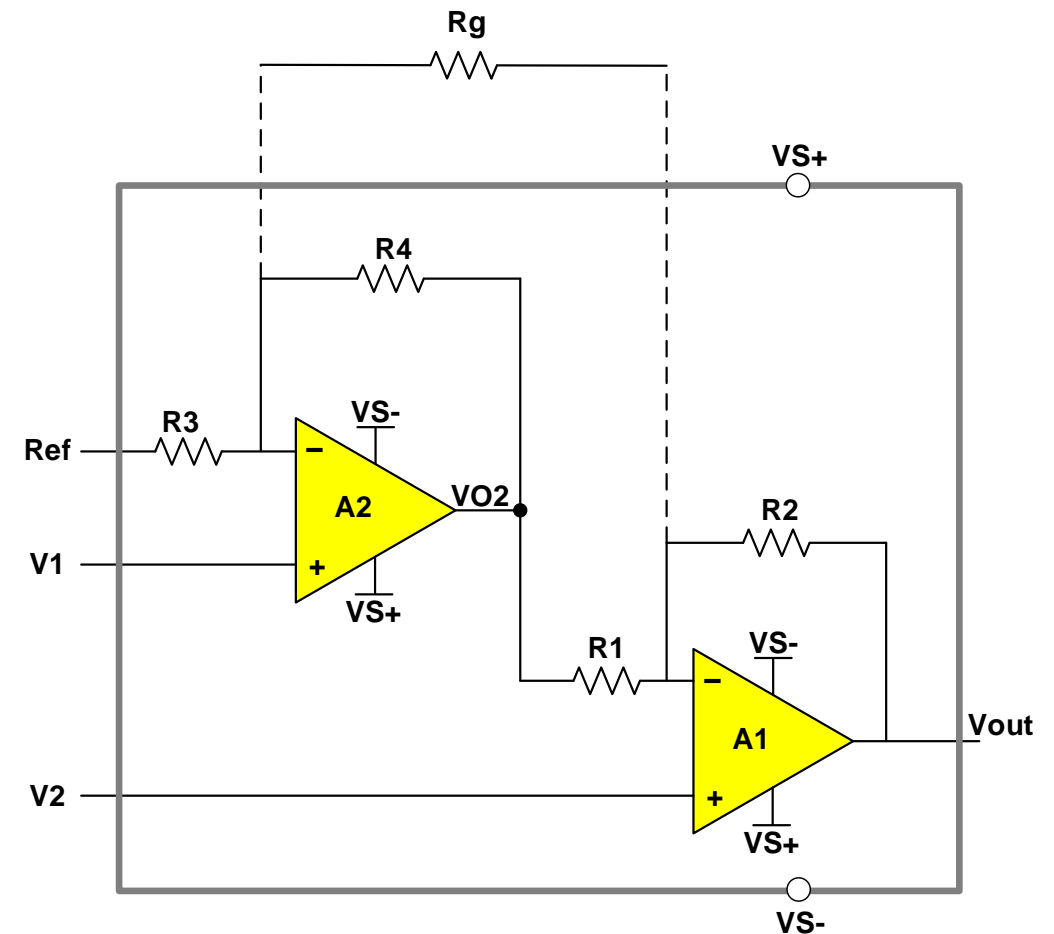- a) The path from V1 to Vout has an additional phase shift of A2
- a) The two-amp IA must be configured in gains > 1 V/V
- a) The two-amp IA consumes more power
- b) There is trade-off between VCM and Ref to Gain



Quiz: (IA) topologies: three-amp || Question

2. Which of the following statements is false regarding the reference pin on a two-amp IA?
- a) The ref pin must be driven by a low-impedance source
 - b) The ref pin is used to level-shift the output of the IA
 - c) The ref pin should be able to source and sink current
 - d) The ref pin may be driven by a resistor divider so long as the resistors are low tolerance


Quiz: (IA) topologies: two-amp || Answer

2. Which of the following statements is false regarding the reference pin on a two-amp IA?
- a) The ref pin must be driven by a low-impedance source
 - b) The ref pin is used to level-shift the output of the IA
 - c) The ref pin should be able to source and sink current
 - d) The ref pin may be driven by a resistor divider so long as the resistors are low tolerance**

Quiz: (IA) topologies: two-amp || Question

3. In a two-amp IA, which resistors do we aim to match?

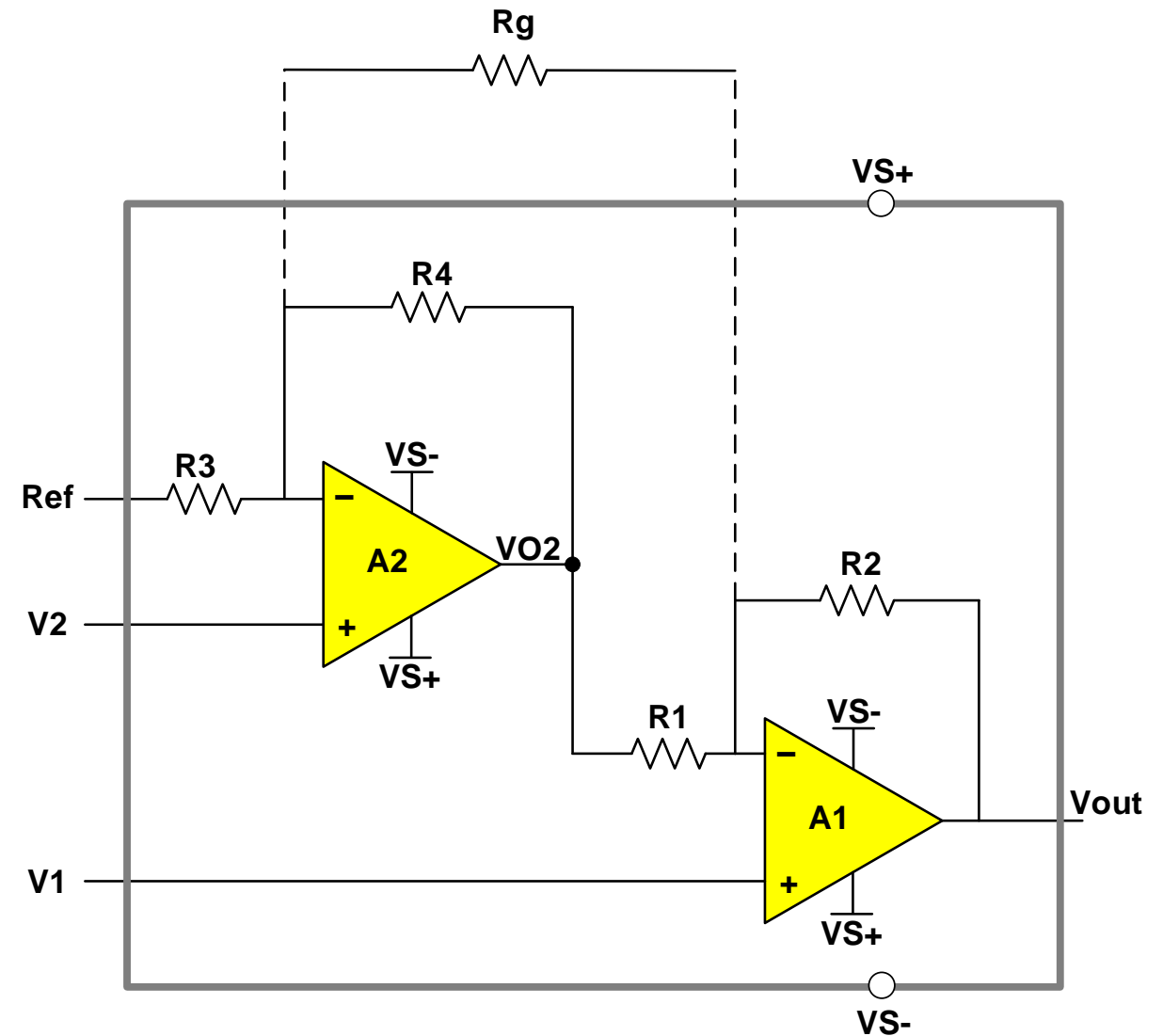- a) $R4 = R1$ and $R2 = R3$
- b) $R4 = R3$ and $R2 = R1$




Quiz: (IA) topologies: two-amp || Answer

3. In a two-amp IA, which resistors do we aim to match?

a) $R4 = R1$ and $R2 = R3$

b) $R4 = R3$ and $R2 = R1$

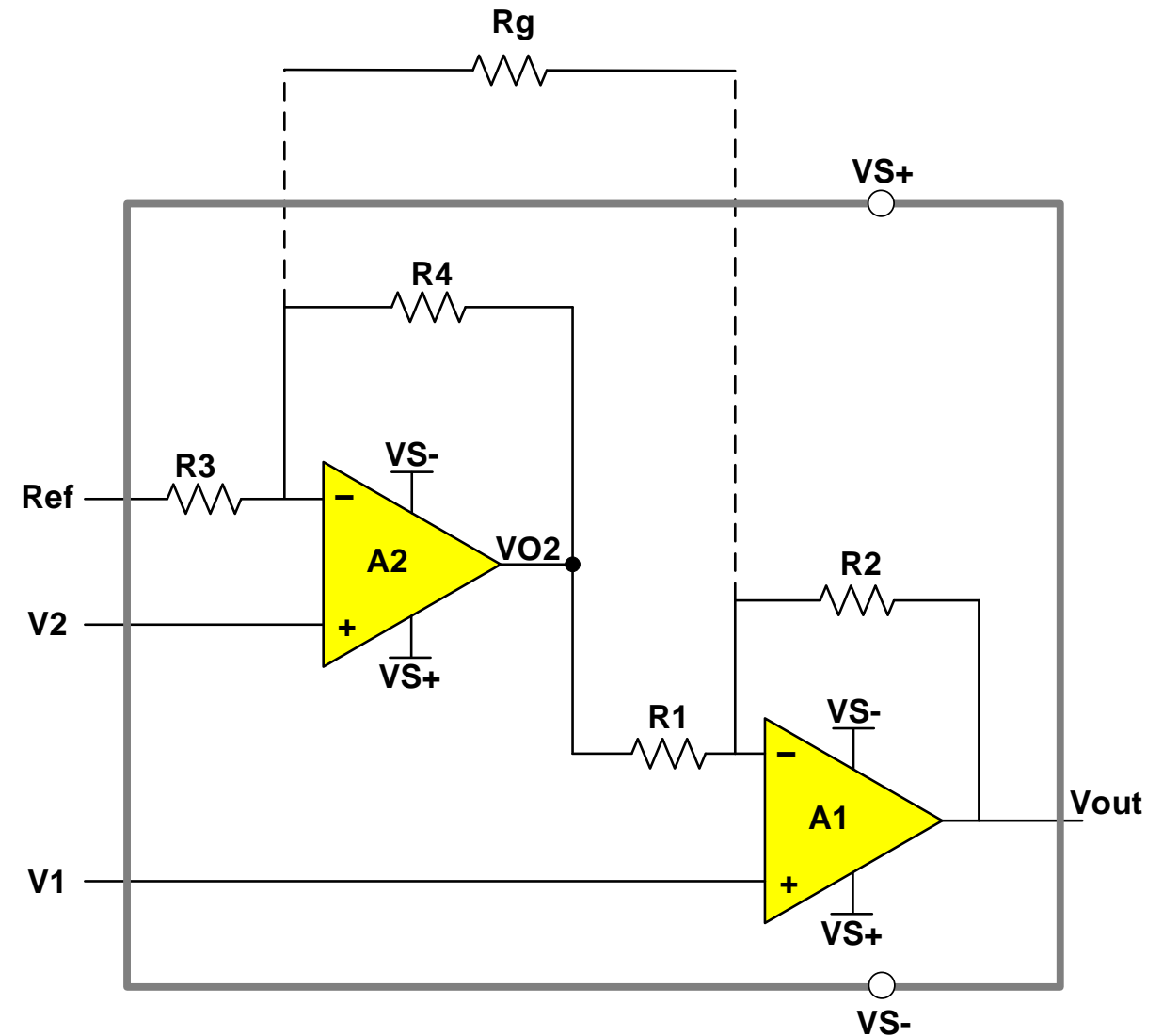

Quiz: (IA) topologies: three-amp || Question

4. What is the gain equation of a two-amp IA, assuming we match R4 to R1 and R3 to R2?

a) $\text{Gain} = 1 + 2 \times R2$

b) $\text{Gain} = 1 + \frac{R1}{R2}$

c) $\text{Gain} = 1 + \frac{R2}{R1}$

d) $\text{Gain} = 2 \times (R1 + R2)$

HINT:

Go to the product datasheet:

<https://www.ti.com/lit/ds/symlink/ina126.pdf>

Quiz: (IA) topologies: two-amp || Answer

4. What is the gain equation of a two-amp IA, assuming we match R4 to R1 and R3 to R2?

a) $\text{Gain} = 1 + 2 \times R2$

b) $\text{Gain} = 1 + \frac{R1}{R2}$

c) **Gain = $1 + \frac{R2}{R1}$**

d) $\text{Gain} = 2 \times (R1 + R2)$

HINT:

Go to the product datasheet:

<https://www.ti.com/lit/ds/symlink/ina126.pdf>

Quiz: (IA) topologies: two-amp || Question

5. Using the INA126 (TI's micro-power IA), what value of R_g do you need to achieve a signal gain of 105V/V?

- a) $R_g = 100\Omega$
- b) $R_g = 200\Omega$
- c) $R_g = 800k\Omega$
- d) $R_g = 800\Omega$

HINT:

Go to the product datasheet:

<https://www.ti.com/lit/ds/symlink/ina126.pdf>

Quiz: (IA) topologies: two-amp || Answer

5. Using the INA126 (TI's micro-power IA), what value of R_g do you need to achieve a signal gain of 105V/V?

- a) $R_g = 100\Omega$
- b) $R_g = 200\Omega$
- c) $R_g = 800k\Omega$
- d) **$R_g = 800\Omega$**

HINT:

Go to the product datasheet:


<https://www.ti.com/lit/ds/symlink/ina126.pdf>

$$\text{Gain} = \left(5 + \frac{80k\Omega}{R_g} \right)$$

Quiz: (IA) topologies: two-amp || Question

6. What is the differential gain of the following circuit?

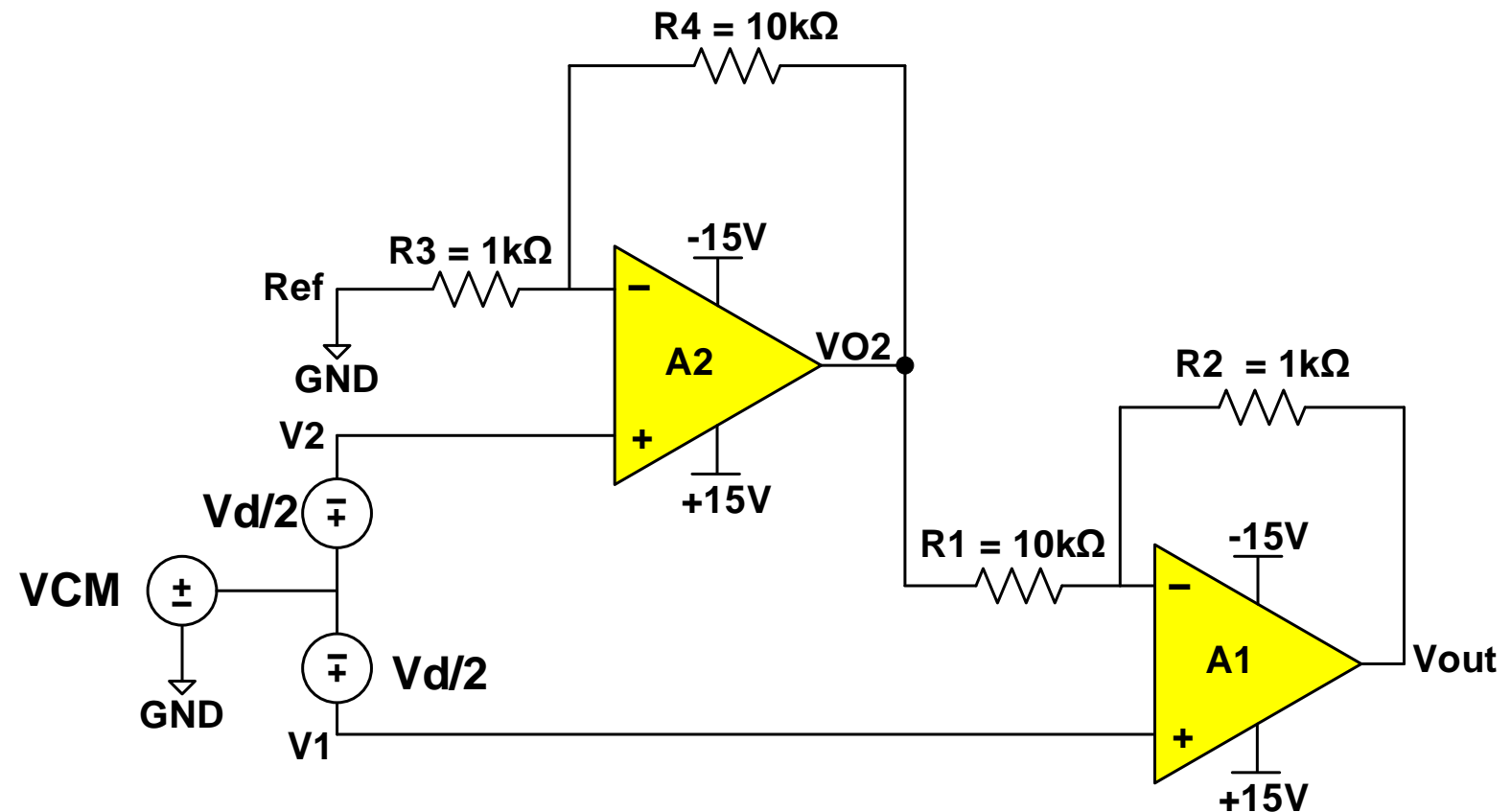
- a) Gain = 1.1V/V
- b) Gain = 2V/V
- c) Gain = 0.1V/V
- d) Gain = 10V/V



Quiz: (IA) topologies: two-amp || Answer

6. What is the differential gain of the following circuit?

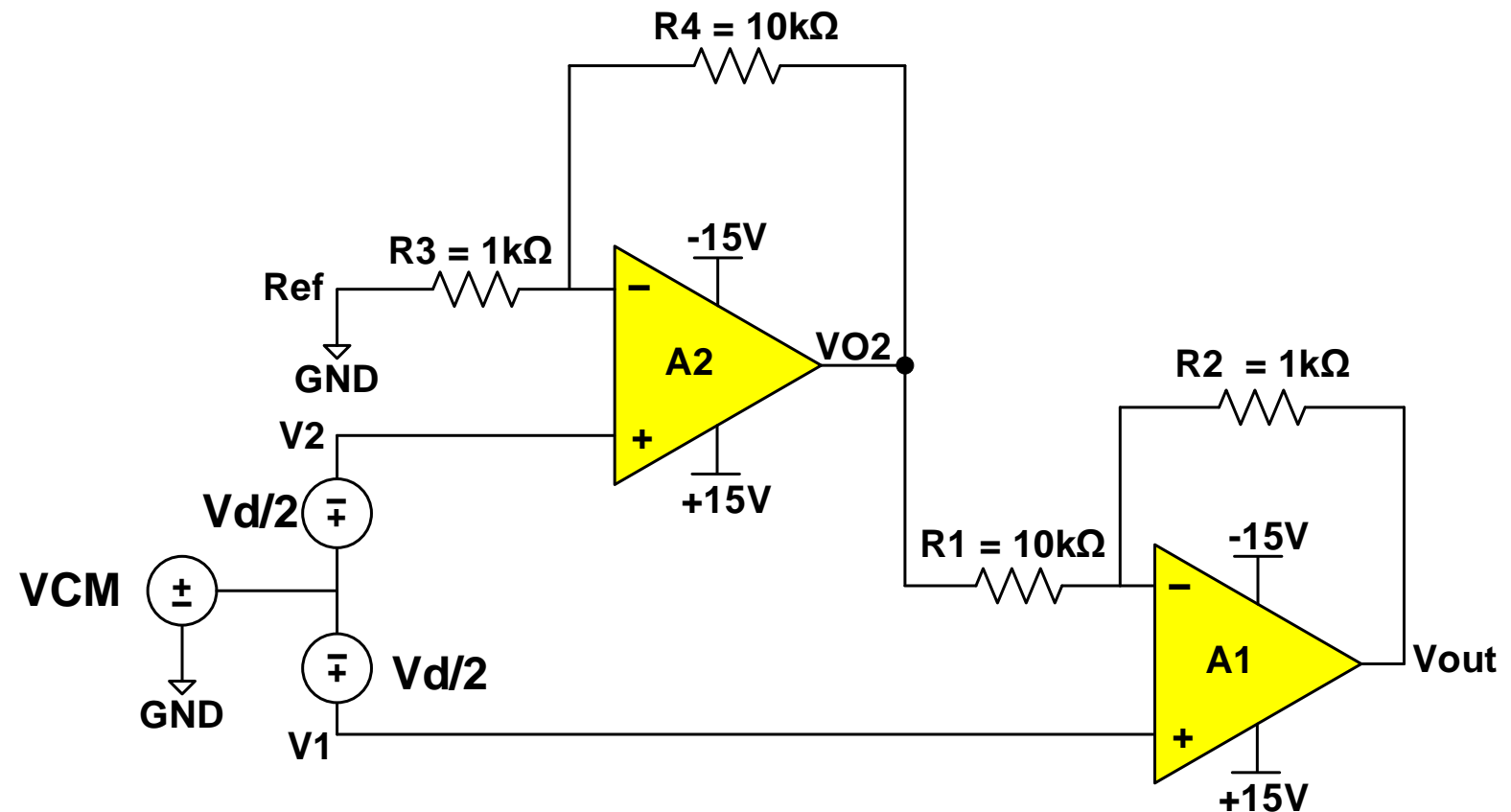- a) Gain = 1.1V/V
- b) Gain = 2V/V
- c) Gain = 0.1V/V
- d) Gain = 10V/V



Quiz: (IA) topologies: two-amp || Question

7. Using the INA156 (TI's rail-to-rail output swing IA optimized for low-voltage, single-supply operation), create a boundary plot for the following conditions:

- Voltage supply = 5V single supply
- Gain = 10V/V
- Reference = 2.5V
- Common mode voltage = 2V

HINT:

Use the INA Boundary Plot calculator in the **Analog Engineer's Calculator**:

<https://www.ti.com/tool/ANALOG-ENGINEER-CALC>

Quiz: (IA) topologies: two-amp || Answer


7. Using the INA156 (TI's rail-to-rail output swing IA optimized for low-voltage, single-supply operation), create a boundary plot for the following conditions:

- Voltage supply = 5V single supply
- Gain = 10V/V
- Reference = 2.5V
- Common mode voltage = 2V

HINT:

Use the INA Boundary Plot calculator in the **Analog Engineer's Calculator**:
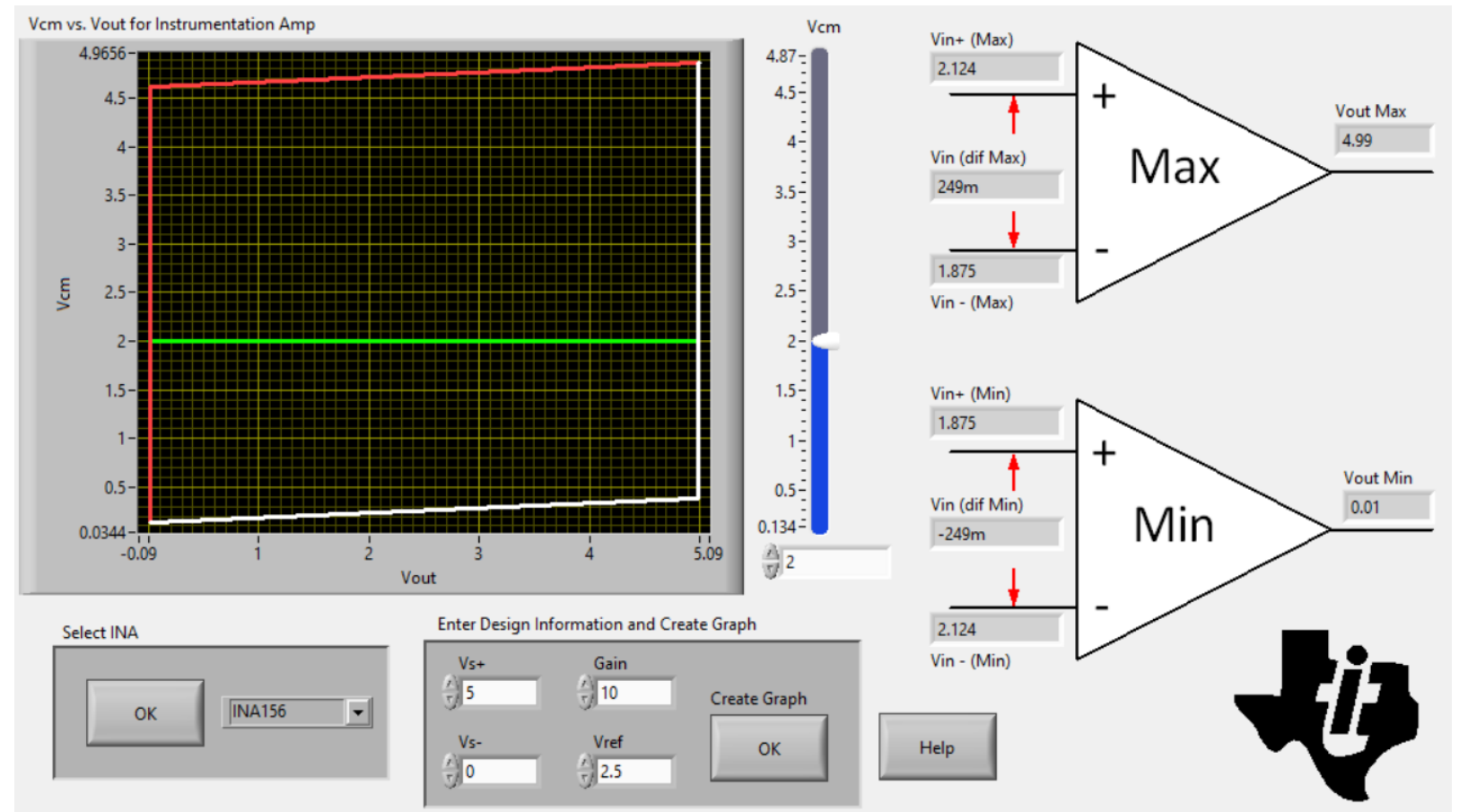
<https://www.ti.com/tool/ANALOG-ENGINEER-CALC>



Quiz: (IA) topologies: two-amp || Question

8. True or false: In an integrated two-amp IA, all resistors are absolutely matched in production

Quiz: (IA) topologies: two-amp || Answer

8. True or false: In an integrated two-amp IA, all resistors are absolutely matched in production

TRUE

Quiz: (IA) topologies: two-amp || Question

9. Which of the following statements is true regarding the relationship between Ref and VCM to Gain?

- a) The further apart Ref is to VCM, lower gains can be achieved
- b) The closer Ref is to VCM, lower gains can be achieved
- c) If Ref = VCM, gain < 1 V/V can be achieved
- d) If Ref \ll VCM, any gain can be achieved

Quiz: (IA) topologies: two-amp || Answer

9. Which of the following statements is true regarding the relationship between Ref and VCM to Gain?

- a) The further apart Ref is to VCM, lower gains can be achieved
- b) The closer Ref is to VCM, lower gains can be achieved**
- c) If Ref = VCM, gain < 1 V/V can be achieved
- d) If Ref \ll VCM, any gain can be achieved

To find more Instrumentation Amplifier technical resources and search products, visit [ti.com/inas](https://www.ti.com/inas)