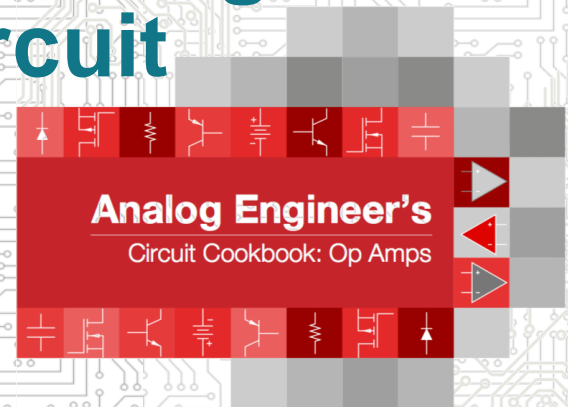


How to Design Inverting Op Amp with Non-Inverting Positive Reference Voltage Circuit


General Purpose Amplifiers

www.ti.com/general-amps

www.ti.com/circuitcookbooks




Circuit Description

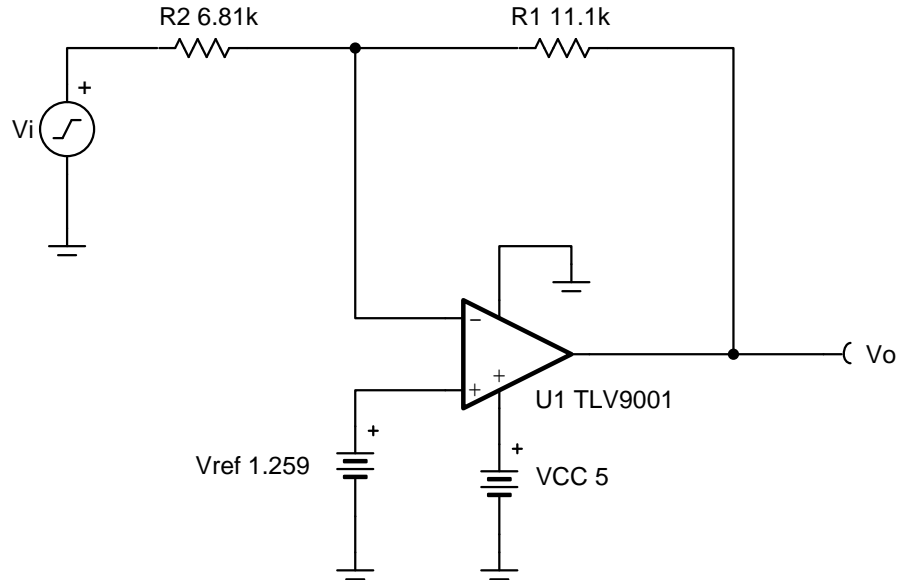

$$V_o = -V_i \times \frac{R_1}{R_2} + V_{ref} \times \left(1 + \frac{R_1}{R_2} \right)$$

Design Steps

Input		Output		Supply		
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}	V_{ref}
-1V	2V	0.05V	4.95V	5V	0V	1.259V

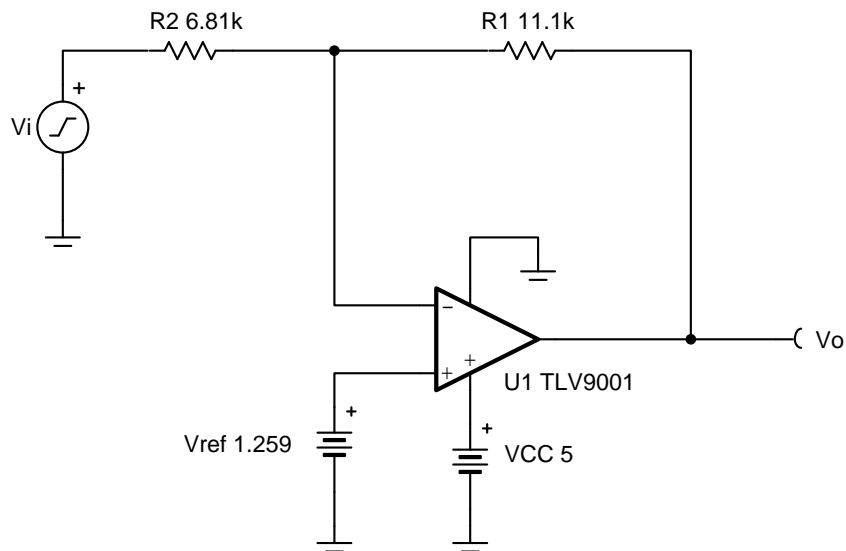


Inverting Gain Non-Inverting Gain

$$V_o = V_i \times \frac{-R_1}{R_2} + V_{ref} \times \left(1 + \frac{R_1}{R_2}\right)$$

Positive Reference Voltage

Design Steps

Input		Output		Supply		
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}	V_{ref}
-1V	2V	0.05V	4.95V	5V	0V	1.259V

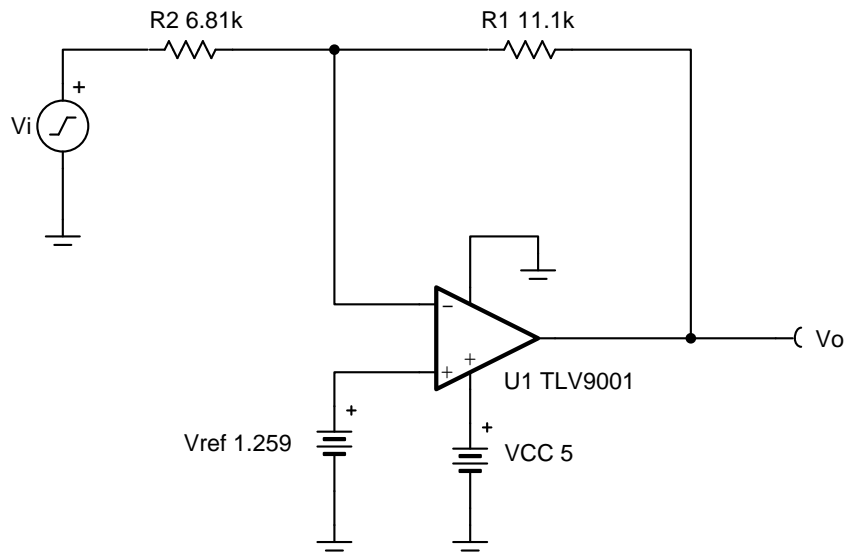


$$G_{input} = -\frac{V_{oMax} - V_{oMin}}{V_{iMax} - V_{iMin}}$$

$$G_{input} = -\frac{4.95V - 0.05V}{2V - (-1V)} = -1.633V/V$$

Design Steps

Input		Output		Supply		
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}	V_{ref}
-1V	2V	0.05V	4.95V	5V	0V	1.259V

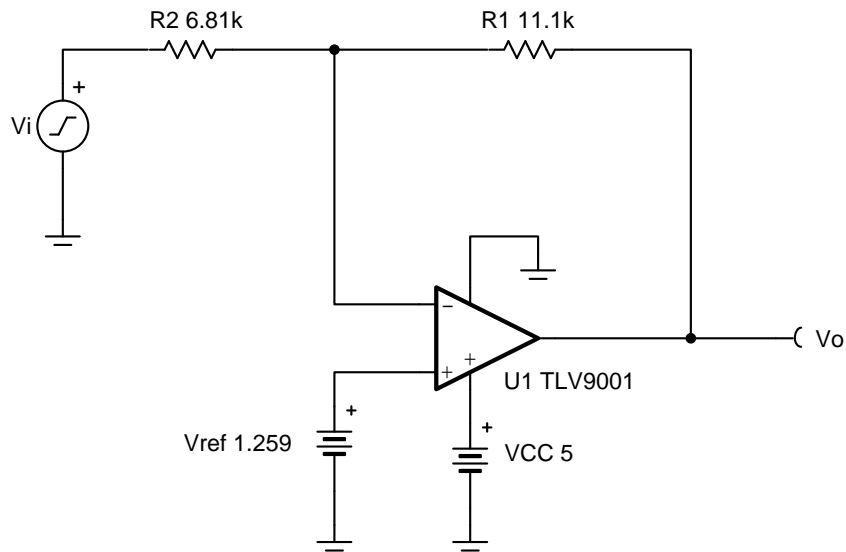


$$G_{input} = -\frac{R_1}{R_2}$$

$$R_1 = -G_{input} \times R_2 \rightarrow G_{input} \times R_2$$

$$R_1 = 1.633 \frac{V}{V} \times 6.81k\Omega = 11.123k\Omega \approx 11.1k\Omega$$

Design Steps

Input		Output		Supply		
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}	V_{ref}
-1V	2V	0.05V	4.95V	5V	0V	1.259V


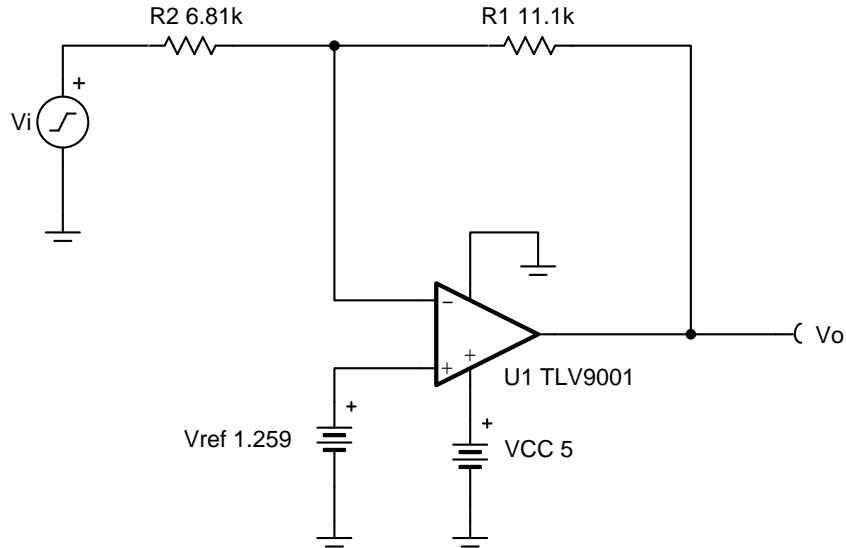


$$V_{ref} = \frac{V_{oMin} + V_{iMax} \times \left(\frac{R_1}{R_2}\right)}{1 + \frac{R_1}{R_2}}$$

$$V_{ref} = 1.259V$$



DC Results

Input		Output		Supply		
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}	V_{ref}
-1V	2V	0.05V	4.95V	5V	0V	1.259V

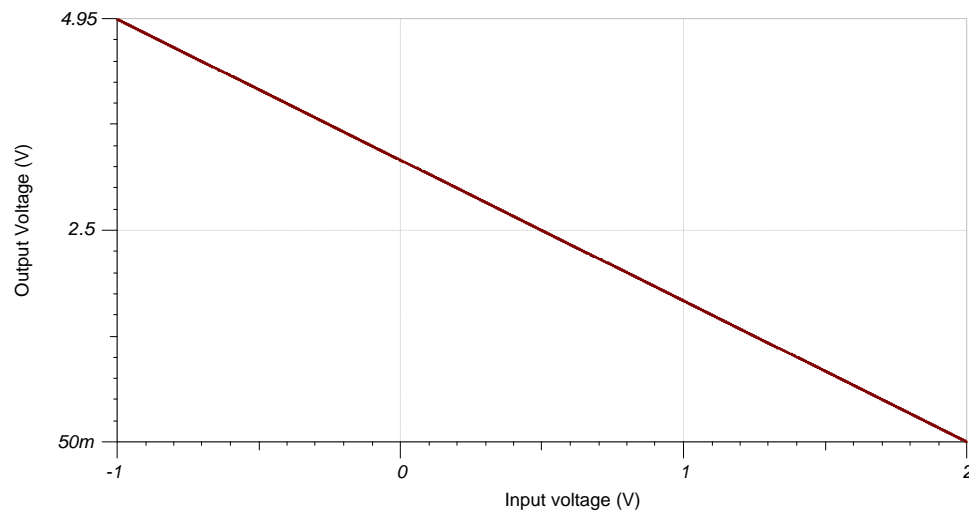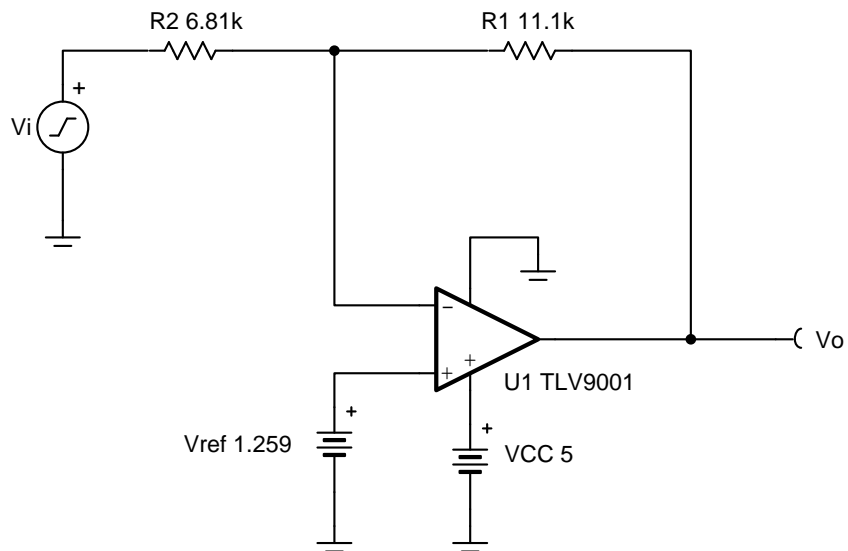


AC Results

Input		Output		Supply		
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}	V_{ref}
-1V	2V	0.05V	4.95V	5V	0V	1.259V

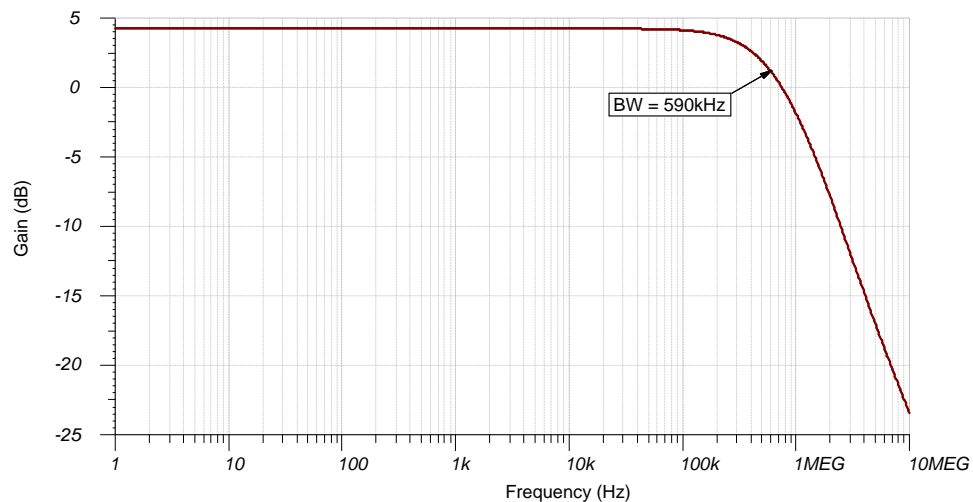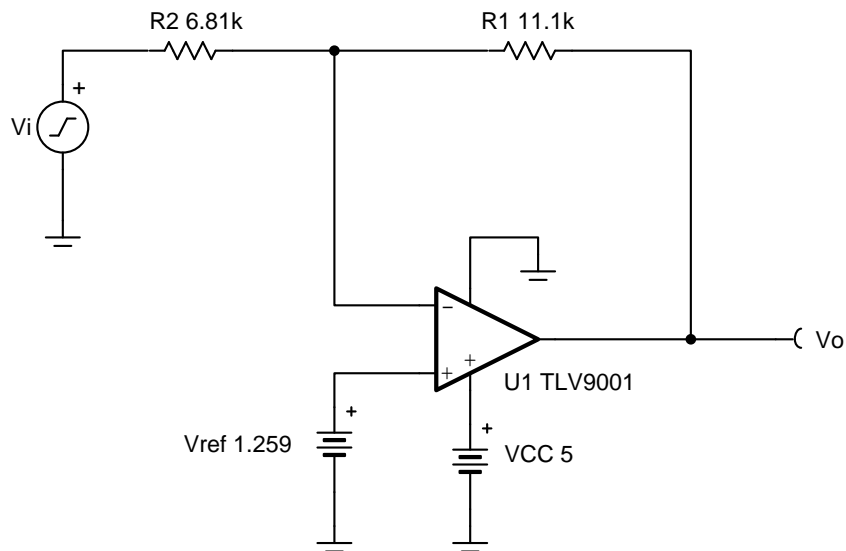

Design Notes

Input		Output		Supply		
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}	V_{ref}
-1V	2V	0.05V	4.95V	5V	0V	1.259V

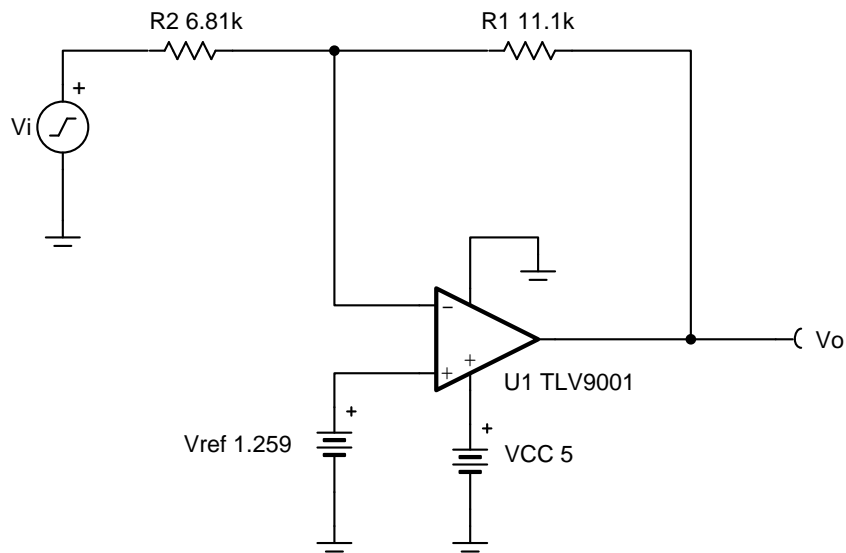

Design Notes:

1. V_{ref} can be created with a voltage divider.
2. Input impedance of the circuit is equal to $R2$. Therefore V_i should be low impedance.
3. The cutoff frequency of the circuit is dependent on the gain bandwidth product (GBP) of the amplifier. Additional filtering can be accomplished by adding a capacitor in parallel with $R1$.

Design Resources

EE Cookbook: Op Amp

www.ti.com/circuitcookbooks

Step-by-step circuit design of common op amp building block circuits.

TI Designs

www.TI.com/tidesigns

Ready-to-use reference designs with theory, calculations, simulations schematics, PCB files, bench test results

Analog Engineer's Pocket Reference

www.TI.com/analogrefguide

PDF, iTunes app and hardcopy available
PCB, analog, mixed signal design formulae
Conversions, tables, equations

TI Precision Labs

www.TI.com/precisionlabs

Quiz questions, problems, solutions
Labs and evaluation module (EVM) available

TINA-TI™ simulation software

www.TI.com/tool/tina-ti

Complete SPICE simulator DC, AC, transient, noise analysis
Schematic entry and post-processor for waveform math

DIYAMP-EVM

www.TI.com/DIYAMP-EVM

Evaluation module providing engineers with SC70, SOT23, SOIC packaging and 12 popular amplifier configurations

The Signal

www.TI.com/thesignal

PDF, iTunes app and hardcopy available
A compendium of blog posts on op amp design topics including offset voltage, input bias current, stability, noise and more

Analog Wire Blog

www.TI.com/analogwire

Technical blogs written by analog experts
Tips, tricks, and design techniques

TI E2E™ Community

www.TI.com/e2e

Support forums for all TI products

Op Amp Parametric Quick Search

www.TI.com/amplifiers

Search for precision, high-speed, general-purpose, ultra-low-power, audio and power op amps

Op Amp Parametric Cross-Reference

www.TI.com/opampcrossreference

Find similar TI op amps using competitive part numbers

www.ti.com/circuitcookbooks



© Copyright 2021 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)