




# Linear Regulator Fundamentals

## 2.5 PMOS


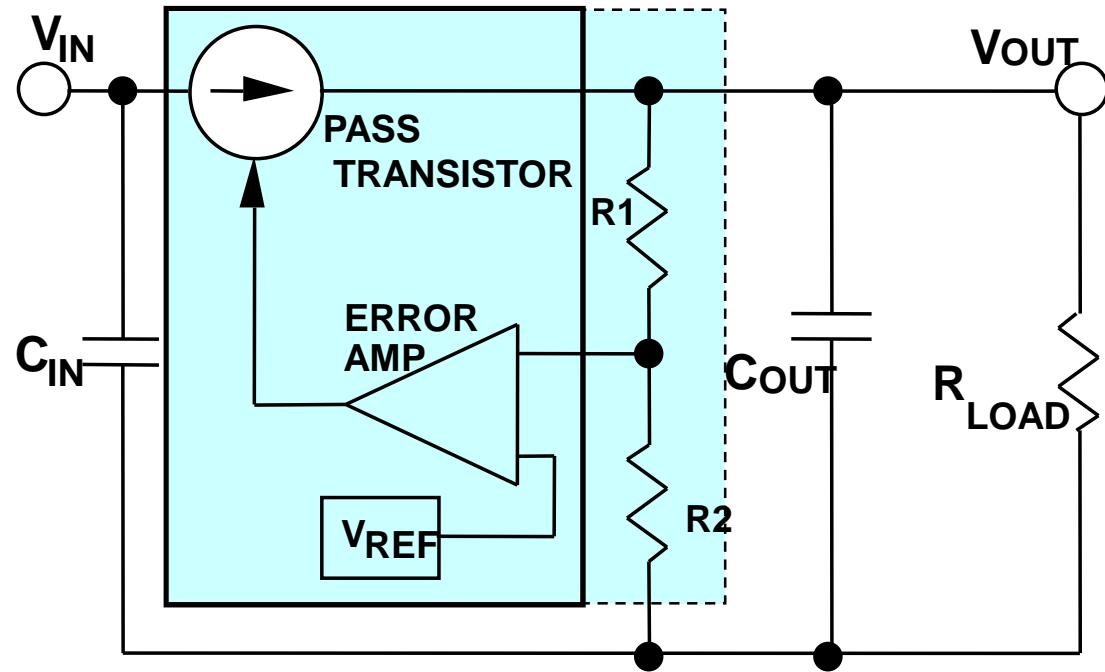
# Linear-Regulator Operation


- Voltage feedback samples the output R1 and R2 may be internal or external
- Feedback controls pass transistor's current to the load




 
# P-FET-LDO Linear Regulators


- Drop-out voltage set by by FET  $R_{DS-ON}$
- Very low quiescent (ground pin) current
- Ground-pin current independent of load



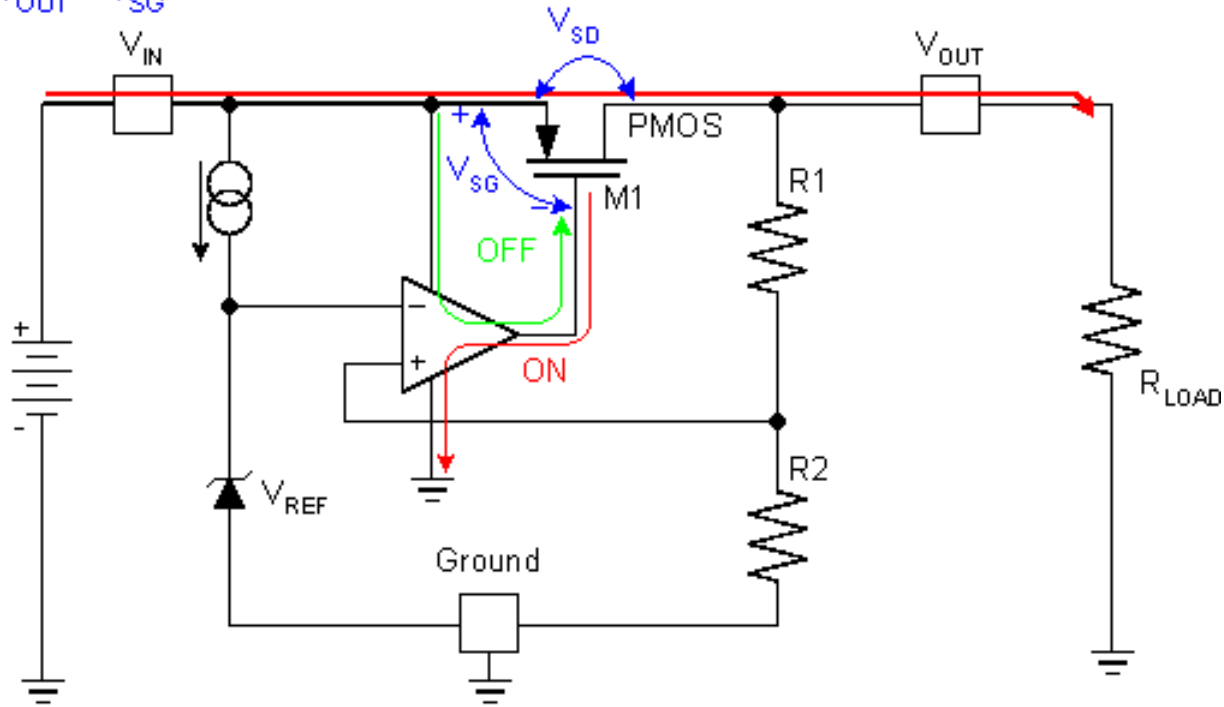
# Driving PMOS LDO Pass Element




$$V_{IN} > (V_{OUT} + (R_{SD(ON)} \times I_{SD}))$$
$$V_{OUT} > V_{SG}$$



# Gate Drive vs. Low Load Current

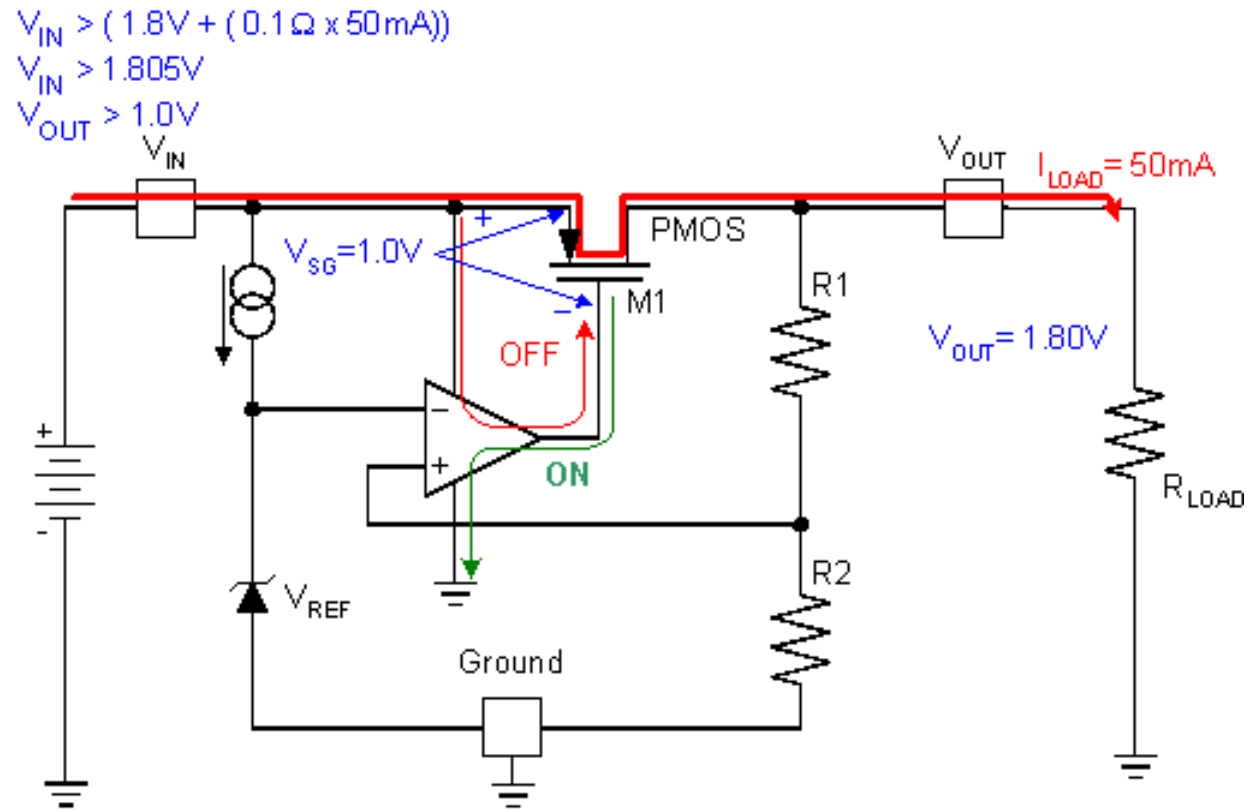

# Gate Drive vs. High Load Current

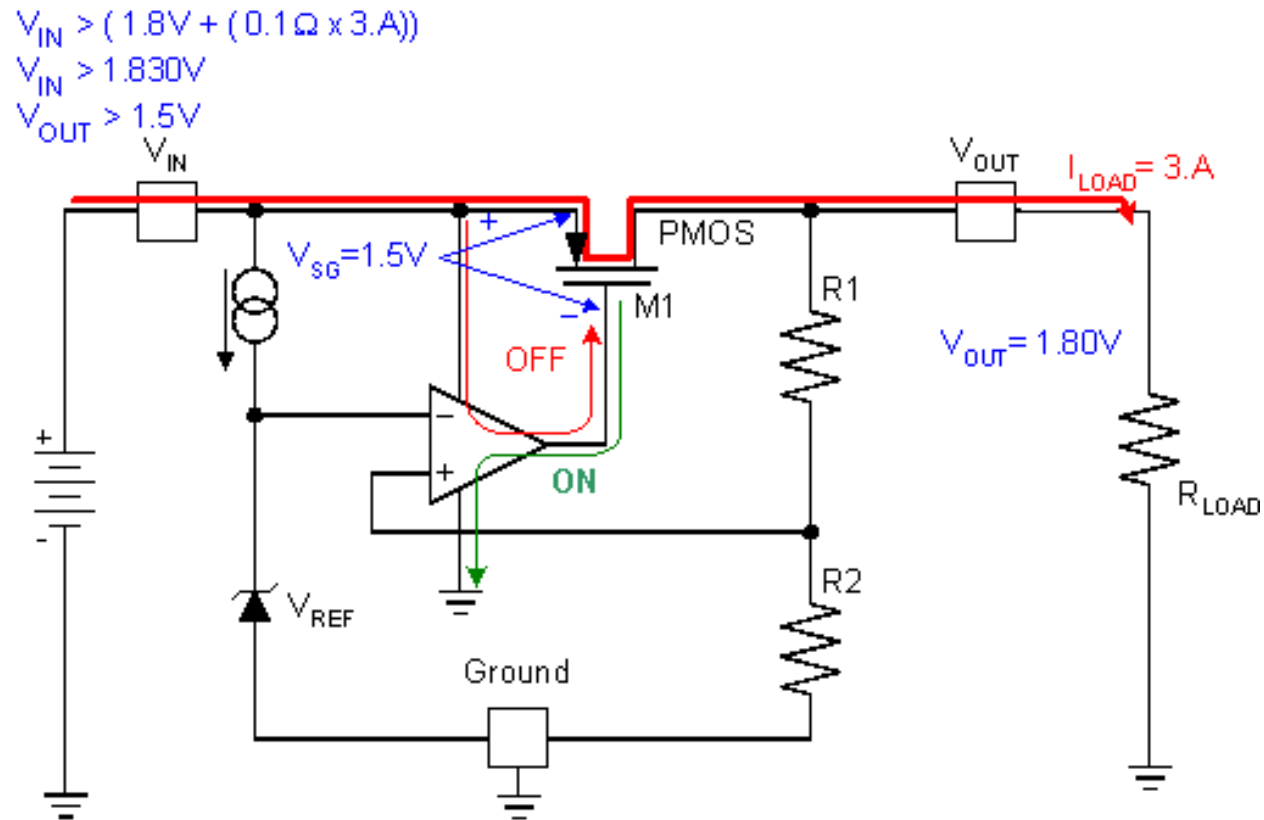

# Summary



- The PMOS LDO has the following Characteristics:
  - Requires that the input voltage be higher than the output voltage based on the load current and the On Resistance of the pass element:
    - $V_{IN} > R_{DS(on)} \times I_{OUT}$
  - Requires that the output voltage be higher than the  $V_{GS}$  requirement of the pass element
  - Requires careful selection of the output capacitor value and ESR ratings
  - To achieve similar  $R_{DS(on)}$  performance a PMOS transistor will require a larger die area than NMOS transistors
  - The larger die area will affect pricing, and might affect performance



**Thank you!**