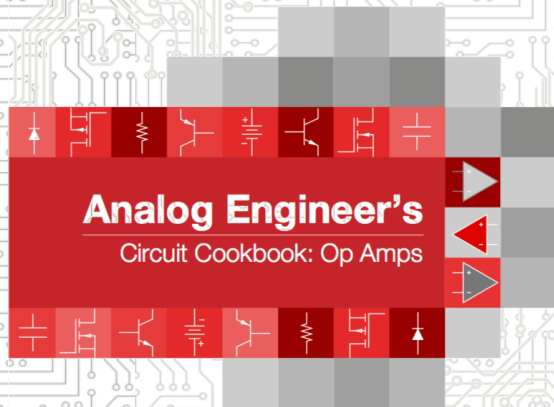


How to Design Low-noise and long-range PIR sensor conditioner circuit


General Purpose Amplifiers

www.ti.com/general-amps

www.ti.com/circuitcookbooks




Circuit Description

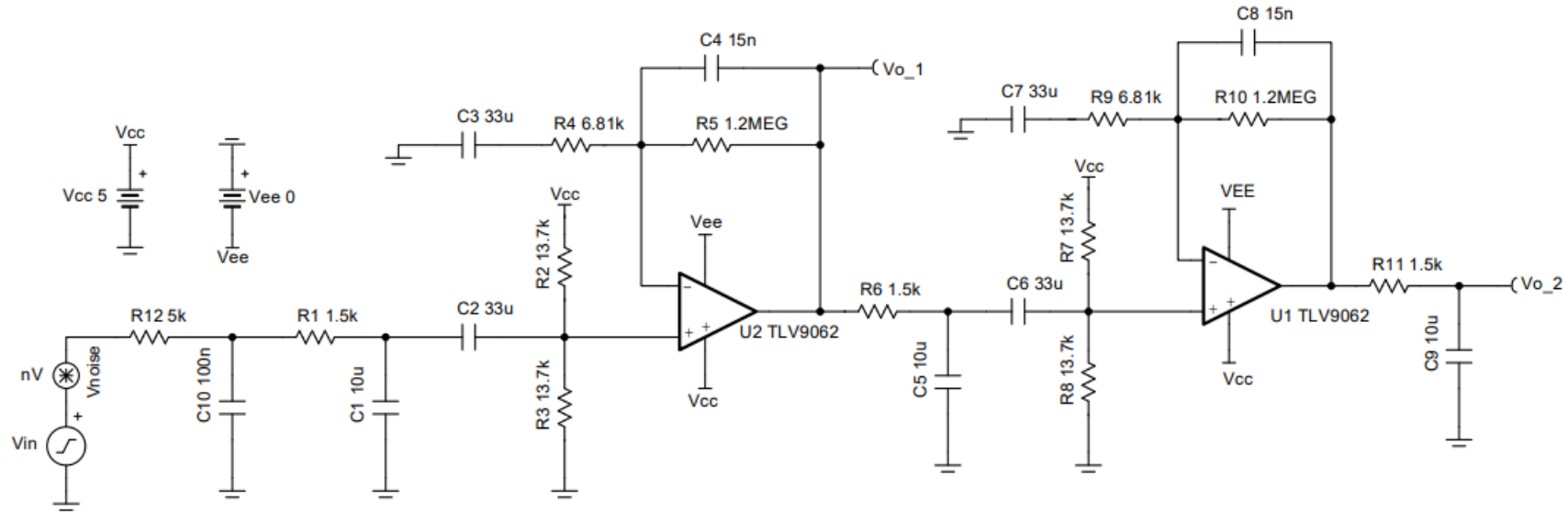

Design Steps

AC Gain	Filter Cutoff Frequency		Supply	
90 dB	f_L	f_H	V_{CC}	V_{EE}
	0.7 Hz	10 Hz	5V	0V

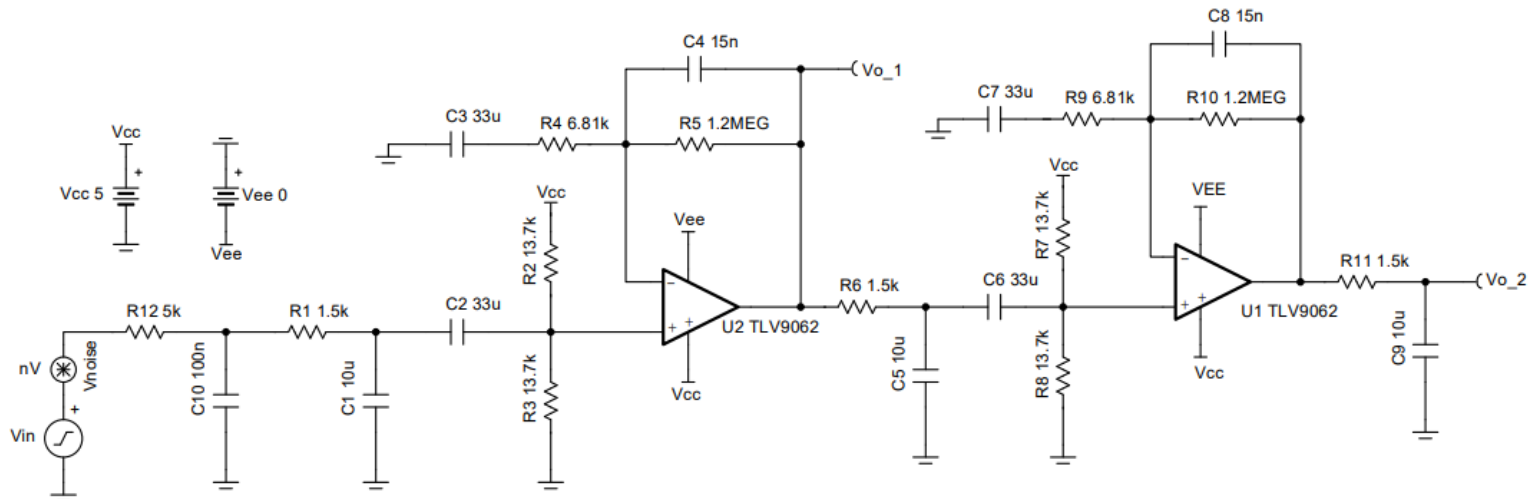


Design Steps

AC Gain	Filter Cutoff Frequency		Supply	
90 dB	f_L	f_H	V_{cc}	V_{ee}
	0.7 Hz	10 Hz	5V	0V

$$C1 = C5 = C9 = 10\mu F$$


$$R1 = R6 = R11 = \frac{1}{2 \times \pi \times f_L \times C1}$$
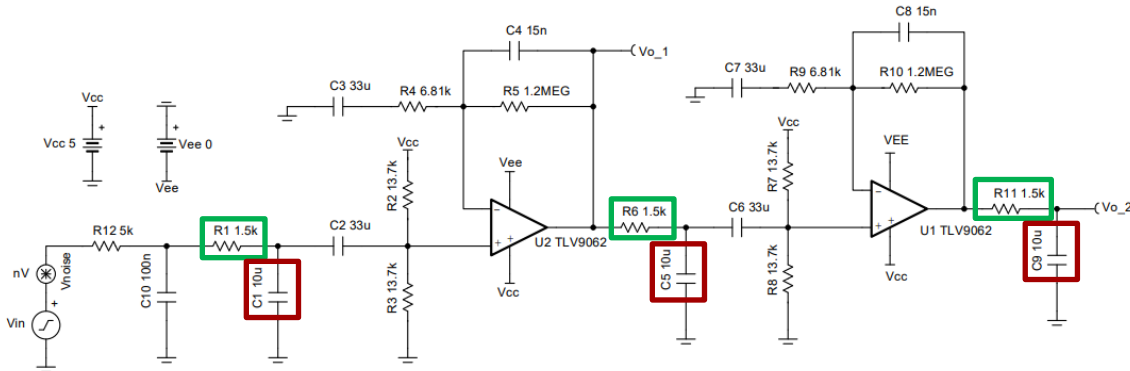
$$R1 = R6 = R11 = \frac{1}{2 \times \pi \times 0.7\text{Hz} \times 10\mu F} = 1.592\text{k}\Omega \approx 1.5\text{k}\Omega$$



Design Steps

AC Gain	Filter Cutoff Frequency		Supply	
90 dB	f_L	f_H	V_{cc}	V_{ee}
	0.7 Hz	10 Hz	5V	0V

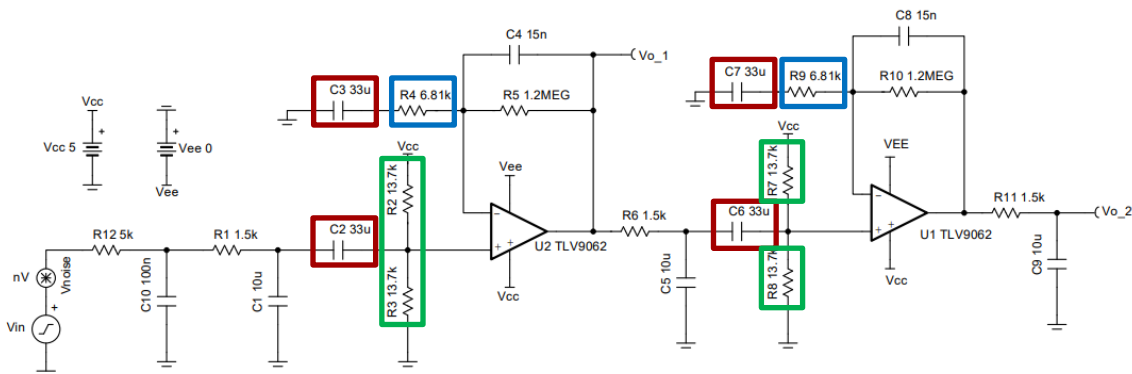

$$C2 = C3 = C6 = C7 = 33\mu F$$

$$R4 = R9 = \frac{1}{2 \times \pi \times f_H \times C2}$$

$$R4 = R9 = \frac{1}{2 \times \pi \times 10\text{Hz} \times 33\mu F} = 6.89\text{ k}\Omega \approx 6.81\text{ k}\Omega$$

$$R2 = R3 = R7 = R8 = 2 \times R4 = 13.62\text{ k}\Omega \approx 13.7\text{ k}\Omega$$

Design Steps


AC Gain	Filter Cutoff Frequency		Supply	
90 dB	f_L	f_H	V_{CC}	V_{EE}
	0.7 Hz	10 Hz	5V	0V

$$Gain = \frac{AC\ Gain}{2} = \frac{90dB}{2} = 45dB$$

$$Gain = 1 + \frac{R5}{R4}$$


$$R5 = (Gain - 1) \times R4$$
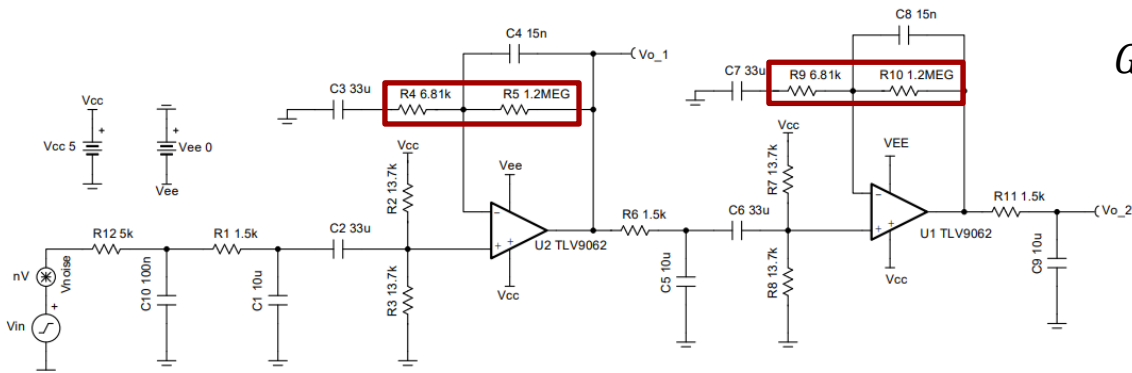
$$R5 = (177.828V/V - 1) \times 6.81k\Omega = 1.2M\Omega$$



Design Steps

AC Gain	Filter Cutoff Frequency		Supply	
90 dB	f_L	f_H	V_{CC}	V_{EE}
	0.7 Hz	10 Hz	5V	0V


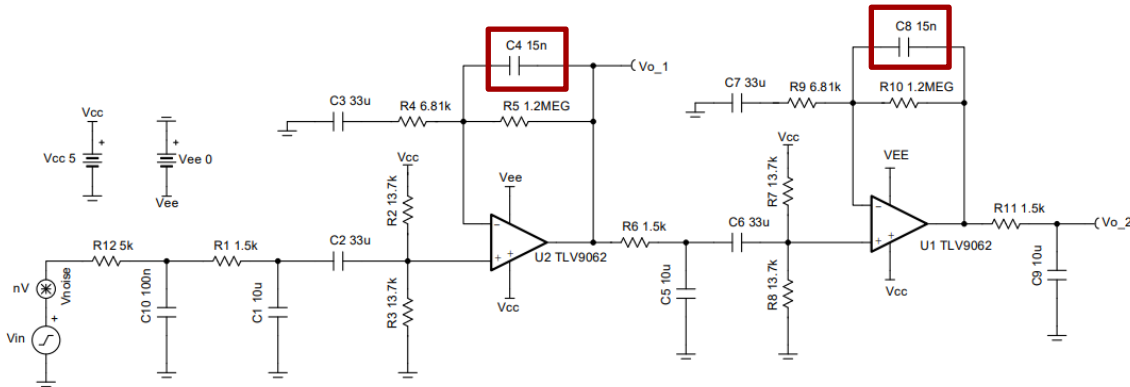


$$C4 = C8 = \frac{1}{2 \times \pi \times f_H \times R5}$$

$$C4 = C8 = \frac{1}{2 \times \pi \times 10\text{Hz} \times 1.2\text{M}\Omega} = 13.263\text{nF} \approx 15\text{nF}$$



AC Results

AC Gain	Filter Cutoff Frequency		Supply	
90 dB	f_L	f_H	V_{CC}	V_{EE}
	0.7 Hz	10 Hz	5V	0V

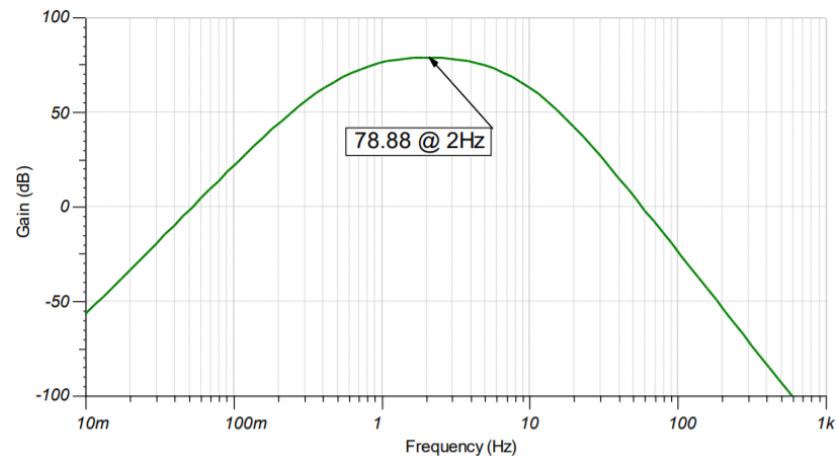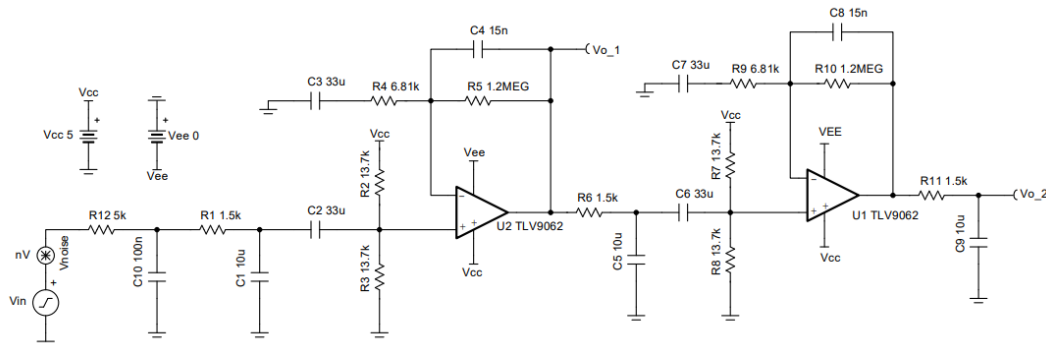

Noise Results

AC Gain	Filter Cutoff Frequency		Supply	
90 dB	f_L	f_H	V_{CC}	V_{EE}
	0.7 Hz	10 Hz	5V	0V

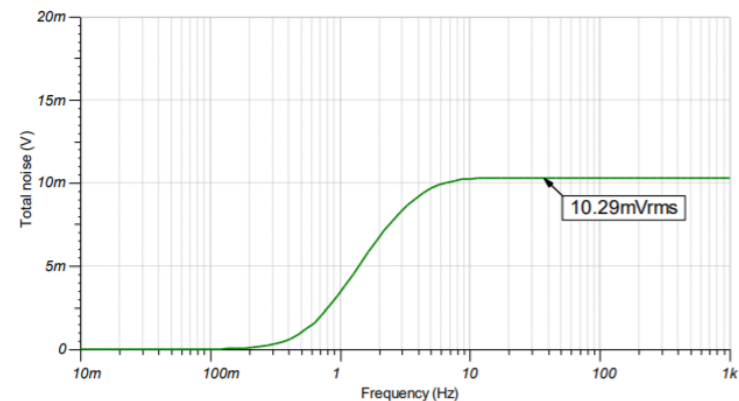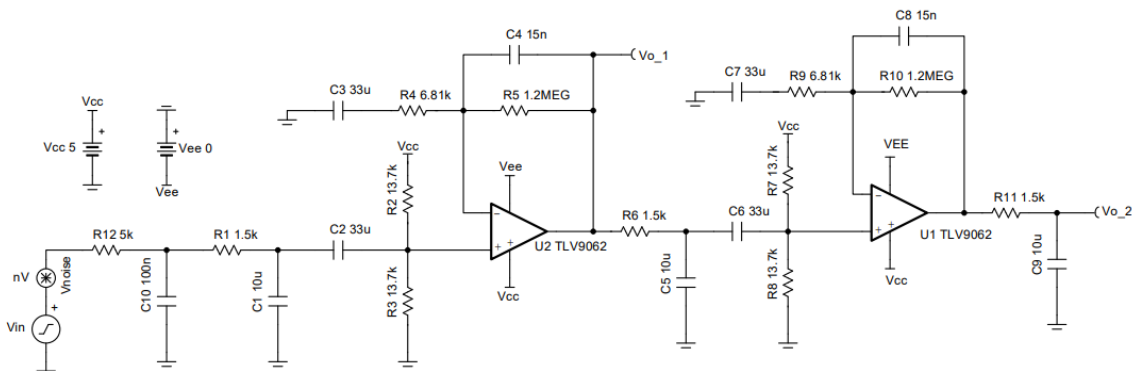


Design Notes

AC Gain	Filter Cutoff Frequency		Supply	
90 dB	f_L	f_H	V_{CC}	V_{EE}
	0.7 Hz	10 Hz	5V	0V

Design Notes:

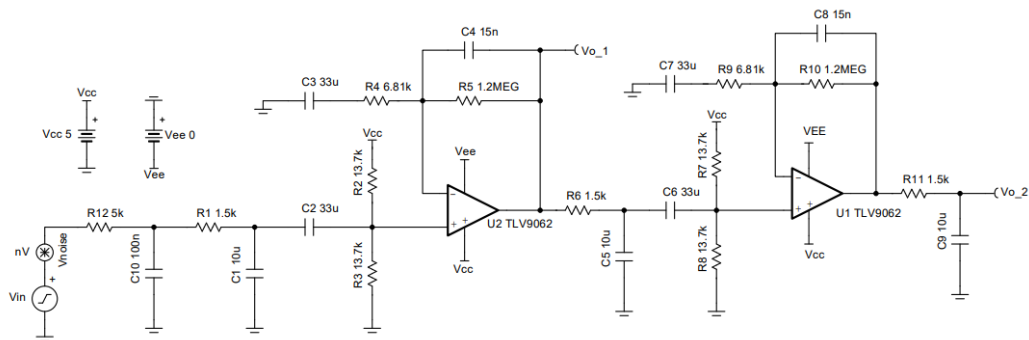1. For low-noise, long-range PIR sensor conditioner circuits be sure to use two or more amplifier stages to allow for sufficient loop gain.
2. Additional low-pass and high-pass filters can be added to further reduce noise.
3. RC filters on the output of the amplifiers are required to reduce the contribution of the intrinsic noise of the amplifier.



Design Resources

EE Cookbook: Op Amp

www.ti.com/circuitcookbooks

Step-by-step circuit design of common op amp building block circuits.

TI Designs

www.TI.com/tidesigns

Ready-to-use reference designs with theory, calculations, simulations schematics, PCB files, bench test results

Analog Engineer's Pocket Reference

www.TI.com/analogrefguide

PDF, iTunes app and hardcopy available
PCB, analog, mixed signal design formulae
Conversions, tables, equations

TI Precision Labs

www.TI.com/precisionlabs

Quiz questions, problems, solutions
Labs and evaluation module (EVM) available

TINA-TI™ simulation software

www.TI.com/tool/tina-ti

Complete SPICE simulator DC, AC, transient, noise analysis
Schematic entry and post-processor for waveform math

DIYAMP-EVM

www.TI.com/DIYAMP-EVM

Evaluation module providing engineers with SC70, SOT23, SOIC packaging and 12 popular amplifier configurations

The Signal

www.TI.com/signalbook

PDF, iTunes app and hardcopy available
A compendium of blog posts on op amp design topics including offset voltage, input bias current, stability, noise and more

Analog Wire Blog

www.TI.com/analogwire

Technical blogs written by analog experts
Tips, tricks, and design techniques

TI E2E™ Community

www.TI.com/e2e

Support forums for all TI products

Op Amp Parametric Quick Search

www.TI.com/amplifiers

Search for precision, high-speed, general-purpose, ultra-low-power, audio and power op amps

Op Amp Parametric Cross-Reference

www.TI.com/opampcrossreference

Find similar TI op amps using competitive part numbers

www.ti.com/circuitcookbooks



© Copyright 2019 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)