

LDO or Switcher? ...That is the Question

Choosing between an LDO or DC/DC Converter

Frank De Stasi

Texas Instruments

Agenda

- **LDO Basics**
 - Operation
 - Pros & cons
- **Switcher Basics**
 - Nano module overview
 - Operation
 - Pros & cons
- **Example Comparisons**


LDO operation

- Linear Regulator
 - Most linear regulators are termed “LDO” (Low Drop Out)
 - Drop-out = Lowest ($V_{IN} - V_{OUT}$) while still in regulation
 - Allows regulation of rails that are close together with good efficiency
 - Allows better utilization of discharging battery voltage
 - Usually requires an input and output capacitor
 - Some only require an input capacitor
 - Can only produce an output voltage that is less than the input.

LDO operation


- **Linear Closed Loop System**

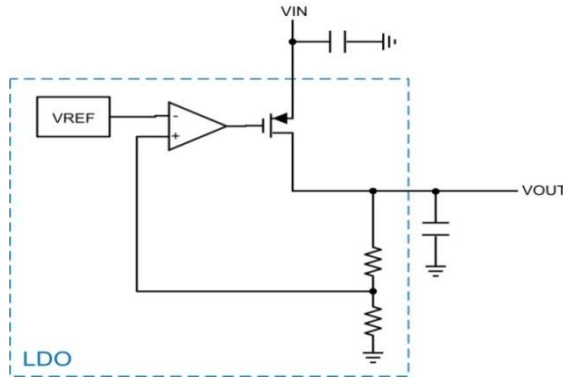- V_{OUT} is sampled by feedback resistors and compared to V_{REF} with the op-amp
 - Op-amp amplifies changes in V_{OUT} and controls the MOSFET to regulate the output
- The MOSFET is used as a linear resistor between V_{IN} and V_{OUT}
 - All of the load current flows through the MOSFET
 - Large power loss in regulator when V_{IN} is much greater than V_{OUT} ; and/or the load current is large




LDO operation

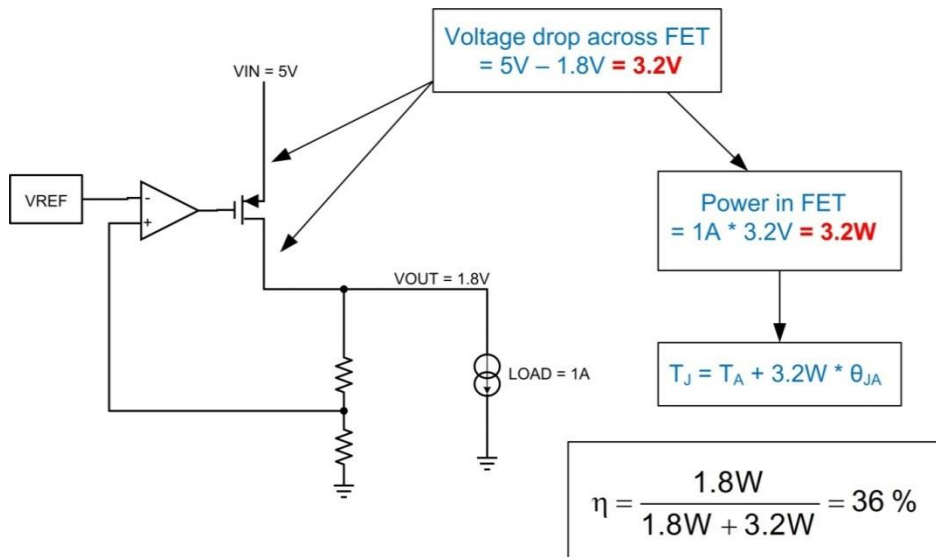- Large power dissipation at high input-to-output voltage differential
 - More loss than output power is this example!
 - No advantage of “low drop-out”
 - Higher power loss means higher PCB temperature



LDO operation

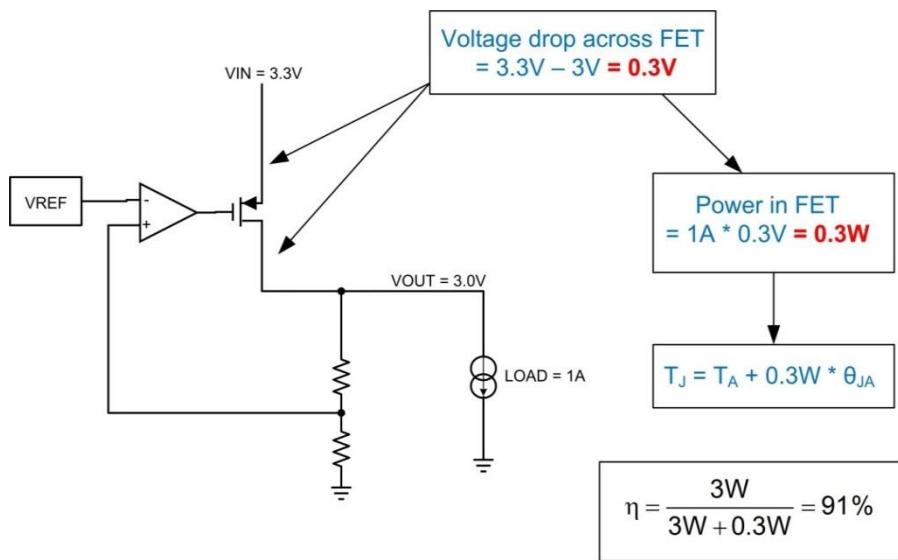- Real advantage when input & output voltages are close together
 - Use this fact when you can arrange two rails that are close in voltage



LDO pros & cons

- **Pros**

- Small size
 - Small packages available
- Low noise
 - No EMI
- Simple to use
 - Easy PCB layout
- Can be inexpensive




- **Cons**

- Low efficiency
 - When $V_{IN} \gg V_{OUT}$
- Higher board temperature
- Can only reduce input

LMZ20501 SIMPLE SWITCHER® Nano Module

Features



- Integrated Inductor
- Miniature 3.5 mm x 3.5 mm x 1.75 mm Package
- 1 A Maximum Load Current
- Input Voltage Range of 2.7 V to 5.5 V
- Adjustable Output Voltage Range of 0.8 V to 3.6 V
- $\pm 1\%$ Feedback Tolerance Over Temperature
- 2.4 μA (max) Quiescent Current In Shutdown
- 3 MHz Fixed PWM Switching Frequency
- -40°C to 125°C Junction Temperature Range
- Power Good Flag Function
- Pin-Selectable Switching Modes
- Internal Compensation and Soft-Start
- Current Limit, Thermal Shutdown, and UVLO Protection

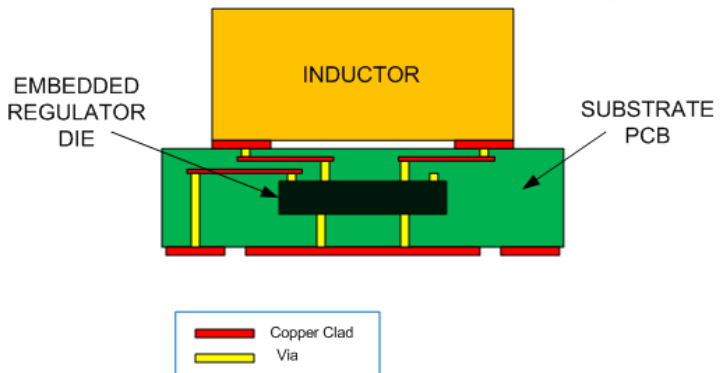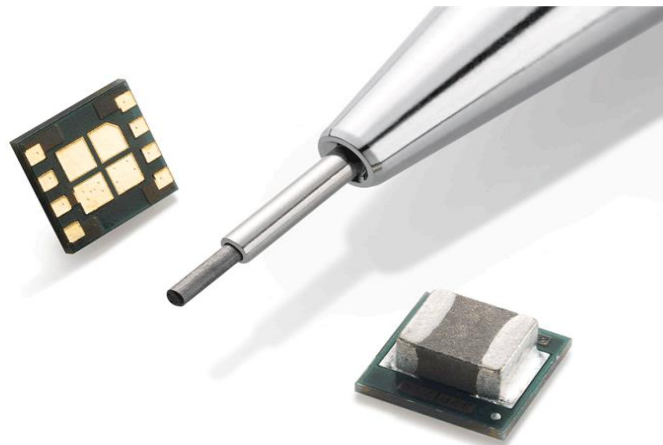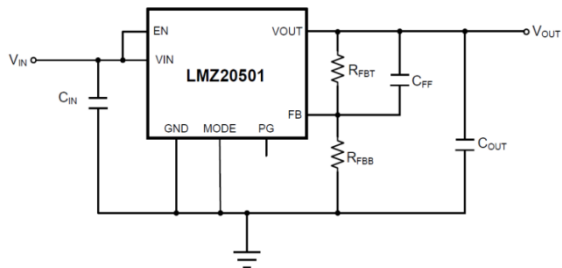

LMZ21700 SIMPLE SWITCHER[®] Nano Module

Features


- Integrated Inductor
- Miniature 3.5 mm x 3.5 mm x 1.75 mm Package
- 35 mm² Solution Size (Single Sided)
- -40 °C to 125 °C Junction Temperature Range
- Adjustable Output Voltage
- Integrated Compensation
- Adjustable Soft Start Function
- Starts into Pre-Biased Loads
- Power Good and Enable Pins
- Seamless Transition to Power-Save Mode
- Up to 650 mA Output Current
- Input Voltage Range 3 V to 17 V
- Output Voltage Range 0.9 V to 6 V
- Efficiency up to 95 %
- 1.5 μ A Shutdown Current
- 17 μ A Quiescent Current

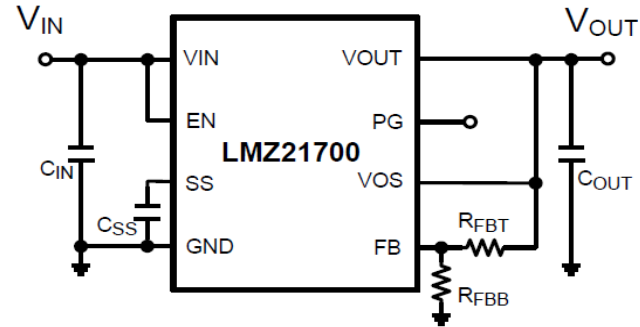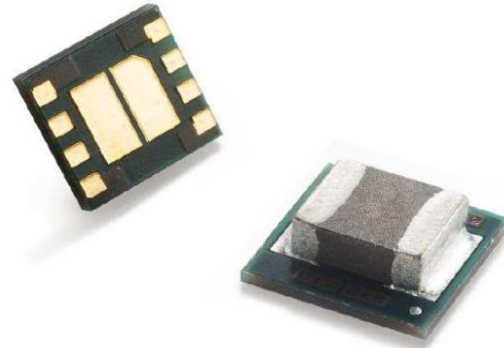

Step-down converter module

- **Inductive Switching Regulator**

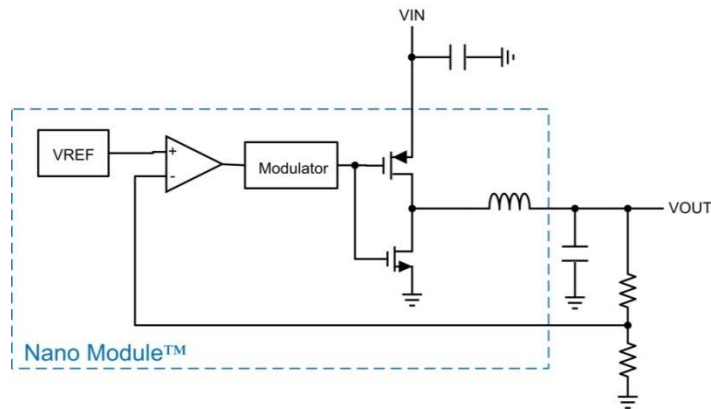- Provides high efficiency over large range of input voltage and load current
 - Special modes provide good efficiency at very light load currents
 - Inductor allows storing energy, which improves efficiency
- High switching frequency
 - Allows smaller input and output capacitors
- The Inductor is integrated into the package
 - Saves PCB space
 - Simplifies component selection




Step-down converter module

- **Inductive Switching Regulator**

- V_{OUT} is sampled by feedback resistors and compared to V_{REF} with the op-amp
 - Op-amp amplifies changes in V_{OUT} and controls the modulator
 - Modulator controls the MOSFET switches.
- Uses MOSFETS as switches to control output power
 - Very small voltage drop across switches
 - Some additional small loss due to charging MOSFET capacitance
- High efficiency over wide input voltage ranges
 - MOSFET voltage drop does not depend on input and output voltage; like an LDO

Step-down converter operation

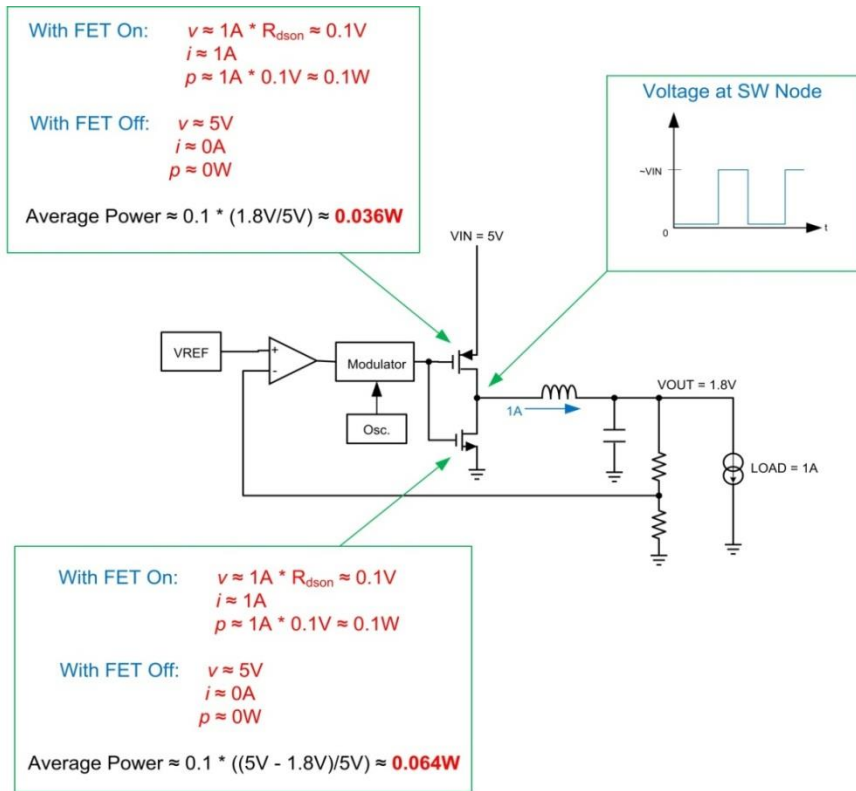

Step-down converter operation

- Compare total losses for LDO & switcher: $V_{in} = 5V$, $V_{out} = 1.8V$, $I_{out} = 1A$

- For example DC/DC converter:

– $\approx 0.1W$

$$\eta = \frac{1.8W}{1.8W + 0.1W} = 95 \%$$

- For example LDO:

– $\approx 3.2W$

$$\eta = \frac{1.8W}{1.8W + 3.2W} = 36 \%$$

Switcher pros & cons

- **Pros**

- High efficiency
- Easier heat dissipation
- Lower PCB temperature
- Flexible conversion
 - Can be used as an inverter

- **Cons**

- More complex layout
 - PCB layout is critical
- Switching noise
 - EMI
- Can be more expensive

Example 1


- $V_{in} = 3.3V$ to $5.5V$
- $V_{out} = 1.8V$
- $I_{out} = 0.5A$
- Ambient Temperature = $25^{\circ}C$

- Key Issues in Application
 - Power dissipation
 - Size

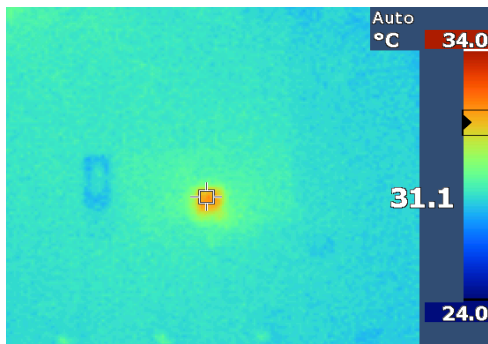Example 1

LMZ21700 Nano Module


- PCB area $\approx 1700\text{mm}^2$
- Solution size $\approx 100\text{mm}^2$
- Max temperature $\sim 32^\circ\text{C}$



Thermal Camera Image

LP38693 LDO

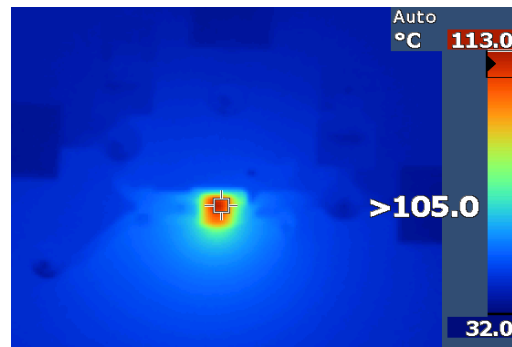- PCB area $\approx 2600\text{mm}^2$
- Solution size $\approx 100\text{mm}^2$
- Max temperature $> 105^\circ\text{C}$



Thermal Camera Image

Conclusion

- LMZ21700 is much cooler; can achieve design objectives
- LP38693 is much hotter; even with more PCB area than LMZ21700
- **LMZ21700 is Winner**

Example 2


- $V_{in} = 5.5V$
- $V_{out} = 1.8V$
- $I_{out} = 1A$

- Key Issues in Application
 - Noise on output
 - EMI

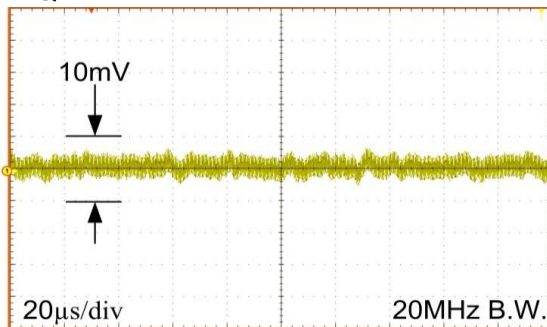Example 2

LMZ20501 Nano Module


- Meets input and output specs
- EN and PGOOD
- +/- 1.5% output accuracy
- $I_Q \approx 80\mu\text{A}$ at no load



Output Voltage Ripple

TPS72518 LDO

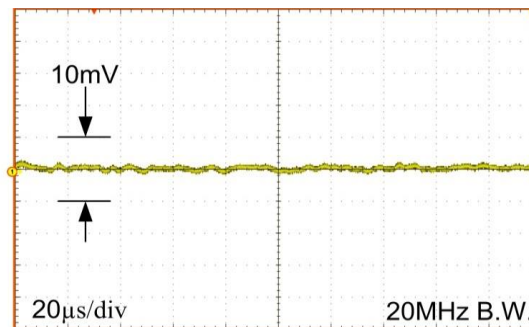- Meets input and output specs
- EN and PGOOD
- +/- 2% output accuracy
- $I_Q \approx 80\mu\text{A}$ at no load



Output Voltage Ripple

Conclusion

- Both solutions achieve the nominal application specifications
- Both have nearly the same features and key specifications
- The TPS72518 is specified for 150 μ V noise
 - No EMI issues
- **TPS72518 is Winner**

Example 3

- $V_{in} = 5V$
- $V_{out} = 3.3V$
- $I_{out} = 0.5A$

- Key Issues in Application
 - Drop-out voltage for V_{out} -0.1V at 0.5A

Example 3

LMZ21700 Nano Module

- Meets input and output specs
- Rated maximum load = 650mA
- EN and PGOOD
- Drop-out voltage = **107mV @ 500mA**

TPS7133 LDO

- Meets input and output specs
- Rated maximum load = 500mA
- EN and PGOOD
- Drop-out voltage = **250mV @ 500mA**

Conclusion

- Both solutions achieve the nominal application specifications
- Both have nearly the same features.
- The LMZ21700 drop-out is less than half that of the TPS7133
- **LMZ21700 is Winner**

Example 4

- $V_{in} = 3.3V$
- $V_{out} = 1.8V$
- $I_{out} = 1A$

- Key Issues in Application
 - Minimum input voltage

Example 4

LMZ20501 Nano Module

- Meets nominal input and output specifications
- EN and PGOOD
- +/- 1.5% output accuracy
- Minimum rated input voltage = **2.7V**

TPS72518 LDO

- Meets nominal input and output specifications
- EN and PGOOD
- +/- 2% output accuracy
- Minimum input voltage = **2.01V**

Conclusion

- Both solutions achieve the nominal application specifications and have the same features
- The TPS72518 has a drop-out of 210mV at 1A
→ $1.8\text{V} + 0.21\text{V} = \mathbf{2.01\text{V}}$
- The LMZ20501 has a minimum input voltage of 2.7V regardless of other conditions.

- **TPS72518 is Winner**

Example 5


- $V_{in} = 3.3V$
- $V_{out} = 1.8V$
- $I_{out} = 1A$

- Key Issues in Application
 - Solution size

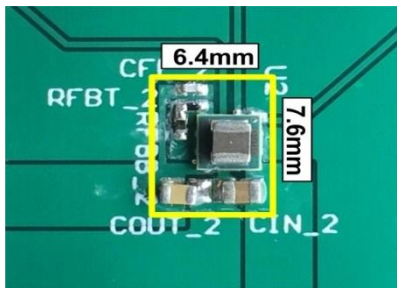Example 5


LMZ20501 Nano Module

- Meets nominal input and output specifications
- EN and PGOOD
- +/- 1.5% output accuracy
- Solution size = 49 mm²



TPS7A37 LDO

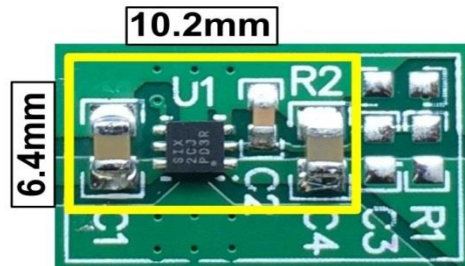- Meets nominal input and output specifications
- EN
- +/- 1% output accuracy
- Solution size = 65 mm²



Conclusion

- Both solutions achieve the nominal application specifications and have similar features
- Solution size for LMZ20501:
 - 6.4 mm x 7.6 mm = **49 mm²**
- Solution size for TPS7A37:
 - 6.4 mm x 10.2 mm = **65 mm²**
- 25% Less board space with LMZ20501
- **LMZ20501 is Winner**

Summary

- **Use an LDO when your application requires:**
 - Low output voltage noise
 - No EMI
 - Operation at very low input voltages
 - The input voltage is close to the output voltage
- **Use a Nano-Module™ DC/DC converter when your application requires:**
 - Very high efficiency
 - Low PCB temperature
 - Small solution size
 - Large variations in input voltage

**For more information, visit
www.simpleswitcher.com**

