

Linear OPAMP Characterization: Output Swing


Presented by: Joseph Serritella

Prepared by: Joseph Serritella, Daryl Hiser, Ray Ochotorena

OPAMP verification

OPAMP electrical characterization:

- Characterizing the electrical behavior of an integrated circuit is critical during application troubleshooting
 - Non-conformances can be identified by comprehending device-level characteristics in addition to system performance
- OPAMP electrical characterization series will review the following topics:
 - Voltage offset (V_{OS})
 - V_{CM} / Common Mode Rejection Ratio (CMRR)
 - Power Supply Rejection ratio (PSRR)
 - **Output swing**
 - Output swing
 - Quiescent current
 - Open loop gain (A_{OL})

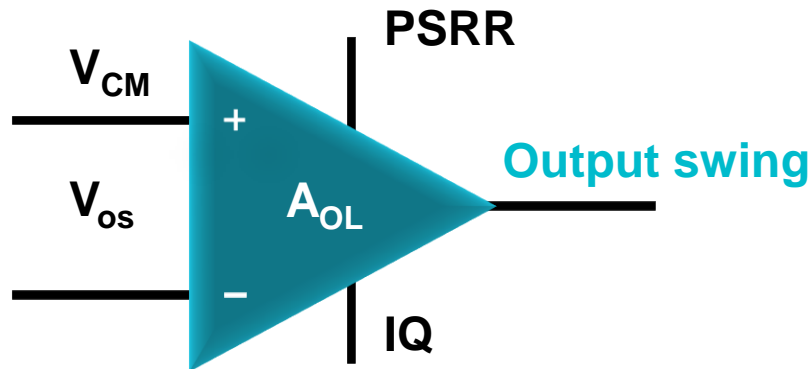

Prerequisites

Electrical characterization: Output Swing / Slam

- Output swing and slam measurement methods are reviewed
- Following prerequisites are recommended prior to proceeding through the handbook

Prerequisites:

TI-Precision Labs (TIPL) courses:

Op Amps: Input and Output Limitations
TI.com/output-limitations

Pocket reference:

Training: Analog Engineer's Pocket Reference
ti.com/analogrefguide

Application handbook:

A-B-A: Board Level Troubleshooting
ti.com/board-level-troubleshooting

Simulation tools:

Simulations are presented within the handbook. It is recommended to install TINA-TI
TINA-TI can be downloaded for free on ti.com: TI.com/tina-ti

OPAMP test loops

Overview:

- Analyzing datasheet parameters may appear a daunting task!
- Multiple datasheet parameters can be derived using various circuits.


False Summing Junction (FSJ):

- Commonly used circuit to measure offset voltage of an amplifier
 - **Benefits:**
 - Simplistic
 - Stable
 - Small
 - **Disadvantages:**
 - Feedback resistor load in parallel with other added loads
 - Loop drive function of DUT V_{OS}
- Majority of DC parameters determined with 4 resistors!

Measuring opamp specifications:

- **VOS:** differential input voltage required to force output to mid-supply
- **Output swing:** can also be measured by using VOC to force the output voltage near the positive or negative supply
- **Output control voltage (VOC):** Calibrate the out voltage to zero volts
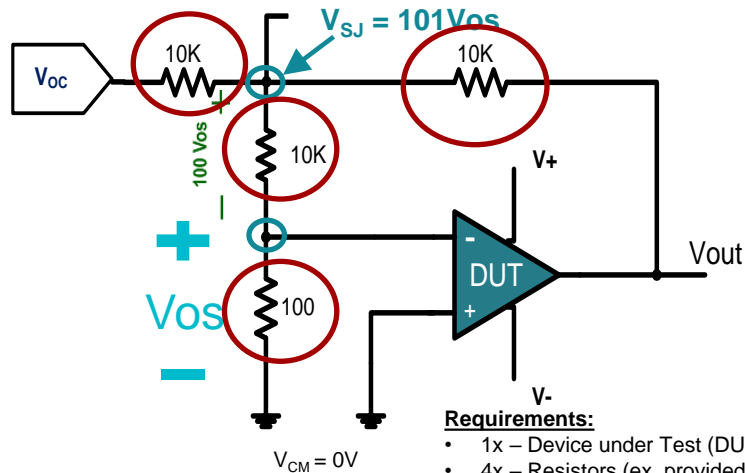
$$V_{OC} = -(V_{OUT} + V_{OS}(302)) + 2V_{CM}$$



Requirements:

- 1x – Device under Test (DUT)
- 4x – Resistors (ex. provided)
 - Resistor values can be varied depending on device

Example:

- $V_{+} = +10V$
- $V_{-} = -10V$
- $V_{OUT} = 0V$
- $V_{OC} = 0V$ (ideal opamp)


Results:

- $V_{SJ} = 1.01mV$
- $1.01mV = (101)V_{OS} = V_{SJ}$
 $10\mu V = V_{OS}$

Output swing - OPA192

Measurement preparation:

- Output swing and output slam are **not the same** as offset voltage (VOS)!
 - Offset voltage is defined when $V_{OUT} = V_{CM} = \text{Mid-supply}$
- **Output swing:** How close the output voltage of the opamp can reach the positive or negative supply voltage
 - Therefore $V_{OUT} \neq \text{Mid-supply}$, thus VOS is not defined
 - V_{OL} (output low) and V_{OH} (output high) denote a similar spec
- Review data sheet test conditions prior to evaluating **output swing**
 - Confirm supply voltage, input common mode voltage and output load conditions

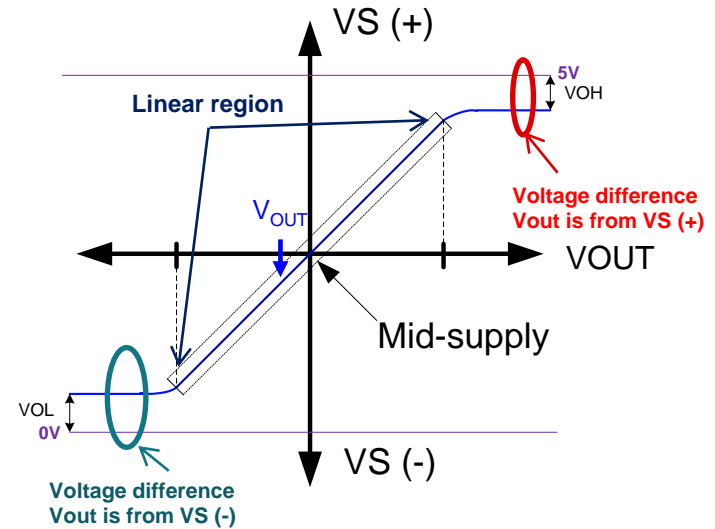

6.7 Electrical Characteristics: $V_S = \pm 4 \text{ V}$ to $\pm 18 \text{ V}$ ($V_S = +8 \text{ V}$ to $+36 \text{ V}$)


At $T_A = +25^\circ\text{C}$, $V_{CM} = V_{OUT} = V_S / 2$, and $R_{LOAD} = 10 \text{ k}\Omega$ connected to $V_S / 2$, unless otherwise noted.

PARAMETER	TEST CONDITIONS		MIN	TYP	MAX	UNIT
V_O Voltage output swing from rail	Positive rail	No load		5	15	mV
		$R_{LOAD} = 10 \text{ k}\Omega$		95	110	
		$R_{LOAD} = 2 \text{ k}\Omega$		430	500	
	Negative rail	No load		5	15	
		$R_{LOAD} = 10 \text{ k}\Omega$		95	110	
		$R_{LOAD} = 2 \text{ k}\Omega$		430	500	

*<http://www.ti.com/lit/ds/symlink/opa192.pdf>

Output swing

Bench setup and measurements:

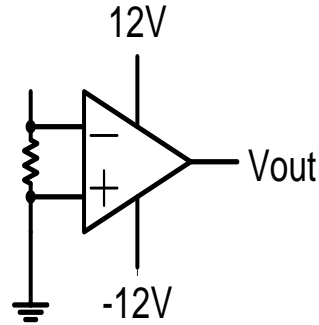

Output swing positive rail:

- **DUT:** OPA192IDGK
- $V_+ = +12V$
- $V_- = -12V$
- $V_{force} = 12V$
- $R_{load} = \text{no load}$
- Measure V_{OUT}

Use the offset correction factor (VOC) to Vout