

# Inverter/PFC Converter Topology - Overview

**Industrial Systems, SEM**


**Texas Instruments**

**Harald Parzhuber**

TI Information – Selective Disclosure


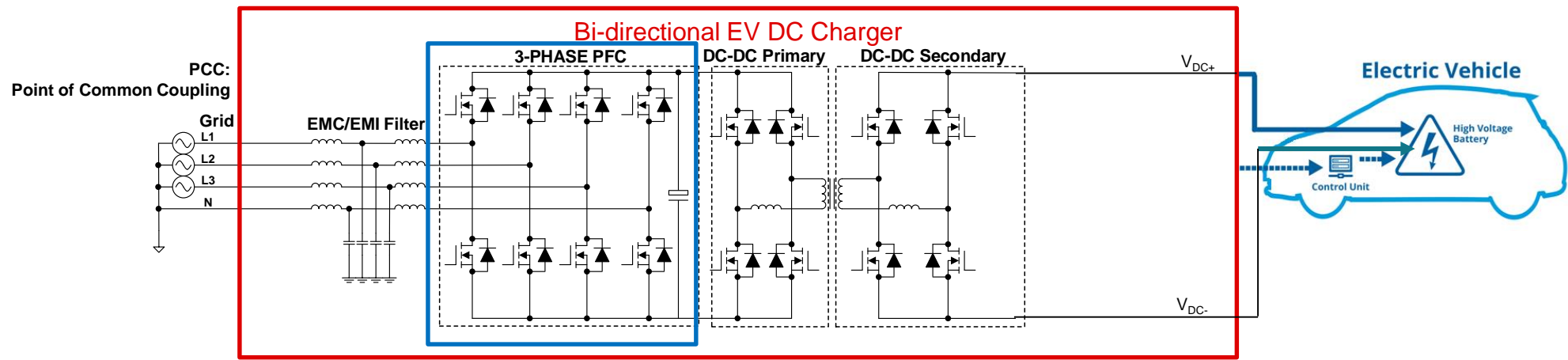
# Power Conversion Building Blocks of a DC-Charger




Inverter/PFC will be covered in this video


# Topologies Overview on Inverter/PFC Power Stage

Topology	2L two level converter	T-Type 3L three level T-Type	ANPC 3L active neutral point converter	NPC 3L neutral point converter	FC3L Flying Capacitor 3L
----------	---------------------------	---------------------------------	--	--------------------------------------	-----------------------------



Inverter Operation  
from DC to AC

 

PFC Operation  
from AC to DC

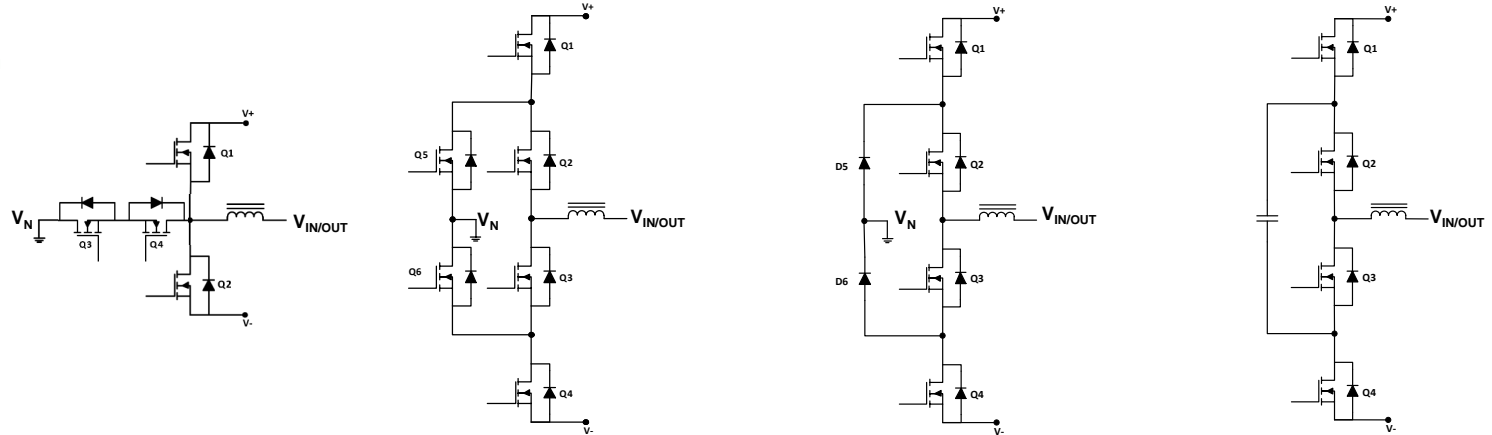

# T-Type 3L – basic operation principle

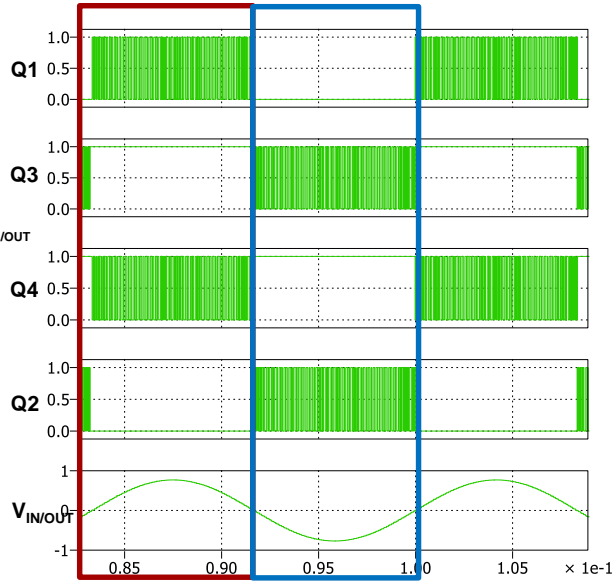 


For positive Sine-wave ( $V_N \leq V_{IN/OUT} \leq V_+$ ) :

- Q1 and Q4 in red circle are switching  $f_{PWM}$ . Q3 is permanently in ON-state
- Dead time between Q1 and Q4 needs to be accounted for

For negative Sine-wave ( $V_- \leq V_{IN/OUT} \leq V_N$ ) :

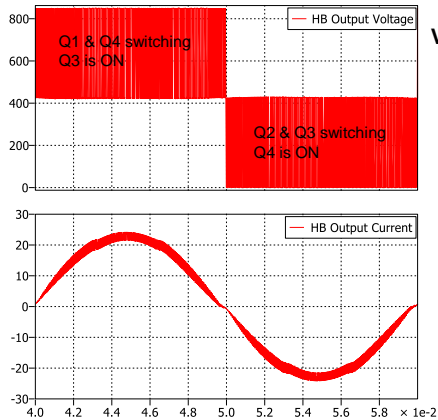- Q2 and Q3 in blue circle are switching  $f_{PWM}$ . Q4 is permanently in ON-state
- Dead time between Q2 and Q3 needs to be accounted for







Output Ripple frequency  $f_{RIPPLE}$  equal to  $f_{PWM}$

- $f_{RIPPLE}$  defines size of filter components (magnetics and capacitors) for a given frequency

Q1 & Q2 need be  $V_{DC}$  – rated (i.e. for VDC 800V – 1200V rated)

Q3 & Q4 can be  $\frac{1}{2} V_{DC}$  – rated (i.e. for VDC 800V – 600V rated)

# ANPC 3L – basic operation principle

   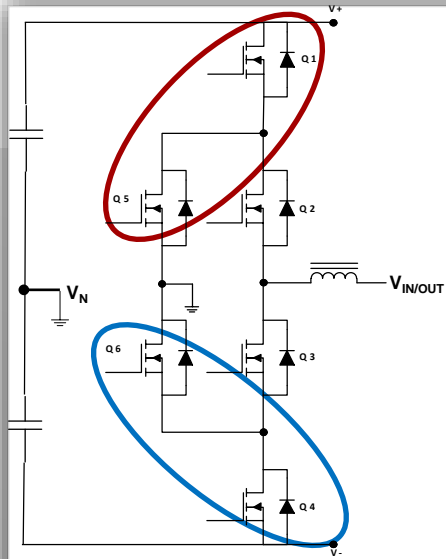

TI Information – Selective Disclosure

For positive Sine-wave ( $V_N \leq V_{IN/OUT} \leq V_+$ ):

- Q1 and Q5 in red circle are switching  $f_{PWM}$ . Q2 is permanently in ON-state
- Additionally Q6 is switching with Q1 to keep  $\frac{1}{2} V_{DC}$  across Q3 / Q4

For negative Sine-wave ( $V_- \leq V_{IN/OUT} \leq V_N$ ):

- Q4 and Q6 in blue circle are switching  $f_{PWM}$ . Q3 is permanently in ON-state
- Additionally Q5 is switching with Q4 to keep  $\frac{1}{2} V_{DC}$  across Q1 / Q2

Output Ripple frequency  $f_{RIPPLE}$  equal to  $f_{PWM}$





- Again  $f_{RIPPLE}$  defines size of filter components (magnetics and capacitors)

All switches can be  $\frac{1}{2} V_{DC}$  – rated (i.e. for VDC 800V – 600V rated)

Q2 & Q3 are switching at  $f_{AC}$  (i.e. 50/60Hz)

Critical shutdown sequencing – balancing of voltages to  $\frac{1}{2} V_{DC}$

# NPC 3L – basic operation principle

  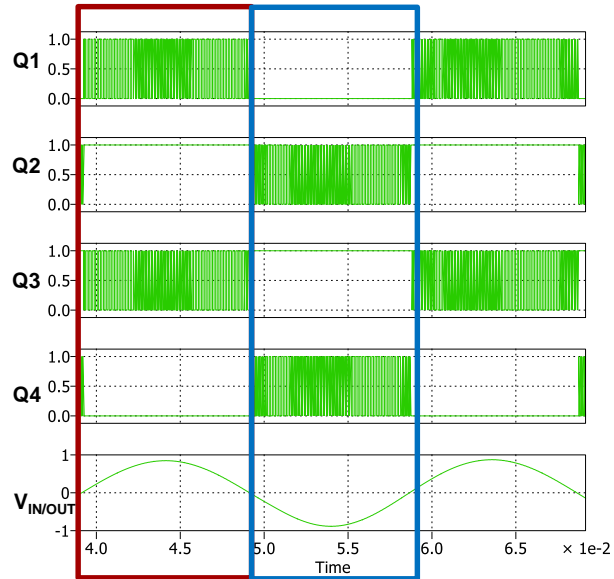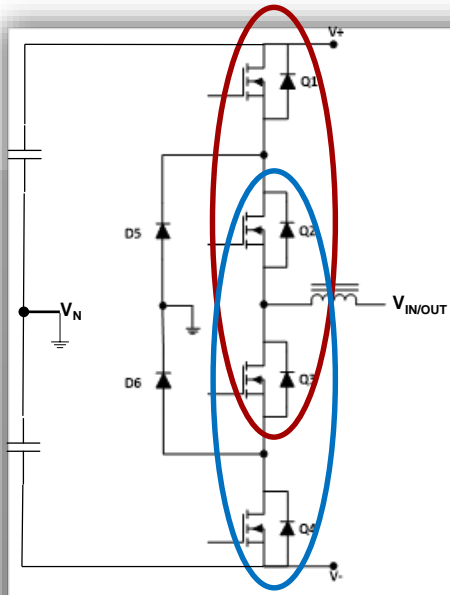

TI Information – Selective Disclosure

For positive Sine-wave ( $V_N \leq V_{IN/OUT} \leq V_+$ ):

- Q1 in red circle switching  $f_{PWL}$ . Q2 is permanently in ON-state
- Q3 is switching complementary with Q1 to keep  $\frac{1}{2} V_{DC}$  across Q3 / Q4

For negative Sine-wave ( $V_- \leq V_{IN/OUT} \leq V_N$ ):

- Q4 in blue circle switching  $f_{PWL}$ . Q3 is permanently in ON-state
- Q2 is switching complementary with Q4 to keep  $\frac{1}{2} V_{DC}$  across Q1 / Q2

Output Ripple frequency  $f_{RIPPLE}$  equal to  $f_{PWM}$






All switches can be  $\frac{1}{2} V_{DC}$  – rated (i.e. for VDC 800V – 600V rated)

Q2 & Q3 are switching at  $f_{AC}$  (i.e. 50/60Hz)

Efficiency is lower than ANPC

Critical shutdown sequencing – balancing of voltages to  $\frac{1}{2} V_{DC}$

# FC3L – basic operation principle

    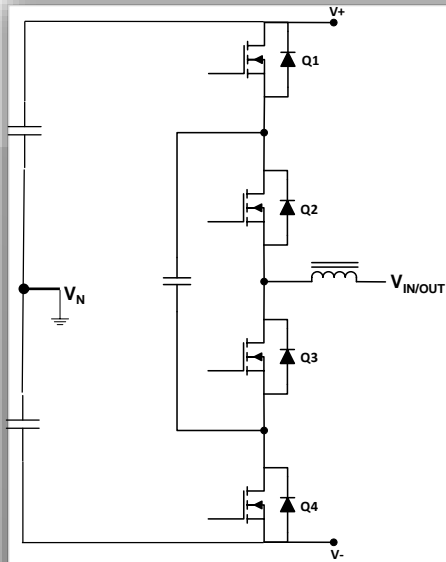

All FETs are switching  $f_{PWL}$ .

Pairs Q1/Q4 and Q2/Q3 are complementary to each other

For positive Sine-wave ( $V_N \leq V_{IN/OUT} \leq V_+$ ):

- At the +peak Q1/Q4 and Q2/Q3 are 180° phase-shifted to each other and Q1/Q2 are more in ON-state than Q3/Q4

For negative Sine-wave ( $V_- \leq V_{IN/OUT} \leq V_N$ ):

- At the -peak Q1/Q4 and Q2/Q3 are 180° phase-shifted to each other and Q1/Q2 are more in OFF-state than Q3/Q4

At zero Crossing:

- Duty cycle of Q1/Q4 and Q2/Q3 is each 50%

Output Ripple frequency  $f_{RIPPLE}$  equal to  $2 \times f_{PWM}$


- This defines smaller size of filter components (magnetics and capacitors)

All switches can be  $\frac{1}{2} V_{DC}$  – rated (i.e. for VDC 800V – 600V rated)

Initial Charging of Flying Cap to  $\frac{1}{2} V_{DC}$  is critical

Critical shutdown sequencing – balancing of voltages to  $\frac{1}{2} V_{DC}$
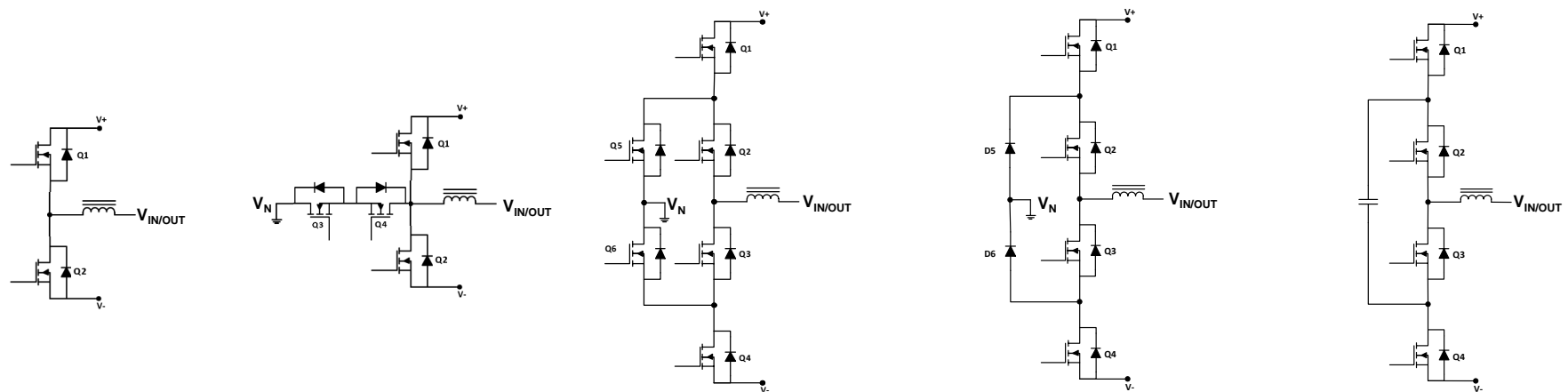
# Multilevel Topologies Summary on Inverter/PFC Power Stage



	<b>2L</b> <u>TIDA-01606 in 2L</u>	<b>T-Type 3L</b> <u>TIDA-01606</u>	<b>ANPC</b> <u>TIDA-010210</u>	<b>NPC 3L</b> <u>derived from ANPC</u>	<b>FC3L</b> <u>Flying Capacitor 3L</u>
<b>Benefits</b>	<ul style="list-style-type: none"> <li>• Simple control scheme</li> <li>• 2 switches only</li> <li>• 2 PWM</li> </ul>	<ul style="list-style-type: none"> <li>• Easy control scheme</li> <li>• Q3/Q4 see ½ V<sub>DC</sub></li> <li>• Better EMI than 2L</li> <li>• f<sub>RIPPLE</sub> = f<sub>PWM</sub></li> </ul>	<ul style="list-style-type: none"> <li>• Good efficiency</li> <li>• All switches see ½ V<sub>DC</sub></li> <li>• Better EMI than 2L</li> <li>• f<sub>RIPPLE</sub> = f<sub>PWM</sub></li> </ul>	<ul style="list-style-type: none"> <li>• Lower cost than ANPC</li> <li>• All switches see ½ V<sub>DC</sub></li> <li>• Better EMI than 2L</li> <li>• f<sub>RIPPLE</sub> = f<sub>PWM</sub></li> <li>• 4 PWM</li> </ul>	<ul style="list-style-type: none"> <li>• Highest efficiency</li> <li>• Only 4 HF FETs (&amp; 1Cap)</li> <li>• f<sub>RIPPLE</sub> = 2 x f<sub>PWM</sub></li> <li>• Smallest magnetics</li> <li>• Lowest EMI</li> </ul>
<b>Challenges</b>	<ul style="list-style-type: none"> <li>• Q1/Q2 see full V<sub>DC</sub></li> <li>• High EMI for higher f<sub>PWM</sub></li> <li>• Passives are biggest</li> </ul>	<ul style="list-style-type: none"> <li>• Q1/Q2 see full V<sub>DC</sub></li> <li>• 4 PWM</li> </ul>	<ul style="list-style-type: none"> <li>• More complex control scheme</li> <li>• Shutdown sequencing critical</li> <li>• 6 PWM</li> </ul>	<ul style="list-style-type: none"> <li>• Lower efficiency than ANPC</li> <li>• More complex control</li> <li>• Shutdown sequencing critical</li> </ul>	<ul style="list-style-type: none"> <li>• Initial charging of flying capacitor</li> <li>• Shutdown sequencing critical</li> </ul>

TI Information – Selective Disclosure

Visit:  
<https://ti.com/tool/TIDA-01606>  
<https://ti.com/tool/TIDA-010210>






# Multilevel topologies benefits

## Multilevel topologies in PFC/Inverter Stage

- Three level topologies keep the switching voltage to half of a 2-level converter which **improves overall EMI**
- Multilevel topology enables **FETs with significantly lower switching and conduction losses** which improves efficiency by using FETs with half the blocking voltage for the same DC bus voltage
- Faster  $f_{PWM}$  enables smaller passives with up to **50% reduction in size** for a 3-level converter vs. a 2-level converter. Can be further improved with 3-level flying cap topology.



# Outlook

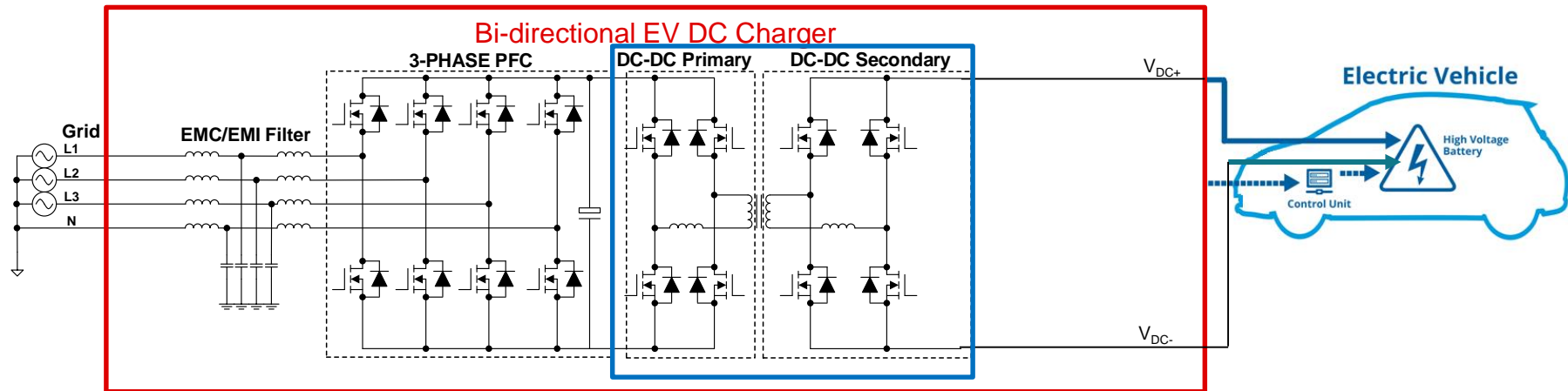

Isolated DC/DC converter will be covered in next video

**THANKS**