

# Linear Op Amps: Quick Checks for Oscillations

Presented by: Ashley Kang

Prepared by: Ashley Kang, Jacob Freet

# Prerequisites

## Electrical characterization: Stability

- Following prerequisites are recommended prior to proceeding though the handbook

## Prerequisites:

### TI-Precision Labs (TIPL) courses:

TIPL - Op Amps: Stability

[ti.com/op-amps-stability-training](https://ti.com/op-amps-stability-training)

### Pocket reference:

Training: Analog Engineer's Pocket Reference

[ti.com/analogrefguide](https://ti.com/analogrefguide)

### Application handbook:

A-B-A: Board Level Troubleshooting

[ti.com/board-level-troubleshooting](https://ti.com/board-level-troubleshooting)

## Simulation tools:

Simulations are presented within the handbook. It is recommended to install TINA-TI

TINA-TI can be downloaded for free on ti.com: [ti.com/tina-ti](https://ti.com/tina-ti)

# Detecting oscillations using OPA846

## Overview:

- Detecting oscillations for a linear amplifier can be challenging.
- Three different techniques will be covered to measure oscillations:
  - Supply Current (Quiescent Current)
  - Output waveform via oscilloscope
  - Antenna method
- The OPA846 has been configured to a low gain amplifier.
  - The datasheet defines that the device is stable for gains  $> 7$ .

## Bench setup:

- TINA-TI simulation can be used to simulate oscillation behavior.
- Representative image of how the EVM is configured, adding to oscillation effect
  - Low gain set by feedback loop
  - Capacitor attached to the output / inverting input pin

<http://www.ti.com/lit/ds/symlink/opa846.pdf>

## FEATURES

- HIGH BANDWIDTH: 400MHz (G = +10)
- LOW INPUT VOLTAGE NOISE:  $1.2\text{nV}/\sqrt{\text{Hz}}$
- VERY LOW DISTORTION:  $-100\text{dBc}$  (5MHz)
- HIGH SLEW RATE:  $625\text{V}/\mu\text{s}$
- HIGH DC ACCURACY:  $V_{IO} \pm 150\mu\text{V}$
- LOW SUPPLY CURRENT: 12.6mA
- HIGH GAIN BANDWIDTH PRODUCT: 1750MHz
- STABLE FOR GAINS  $\geq 7$

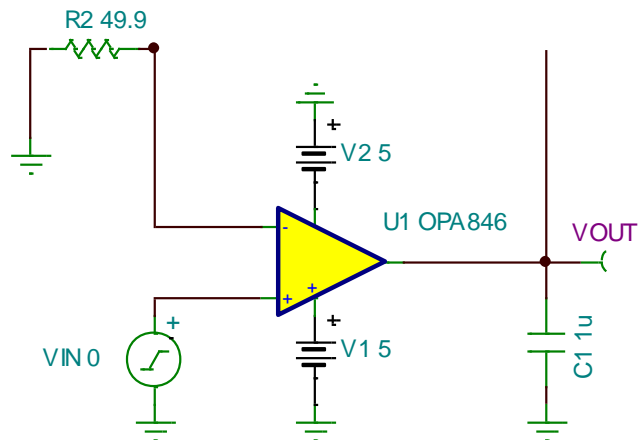


Figure: Representative circuit diagram created in TINA-TI.

# Detecting oscillations

## Test #1: Supply Current (IQ)

- Measuring a high supply current (or quiescent current) can be an indicator of oscillations.
  - High supply current can be a symptom of oscillations. Not all oscillating parts will have a high supply current.
- This can be measured by connecting the multimeter in series to the supply pin.


PARAMETER	CONDITIONS	OPA846ID, IDBV						TEST LEVEL <sup>(3)</sup>	
		TYP	MIN/MAX OVER TEMPERATURE				UNITS		MIN/ MAX
		+25°C	+25°C <sup>(1)</sup>	0°C to 70°C <sup>(2)</sup>	-40°C to +85°C <sup>(2)</sup>				
<b>POWER SUPPLY</b>									
Specified Operating Voltage		±5				V	typ	C	
Maximum Operating Voltage			±6	±6	±6	V	max	A	
Maximum Quiescent Current	$V_S = \pm 5V$	12.6	<b>12.9</b>	13.0	13.2	mA	max	A	
Minimum Quiescent Current	$V_S = \pm 5V$	12.6	<b>12.3</b>	12.1	11.8	mA	min	A	
Power-Supply Rejection Ratio (-PSRR)	$-V_S = -4.5$ to $-5.5$ (Input Referred)	95	<b>90</b>	88	85	dB	min	A	

<http://www.ti.com/lit/ds/symlink/opa846.pdf>

# Detecting oscillations
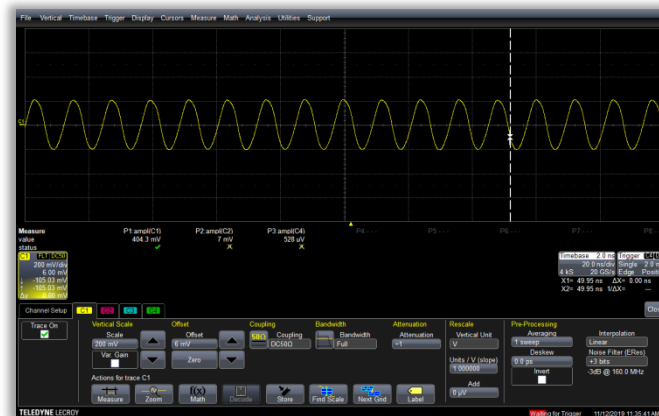
## Test #2: Output Waveform

- Oscillations can be observed by monitoring the output waveform on an oscilloscope.
  - Oscilloscope bandwidth should match or be greater than the bandwidth of the TI device.
  - **Example: OPA846**
    - Since the part is operating in the non-linear region, the waveform shape and frequency will vary.
- No input signal is needed in this case as the oscillations are high magnitude.
  - If there are low-level oscillations present, a spectrum analyzer would be needed.



## Test #3: Antenna Method

- If the output signal is not readily accessible, a loop antenna connected to an oscilloscope can be used.
- Current is induced in the coil by the magnetic field created by the output oscillations.
  - This waveform can be then seen on the oscilloscope.

