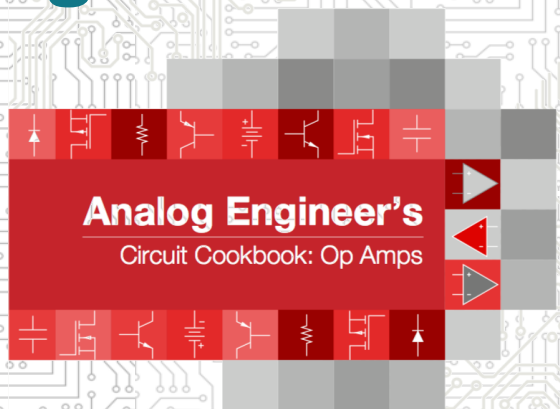


How to Design Single-supply strain gauge bridge amplifier circuit


General Purpose Amplifiers

www.ti.com/general-amps

www.ti.com/circuitcookbooks




Circuit Description

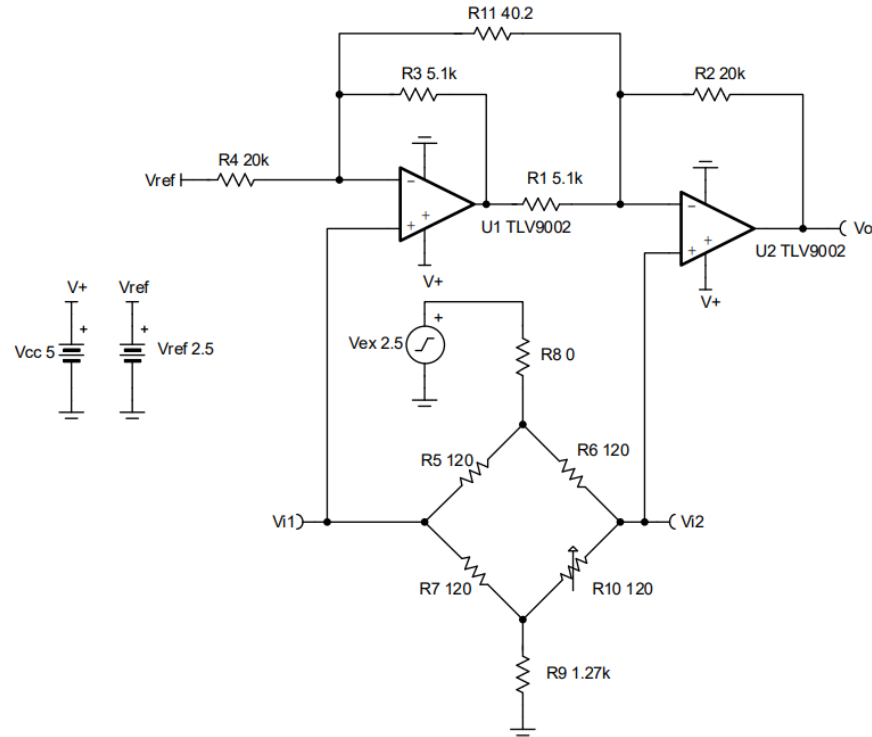

$$V_O = (I_i \times R_1) \times \left(1 + \frac{R_3}{R_2} \right)$$

Design Steps

Input $V_{iDiff} (V_{i2} - V_{i1})$		Output		Supply		
V_{iDiff_Min}	V_{iDiff_Max}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}	V_{ref}
-2.22 mV	2.27 mV	225 mV	4.72 V	5 V	0 V	2.5 V
Strain Gauge Res. Variation (R_{10})		V_{cm}		Gain		
115Ω - 125Ω		2.15 V		1001 V/V		

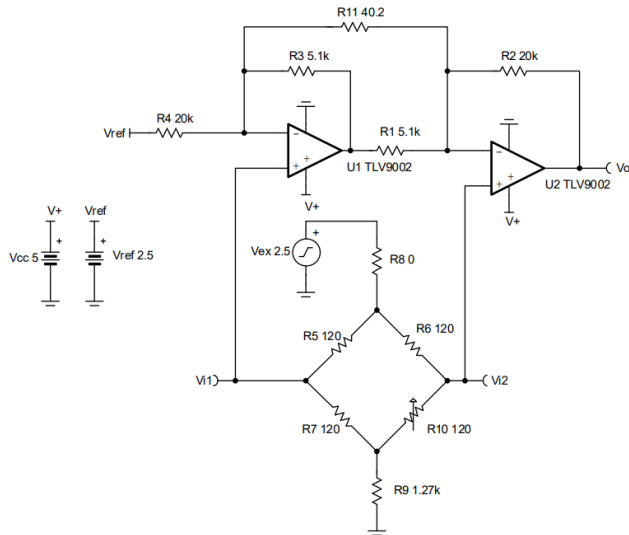

Differential Input Voltage


$$V_o = (V_{i2} - V_{i1}) \times \left(1 + \frac{R4}{R3} + \frac{2 \times R2}{R11} \right) + V_{ref}$$

Reference Voltage

Gain

Design Steps

Input V_{iDiff} ($V_{i2} - V_{i1}$)		Output		Supply		
V_{iDiff_Min}	V_{iDiff_Max}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}	V_{ref}
-2.22 mV	2.27 mV	225 mV	4.72 V	5 V	0 V	2.5 V
Strain Gauge Res. Variation (R_{10})		V_{cm}		Gain		
115 Ω - 125 Ω		2.15 V		1001 V/V		

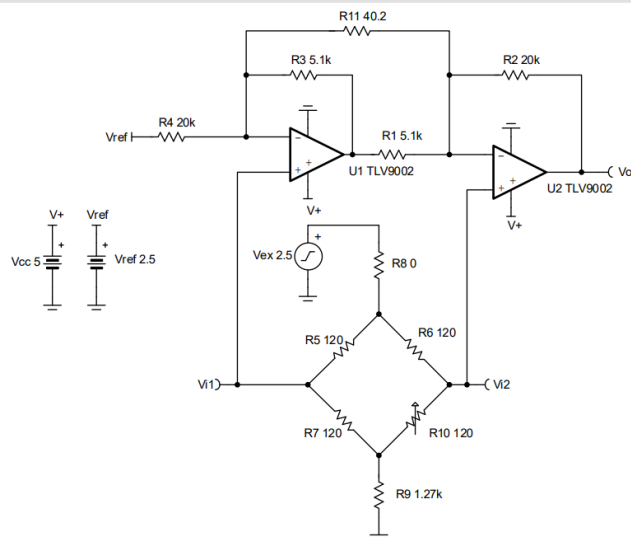

$$R5 = R6 = R7 = 120 \Omega$$


$$V_{cm} = \frac{\frac{R_{bridge}}{2} + R5}{R_{bridge} + R8 + R9} \times V_{ex}$$

$$R8 = 0 \Omega$$

$$R9 = 1.23 \text{ k}\Omega \approx 1.27 \text{ k}\Omega$$

Design Steps

Input V_{iDiff} ($V_{i2} - V_{i1}$)		Output		Supply		
V_{iDiff_Min}	V_{iDiff_Max}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}	V_{ref}
-2.22 mV	2.27 mV	225 mV	4.72 V	5 V	0 V	2.5 V
Strain Gauge Res. Variation (R_{10})		V_{cm}		Gain		
115 Ω - 125 Ω		2.15 V		1001 V/V		

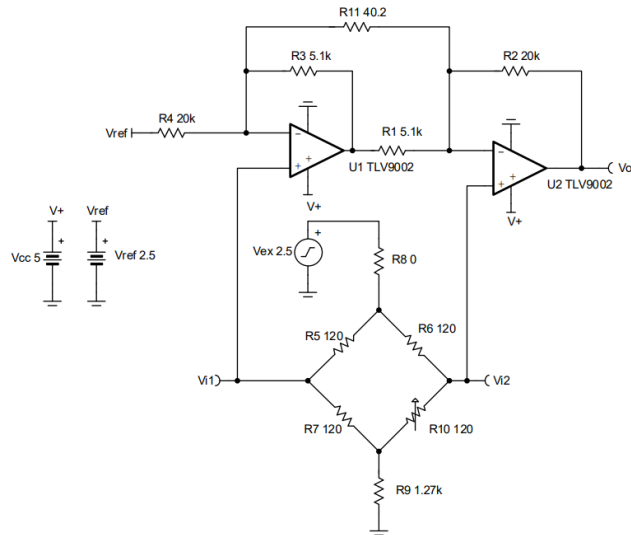

$$R1 = R3 = 5.1 \text{ k}\Omega$$



$$R2 = R4 = 20 \text{ k}\Omega$$

$$Gain = 1 + \frac{R4}{R3} + \frac{2 \times R2}{R11} = 1001 \frac{V}{V}$$

$$R11 = 40.15 \text{ } \Omega \approx 40.2 \text{ } \Omega$$


DC Results

Input V_{iDiff} ($V_{i2} - V_{i1}$)		Output		Supply		
V_{iDiff_Min}	V_{iDiff_Max}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}	V_{ref}
-2.22 mV	2.27 mV	225 mV	4.72 V	5 V	0 V	2.5 V
Strain Gauge Res. Variation (R_{10})		V_{cm}		Gain		
115 Ω - 125 Ω		2.15 V		1001 V/V		

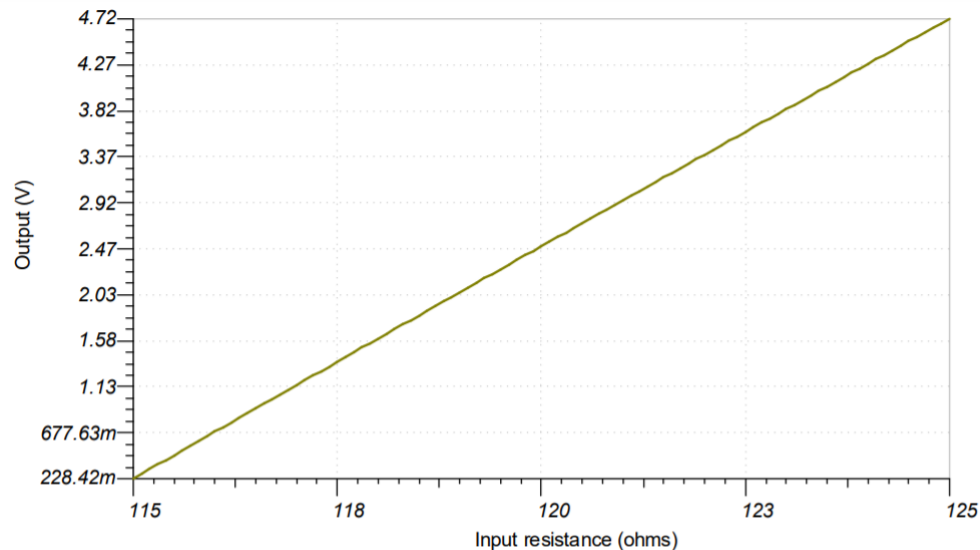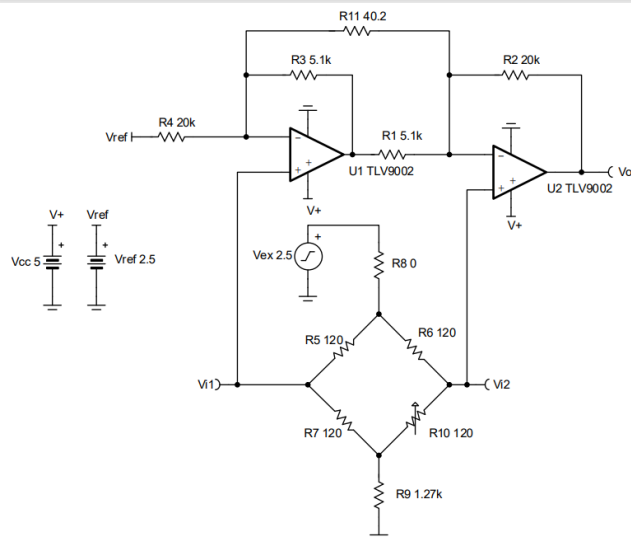

Design Notes

Input V_{iDiff} ($V_{i2}-V_{i1}$)		Output		Supply		
V_{iDiff_Min}	V_{iDiff_Max}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}	V_{ref}
-2.22 mV	2.27 mV	225 mV	4.72 V	5 V	0 V	2.5 V
Strain Gauge Res. Variation (R_{10})		V_{cm}		Gain		
115 Ω - 125 Ω		2.15 V		1001 V/V		

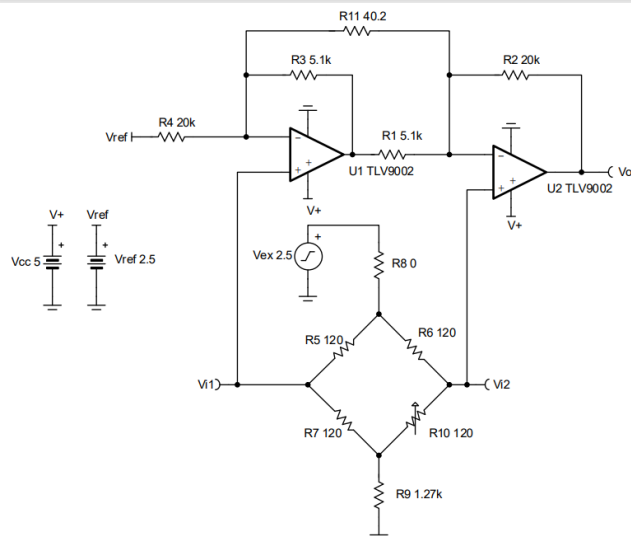

Design Notes:

1. For single-supply strain gauge bridge amplifier circuits, resistors R5, R6, and R7 of the Wheatstone bridge must match the strain gauge nominal resistance and be equal to avoid creating a bridge offset voltage.
2. Vref biases the output voltage to mid-supply to allow differential measurements in the positive and negative directions.
3. Low tolerance resistors must be used to minimize the offset and gain errors due to the bridge resistors.

Design Resources

EE Cookbook: Op Amp

www.ti.com/circuitcookbooks

Step-by-step circuit design of common op amp building block circuits.

TI Designs

www.TI.com/tidesigns

Ready-to-use reference designs with theory, calculations, simulations schematics, PCB files, bench test results

Analog Engineer's Pocket Reference

www.TI.com/analogrefguide

PDF, iTunes app and hardcopy available
PCB, analog, mixed signal design formulae
Conversions, tables, equations

TI Precision Labs

www.TI.com/precisionlabs

Quiz questions, problems, solutions
Labs and evaluation module (EVM) available

TINA-TI™ simulation software

www.TI.com/tool/tina-ti

Complete SPICE simulator DC, AC, transient, noise analysis
Schematic entry and post-processor for waveform math

DIYAMP-EVM

www.TI.com/DIYAMP-EVM

Evaluation module providing engineers with SC70, SOT23, SOIC packaging and 12 popular amplifier configurations

The Signal

www.TI.com/signalbook

PDF, iTunes app and hardcopy available
A compendium of blog posts on op amp design topics including offset voltage, input bias current, stability, noise and more

Analog Wire Blog

www.TI.com/analogwire

Technical blogs written by analog experts
Tips, tricks, and design techniques

TI E2E™ Community

www.TI.com/e2e

Support forums for all TI products

Op Amp Parametric Quick Search

www.TI.com/amplifiers

Search for precision, high-speed, general-purpose, ultra-low-power, audio and power op amps

Op Amp Parametric Cross-Reference

www.TI.com/opampcrossreference

Find similar TI op amps using competitive part numbers

www.ti.com/circuitcookbooks



© Copyright 2019 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)