

# Linear OPAMP Characterization: Offset Voltage


Presented by: Joseph Serritella

Prepared by: Joseph Serritella, Daryl Hiser, Ray Ochotorena, Mark Irwin

# OPAMP verification
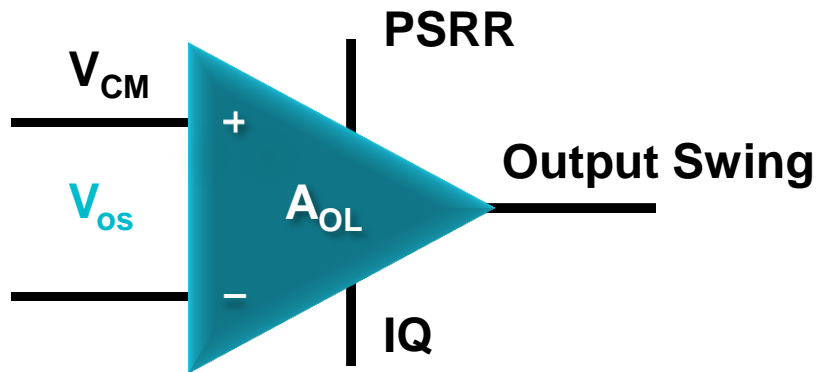
## OPAMP Electrical Characterization:

- Characterizing the electrical behavior of an integrated circuit is critical during application troubleshooting
  - Non-conformances can be identified by comprehending device level characteristics in addition to system performance
- OPAMP electrical characterization series will review following topics:
  - **Voltage offset ( $V_{os}$ )**
  - $V_{CM}$  / Common mode rejection ratio (CMRR)
  - Power supply rejection ratio (PSRR)
  - Output swing
  - Quiescent current
  - Open loop gain ( $A_{OL}$ )



# Prerequisites

## Electrical characterization: VOS

- Common mode rejection ratio measurements methods are reviewed
- Following prerequisites are recommended prior to proceeding though the handbook

## Prerequisites:

### TI-Precision Labs (TIPL) courses:

VOS: TIPL - Op Amps: Vos and IB

[ti.com/training-opamps-vos](http://ti.com/training-opamps-vos)

### Pocket Reference:

Training: Analog Engineer's Pocket Reference

[ti.com/analogrefguide](http://ti.com/analogrefguide)

### Application handbook:

A-B-A: Board Level Troubleshooting

[ti.com/board-level-troubleshooting](http://ti.com/board-level-troubleshooting)

## Simulation tools:

Simulations are presented within the handbook. It is recommended to install TINA-TI

TINA-TI can be downloaded for free on ti.com: <http://www.ti.com/tool/tina-ti>

# OPAMP test loops

## Overview:

- Analyzing datasheet parameters may appear a daunting task!
- Multiple parameters can be derived easily from offset ( $V_{OS}$ ).
  - PSRR, CMRR, and AOL can be calculated by monitoring shifts


## False Summing Junction (FSJ):

- Accurate VOS measurements can be obtained through test loops
  - **Benefits:**
    - Simplistic
    - Stable
    - Small
  - **Disadvantages:**
    - Feedback resistor load in parallel with other added loads
    - Loop drive function of DUT  $V_{OS}$
- Majority of DC parameters determined with 4 resistors!
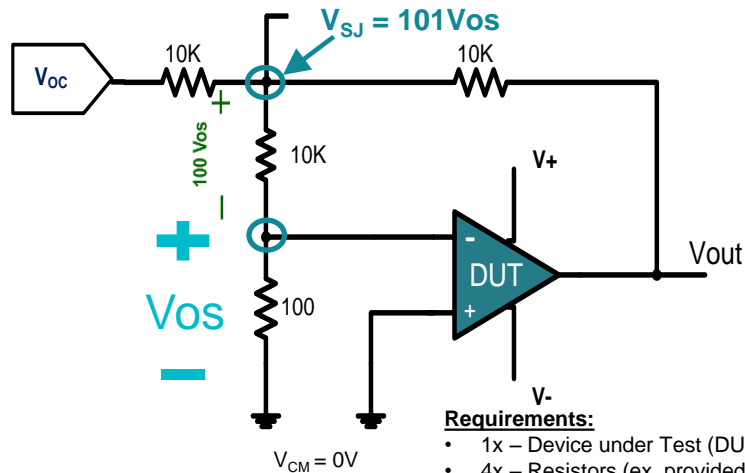
## Measuring VOS:

- **VOS:** differential input voltage required to force output to mid-supply
  - best measured at the summing junction ( $V_{SJ}$ )
- **Output control voltage (VOC):** Calibrate the out voltage to zero volts
  - Know as offset correction factor (derived from Kirchhoff's Voltage Law):

$$V_{OC} = -(V_{OUT} + VOS(302)) + 2V_{CM}$$



### Requirements:

- 1x – Device under Test (DUT)
- 4x – Resistors (ex. provided)
  - Resistor values can be varied depending on device

### Example:

- $V_+ = +10V$
- $V_- = -10V$
- $V_{OUT} = 0V$
- $V_{OC} = 0V$  (ideal opamp)


### Results:

- $V_{SJ} = 1.01mV$
- $1.01mV = (101)V_{OS} = V_{SJ}$   
 $10\mu V = V_{OS}$

# False summing junction

## Simulation Overview:

- TINA-TI can be utilized to simulate a false summing junction circuit
  - **Figure 1 example:** OPA192
  - A reference design downloaded through TI.com
    - Link:  
<http://www.ti.com/product/OPA192/technicaldocuments>
- Review the TI datasheet prior to completing simulations
  - Verify: Supply range, VCM range and remaining parameters.

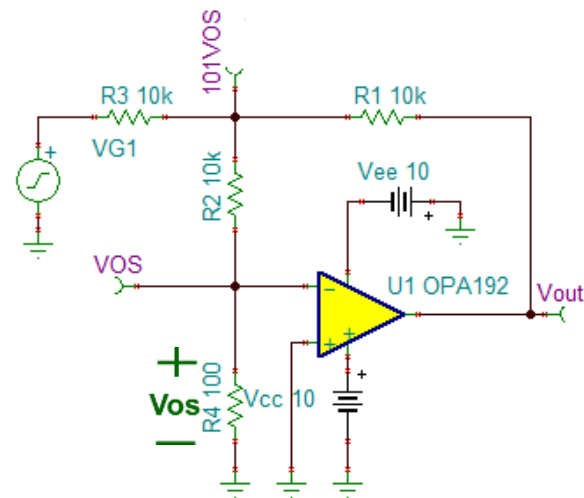

**Figure:** Representative circuit diagram created in TINA-TI.

# Datasheet offset voltage

**VOS test conditions** are provided within the TI product datasheet

- **Ensure**  $V_{OUT}$  approximately equal to mid-supply
- **Note:** High speed amplifiers measurements may require a solder down solution

## 6.7 Electrical Characteristics: $V_S = \pm 4\text{ V to } \pm 18\text{ V}$ ( $V_S = +8\text{ V to } +36\text{ V}$ )

At  $T_A = +25^\circ\text{C}$ ,  $V_{CM} = V_{OUT} = V_S / 2$ , and  $R_{LOAD} = 10\text{ k}\Omega$  connected to  $V_S / 2$ , unless otherwise noted.

PARAMETER	TEST CONDITIONS	MIN	TYP	MAX	UNIT	
<b>OFFSET VOLTAGE</b>						
$V_{OS}$	Input offset voltage		$T_A = 0^\circ\text{C to } 85^\circ\text{C}$	$\pm 5$	$\pm 25$	$\mu\text{V}$
			$T_A = -40^\circ\text{C to } +125^\circ\text{C}$	$\pm 8$	$\pm 50$	
	$V_{CM} = (V+) - 1.5\text{ V}$	$T_A = 0^\circ\text{C to } 85^\circ\text{C}$	$\pm 10$	$\pm 75$		
		$T_A = -40^\circ\text{C to } +125^\circ\text{C}$	$\pm 10$	$\pm 40$		
			$\pm 25$	$\pm 150$		
			$\pm 50$	$\pm 250$		