

Quiz: Instrumentation Amplifier (IA) topologies: two-amp

TI Precision Labs – Instrumentation Amplifiers


Presented by Tamara Alani

Prepared by Tamara Alani

Quiz: (IA) topologies: two-amp || Question

1. What are some challenges associated with the two-amp IA topology? Select all that apply.

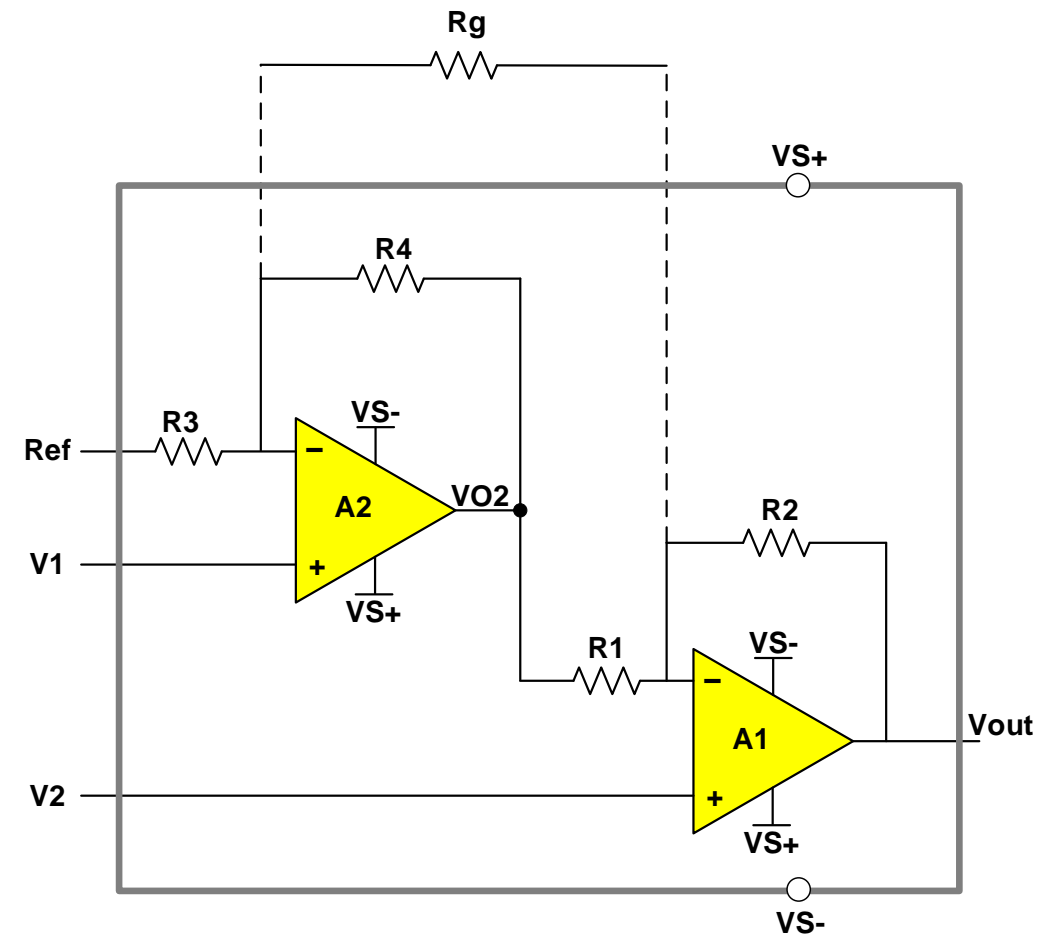
- a) The path from V1 to Vout has an additional phase shift of A2
- a) The two-amp IA must be configured in gains > 1 V/V
- a) The two-amp IA consumes more power
- b) There is trade-off between VCM and Ref to Gain



Quiz: (IA) topologies: two-amp || Answer

1. What are some challenges associated with the two-amp IA topology? Select all that apply.

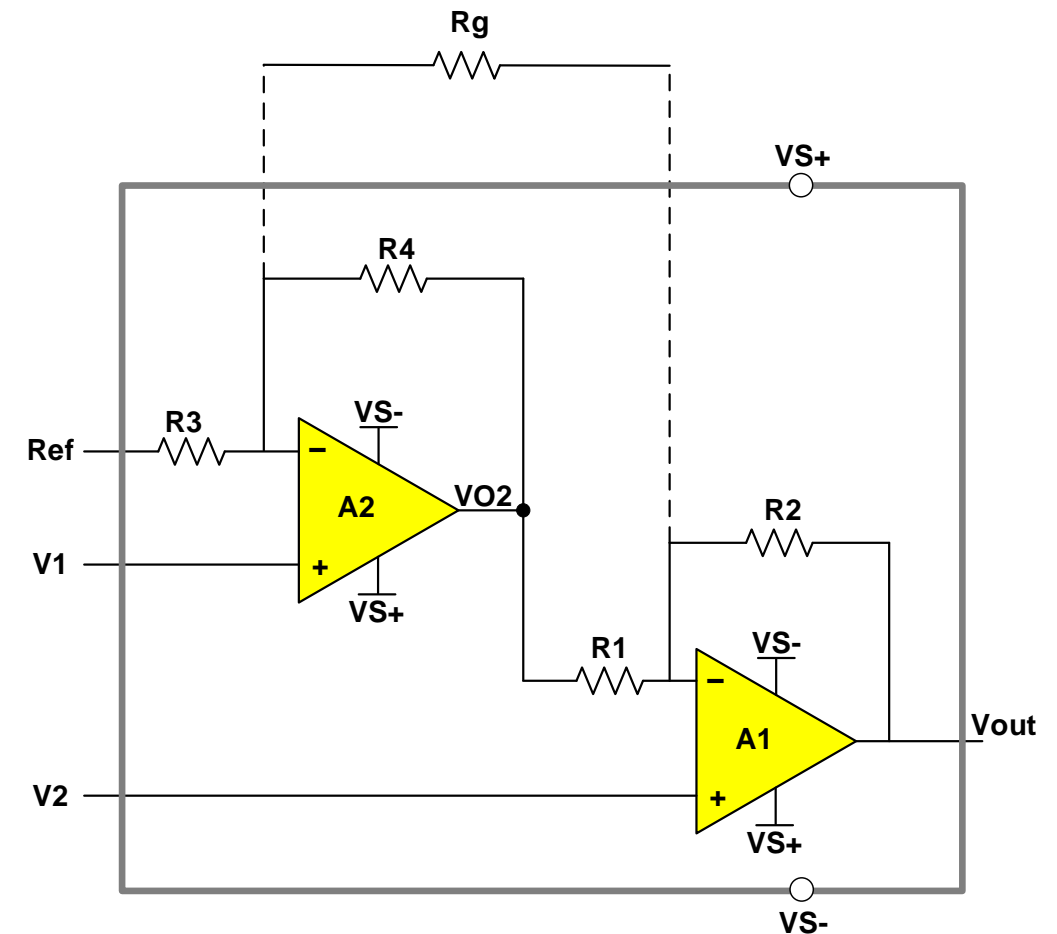- a) The path from V1 to Vout has an additional phase shift of A2
- a) The two-amp IA must be configured in gains > 1 V/V
- a) The two-amp IA consumes more power
- b) There is trade-off between VCM and Ref to Gain



Quiz: (IA) topologies: three-amp || Question

2. Which of the following statements is false regarding the reference pin on a two-amp IA?
- a) The ref pin must be driven by a low-impedance source
 - b) The ref pin is used to level-shift the output of the IA
 - c) The ref pin should be able to source and sink current
 - d) The ref pin may be driven by a resistor divider so long as the resistors are low tolerance


Quiz: (IA) topologies: two-amp || Answer

2. Which of the following statements is false regarding the reference pin on a two-amp IA?
- a) The ref pin must be driven by a low-impedance source
 - b) The ref pin is used to level-shift the output of the IA
 - c) The ref pin should be able to source and sink current
 - d) The ref pin may be driven by a resistor divider so long as the resistors are low tolerance**

Quiz: (IA) topologies: two-amp || Question

3. In a two-amp IA, which resistors do we aim to match?

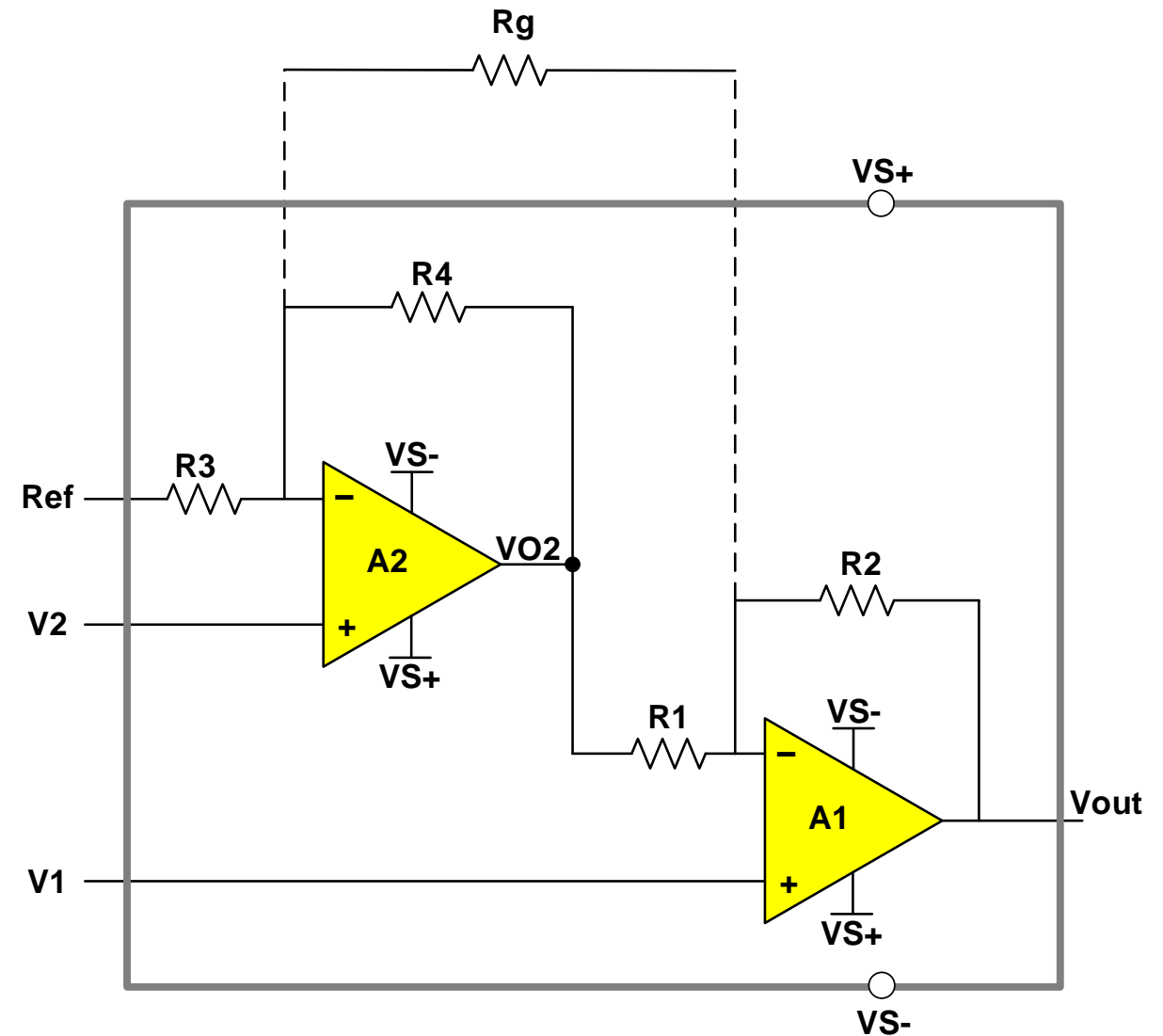- a) $R4 = R1$ and $R2 = R3$
- b) $R4 = R3$ and $R2 = R1$




Quiz: (IA) topologies: two-amp || Answer

3. In a two-amp IA, which resistors do we aim to match?

a) $R4 = R1$ and $R2 = R3$

b) $R4 = R3$ and $R2 = R1$

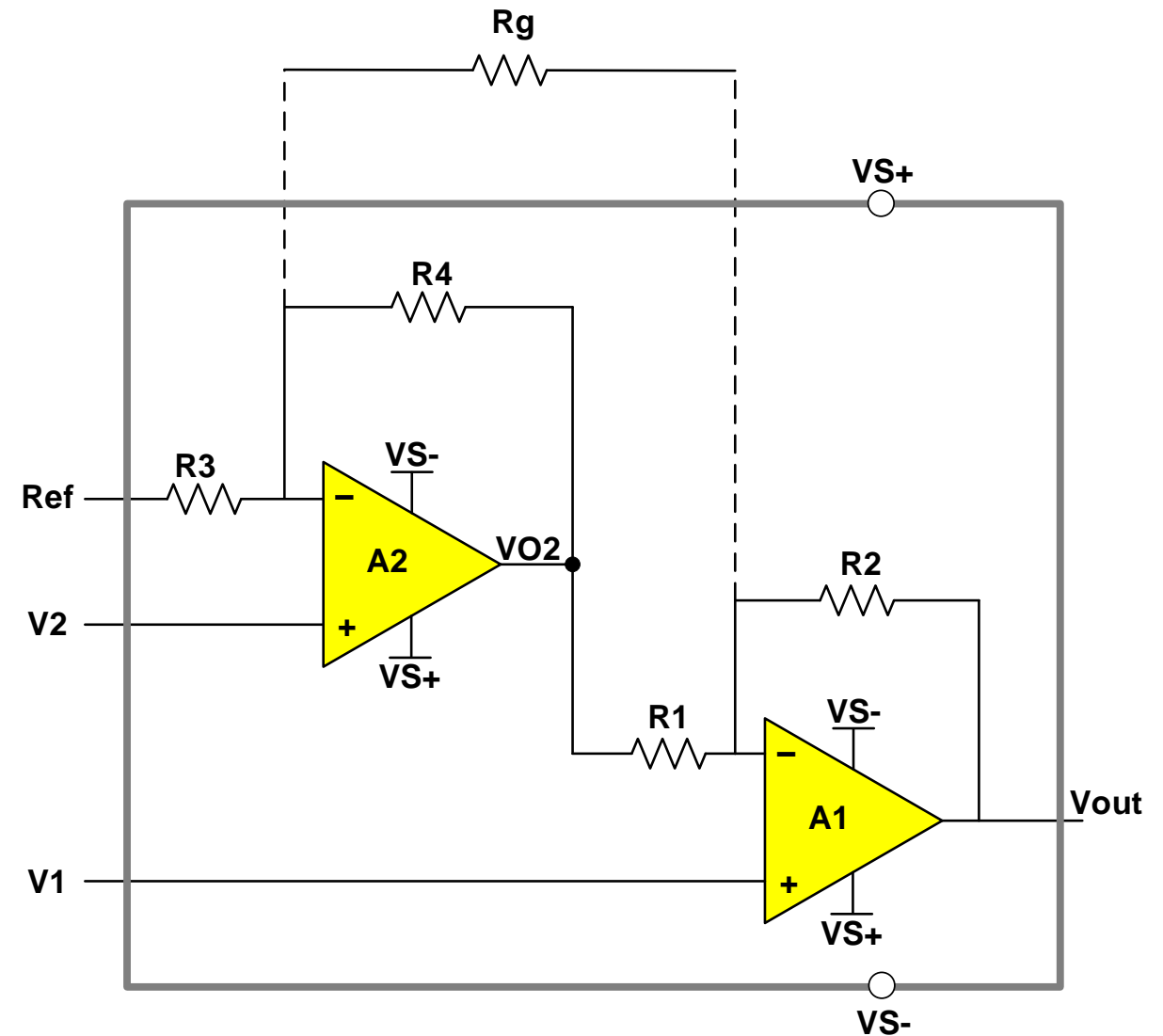

Quiz: (IA) topologies: three-amp || Question

4. What is the gain equation of a two-amp IA, assuming we match R4 to R1 and R3 to R2?

a) $\text{Gain} = 1 + 2 \times R2$

b) $\text{Gain} = 1 + \frac{R1}{R2}$

c) $\text{Gain} = 1 + \frac{R2}{R1}$

d) $\text{Gain} = 2 \times (R1 + R2)$

HINT:

Go to the product datasheet:

<https://www.ti.com/lit/ds/symlink/ina126.pdf>

Quiz: (IA) topologies: two-amp || Answer

4. What is the gain equation of a two-amp IA, assuming we match R4 to R1 and R3 to R2?

a) $\text{Gain} = 1 + 2 \times R2$

b) $\text{Gain} = 1 + \frac{R1}{R2}$

c) **Gain = $1 + \frac{R2}{R1}$**

d) $\text{Gain} = 2 \times (R1 + R2)$

HINT:

Go to the product datasheet:

<https://www.ti.com/lit/ds/symlink/ina126.pdf>

Quiz: (IA) topologies: two-amp || Question

5. Using the INA126 (TI's micro-power IA), what value of R_g do you need to achieve a signal gain of 105V/V?

- a) $R_g = 100\Omega$
- b) $R_g = 200\Omega$
- c) $R_g = 800k\Omega$
- d) $R_g = 800\Omega$

HINT:

Go to the product datasheet:

<https://www.ti.com/lit/ds/symlink/ina126.pdf>

Quiz: (IA) topologies: two-amp || Answer

5. Using the INA126 (TI's micro-power IA), what value of R_g do you need to achieve a signal gain of 105V/V?

- a) $R_g = 100\Omega$
- b) $R_g = 200\Omega$
- c) $R_g = 800k\Omega$
- d) **$R_g = 800\Omega$**

HINT:

Go to the product datasheet:


<https://www.ti.com/lit/ds/symlink/ina126.pdf>

$$\text{Gain} = \left(5 + \frac{80k\Omega}{R_g} \right)$$

Quiz: (IA) topologies: two-amp || Question

6. What is the differential gain of the following circuit?

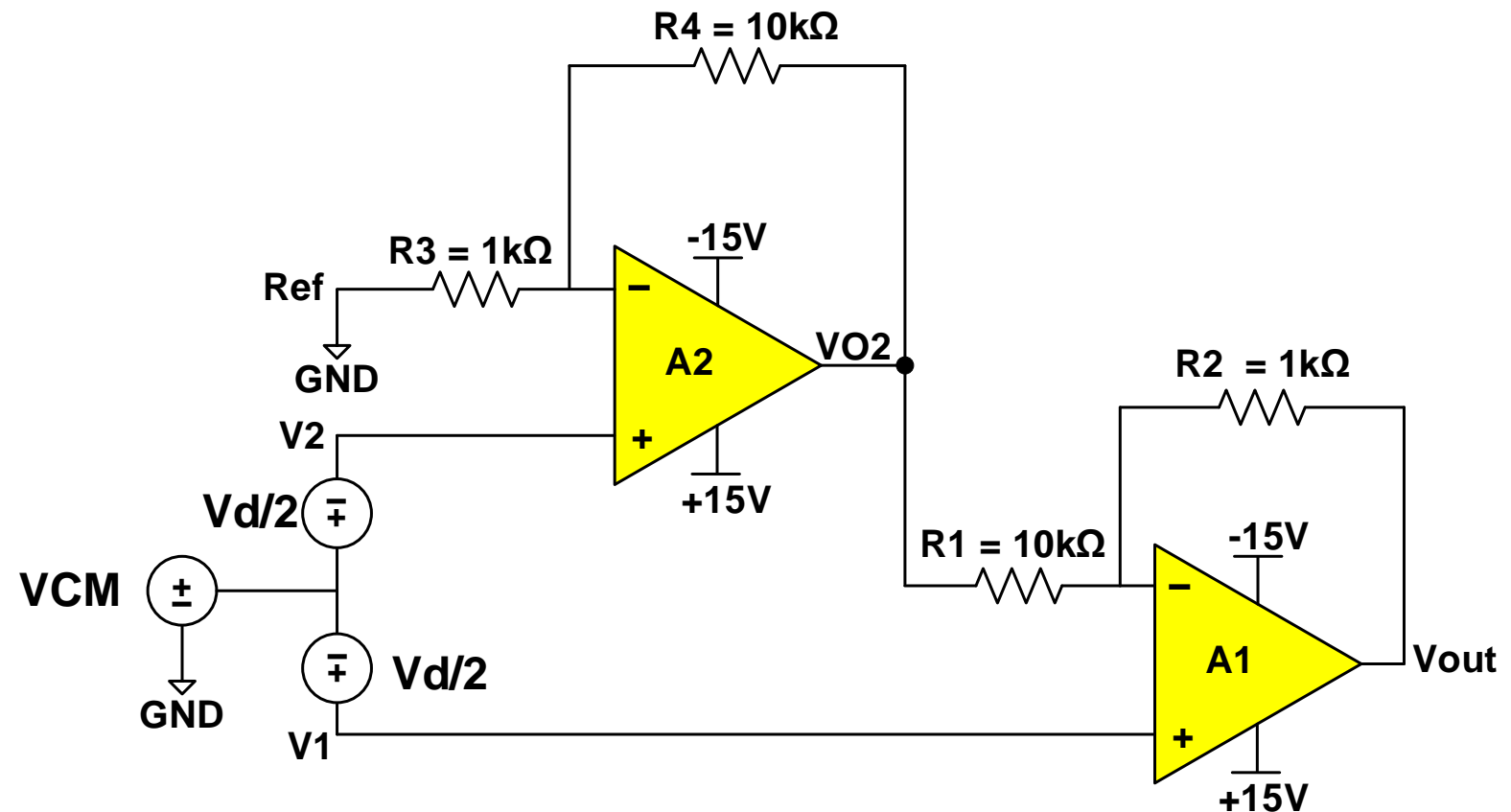
- a) Gain = 1.1V/V
- b) Gain = 2V/V
- c) Gain = 0.1V/V
- d) Gain = 10V/V



Quiz: (IA) topologies: two-amp || Answer

6. What is the differential gain of the following circuit?

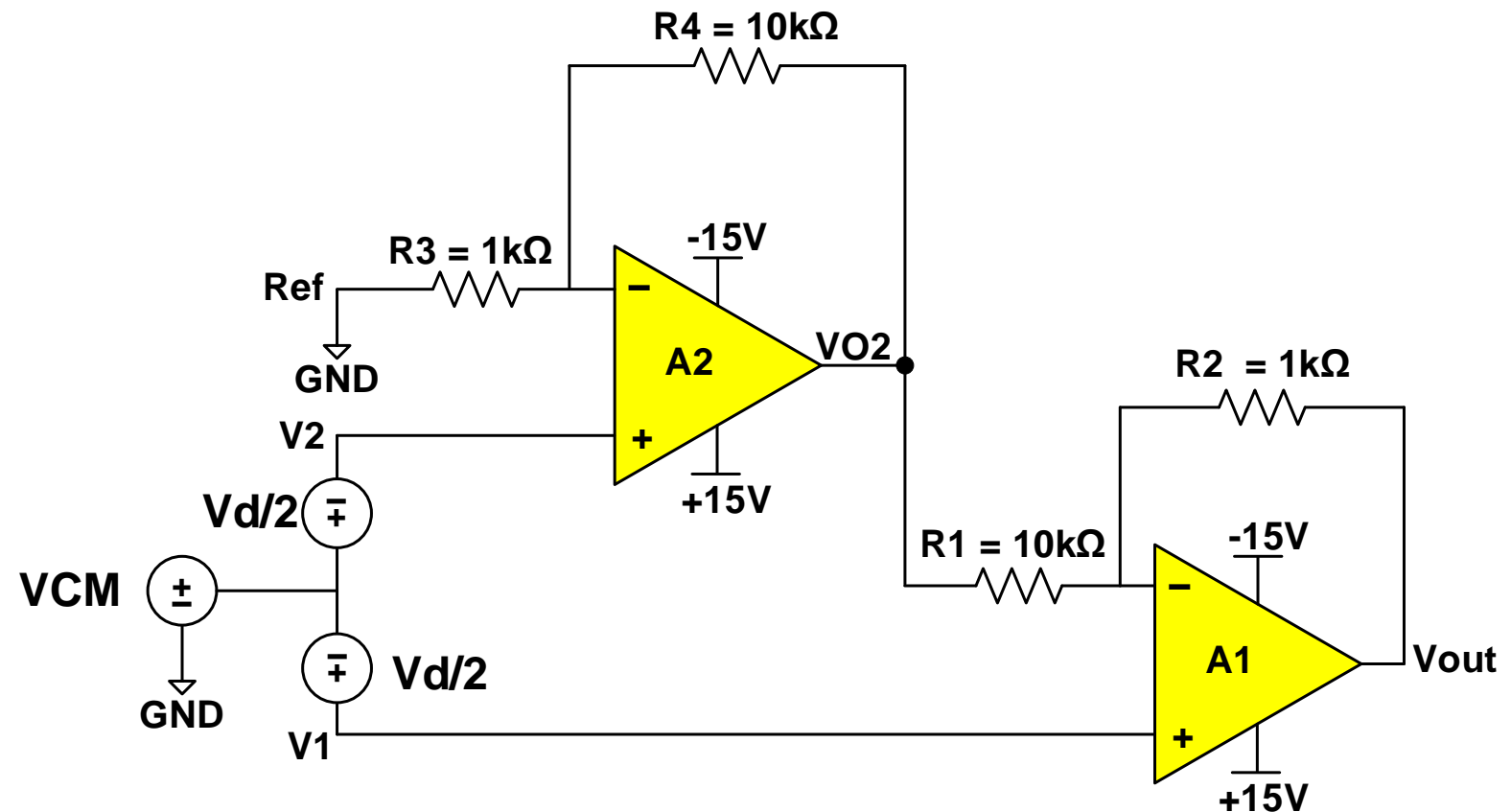- a) Gain = 1.1V/V
- b) Gain = 2V/V
- c) Gain = 0.1V/V
- d) Gain = 10V/V



Quiz: (IA) topologies: two-amp || Question

7. Using the INA156 (TI's rail-to-rail output swing IA optimized for low-voltage, single-supply operation), create a boundary plot for the following conditions:

- Voltage supply = 5V single supply
- Gain = 10V/V
- Reference = 2.5V
- Common mode voltage = 2V

HINT:

Use the INA Boundary Plot calculator in the **Analog Engineer's Calculator**:

<https://www.ti.com/tool/ANALOG-ENGINEER-CALC>

Quiz: (IA) topologies: two-amp || Answer


7. Using the INA156 (TI's rail-to-rail output swing IA optimized for low-voltage, single-supply operation), create a boundary plot for the following conditions:

- Voltage supply = 5V single supply
- Gain = 10V/V
- Reference = 2.5V
- Common mode voltage = 2V

HINT:

Use the INA Boundary Plot calculator in the **Analog Engineer's Calculator**:
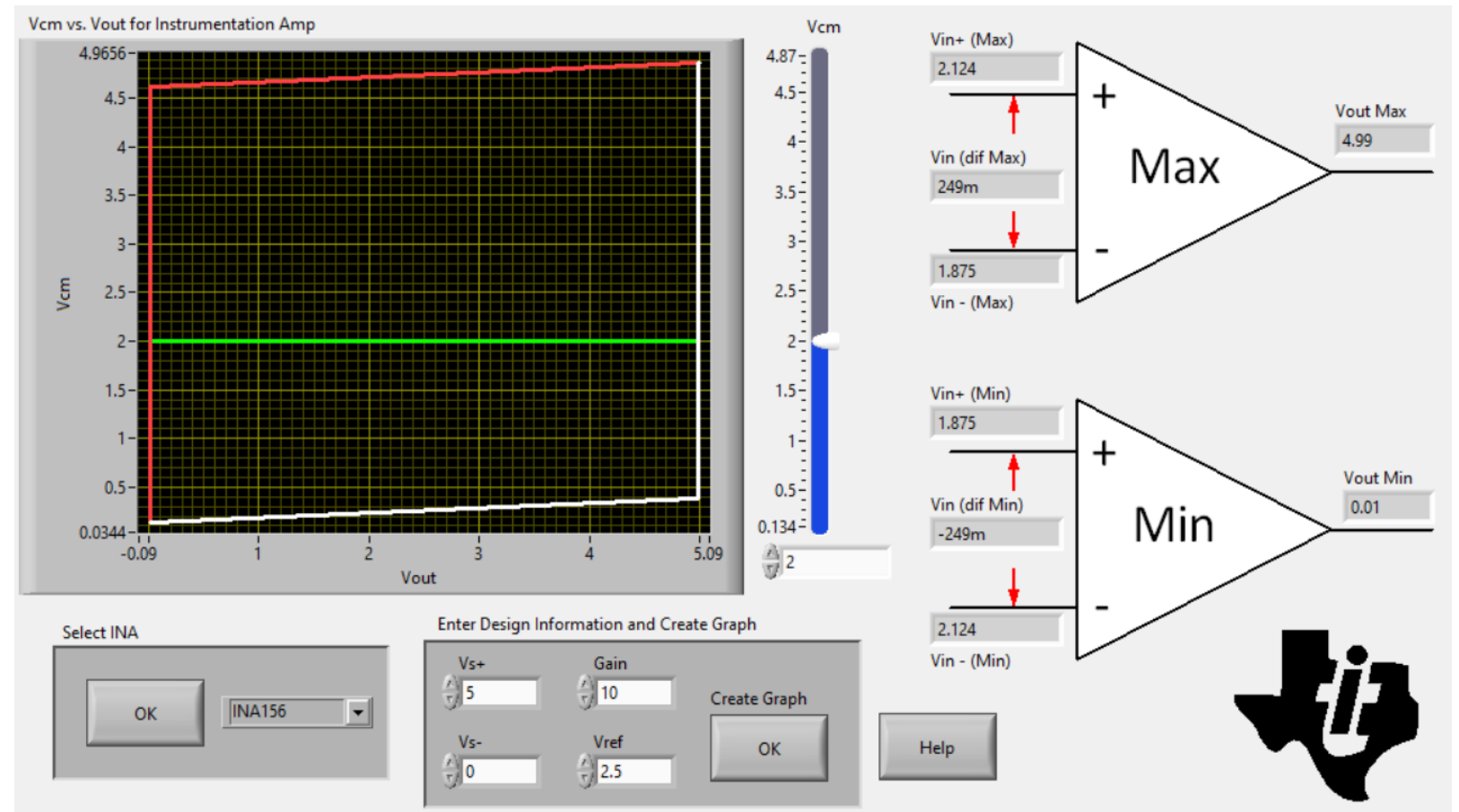
<https://www.ti.com/tool/ANALOG-ENGINEER-CALC>



Quiz: (IA) topologies: two-amp || Question

8. True or false: In an integrated two-amp IA, all resistors are absolutely matched in production

Quiz: (IA) topologies: two-amp || Answer

8. True or false: In an integrated two-amp IA, all resistors are absolutely matched in production

TRUE

Quiz: (IA) topologies: two-amp || Question

9. Which of the following statements is true regarding the relationship between Ref and VCM to Gain?

- a) The further apart Ref is to VCM, lower gains can be achieved
- b) The closer Ref is to VCM, lower gains can be achieved
- c) If Ref = VCM, gain < 1 V/V can be achieved
- d) If Ref \ll VCM, any gain can be achieved

Quiz: (IA) topologies: two-amp || Answer

9. Which of the following statements is true regarding the relationship between Ref and VCM to Gain?

- a) The further apart Ref is to VCM, lower gains can be achieved
- b) The closer Ref is to VCM, lower gains can be achieved**
- c) If Ref = VCM, gain < 1 V/V can be achieved
- d) If Ref \ll VCM, any gain can be achieved

To find more Instrumentation Amplifier technical resources and search products, visit [ti.com/inas](https://www.ti.com/inas)